



Eastern Mediterranean University

"For Your International Career"

Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

INFE221 – Electrical Circuits

**Midterm Exam
Spring 2014-15**

29 April 2015

Duration: 100 minutes

Instructor: M. K. Uyguroğlu

STUDENT'S	
NUMBER	
NAME	SOLUTIONS
SURNAME	
GROUP NO.	

Problem		Points
1		20
2		40
3		20
4		20
TOTAL		100

Problem 1

Find i and R_{eq} if $v_{ab} = 40$ V in the circuit of Fig. P1

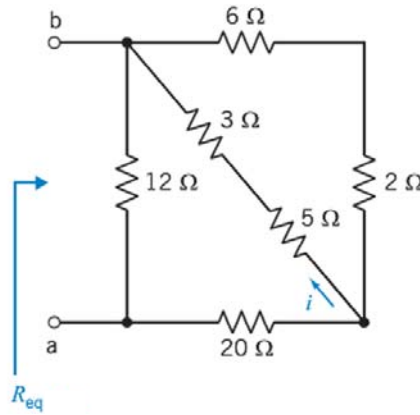


Figure P1

$$R_{eq} = 12 // (20 + \underbrace{(3+5)}_8) // \underbrace{(6+2)}_8 = 8\Omega$$


$$\underbrace{\underbrace{24}_4}_8$$

Using voltage division principle

$$v = 40 \frac{4}{24} = \frac{40}{6} \text{ V}$$

Therefore

$$i = \frac{v}{8} = \frac{40}{48} = \frac{5}{6} \text{ A}$$

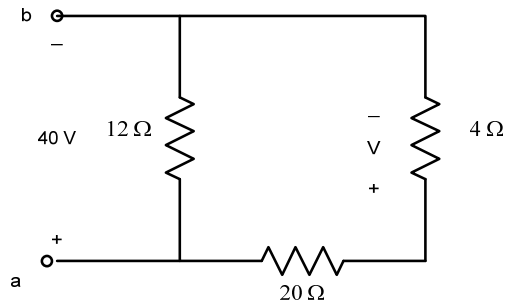

Problem 2

Find v in the circuit of Fig. P2 by using

- (a) Nodal Analysis
- (b) Mesh Analysis
- (c) Superposition
- (d) Thevenin's and Norton's theorems.


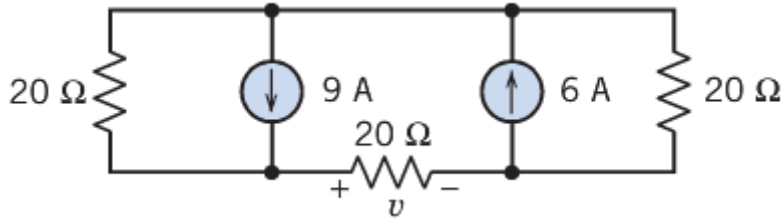


Figure P2

Nodal Analysis

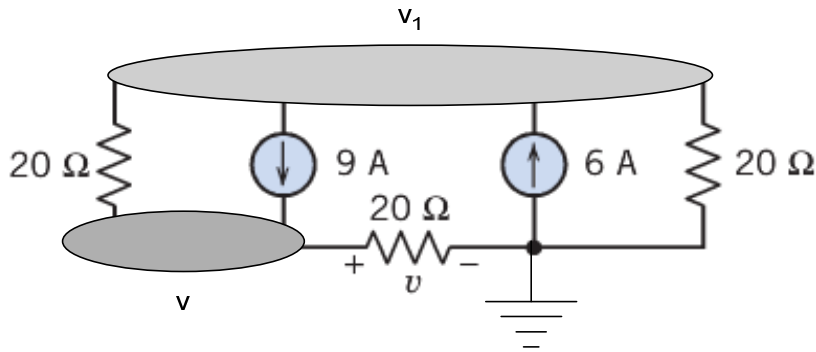

KCL at v :

$$\left(\frac{1}{20} + \frac{1}{20}\right)v - \frac{1}{20}v_1 = 9$$

multiply both sides by 20 yields:

$$2v - v_1 = 180 \dots \dots \dots (1)$$

KCL at v_1 :

$$-\frac{1}{20}v + \left(\frac{1}{20} + \frac{1}{20}\right)v_1 = 6 - 9 = -3$$

multiply bot sides by 20 yields:


$$-v + 2v_1 = -60 \dots \dots \dots (2)$$

Multiplication of Eq.(1) by 2 and addition of Eqs(1) and (2) gives:

$$3v = 300$$

$$\boxed{v = 100 \text{ V}}$$

Mesh Analysis:

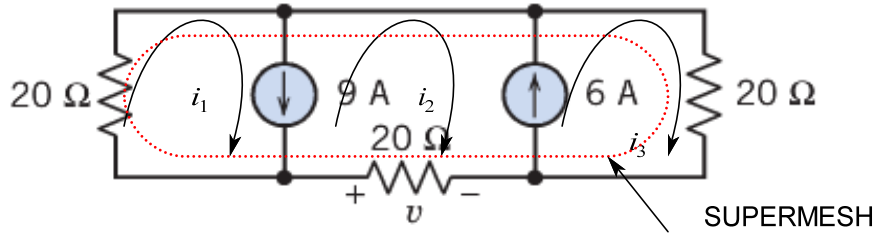

KVL around the SUPERMESH

$$20i_1 + 20i_2 + 20i_3 = 0$$

Where

$$i_1 - i_2 = 9 \Rightarrow i_2 = i_1 - 9$$

And

$$i_3 - i_2 = 6 \Rightarrow i_3 = 6 + i_2 = 6 + i_1 - 9 = i_1 - 3$$

Therefore,

$$20i_1 + 20(i_1 - 9) + 20(i_1 - 3) = 0$$

$$60i_1 = 240$$


$$i_1 = 4 \text{ A}$$

$$i_2 = -5 \text{ A}$$

$$i_3 = 1 \text{ A}$$

$$v = -20i_2 = 100 \text{ V}$$


SUPERPOSITION

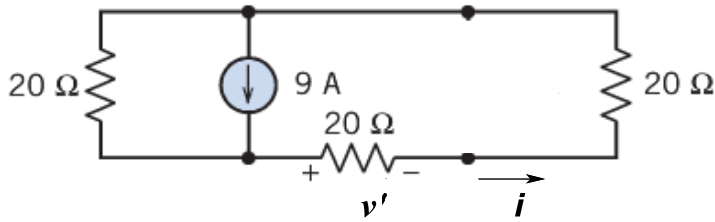

Using current division principle

$$i = 9 \frac{20}{20 + 40} = 3 \text{ A}$$



$$v' = 20i = 60 \text{ V}$$

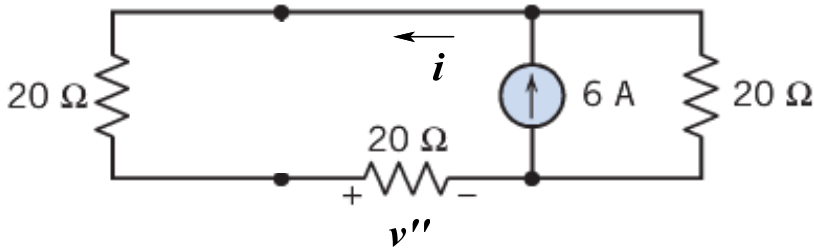

$$v'' = 20i = 20 \left(6 \frac{20}{60} \right) = 40 \text{ V}$$


$$v = v' + v'' = 60 + 40 = 100 \text{ V}$$

THEVENIN'S and NORTON Theorem

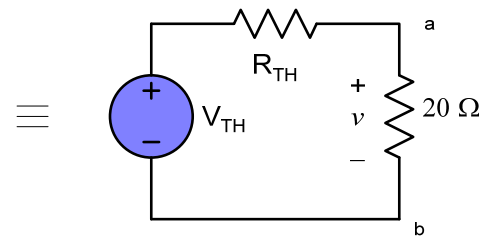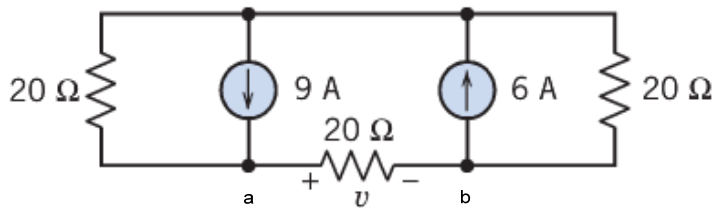


INFE221 Electric Circuits – Midterm Exam

R_{TH}

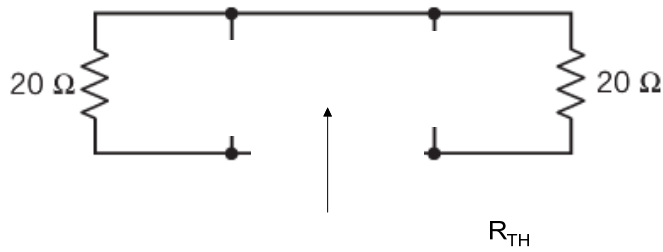

$$R_{TH} = 20 + 20 = 40\ \Omega$$

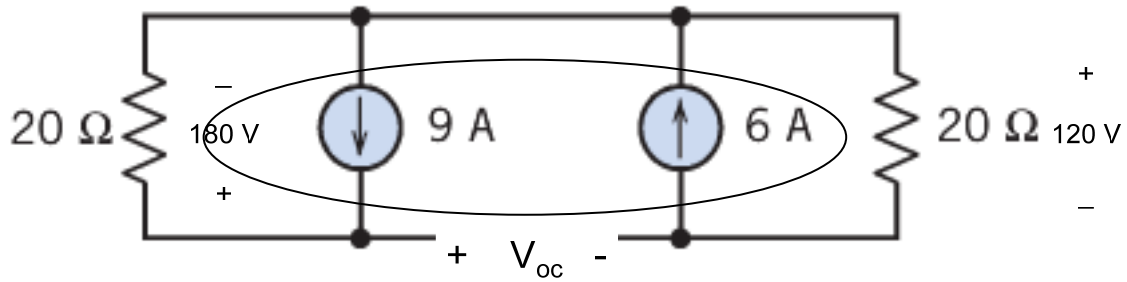


KVL around the outer loop:

$$180 + 120 - V_{oc} = 0$$

$$V_{oc} = 300\text{ V}$$
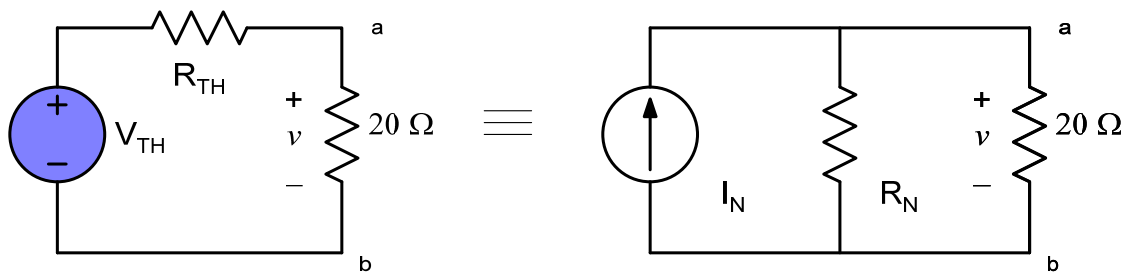
$$v = V_{TH} \frac{20}{20 + R_{TH}} = 300 \frac{20}{60} = 100\text{ V}$$



$$I_N = \frac{V_{TH}}{R_{TH}} = \frac{300}{40} = 7.5\text{ A}$$

$$R_N = R_{TH} = 40\ \Omega$$

$$v = 20 \left(I_N \frac{R_N}{R_N + 20} \right) = 150 \frac{40}{60} = 100\text{ V}$$

Problem 3

Find v in the circuit of Fig.P3.

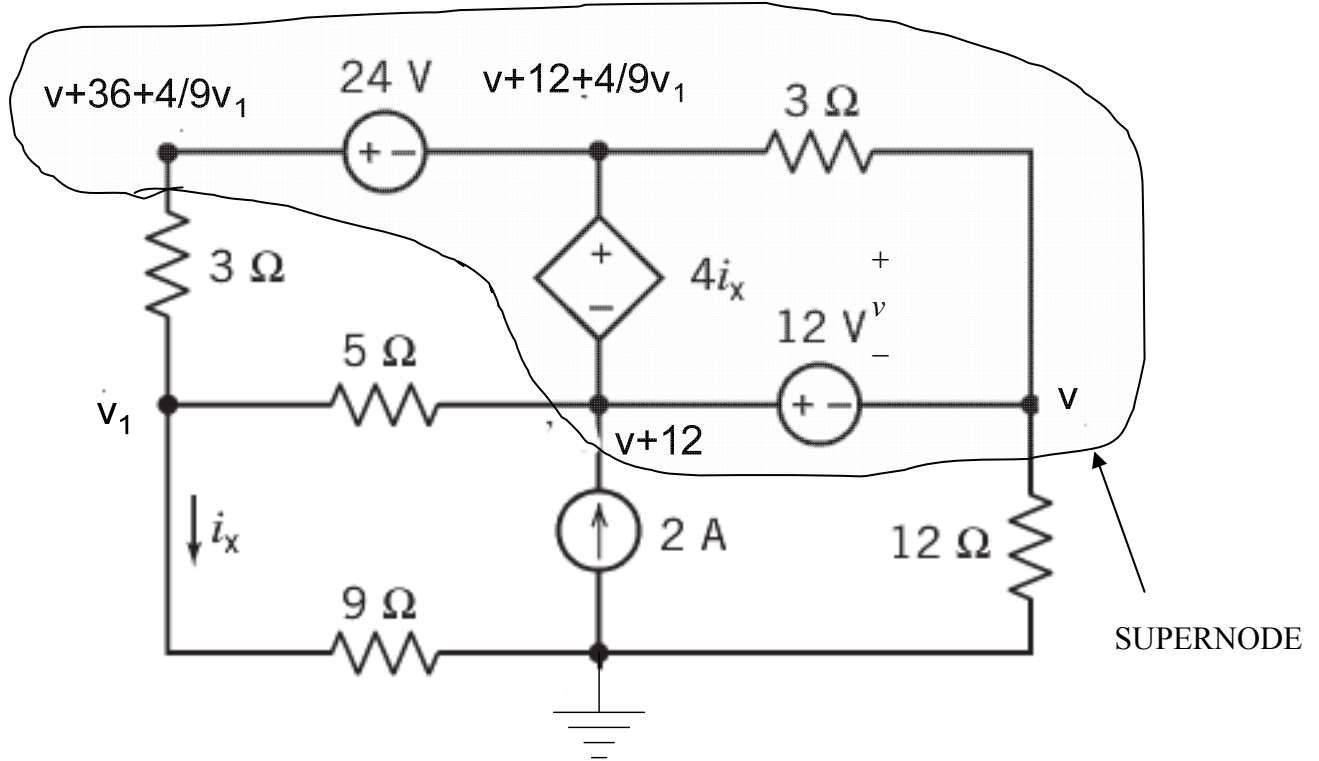


Figure P3

KCL at v_1 ;

$$\left(\frac{1}{3} + \frac{1}{5} + \frac{1}{9}\right)v_1 - \frac{1}{3}\left(v + 36 + \frac{4}{9}v_1\right) - \frac{1}{5}(v + 12) = 0$$

KCL at SUPERNODE

$$-\left(\frac{1}{3} + \frac{1}{5}\right)v_1 + \frac{1}{3}\left(v + 36 + \frac{4}{9}v_1\right) + \frac{1}{5}(v + 12) + \frac{1}{12}v = 2$$

$$-\frac{8}{15}v + \frac{67}{135}v_1 = \frac{72}{5}$$

$$\frac{37}{60}v - \frac{52}{135}v_1 = -\frac{62}{5}$$

$$\boxed{v = -6.037 \text{ V}}$$

Problem 4

Find v and i for the circuit of Fig.P4


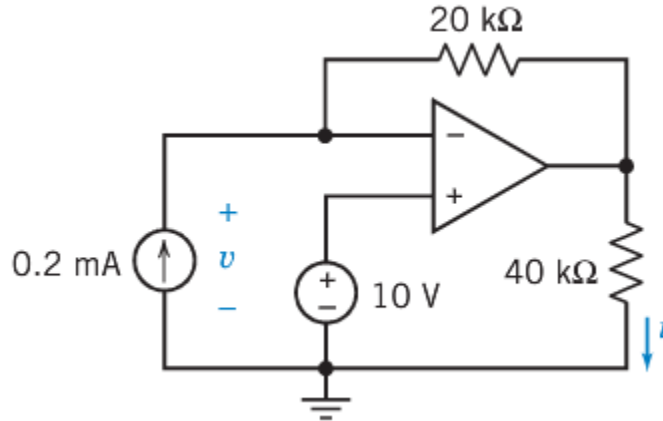


Figure P4

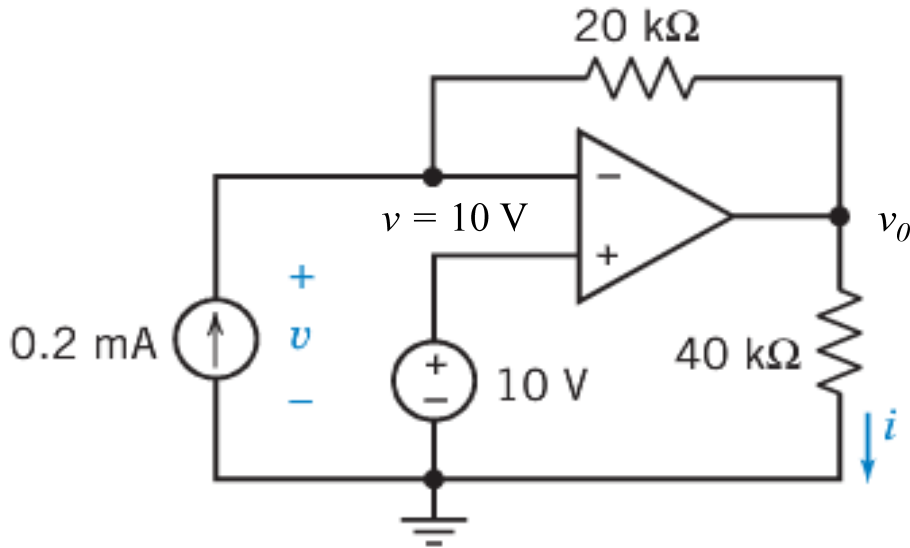

$$v = 10 \text{ V}$$

KCL at inverting input terminal:

$$\frac{v_o - 10}{20k} + 0.2m = 0$$

multiply both sides by 20k yields:

$$v_o - 10 + 4 = 0$$

$$\boxed{v_o = 6 \text{ V}}$$

$$i = \frac{v_o}{40k} = \frac{6}{40k} = 0.15 \text{ mA}$$