



Faculty of Engineering

DEPARTMENT of ELECTRICAL AND ELECTRONIC ENGINEERING

EENG (INFE)115 Introduction to Logic Design

Instructors:

M. K. Uygurođlu
H. Abou Rajab

Final EXAMINATION

January 14, 2016

Duration: 120 minutes

Number of Questions: 4

Good Luck

| STUDENT'S | |
|-----------|-----------|
| NUMBER | |
| NAME | SOLUTIONS |
| SURNAME | |


| Question | | Points |
|--------------|--|--------|
| 1 | | 30 |
| 2 | | 30 |
| 3 | | 30 |
| 4 | | 30 |
| <i>TOTAL</i> | | 120 |

Read the following instructions carefully:

1. **Calculators** are not allowed.
2. Switch off **mobile phones** and **do not borrow** any stationery from your friends.
3. In your solutions, **show all details** you claim credit for.

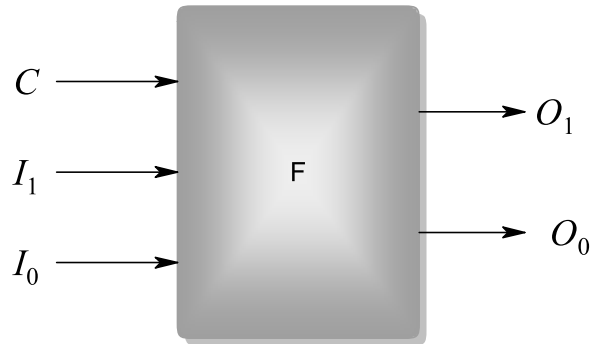Question 1

A combinational circuit has three inputs (C, I_1, I_0) and two outputs (O_1, O_0):



The function implemented by F is the following: If $C=0$, then O_1O_0 becomes I_1I_0 . If $C=1$, then O_1O_0 becomes $(I_1I_0)+1$. For example, if $C=1$ and I_1I_0 is 01, O_1O_0 becomes 10. Note that if I_1I_0 is 11 and $C=1$, then the output value wraps around 00, without any overflow.

a) Fill the Truth Table.

| C | I_1 | I_0 | O_1 | O_0 |
|-----|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |

b) Write the Boolean expression for O_1 and O_0 in sum of minterms form.

$$O_1 = \sum(2, 3, 5, 6)$$

$$O_0 = \sum(1, 3, 4, 6)$$

c) Fill in the K-Maps for O_1 and O_0 , and find the Boolean expression for the minimum sum of products implementation.


| | | | | |
|-----------|----|----|----|----|
| $I_1 I_0$ | 00 | 01 | 11 | 10 |
| C | | | | |
| 0 | | | 1 | 1 |
| 1 | | 1 | | 1 |

$$O_1 = C'I_1 + I_1I'_0 + CI'_1I_0 = I_1 \oplus (CI_0)$$


| | | | | |
|-----------|----|----|----|----|
| $I_1 I_0$ | 00 | 01 | 11 | 10 |
| C | | | | |
| 0 | | 1 | 1 | |
| 1 | 1 | | | 1 |

$$O_0 = C'I_0 + CI'_0 = C \oplus I_0$$

 d) Draw the logic diagram for O_1 and O_0 . Then convert all gates with NAND gates.



≡

 


Question 2

Implement the following Boolean function with a 4×1 multiplexer, a 2-to-4-line decoder, two inverters and an OR gate.

$$F(A, B, C, D) = ABC' + AB'C + ABD' + AB'D + A'B'CD' + A'BCD + A'B'C'D$$

Connect inputs *A* and *B* to the selection lines of the multiplexer.

| A | B | C | D | F | |
|---|---|---|---|---|-------------------------|
| 0 | 0 | 0 | 0 | 0 | $I_0 = C'D + CD'$ |
| 0 | 0 | 0 | 1 | 1 | |
| 0 | 0 | 1 | 0 | 1 | |
| 0 | 0 | 1 | 1 | 0 | |
| 0 | 1 | 0 | 0 | 0 | $I_1 = CD$ |
| 0 | 1 | 0 | 1 | 0 | |
| 0 | 1 | 1 | 0 | 0 | |
| 0 | 1 | 1 | 1 | 1 | |
| 1 | 0 | 0 | 0 | 0 | $I_2 = C + D = (C'D)'$ |
| 1 | 0 | 0 | 1 | 1 | |
| 1 | 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 1 | 1 | |
| 1 | 1 | 0 | 0 | 1 | $I_3 = C' + D' = (CD)'$ |
| 1 | 1 | 0 | 1 | 1 | |
| 1 | 1 | 1 | 0 | 1 | |
| 1 | 1 | 1 | 1 | 0 | |

 

Question 3

Use T flip-flops to design a synchronous decimal counter that counts the repeated Excess-3 binary sequence; 0011 to 1100. Treat unused states as don't care conditions.

| Present State | | | | Next State | | | | Flip-Flop Inputs | | | |
|---------------|---|---|---|------------|---|---|---|------------------|----------------|----------------|----------------|
| A | B | C | D | A | B | C | D | T _A | T _B | T _C | T _D |
| 0 | 0 | 0 | 0 | | | | | X | X | X | X |
| 0 | 0 | 0 | 1 | | | | | X | X | X | X |
| 0 | 0 | 1 | 0 | | | | | X | X | X | X |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | | | | | X | X | X | X |
| 1 | 1 | 1 | 0 | | | | | X | X | X | X |
| 1 | 1 | 1 | 1 | | | | | X | X | X | X |

| | | | | | |
|----|----|----|----|----|----|
| | | CD | | | |
| | | 00 | 01 | 11 | 10 |
| AB | 00 | x | x | 1 | x |
| | 01 | 1 | 1 | 1 | 1 |
| | 11 | 1 | x | x | x |
| | 10 | 1 | 1 | 1 | 1 |

$T_D = 1$

| | | | | | |
|----|----|----|----|----|----|
| | | CD | | | |
| | | 00 | 01 | 11 | 10 |
| AB | 00 | x | x | 1 | x |
| | 01 | 0 | 1 | 1 | 0 |
| | 11 | 1 | x | x | x |
| | 10 | 0 | 1 | 1 | 0 |


$T_C = AB + D$

| | | | | | |
|----|----|----|----|----|----|
| | | CD | | | |
| | | 00 | 01 | 11 | 10 |
| AB | 00 | x | x | 1 | x |
| | 01 | 0 | 0 | 1 | 0 |
| | 11 | 1 | x | x | x |
| | 10 | 0 | 0 | 1 | 0 |

$T_B = CD + AB$

| | | | | | |
|----|----|----|----|----|----|
| | | CD | | | |
| | | 00 | 01 | 11 | 10 |
| AB | 00 | x | x | 0 | x |
| | 01 | 0 | 0 | 1 | 0 |
| | 11 | 1 | x | x | x |
| | 10 | 0 | 0 | 0 | 0 |

$T_A = AB + BCD$

 

Question 4

Consider the synchronous sequential circuit whose state table is given below. The circuit has one input x and one output y. Design the circuit using

- D flip-flops.**
- T flip-flops**
- Which design is simpler; i.e.; uses less number of gates, (a) or (b)?

| Present State | | Input | Next State | | Output | Flip-Flop Inputs | | | |
|---------------|---|-------|------------|---|--------|------------------|----------------|----------------|----------------|
| A | B | x | A | B | y | D _A | D _B | T _A | T _B |
| 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |

| A \ Bx | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 |

$D_A = A'x'$

| A \ Bx | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |


$D_B = A'B'x + AB + Bx' = B \oplus (A'x)$

| A \ Bx | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

$T_A = A + x'$

| A \ Bx | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |

$T_B = A'x$

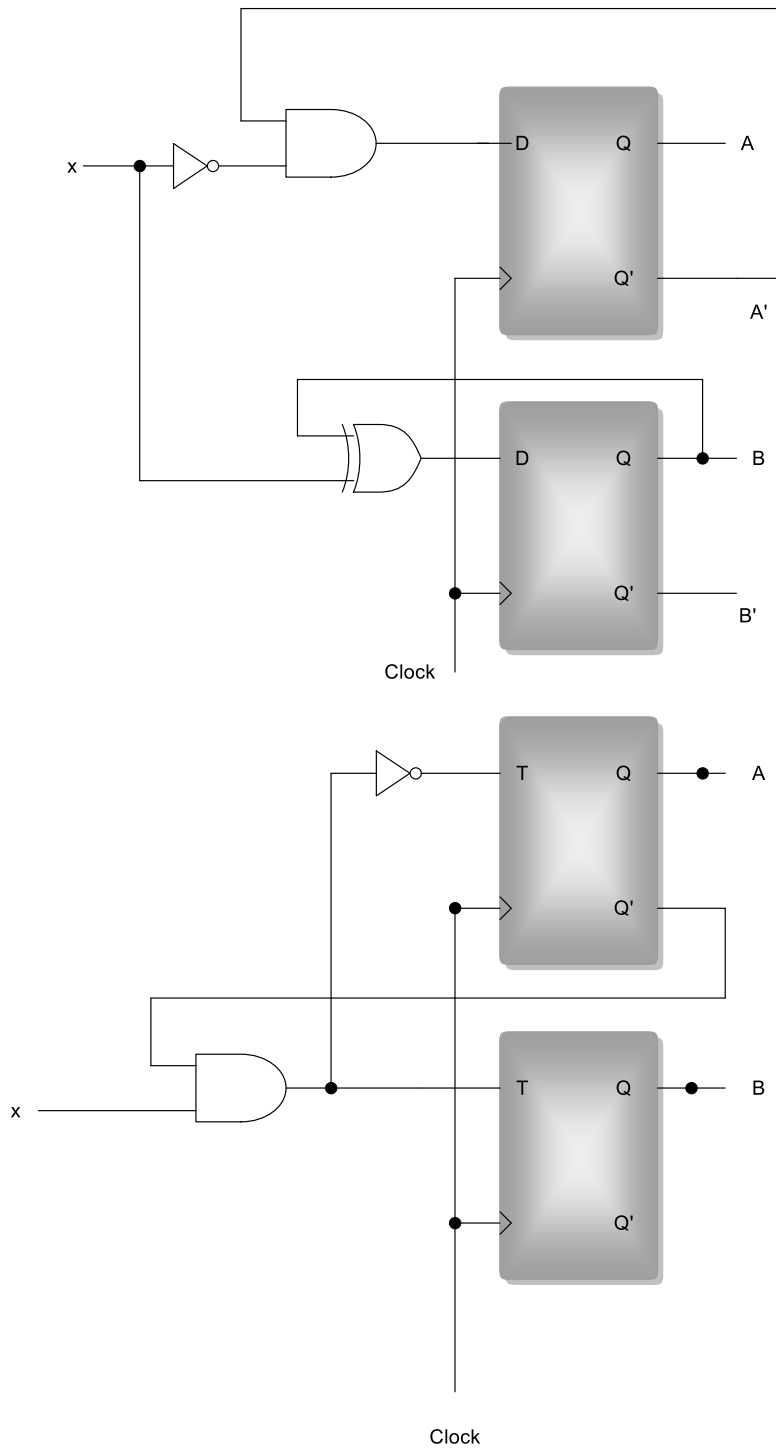

T design is simpler than D design.