



Eastern Mediterranean University

"For Your International Career"

Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

INFE221 – Electrical Circuits

**Final Exam
Fall 2015-16**

16 January 2015
Duration: 120 minutes

Instructor: M. K. Uyguroğlu

STUDENT'S	
NUMBER	
NAME	SOLUTIONS
SURNAME	

Problem		Points
1		25
2		25
3		25
4		25
TOTAL		100

Problem 1

Determine the output voltage V_o in the circuit of Fig. P1

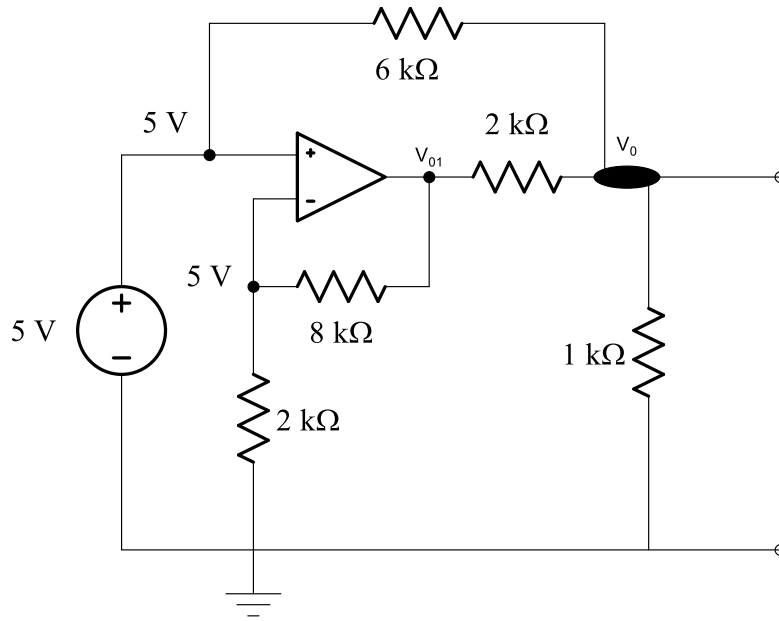


Figure P1

KCL at inverting input terminal yields:

$$\frac{5}{2k} + \frac{5 - V_{o1}}{8k} = 0$$

Multiply both sides by $8k$

$$20 + 5 - V_{o1} = 0 \Rightarrow \boxed{V_{o1} = 25 \text{ V}}$$

KCL at V_o :

$$\frac{V_o - 5}{6k} + \frac{V_o}{1k} + \frac{V_o - V_{o1}}{2k} = 0$$

Multiply both sides by $6k$ and substitute the value of V_{o1} :

$$V_o - 5 + 6V_o + 3V_o - 75 = 0$$

$$10V_o = 80$$

$$\boxed{V_o = 8 \text{ V}}$$

Problem 2

Consider the circuit in Fig. P2. Under dc conditions, find:

- (a) the power dissipated in 6Ω resistor and
- (b) the energy stored in the capacitor and the inductors.


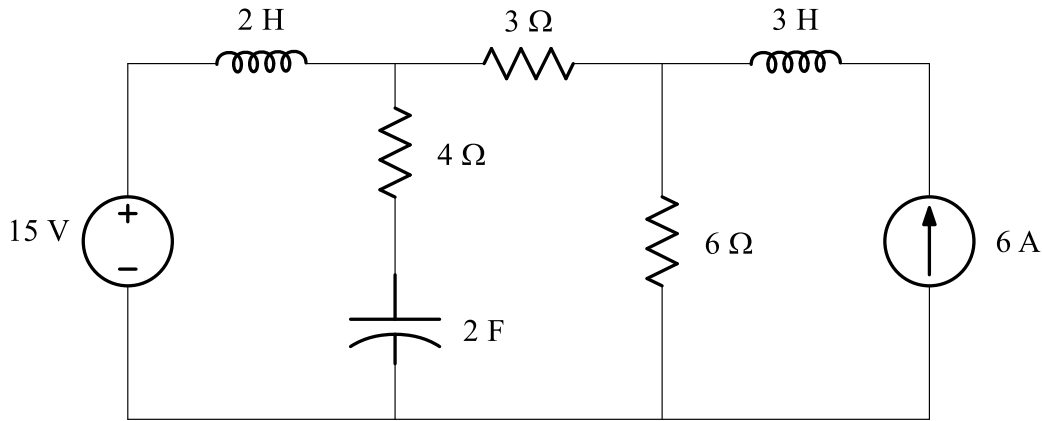


Figure P2

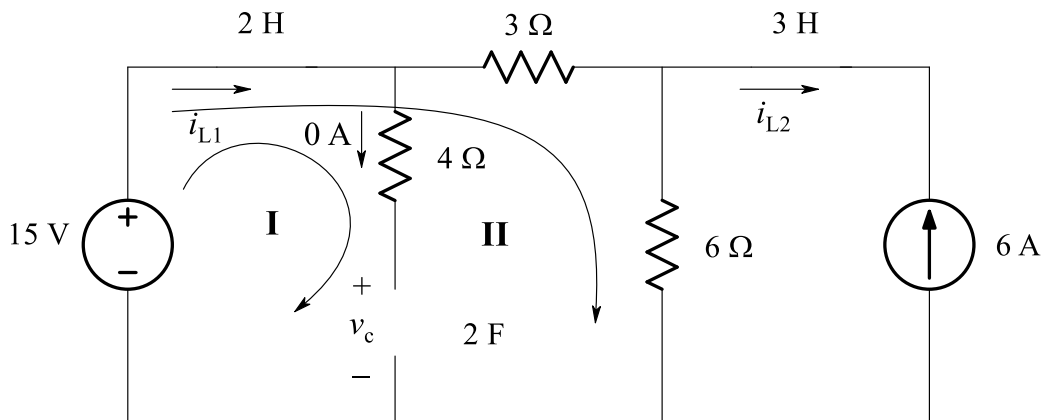Under dc conditions, Inductors act like short circuits and capacitor acts like open circuit. Therefore the circuit becomes:



KVL around loop I:

$$-15 + v_c = 0$$

$$v_c = 15 \text{ V}$$

It is obvious that $i_{L2} = -6 \text{ A}$

Now, KVL around loop II:

$$-15 + 3i_{L1} + 6(i_{L1} - i_{L2}) = 0$$

$$9i_{L1} = 15 + 6i_{L2} = 15 + 6(-6) = -21 \text{ A}$$

$$i_{L1} = \frac{-21}{9} = -\frac{7}{3} \text{ A}$$

The power dissipated in 6Ω resistor:

$$P_{6\Omega} = i^2 R = (i_{L1} - i_{L2})^2 6 = \left(-\frac{7}{3} - (-6)\right)^2 6$$

$$P_{6\Omega} = \left(\frac{11}{3}\right)^2 6 = \frac{121}{9} 6 = \frac{121}{3} 2 = \frac{242}{3} = 80.67 \text{ W}$$

The energy stored by 2 H inductor:

$$W_{2H} = \frac{1}{2} 2 \left(\frac{-7}{3}\right)^2 = \frac{49}{9} \text{ J}$$

The energy stored by 3 H inductor:

$$W_{3H} = \frac{1}{2} 3(-6)^2 = 54 \text{ J}$$

The energy stored by 2F capacitor:

$$W_{2F} = \frac{1}{2} 2(15)^2 = 225 \text{ J}$$

Problem 3

Consider the circuit in Fig.P3. Assume the switch has been open for a long time and is closed at $t = 0$.

Find

- a) $v(0)$
- b) $v(\infty)$
- c) Time constant τ .
- d) $v(t)$ for $t > 0$.


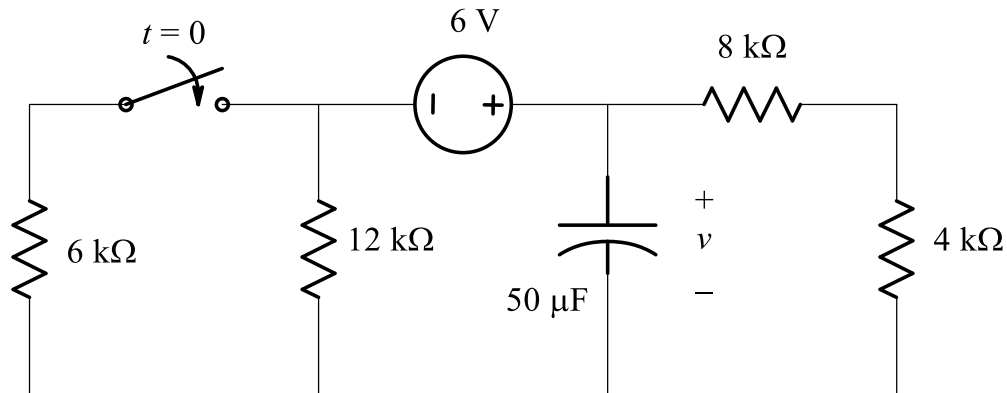


Figure P3

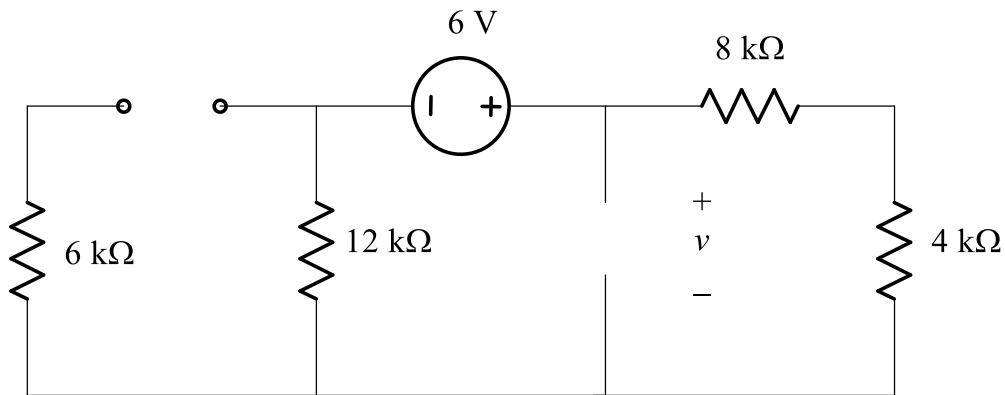At $t = 0^-$ (just before the switching action, the circuit is under dc conditions.)




It is obvious that $v(0^-)$ is the voltage across $8k\Omega$ and $4k\Omega$ resistors. Therefore using voltage division principle:

$$v(0^-) = 6 \times \frac{(8k + 4k)}{8k + 4k + 12k} = 3 \text{ V}$$

Since the capacitor voltage cannot change instantaneously,

$$v(0^+) = v(0^-) = v(0)$$

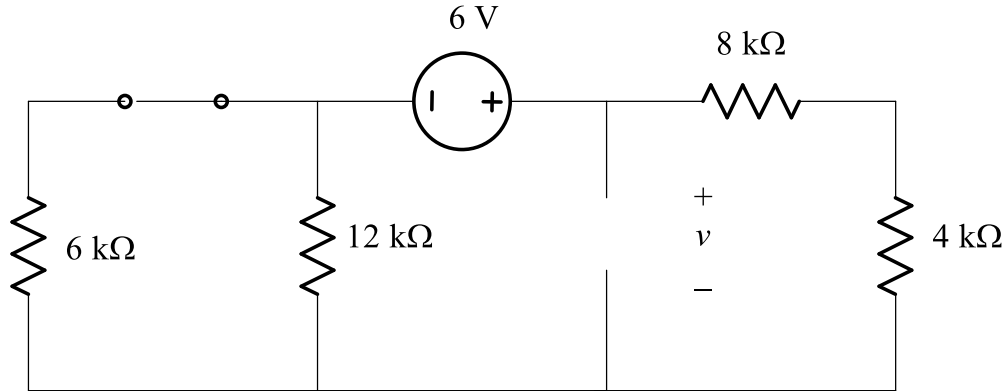At $t = \infty$ the circuit is under dc conditions as well.



$6k\Omega$ and $12k\Omega$ resistors are in parallel.

$$6k // 12k = \frac{6k \times 12k}{6k + 12k} = 4k$$


Therefore

$$v(\infty) = 6 \times \frac{8k + 4k}{8k + 4k + 4k} = 6 \times \frac{12}{16} = \frac{72}{16} = 4.5 \text{ V}$$

Time constant τ is:

$$\tau = R_{eq} C$$

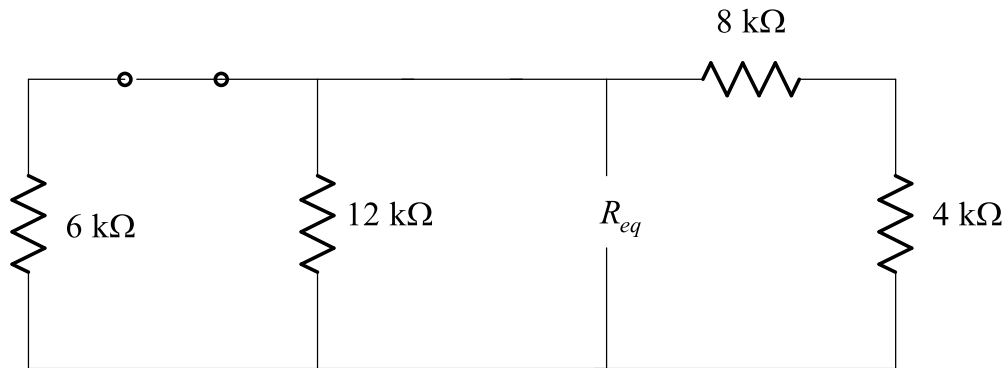In order to find R_{eq} all independent sources are set to zero.



$$R_{eq} = 12k // 6k // (8k + 4k) = 3k$$

$$\tau = 3k \times 50\mu = 150ms$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-\frac{t}{\tau}} = 4.5 + [3 - 4.5] e^{-\frac{t}{150m}} = 4.5 - 1.5e^{-\frac{t}{150m}} = 1.5 \left(3 - e^{-\frac{t}{150m}} \right)$$

Problem 4

Determine i_x in the circuit of Fig. P4 using the phasor approach and superposition principle.


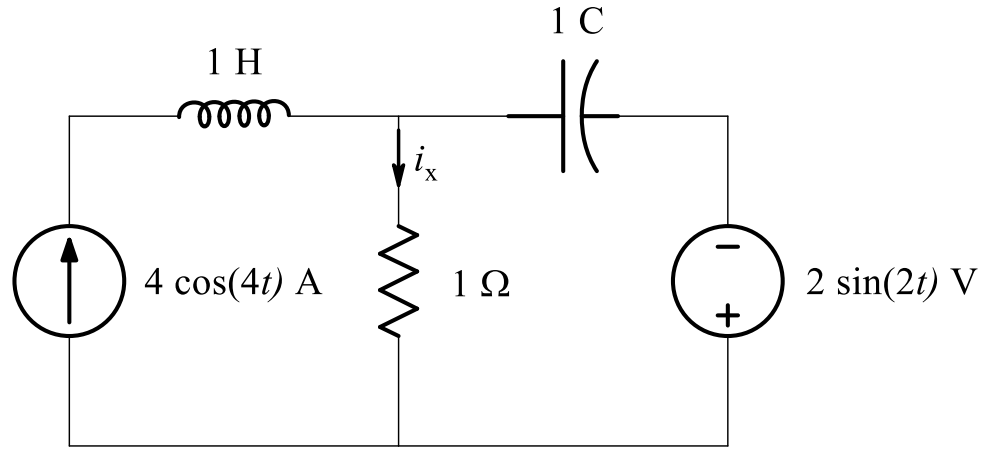


Figure P4

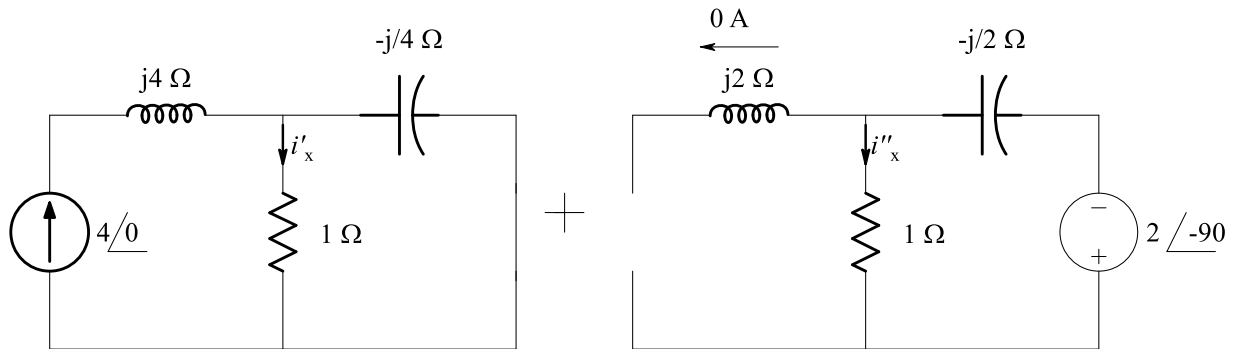

Using current division principle:

$$I'_x = \frac{4\angle 0 \left(\frac{-j}{4} \right)}{1 - \frac{j}{4}} = \frac{4\angle 0 \times \frac{1}{4} \angle -90}{1.0308 \angle -14.036} = \frac{1 \angle -90}{1.0308 \angle -14.036} = 0.97 \angle -75.96$$

$$i'_x = 0.96 \cos(4t - 75.96)$$

In order to find i''_x :

$$I''_x = -\frac{2 \angle -90}{1 - \frac{j}{2}} = -\frac{2 \angle -90}{1.118 \angle -26.565} = -1.79 \angle -63.435 = 1.79 \angle 116.565$$

$$i''_x = 1.79 \cos(2t + 116.565)$$

$$i''_x = 1.79 \sin(2t + 116.565 + 90) = 1.79 \sin(2t + 206.565)$$

Therefore

INFE221 Electric Circuits – Final Exam

$$i_x = i'_x + i''_x = 0.96 \cos(4t - 75.96) + 1.79 \sin(2t + 206.565)$$