



Eastern Mediterranean University

"For Your International Career"

Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

INFE221 – Electrical Circuits

**Final Examination
Fall 2016-17**

04 January 2017
Duration: 120 minutes

Instructor: M. K. Uyguroğlu

STUDENT'S	
NUMBER	
NAME	SOLUTIONS
SURNAME	

Problem		Points
1		30
2		30
3		30
4		30
TOTAL		120

Problem 1

The variable resistor in the circuit in Fig.P1 is adjusted for the maximum power transfer to R_0 .

- a) Find the value of R_0 .
- b) Find the maximum power that can be delivered to R_0 .


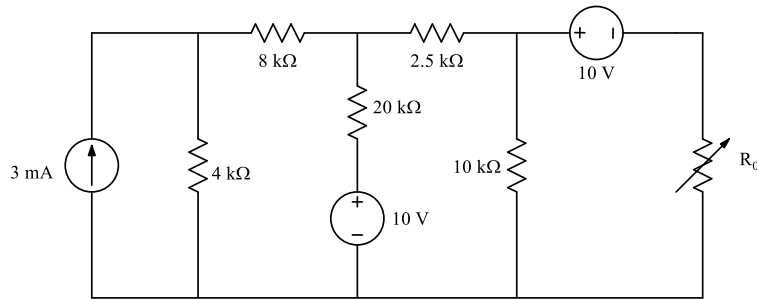


Figure P 1

When $R_0 = R_{TH}$ it will absorb maximum power.

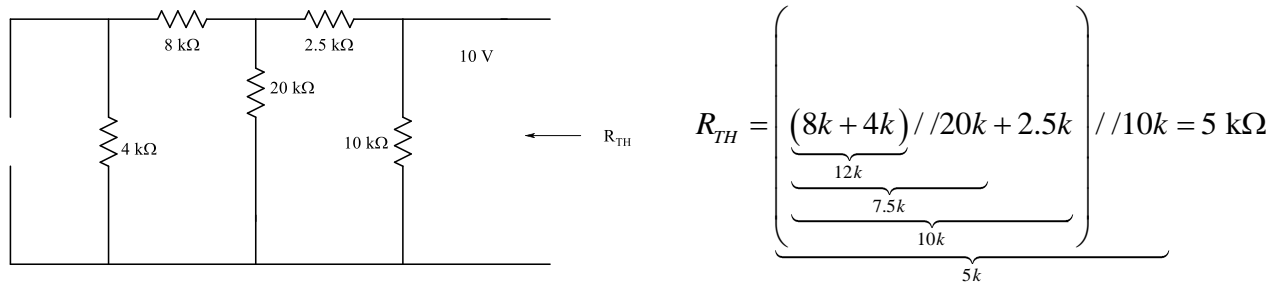
In order to find R_{TH} , set all independent source values to zero.



Therefore when $R_0 = 5\text{ k}\Omega$ it will absorb maximum power.

Maximum Power $P_{\max} = \frac{V_{TH}^2}{4R_{TH}}$

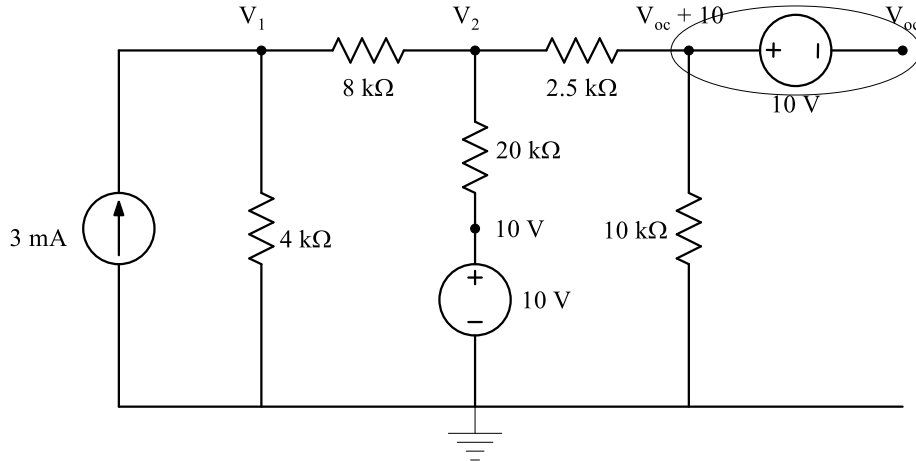For V_{TH} , open circuit voltage will be found.



KCL at V_1 :

$$\frac{V_1}{4k} + \frac{V_1 - V_2}{8k} = 3m \text{ multiply both sides by } 8k: 3V_1 - V_2 = 24 \dots (1)$$

KCL at V_2 :

$$\frac{V_2 - V_1}{8k} + \frac{V_2 - 10}{20k} + \frac{V_2 - V_{oc} - 10}{2.5k} = 0 \text{ multiply both sides by } 40k: 23V_2 - 5V_1 - 16V_{oc} = 180 \dots (2)$$

KCL at $V_{oc} + 10$:

$$\frac{V_{oc} + 10 - V_2}{2.5k} + \frac{V_{oc} + 10}{10k} = 0 \text{ multiply both sides by } 10k: 5V_{oc} - 4V_2 = -50 \dots (3)$$

$$\boxed{V_2 = \frac{5V_{oc} + 50}{4}} \dots (4)$$

Subst. of Eq. (4) into (1) and (2) yields:

$$3V_1 - \frac{5}{4}V_{oc} = 36.5$$

$$-5V_1 + \left(\frac{115}{4} - 16\right)V_{oc} = 180 - \frac{1150}{4} \Rightarrow -5V_1 + 12.75V_{oc} = -107.5$$

or

$$15V_1 - 6.25V_{oc} = 182.5$$

$$-15V_1 + 38.25V_{oc} = -322.5$$

$$32V_{oc} = -140$$

$$V_{oc} = -\frac{140}{32} = -4.375V$$

$$P_{\max} = \frac{(-4.375)^2}{4 \times 5k} = 0.957mW$$

Problem 2

The two op amps in the circuit in Fig. P2 are ideal. Calculate v_{01} and v_{02} .

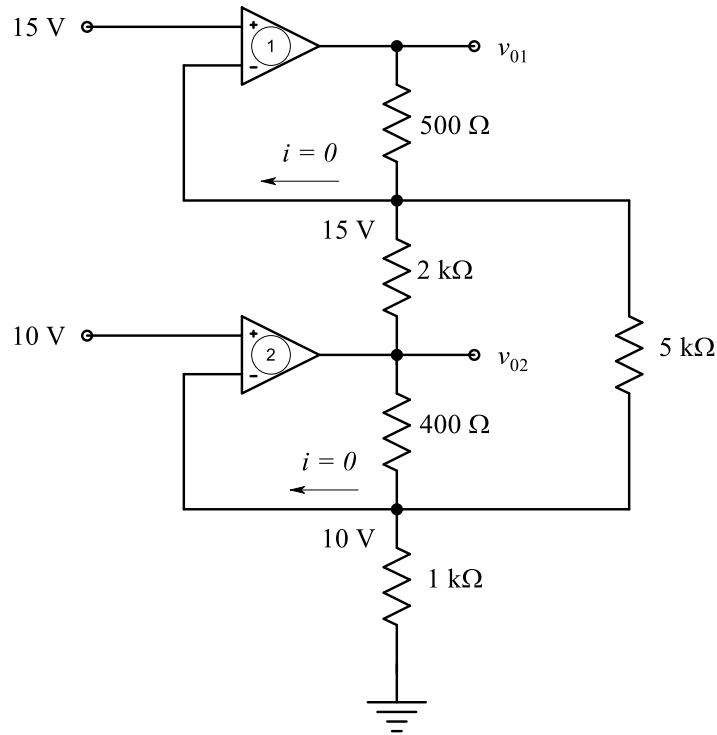


Figure P 2

KCL at inverting input terminal of op amp 2:

$$\frac{10}{1k} + \frac{10 - v_{02}}{0.4k} + \frac{10 - 15}{5k} = 0$$

Multiply both sides by 20k gives:

$$200 + 500 - 50v_{02} + 40 - 60 = 0$$

$$50v_{02} = 680$$

$$v_{02} = 13.6 \text{ V}$$

KCL at the inverting input terminal of op amp 1:

$$\frac{15 - 13.6}{2k} + \frac{15 - 10}{5k} + \frac{15 - v_{01}}{0.5k} = 0$$

Multiply both sides by 10k gives:

$$7 + 10 + 300 - 20v_{01} = 0$$

$$v_{01} = \frac{317}{20} = 15.85 \text{ V}$$

Problem 3

The switch in the circuit shown in Fig. P3 has been open for a long time. The initial charge on the capacitor is zero. At $t = 0$, the switch is closed. Find

- a) $i(t)$ for $t > 0$.
- b) $v(t)$ for $t > 0$.


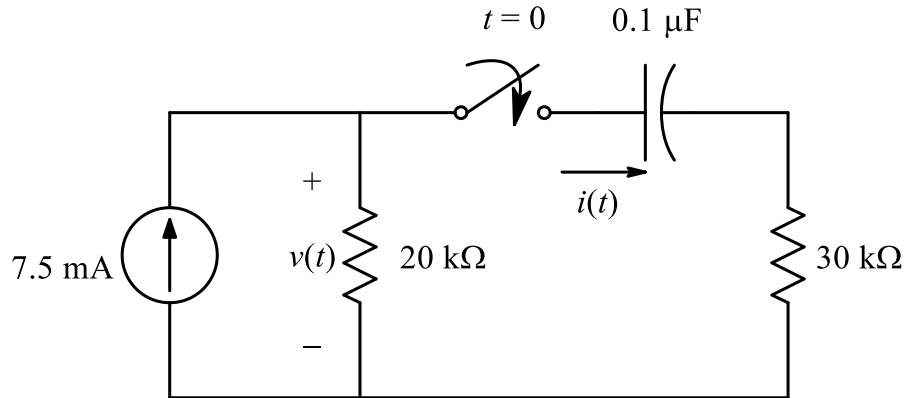


Figure P 3

For $t > 0$:

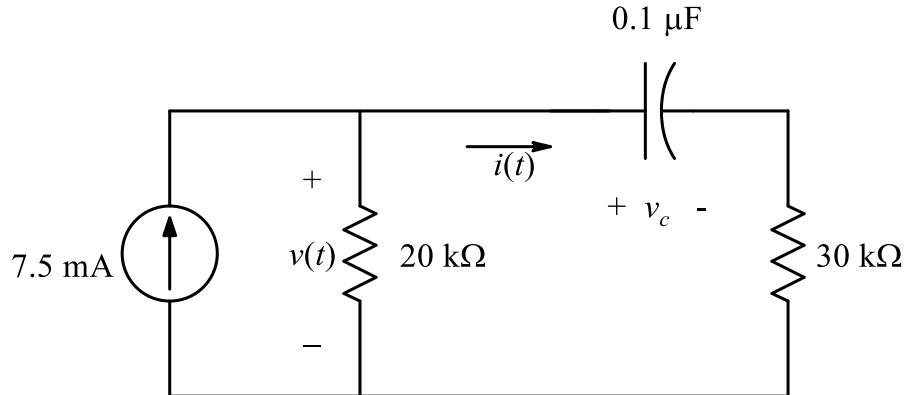

Since there is a DC source in the circuit for $t > 0$, the voltage across the capacitor will be

$$v_c(t) = v_c(\infty) + [v_c(0) - v_c(\infty)]e^{-\frac{t}{\tau}}$$


Where $v_c(0) = 0$ (capacitor is initially uncharged) and $\tau = R_{eq}C$

Equivalent resistance seen by the capacitor is

$$R_{eq} = 20k + 30k = 50k\Omega$$

$$\tau = R_{eq}C = 50k \times 0.1\mu = 5ms.$$

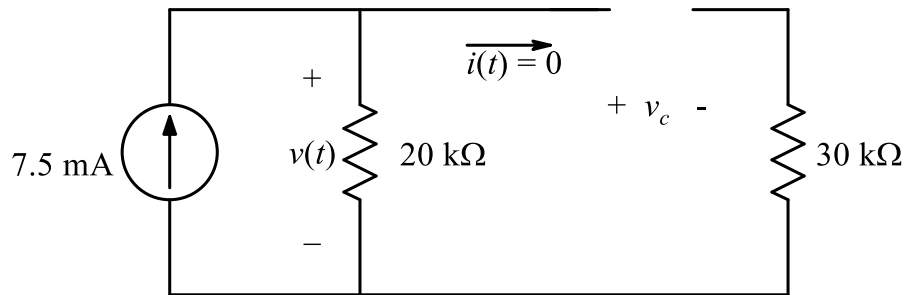At $t = \infty$ the circuit is under dc conditions.




$$v(\infty) = v_c(\infty) = 7.5m \times 20k = 150 \text{ V}$$

Therefore

$$v_c(t) = 150 + [0 - 150]e^{-200t} \text{ V}$$
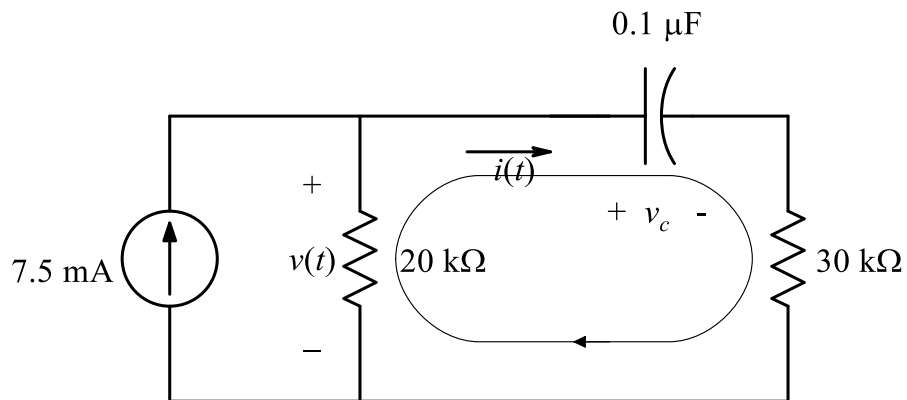
$$i(t) = C \frac{dv_c}{dt} = 0.1 \times 10^{-6} \times 30 \times 10^3 e^{-200t} = 3e^{-200t} \text{ mA.}$$



KVL around the loop:

$$v(t) = v_c(t) + i(t)30k = 150 - 150e^{-200t} + 90e^{-200t}$$

$$v(t) = 150 - 60e^{-200t} \text{ V}$$

Problem 4

The circuit in Fig. P4 is operating in the sinusoidal steady state. Find $v_0(t)$ if $i_s = 3 \cos 200t$ mA.

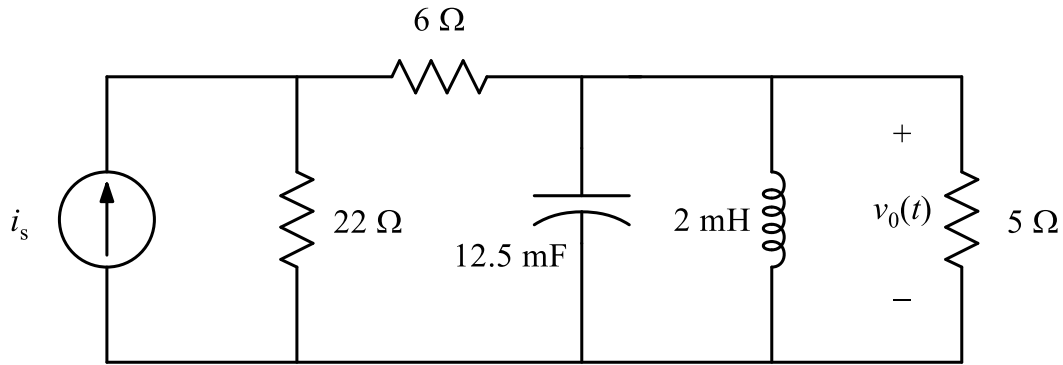


Figure P 4

Given:

Time domain representation	Phasor domain representation
$V_m \cos(\omega t + \phi)$	$V_m \angle \phi$
$\frac{dv}{dt}$	$j\omega \mathbf{V}$
$\int v dt$	$\frac{\mathbf{V}}{j\omega}$

In phasor domain:

$$\omega = 200 \text{ rad/s}$$

$$i_s(t) = 3 \cos 200t \text{ mA} \rightarrow \mathbf{I}_s = 3 \angle 0 \text{ mA}$$

$$6\Omega \rightarrow 6\Omega$$


$$22\Omega \rightarrow 22\Omega$$

$$5\Omega \rightarrow 5\Omega$$

$$12.5 \text{ mF} \rightarrow \frac{1}{j200 \times 12.5 \times 10^{-3}} = -j0.4\Omega$$

$$2 \text{ mH} \rightarrow j200 \times 2 \times 10^{-3} = j0.4\Omega$$

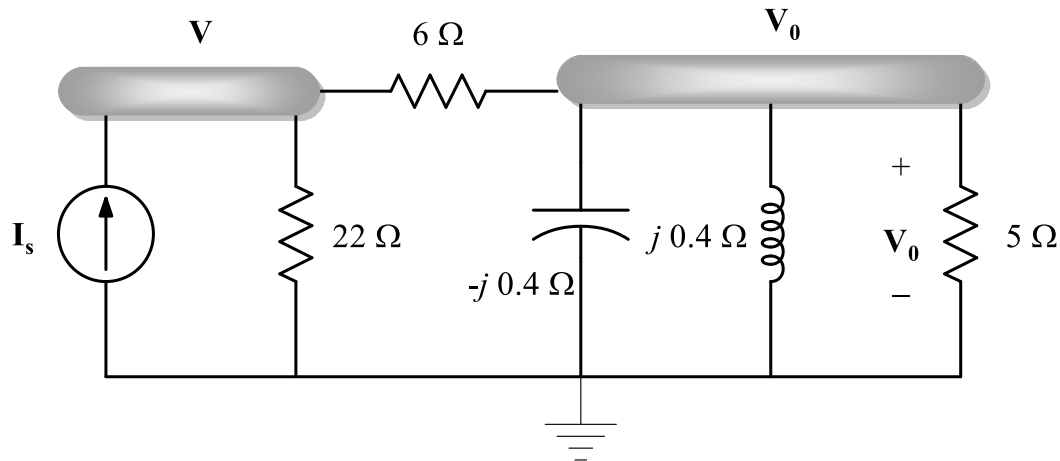Therefore, in phasor domain, the circuit will be



KCL at V:

$$\frac{V}{22} + \frac{V - V_0}{6} = 3 \text{ m} = 3 \text{ m}$$

Multiply both sides by 66:

$$14V - 11V_0 = 198 \text{ m} \dots (1)$$

KCL at V₀:

$$\frac{V_0}{-j0.4} + \frac{V_0}{j0.4} + \frac{V_0}{5} + \frac{V_0 - V}{6} = 0$$

Multiply both sides by 30:

$$-5V + 11V_0 = 0 \dots (2)$$

The addition of Eqns.(1) and (2) yields:

$$9V = 198 \text{ m}$$

$$V = 22 \text{ mV}$$

Using Equation (2)

$$V_0 = \frac{5}{11} V = 10 \text{ mV} \Rightarrow v_0(t) = 10 \cos(200t) \text{ mV}.$$