

HOMEWORK II - ANSWERS

**DUE: Group1, Wednesday 24 MAY 2017 and Group2, Thursday 25 MAY 2017
Tuesday!**

1. Design a combinational code converter that converts a **4-bit** gray code to binary number. (20 pts.)

Decimal	Gray Code				Binary			
	A	B	C	D	w	x	y	z
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	1	0	0	1	0
3	0	0	1	0	0	0	1	1
4	0	1	1	0	0	1	0	0
5	0	1	1	1	0	1	0	1
6	0	1	0	1	0	1	1	0
7	0	1	0	0	0	1	1	1
8	1	1	0	0	1	0	0	0
9	1	1	0	1	1	0	0	1
10	1	1	1	1	1	0	1	0
11	1	1	1	0	1	0	1	1
12	1	0	1	0	1	1	0	0
13	1	0	1	1	1	1	0	1
14	1	0	0	1	1	1	1	0
15	1	0	0	0	1	1	1	1

w's K-MAP



		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	1	1	1	1

$x = A$

x's K - MAP

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	0	0	1	0
	10	1	1	1	1

$x = A'B + AB' = A \oplus B$

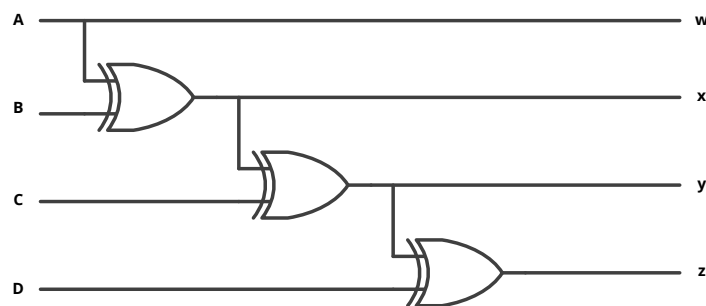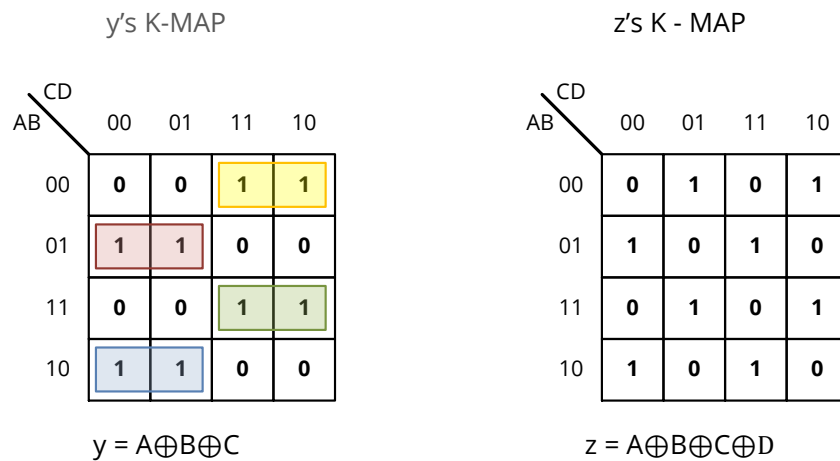

2. Design a combinational circuit with three inputs, A , B , and C , and three outputs, x , y , and z . When the binary input is 0, 1, 2, or 3, the binary output is one greater than the input. When the binary input is 4, 5, 6, or 7, the binary output is two less than the input. **(16 pts.)**

A	B	C	x	y	z
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	1	0	0
1	1	1	1	0	1

x's K-MAP

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	0	0	1	1

$$x = BC + AB$$

y's K - MAP


		BC			
		00	01	11	10
A	0	0	1	0	1
	1	1	1	0	0

$$y = AB' + B'C + A'BC'$$

z's K-MAP


		BC			
		00	01	11	10
A	0	1	0	0	1
	1	0	1	1	0

$$z = AC + A'C'$$

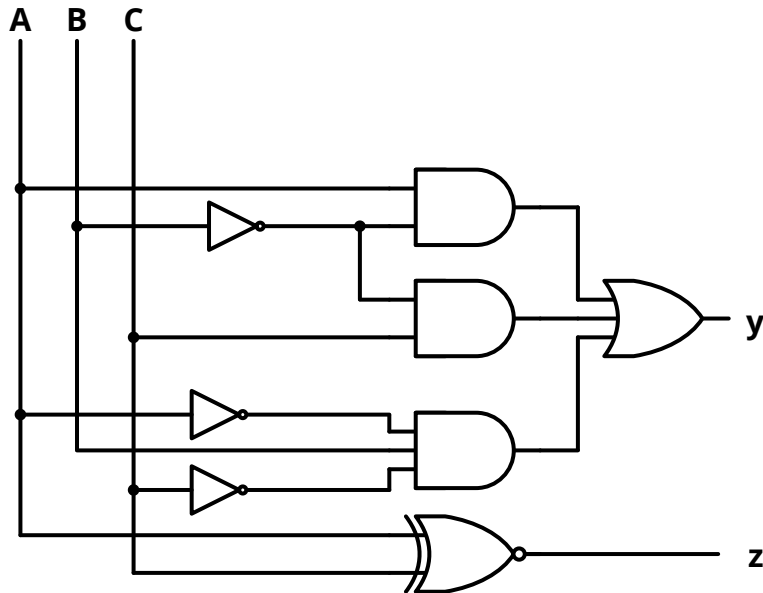

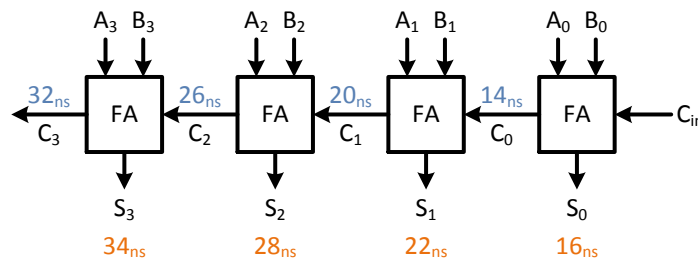3. Assume that the exclusive-OR gate has a propagation delay of 8 ns and that the AND or OR gates have a propagation delay of 3 ns. What is the total propagation delay time in the four-bit adder? (4 pts.)

- From A_i/B_i to C_{i+1} : 3 gate - levels (XOR \rightarrow AND \rightarrow OR) = $(8 + 3 + 3)_{ns} = 14ns$
- From A_i/B_i to S_i : 2 gate - levels (XOR \rightarrow XOR) = $(8 + 8)_{ns} = 16ns$
- From C_i/C_{i+1} : 2 gate levels (AND \rightarrow OR) = $(3+3)_{ns} = 6ns$
- Total Propagation delay time for a 4-bit adder:




4. Implement the following Boolean function with a **8x1 multiplexer**, a **2-to-4-line decoder**, **3 x inverters** and a **OR-gate**. (20 pts.)

$$F(A, B, C, D, E) = \sum (0,1,2,3,5,6,7,8,9,10,13,14,16,19,23,24)$$


A	B	C	D	E	F	
0	0	0	0	0	1	1
0	0	0	0	1	1	
0	0	0	1	0	1	
0	0	0	1	1	1	$D + E = (D'.E')$
0	0	1	0	0	0	
0	0	1	1	0	1	
0	0	1	1	1	1	
0	1	0	0	0	1	$(D.E)'$
0	1	0	0	1	1	
0	1	0	1	0	1	
0	1	0	1	1	0	$D'.E+D.E'$
0	1	1	0	0	0	
0	1	1	0	1	1	
0	1	1	1	0	1	
0	1	1	1	1	0	$(D'.E+D.E)'$
1	0	0	0	0	1	
1	0	0	0	1	0	

1	0	0	1	0	0	
1	0	0	1	1	1	
1	0	1	0	0	0	
1	0	1	0	1	0	D.E
1	0	1	1	0	0	
1	0	1	1	1	1	
1	1	0	0	0	1	D'E'
1	1	0	0	1	0	
1	1	0	1	0	0	
1	1	0	1	1	0	
1	1	1	0	0	0	0
1	1	1	0	1	0	
1	1	1	1	0	0	
1	1	1	1	1	0	
1	1	1	1	1	0	

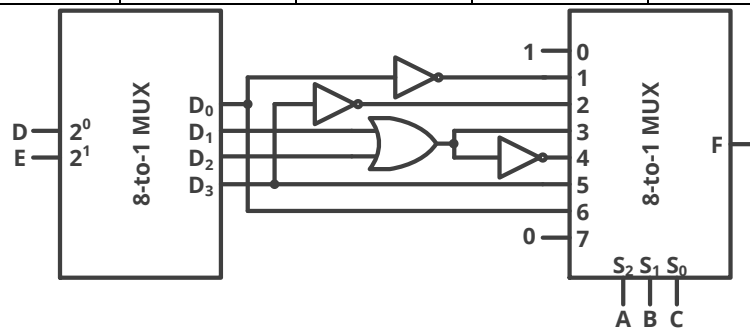

5. Sequential circuit that has two flip-flops A and B and one input x and a constant '1'. It consists of a combinatorial logic connected to the JK flip-flops, as shown in Figure below.
- Derive the next state and output equations.
 - Derive the state table of the sequential circuit.
 - Draw the corresponding state diagram.

(20 pts.)

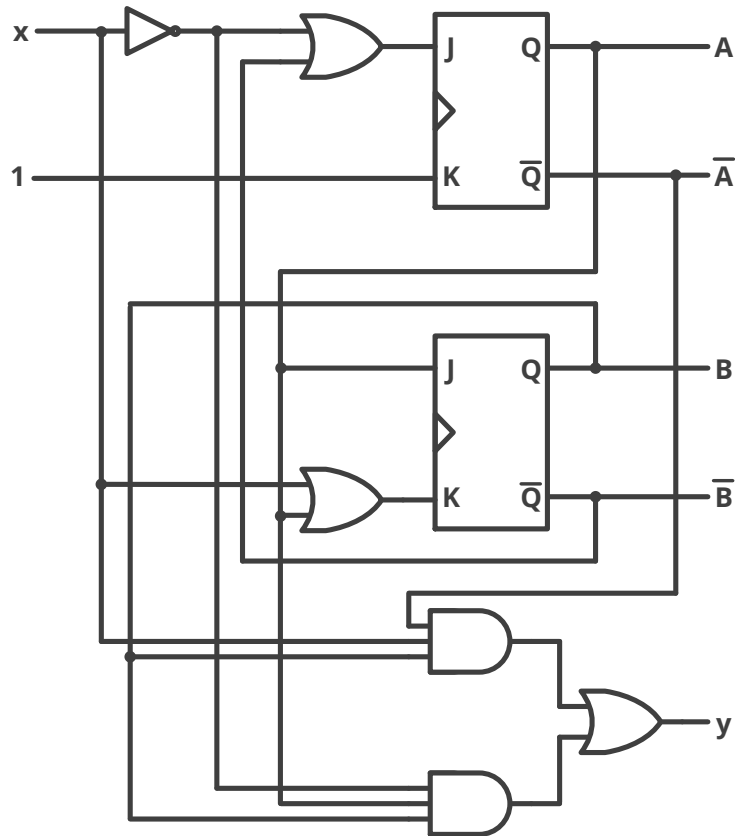

a)

- $JA = B' + x', JB = A$
- $KA = 1, KB = A + x$
- $y = A'.B.x + A.B.x'$
- $QA(t+1) = JA.A' + KA'A = (B'+x')A' + (0)A$
 $= A'B' + A'x'$
- $QB(t+1) = JB.B' + KB'B = A.B' + (A+x)'B$
 $= AB' + A'Bx'$
- $y = A'Bx + ABx'$

b)

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	1	1	0

0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	0	1	0
1	1	0	0	0	1
1	1	1	0	0	0

c)

