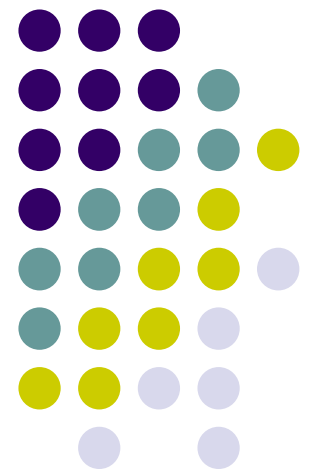



Second Order Circuits

EENG 223


Circuit

Theory I



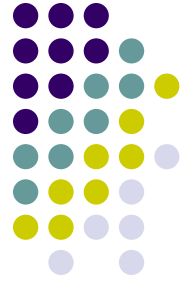


Second Order Circuits

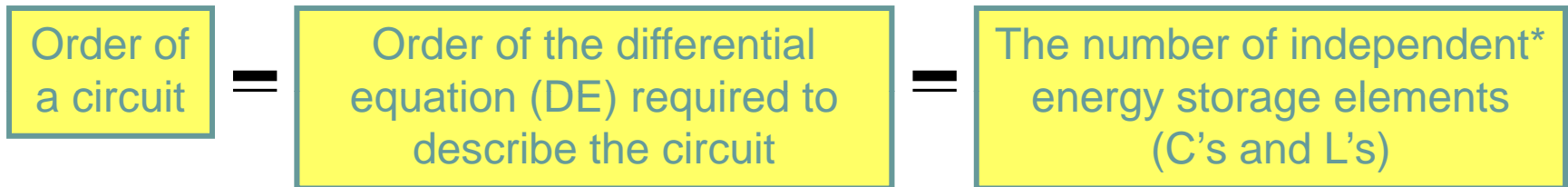

* C's and L's are independent if they cannot be combined with other C's and L's (in series or parallel, for example)


Second Order Circuits

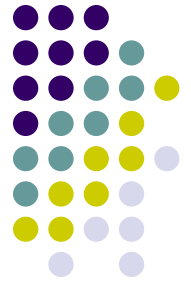

- 2nd-order circuits have 2 independent energy storage elements (inductors and/or capacitors)
- Analysis of a 2nd-order circuit yields a 2nd-order differential equation (DE)
- A 2nd-order differential equation has the form:

$$\frac{d^2x}{dt^2} + a_1 \frac{dx}{dt} + a_0 x(t) = f(t)$$

- Solution of a 2nd-order differential equation requires two initial conditions: $x(0)$ and $x'(0)$
- All higher order circuits (3rd, 4th, etc) have the same types of responses as seen in 1st-order and 2nd-order circuits
- Since 2nd-order circuits have two energy-storage types, the circuits can have the following forms:
 - 1) Two capacitors
 - 2) Two inductors
 - 3) One capacitor and one inductor
 - A) Series RLC circuit
 - B) Parallel RLC circuit
 - C) Others

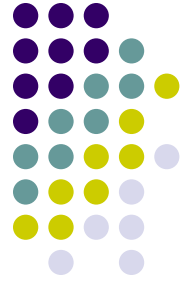

Form of the solution to differential equations

As seen with 1st-order circuits in Chapter 7, the general solution to a differential equation has two parts:

$$x(t) = x_h + x_p = \text{homogeneous solution} + \text{particular solution}$$

or $x(t) = x_n + x_f = \text{natural solution} + \text{forced solution}$


where x_h or x_n is due to the initial conditions in the circuit

and x_p or x_f is due to the forcing functions (independent voltage and current sources for $t > 0$).

The forced response

The forced response is due to the independent sources in the circuit for $t > 0$. Since the natural response will die out once the circuit reaches steady-state (under dc conditions), the forced response can be found by analyzing the circuit at $t = \infty$. In particular,

$$\mathbf{x_f = x(\infty)}$$

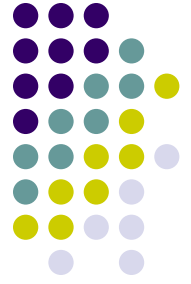

The natural response

A 2nd-order differential equation has the form:

$$\frac{d^2x}{dt^2} + a_1 \frac{dx}{dt} + a_0 x(t) = f(t)$$

where $x(t)$ is a voltage $v(t)$ or a current $i(t)$.

To find the natural response, set the forcing function $f(t)$ (the right-hand side of the DE) to zero.

$$\frac{d^2x}{dt^2} + a_1 \frac{dx}{dt} + a_0 x(t) = 0$$


Substituting the general form of the solution Ae^{st} yields the ***characteristic equation***:

$$s^2 + a_1 s + a_0 = 0$$

Finding the roots of this quadratic (called the ***characteristic roots*** or ***natural frequencies***) yields:

$$s_1, s_2 = \frac{-a_1 \pm \sqrt{(a_1)^2 - 4a_0}}{2}$$

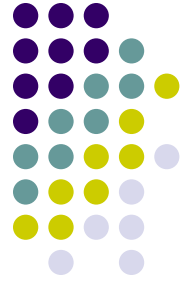The roots of the quadratic equation above may be real and distinct, repeated, or complex. Thus, the natural response to a 2nd-order circuit has 3 possible forms:




1) Overdamped response

Roots are real and distinct [$(a_1)^2 > 4a_0$]

Solution has the form:
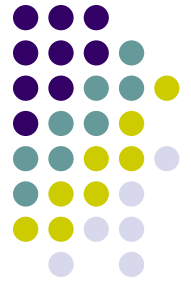
$$\mathbf{x}_n = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$




2) Critically damped response

Roots are repeated [$(a_1)^2 = 4a_0$] so $s_1 = s_2 = s = -a_1/2$

Solution has the form:

$$\mathbf{X}_n = (A_1 t + A_2) e^{st}$$

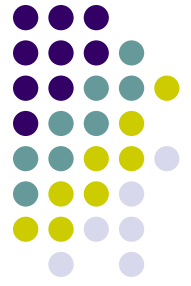

3) Underdamped response

Roots are complex [$(a_1)^2 < 4a_0$] so $s_1, s_2 = \alpha \pm j\beta$

Show that the solution has the form:

$$x_n = e^{\alpha t} \left[A_1 \cos(\beta t) + A_2 \sin(\beta t) \right]$$



Series and Parallel RLC Circuits

Two common second-order circuits are now considered:

- *series RLC circuits*
- *parallel RLC circuits.*

Relationships for these circuits can be easily developed such that the characteristic equation can be determined directly from component values without writing a differential equation for each example.


A general 2nd-order characteristic equation has the form:

A general 2nd-order characteristic equation has the form: $s^2 + 2\alpha s + w_0^2 = 0$


where


α = damping coefficient

w_0 = resonant frequency

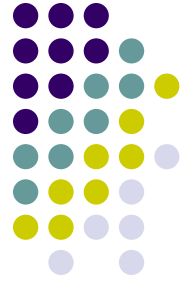


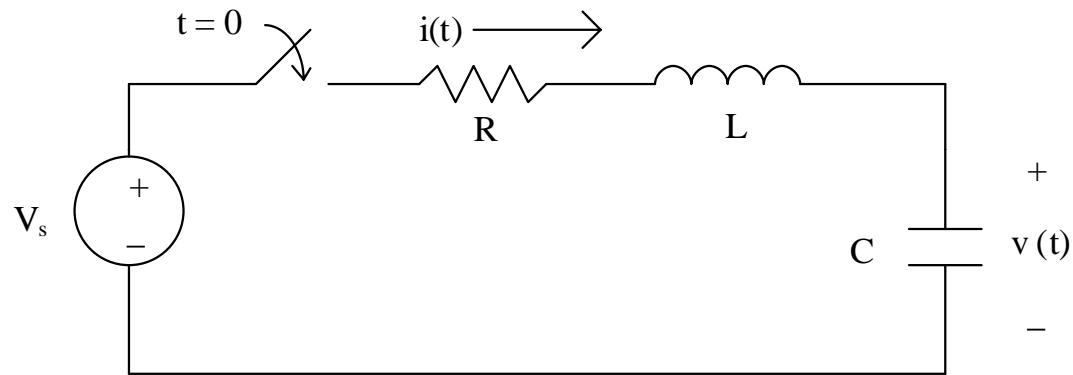
Series RLC Circuit - develop expressions for α and ω_0



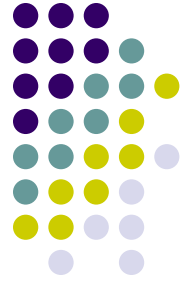

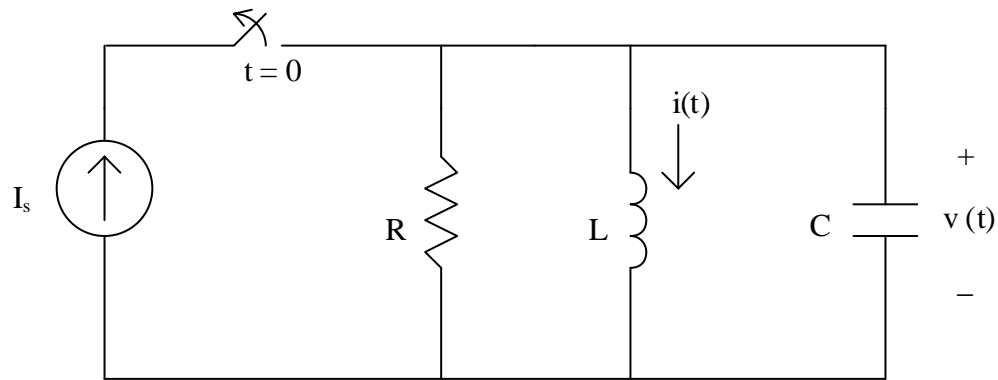Parallel RLC Circuit - develop expressions for α and ω_0



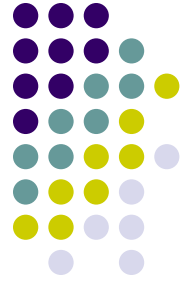

Procedure for analyzing 2nd-order circuits

1. **Find the characteristic equation and the natural response**

- A) Determine if the circuit is a series RLC or parallel RLC (for $t > 0$ with independent sources killed). If the circuit is not series RLC or parallel RLC determine the describing equation of capacitor voltage or inductor current.
- B) Obtain the characteristic equation. Use the standard formulas for α and ω_0 for a series RLC circuit or a parallel RLC circuit. Use these values of α and ω_0 in the characteristic equation as: $s^2 + 2\alpha s + \omega_0^2$.
- C) Find the roots of the characteristic equation (characteristic roots).
- D) Determine the form of the natural response based on the type of characteristic roots:

A) Real distinct roots: $x_n = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

B) Complex roots: $x_n = e^{\alpha t} [A_1 \cos(\beta t) + A_2 \sin(\beta t)]$

C) Repeated roots: $x_n = (A_1 t + A_2) e^{st}$


2. **Find the forced response** - Analyze the circuit at $t = \infty$ to find $x_f = x(\infty)$.

3. **Find the initial conditions**, $x(0)$ and $x'(0)$.

- A) Find $x(0)$ by analyzing the circuit at $t = 0^-$ (find all capacitor voltages and inductor currents)
- B) Analyze the circuit at $t = 0^+$ (use the values for v_C and i_L found at $t = 0^-$ in the circuit) and find $dv_C(0^+)/dt = i_C(0^+)/C$ or $di_L(0^+)/dt = v_L(0^+)/L$.


3. **Find the complete response**

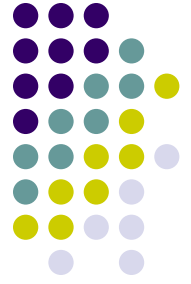
- A) Find the total response, $x(t) = x_n + x_f$.
- B) Use the two initial conditions to solve for the two unknowns in the total response.




Example: Determine $v(t)$ in the circuit shown below for $t > 0$ if :

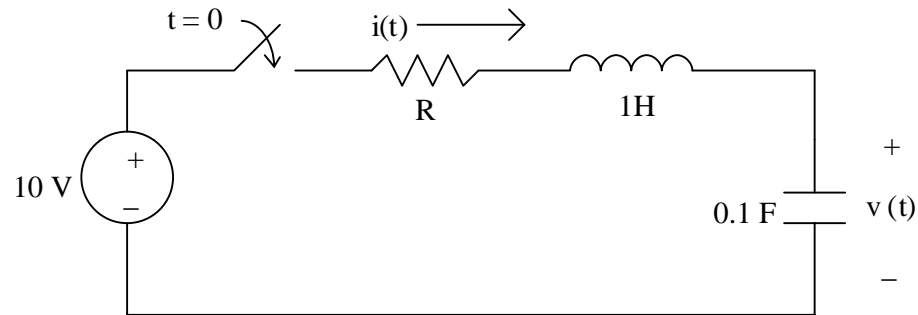- A) $R = 7$
- B) $R = 2$
- C) $R = 2\sqrt{10}$



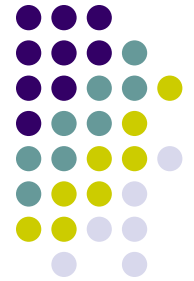

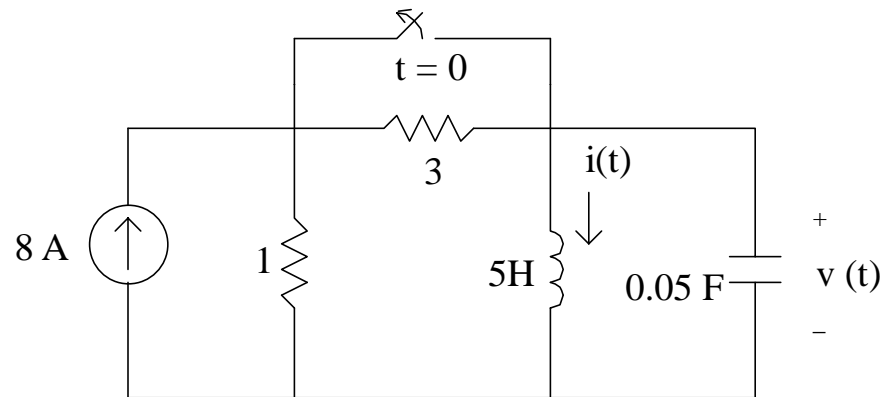Example: Determine $i(t)$ in the circuit shown below for $t > 0$.





Example: Determine $v(t)$ in the circuit shown below for $t > 0$.

