



Faculty of Engineering

DEPARTMENT of ELECTRICAL AND ELECTRONIC ENGINEERING

EENG (INFE) 115

Instructor:

Introduction to Logic Design

G. YEMİŐCIOĐLU

Midterm EXAMINATION

Duration: 90 minutes

April 8, 2017

Number of Questions: 4

Good Luck

STUDENT'S

NUMBER

NAME

SURNAME

GROUP NO.

SOLUTIONS

Question	Achieved	Points
1		25
2		25
3		25
4		25
TOTAL		100

Read the following instructions carefully:

1. Calculators are not allowed.
2. Switch off mobile phones and do not borrow any stationery from your friends.
3. In your solutions, show all details you claim credit for.

Question 1:

a) Convert $(82.6875)_{10}$ to binary. Show your steps. (5 pts.)

82	2 =	41	0	0.6875	x 2 =	1.375	1
41	2 =	20	1	0.375	x 2 =	0.75	0
20	2 =	10	0	0.75	x 2 =	1.50	1
10	2 =	5	0	0.50	x 2 =	1.00	1
5	2 =	2	1				
2	2 =	1	0				
1	2 =	0	1				
			$82 = (1010010)_2$				$0.6875 = (1011)_2$
$(1010010.1011)_2$							

b) Convert $(1011011.0101)_2$ to decimal. Show your steps. (5 pts.)

1	0	1	1	0	1	1	.	0	1	0	1
2^6	2^5	2^4	2^3	2^2	2^1	2^0	.	2^{-1}	2^{-2}	2^{-3}	2^{-4}
1x64	0	1x16	1x8	0	1x2	1	.	0	1x0.25	0	0.0625
64	+0	+16	+8	+0	+2	+1	.	+0	+0.25	+0	+0.0625
91							.	3125			

c) Convert $(6473.2510)_8$ to binary and to hexadecimal. Show your steps. (5 pts.)

6	4	7	3	.	2	5	1	0	oct
110	100	111	011	.	010	101	001	000	bin
1 1 0 1 0 0 1 1 1 0 1 1 . 0 1 0 1 0 1 0 0 1 0 0 0									
	D	3	B	.	5	4	8		hex

d) Convert +63 and +42 to binary, using the signed-2's complement representation and enough digits to accommodate the numbers. Then perform the binary equivalent of (+63) + (-42), (-63) + (+42), and (-63) + (-42). (10 pts.)

63	2 =	31		1	42	2 =	21		0
31	2 =	15		1	21	2 =	10		1
15	2 =	7		1	10	2 =	5		0
7	2 =	3		1	5	2 =	2		1
3	2 =	1		1	2	2 =	1		0
1	2 =	0		1	1	2 =	0		1

$$63 = (111111)_2$$

$$42 = (101010)_2$$

Therefore for sign 2's complement representation of

+63	00111111	-63	11000001
+42	00101010	-42	11010110

(+ 63)	00111111	
+ (- 42)	+ 11010110	
(+21) 100010101 most significant bit is discarded.		

(- 63)	11000001	
+ (+ 42)	+ 00101010	
(- 21) 11101011 signed 2's complement of -21.		

(- 63)	11000001	
+ (- 42)	+ 11010110	
(- 21) 110010111 most significant bit is discarded. The rest is signed 2's complement of -105.		


Question 2:

a) Simplify the following Boolean function $F(x,y,z) = x'y'z' + x'y + xyz' + xz$ to a minimum number of literals using **algebraic manipulation** and implement

$$\begin{aligned}
 &= x'y'z' + x'y + xyz' + xz \\
 &= x' (y'z' + y) + x (yz' + z) \\
 &= x' [(y + y') (y + z')] + x [(y + z) (z + z')] \\
 &= x' [(1) (y + z')] + x [(y + z) (1)] \\
 &= x' (y + z') + x (y + z) \\
 &= x'y + x'z' + xy + xz \\
 &= x'y + xy + x'z' + xz \\
 &= y (x'+x) + x'z' + xz \\
 &= y (1) + x'z' + xz \\
 &= y + x'z' + xz
 \end{aligned}$$

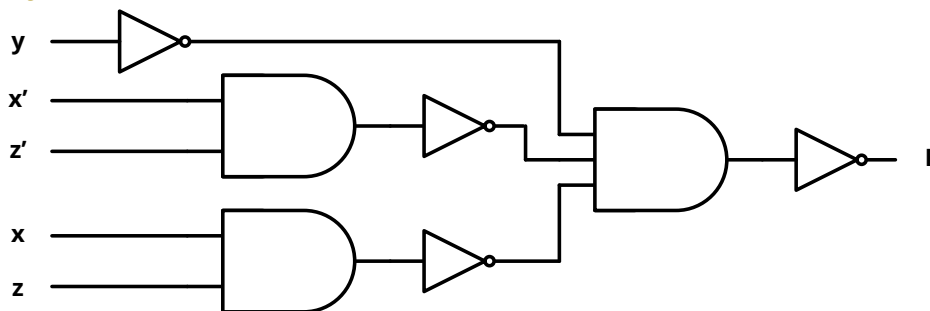
i. With **AND** and **inverter** gates (7.5 pts.)

$$\begin{aligned}
 &[(y)' (x'z')' (xz)']' \text{ implementation with AND and inverters} \\
 &((y)')' + ((x'z')')' + ((xz)')' \\
 &y + x'z' + xz
 \end{aligned}$$



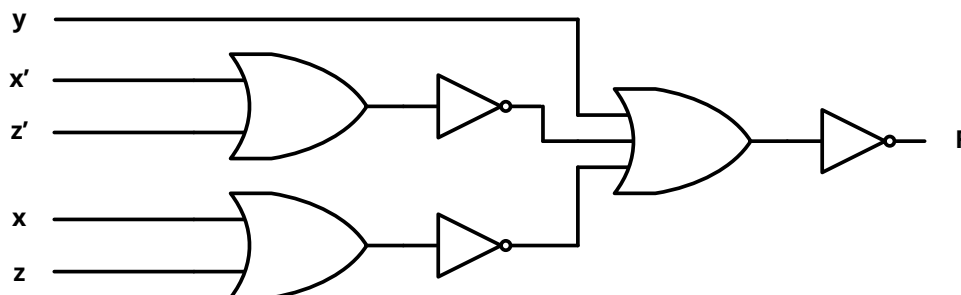ii. With **OR** and **inverter** gates (7.5 pts.)
(15 pts.)

$$\begin{aligned}
 &y + (x+z)' + (x'+z')' \text{ implementation with AND and inverters} \\
 &y + x'z' + xz
 \end{aligned}$$



b) The function $F(A,B,C,D) = A'BCD' + AB'C' + BCD' + ACD$,

i. Construct a truth table for the function given above.

A	B	C	D	A'	B'	C'	D'	A'BCD'	AB'C'	BCD'	ACD	F	Min	Max
0	0	0	0	1	1	1	1	0	0	0	0	0	0	0
0	0	0	1	1	1	1	0	0	0	0	0	0		1
0	0	1	0	1	1	0	1	0	0	0	0	0		2
0	0	1	1	1	1	0	0	0	0	0	0	0		3
0	1	0	0	1	0	1	1	0	0	0	0	0		4
0	1	0	1	1	0	1	0	0	0	0	0	0		5
0	1	1	0	1	0	0	1	1	0	1	0	1	6	
0	1	1	1	1	0	0	0	0	0	0	0	0		7
1	0	0	0	0	1	1	1	0	1	0	0	1	8	
1	0	0	1	0	1	1	0	0	1	0	0	1	9	
1	0	1	0	0	1	0	1	0	0	0	0	0		10
1	0	1	1	0	1	0	0	0	0	0	1	1	11	
1	1	0	0	0	0	1	1	0	0	0	0	0		12
1	1	0	1	0	0	1	0	0	0	0	0	0		13
1	1	1	0	0	0	0	1	0	0	1	0	1	14	
1	1	1	1	0	0	0	0	0	0	0	1	1	15	

ii. Use the truth table of (i) to write the function F in sum of minterms.

$$F(A,B,C,D) = \sum (6,8,9,11,14,15)$$

iii. Use the truth table of (i) to write the function F in product of maxterms.

$$F(A,B,C,D) = \prod (0,1,2,3,4,5,7,10,12,13)$$

(10 pts.)

Question 3:


For a given Boolean function $F(A,B,C,D) = \sum(0,2,5,7,10,13,15)$ which has don't care conditions $d(A,B,C,D) = \sum(4,8,14)$.

		CD			
	AB	00	01	11	10
00		1	0	0	1
01		X	1	1	0
11		0	1	1	X
10		X	0	0	1

a) Determine the sum of products (SOP).

$$F = B'D' + BD$$

b) Implement F with only **NAND** gates.

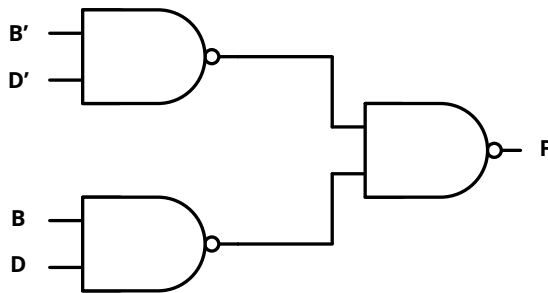


c) Determine the product of sums (POS).

$$F' = BD' + B'D$$

$$F = (B'+D)(B + D')$$

d) Implement F with only **NOR** gates.

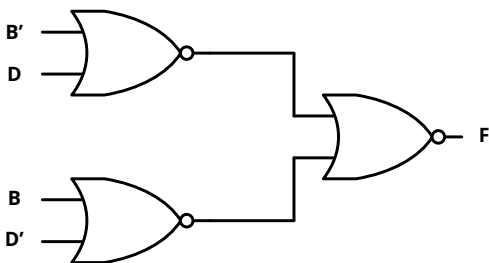

(25 pts.)

Question 4:


Simplify and then implement the Boolean function

$F(A,B,C,D) = \prod(1,2,3,5,6,7,9,11,13,15)$ using two-level forms of logic by using

CD \ AB	00	01	11	10
00	1	0	0	0
01	1	0	0	0
11	1	0	0	1
10	1	0	0	1

a) AND – NOR (SOP)


$$F = (D + A'C)'$$

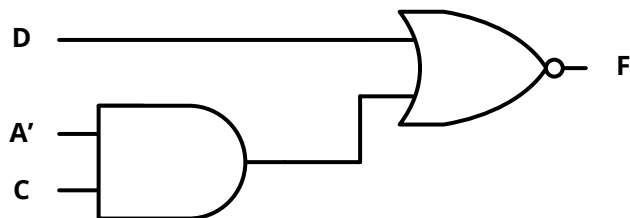

b) OR – NAND (POS)

$$F' = (C'D' + AD')$$

$$F = ((C + D)(A' + D))'$$

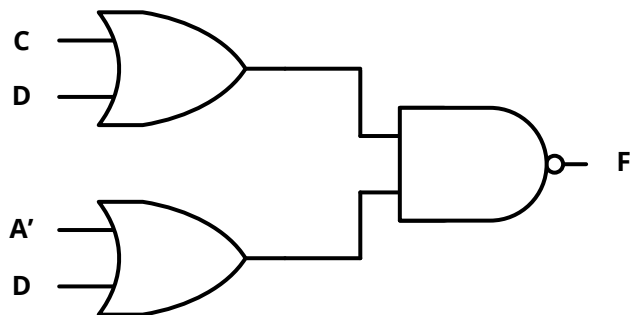

(25 pts.)