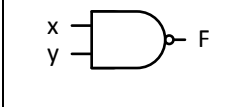



HOMEWORK II DUE: 02 November 2017

1. Identify each of these logic gates by name, and complete their respective truth tables:




Name:

x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

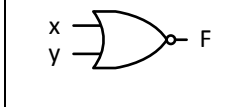


Name:

x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

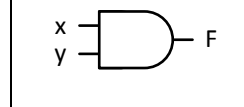


Name:

x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

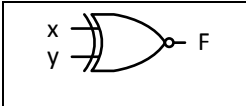


Name:

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

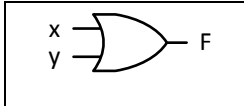


Name:

x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

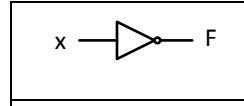


Name:

x	F
0	1
1	0

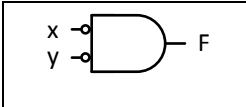


Name:

x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

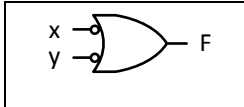

Name:

x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

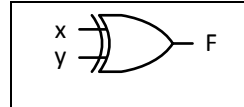

Name:

x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

(10 pts)


2. Use algebraic manipulation to simplify the following expression

a.  $F(A,B,C) = A' + ABC + A(B \oplus C) + AB'C'$

$$\begin{aligned} F &= A' + ABC + A(B \oplus C) + AB'C' \\ &= A' + ABC + AB'C + ABC' + AB'C' \\ &= A' + AB(C+C') + AB'(C+C') \\ &= A' + AB + AB' \\ &= A' + A(B+B') \\ &= A' + A = 1 \end{aligned}$$

(10 pts)

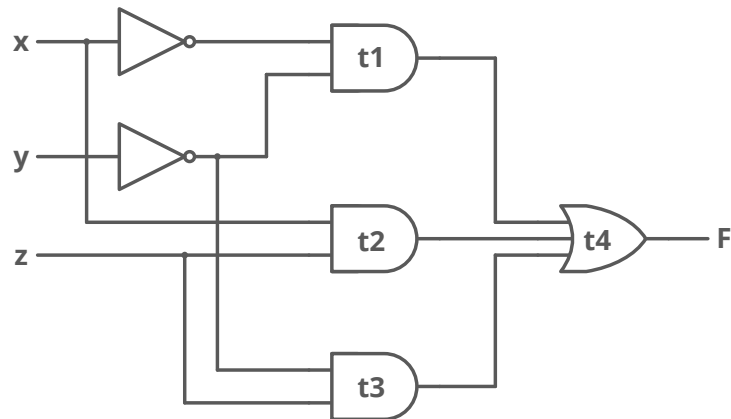3. Convert the following logic gate circuit into a Boolean expression. Write Boolean sub-expression next to each gate.



(10 pts)

$$t1 = x'.y', t2 = x.z, t3 = y'z$$

$$F = x'y' + x.z + y'z$$

4. Use DeMorgan's Theorems to simplify the following expressions:

$$\begin{aligned} F &= (B'D) (A' + C'D) + (BC' + D'A) \\ F &= [(B'D) (A' + C'D) + (BC' + D'A)]' \\ F &= (B'D)' + (A' + C'D)' (BC' + D'A)' \\ F &= (B+D') + A(C+D') (B'+C)(D+A') \end{aligned}$$

(5 pts)

5. Without simplification, write the expressions for F(dual) and F'(complement) corresponding to the Boolean function:

$$\begin{aligned} F &= A + 0.B'(C'+1.D) \\ F(\text{dual}) &= A(1+B'+(C'(0+D))) \\ F' &= A'(1+B+(C(0+D'))) \end{aligned}$$

(5 pts)

6. A Boolean function  $F$  defined on the three input variables  $x$ ,  $y$  and  $z$  is **1** if and only if number of **1(one)** input is **even**. (e.g.,  $F$  is 1 if  $x = 1, y = 0, z = 1$ ). Draw the truth table for the above functions and express it in canonical sum-of-products and product-of-sums form. (10 pts)

$x$	$y$	$z$	$F_1$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


$$F = x'y'z' + x'yz + xy'z + xyz' = m_0 + m_3 + m_5 + m_6$$

$$F(x,y,z) = \sum(0,3,5,6)$$

7. Draw the logic diagram for the following Boolean expression

$$F = x'z + x(y+z)$$

(10 pts)

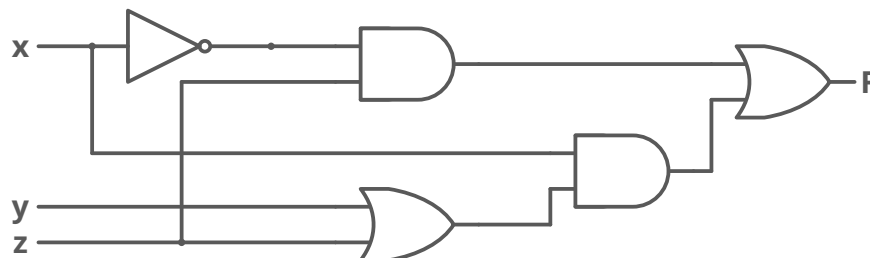

8. Obtain the truth table of the following functions, and express each function in sum-of-minterms and product-of-maxterms form:

$$bd' + acd' + ab'c + a'c'$$

a	b	c	d	a'	b'	c'	d'	bd'	acd'	ab'c	a'c'	F
0	0	0	0	1	1	1	1	0	0	0	1	1
0	0	0	1	1	1	1	0	0	0	0	1	1
0	0	1	0	1	1	0	1	0	0	0	0	0
0	0	1	1	1	1	0	0	0	0	0	0	0
0	1	0	0	1	0	1	1	1	0	0	1	1
0	1	0	1	1	0	1	0	0	0	0	1	1
0	1	1	0	1	0	0	1	1	0	0	0	1
0	1	1	1	1	0	0	0	0	0	0	0	0
1	0	0	0	0	1	1	1	0	0	0	0	0
1	0	0	1	0	1	1	0	0	0	0	0	0
1	0	1	0	0	1	0	1	0	1	1	0	1
1	0	1	1	0	1	0	0	0	0	1	0	1
1	1	0	0	0	0	1	1	1	0	0	0	1
1	1	0	1	0	0	1	0	0	0	0	0	0
1	1	1	0	0	0	0	1	1	1	0	0	1
1	1	1	1	0	0	0	0	0	0	0	0	0

$$F(a,b,c,d) = \sum(0,1,4,5,6,10,11,12,14)$$

$$F(a,b,c,d) = \prod(2,3,7,8,9,13,15)$$

(10 pts)

9. For the Boolean function

$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$


- Obtain the truth table of F.
- Draw the logic diagram, using the original Boolean expression.
- Use Boolean algebra to simplify the function to a minimum number of literals.
- Obtain the truth table of the function from the simplified expression and show that it is the same as the one in part (a).
- Draw the logic diagram from the simplified expression, and compare the total number of gates with the diagram of part (b).

(25 pts)

a.

w	x	y	z	w'	x'	y'	z'	xy'z	x'y'z	w'xy	wx'y	wxy	F
0	0	0	0	1	1	1	1	0	0	0	0	0	0
0	0	0	1	1	1	1	0	0	1	0	0	0	1
0	0	1	0	1	1	0	1	0	0	0	0	0	0
0	0	1	1	1	1	0	0	0	0	0	0	0	0
0	1	0	0	1	0	1	1	0	0	0	0	0	0
0	1	0	1	1	0	1	0	1	0	0	0	0	1
0	1	1	0	1	0	0	1	0	0	1	0	0	1
0	1	1	1	1	0	0	0	0	0	1	0	0	1
1	0	0	0	0	1	1	1	0	0	0	0	0	0
1	0	0	1	0	1	1	0	0	1	0	0	0	1
1	0	1	0	0	1	0	1	0	0	0	1	0	1
1	0	1	1	0	1	0	0	0	0	0	1	0	1
1	1	0	0	0	0	1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	0	1	0	0	0	0	1
1	1	1	0	0	0	0	1	0	0	0	0	1	1
1	1	1	1	0	0	0	0	0	0	0	0	1	1

b.

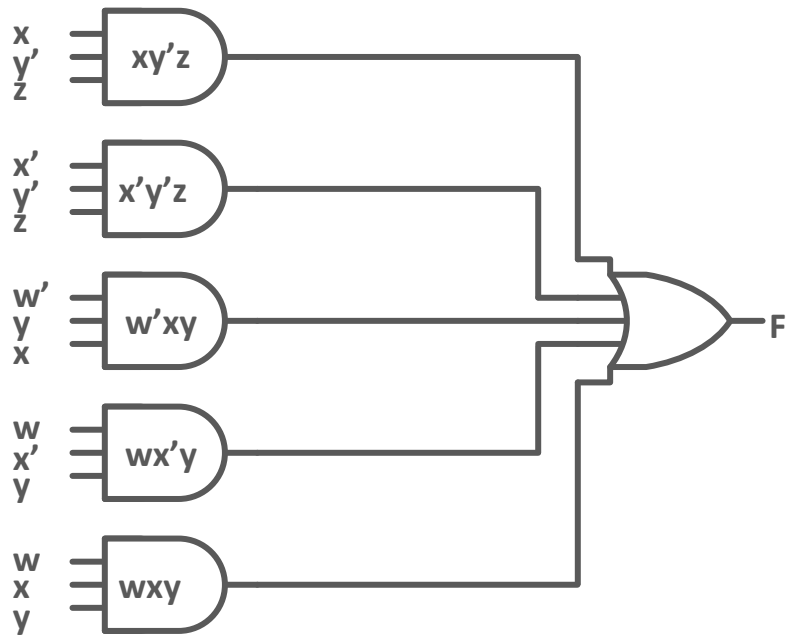

c.  $F = xy'z + x'y'z + w'xy + wx'y + wxy$

$F = y'z(x + x') + w'xy + wy(x' + x)$

$F = y'z + w'xy + wy$

$F = y'z + y(w'x + w)$

$F = y'z + y[(w' + w)(w + x)]$


$F = y'z + y(w + x)$

d.

w	x	y	z	w'	x'	y'	z'	y'z	w+x	y(w+x)	F
0	0	0	0	1	1	1	1	0	0	0	0
0	0	0	1	1	1	1	0	1	0	0	1
0	0	1	0	1	1	0	1	0	0	0	0
0	0	1	1	1	1	0	0	0	0	0	0
1	1	0	0	0	0	1	1	0	1	0	0
0	1	0	1	1	0	1	0	1	1	0	1
0	1	1	0	1	0	0	1	0	1	1	1
0	1	1	1	1	0	0	0	0	1	1	1
1	0	0	0	0	1	1	1	0	1	0	0
1	0	0	1	0	1	1	0	1	1	0	1
1	0	1	0	0	1	0	1	0	1	1	1

1	0	1	1	0	1	0	0	0	1	1	1
1	1	0	0	0	0	1	1	0	1	0	0
1	1	0	1	0	0	1	0	1	1	0	1
1	1	1	0	0	0	0	1	0	1	1	1
1	1	1	1	0	0	0	0	0	1	1	1

e.

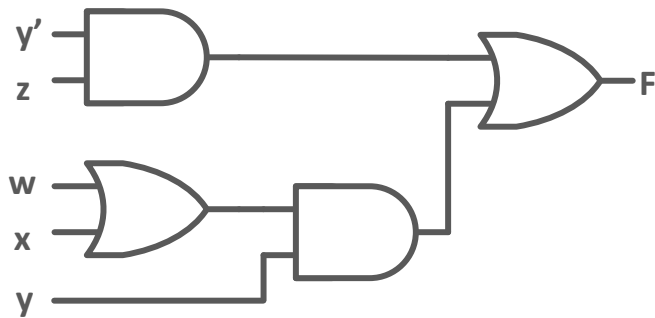

10. Convert the following to the other canonical form:

a.  $F(x,y,z) = \sum(2,3,5,6)$

**$F(x,y,z) = \prod(0,1,4,7)$**

b.  $F(x,y,z) = \prod(0,2,4,5,7)$

**$F(x,y,z) = \sum(1,3,6)$**

(5 pts)