

EASTERN MEDITERRANEAN UNIVERSITY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING

EENG223

CIRCUIT THEORY I

EXPERIMENT 7

PSPICE

Student Name & Student Number

1.....

2.....


3.....

• **The .TF Control Statement**

Computes three characteristics of the circuit

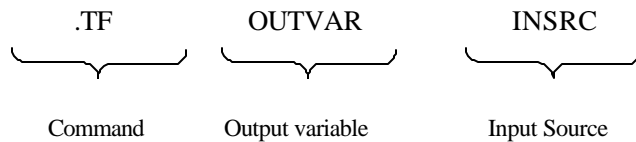
1. Ratio of the output variable to the input variable (transfer function gain).
2. The resistance with respect to the input source.
3. The output resistance with respect to the terminals of the output element.

.TF control statements contain three fields:



You may use the .TF control statement to find the Thevenin equivalent with respect to a designated pair of terminals.

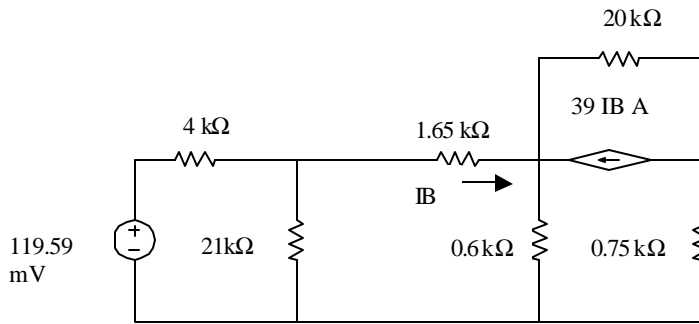
Example 1: Write a Pspice program to find the Thevenin equivalent w.r.t. terminals A,B.



```

SOLUTION OF EX1
V1 1 0 DC 119.59e-3
R1 1 2 4e3
R2 2 0 21e3
VA 2 3 DC 0
R3 3 4 1.65e3
R4 4 0 600
R5 4 5 20e3
F1 5 4 VA 39
R6 5 0 750
.TF V(5,0) V1
.END
    
```

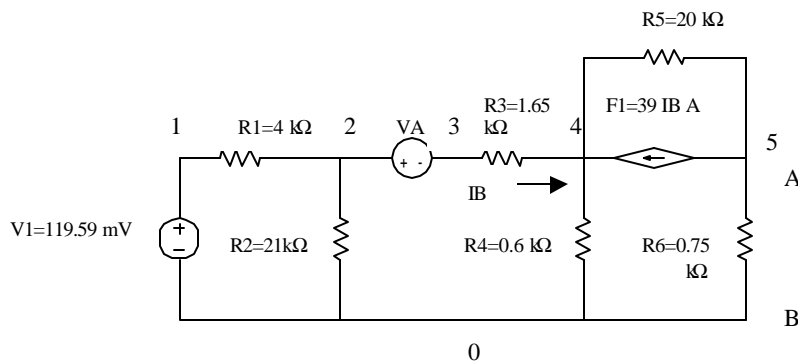The following circuit prepared for Pspice analysis.



```


*** SMALL SIGNAL CHARACTERISTICS

V(5,0)/V1=-8.359E-01
INPUT RESISTANCE AT V1=1.5235E+04
OUTPUT RESISTANCE AT V(5,0)=7.446E+02


VOC=(V(5,0)/V(1))xV(1)=-0.1
RTH=OUTPUT RESISTANCE=7.446E+02
    
```

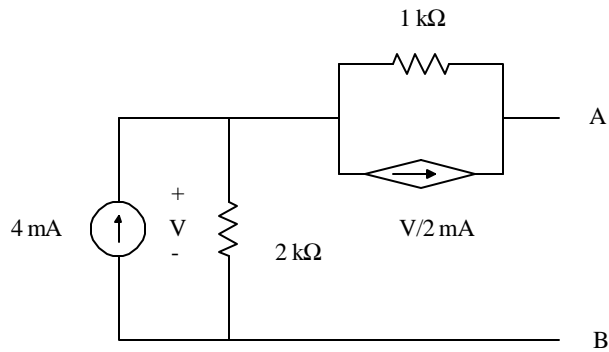Example 2:

Write a Pspice a program to find the Thevenin equivalent circuit w.r.t. terminals A,B.



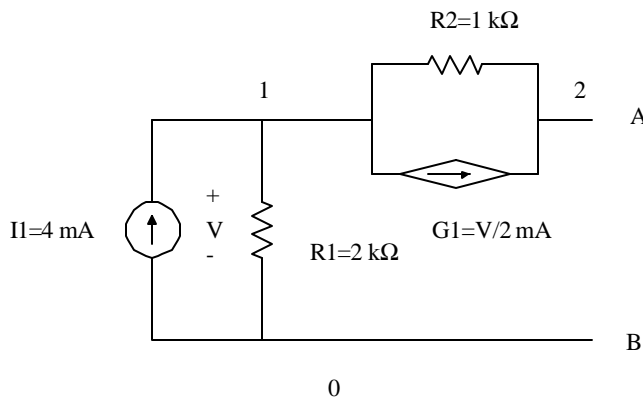The following circuit prepared for Pspice analysis



SOLUTION OF EX2

```

I1  0 1  DC  4M
R1  1 0  2K
R2  1 2  1K
G1  1 2  1 0  0.5M
.TF  V(2,0) I1
.END

```

***SMALL-SIGNAL CHARACTERISTICS

```

V(2,0)/I1=3.000E+03
INPUT RESISTANCE AT I1=2.000E+03
OUTPUT RESISTANCE AT V(2,0)=4.000E+03

```


```

Voc=(V(2,0)/I1)xI1=3.000E+03(4.000E-03)=12 V
RTH= OUTPUT RESISTANCE AT V(2,0)=4.00E+03


```

OPERATIONAL AMPLIFIERS

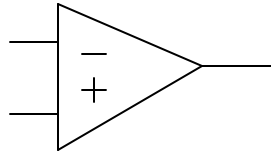- Modeling Op Amps with resistors and dependent sources.




The equivalent circuit:

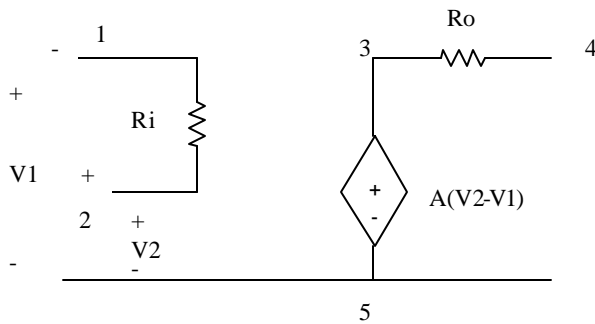

Pspice Description of equivalent circuit

Ri	1	2	Value of Ri
Ro	3	4	Value of Ro
Exxx	3	5	2 1 Value of A

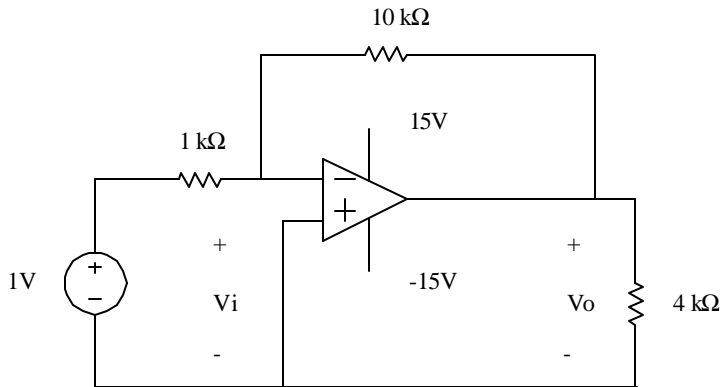Example 3: Use Pspice to find V_i and V_o when $R_i=200\text{ k}\Omega$, $R_o=5\text{ k}\Omega$ and $A=-10^4$.




SOLUTION OF EX3

```

VG 1 0 DC 1
RS 1 2 1000
RI 2 0 200e3
RF 2 4 10e3
E1 3 0 2 0 -10e3
R0 3 4 5e3
R1 4 0 4e3
.DC VG 1 1 1
.PRINT DC V(2,0) V(4,0)
.END

```


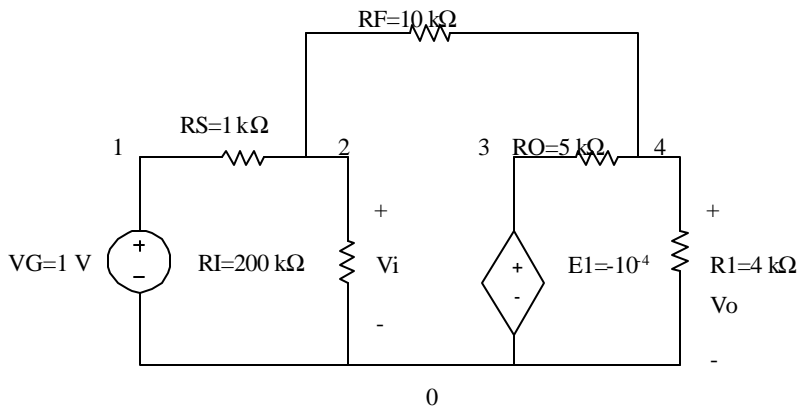


$V(2,0)=0.0027\text{ V} = V_i$
 $V(4,0)=9.969\text{ V} = V_o$

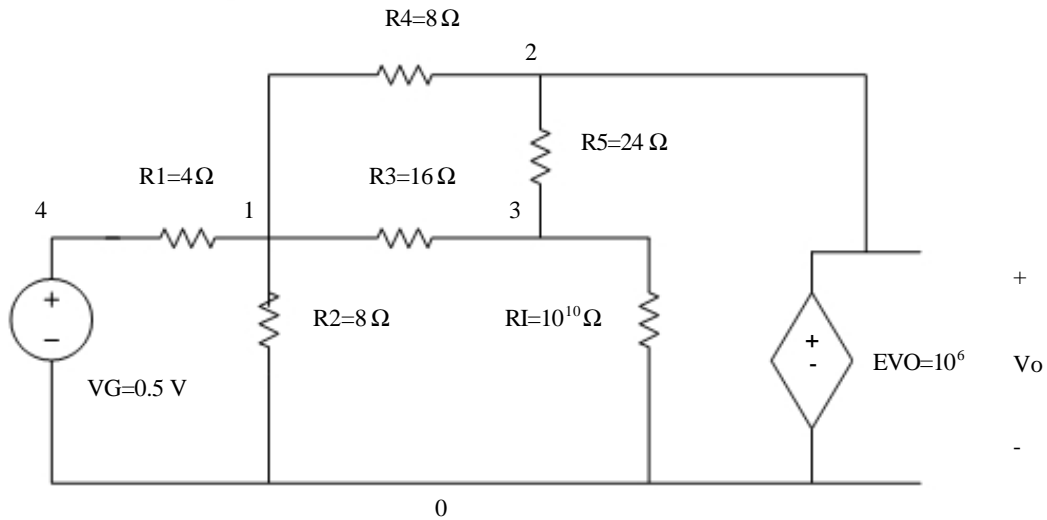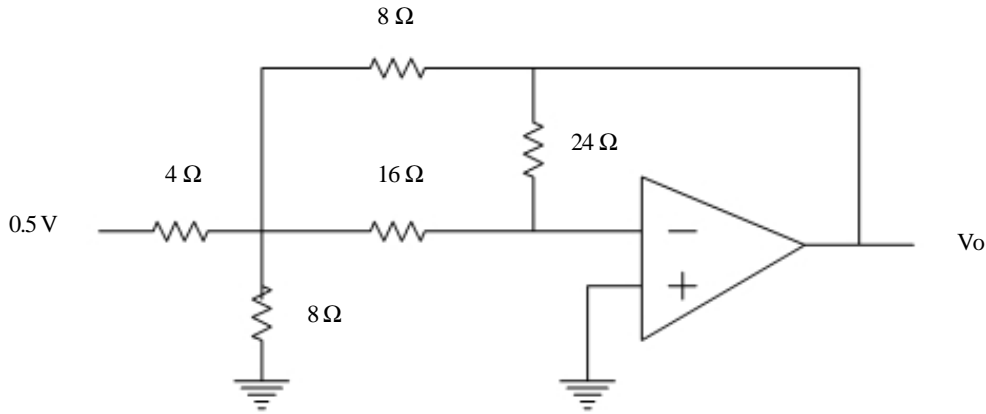Example 4: (An idle opam).

Use Pspice to find V_o when opam is idle.

For an idle opam:
 $R_i \rightarrow \infty$ very large.
 $R_o \rightarrow 0$ very small (0).
 $A \rightarrow \infty$ very large.



SOLUTION OF EX 4

```

VG 4 0 DC 0.5
R1 4 1 4
R2 1 0 8
R3 1 3 16
R4 1 2 8
R5 2 3 24
RI 3 0 1E10
EVO 2 0 3 0 1E6
.DC VG 0.5 0.5 1
.PRINT DC V(2,0)
.END

```

$V(2,0) = -2.500E-01$