



Faculty of Engineering
DEPARTMENT of ELECTRICAL AND ELECTRONIC
ENGINEERING

EENG447

Digital IC Design

Güntay Yemiscioglu

Fall 2017-2018

Final Examination

Duration: 120 mins

Number of Questions: 4

January 10, 2018

Good Luck

Student's

NUMBER

NAME

SOLUTIONS

SURNAME

Question	Achieved	Points
1		30
2		40
3		40
4		10
TOTAL		120


Read the following instructions carefully:

1. Switch off mobile phones and do not borrow any stationery from your friends.
2. In your solutions, show all details you claim credit for.


Question 1 (30 pts):

Consider the logical expression $F = (AB + C(A+B))'$.

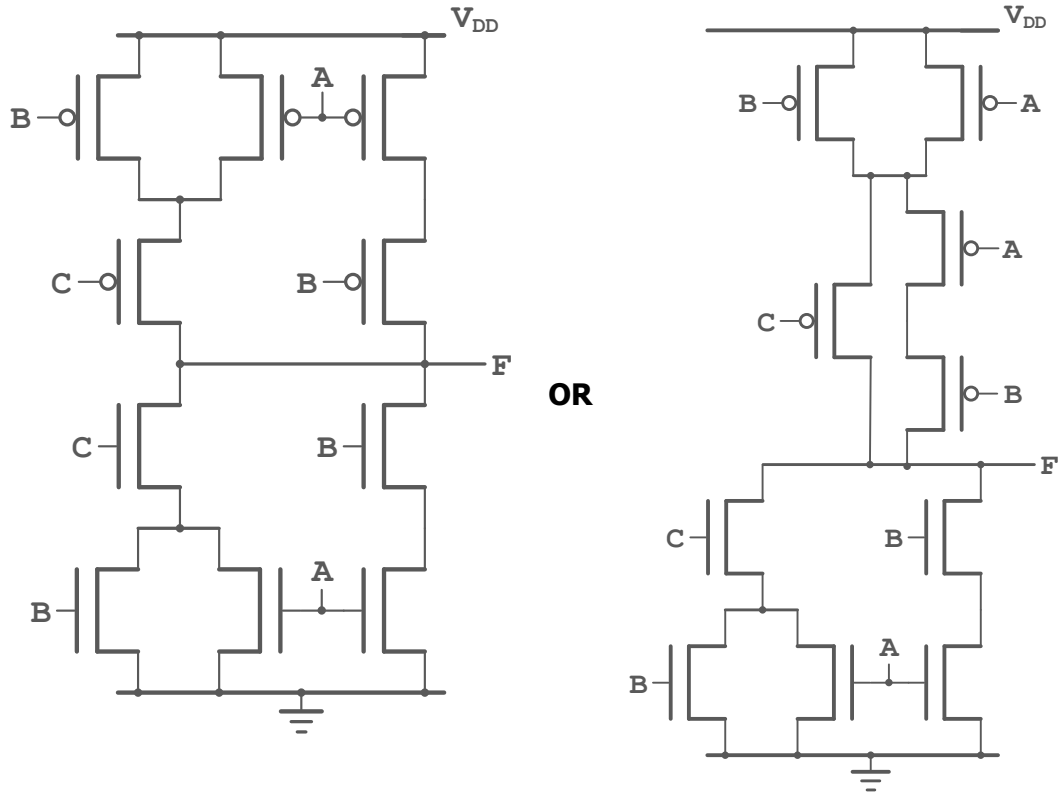- (a) Implement the given function to **transistor-level schematic** diagram for static CMOS logic. **Label** all the input, outputs and global ports. (15 pts)




 - (b) Implement the given function to **stick diagram** layout. Make sure that the implemented circuit is **area efficient**. **Label** all the input, outputs and global ports. (15 pts)




Question 2 (40 pts):

Consider the following stick diagram.

 

 - (a) Implement the electrically equivalent **transistor-level** schematic. **Label** all the input, outputs and global ports. (15 pts)




(b) What logic equation does the circuit implement? (5 pts)

$$F = A' + B' + C' D'$$

$$F = (A B (C + D))'$$

 (c) Implement the electrically equivalent **gate-level** logic circuit. (5 pts)




(d) For the **gate-level** logic circuit implemented in (c) design a set of tests to detect all **single-stuck faults**, showing all the faults covered by each test. (15 pts)

A	B	C	D	STACK FAULTS
0	0	0	0	F/0
0	0	0	1	F/0
0	0	1	0	F/0
0	0	1	1	F/0
0	1	0	0	F/0
0	1	0	1	A/1, F/0
0	1	1	0	A/1, F/0
0	1	1	1	A/1, F/0
1	0	0	0	C/1, F/0
1	0	0	1	B/0, F/0
1	0	1	0	B/0, F/0
1	0	1	1	B/0, F/0
1	1	0	0	C/1, D/1, X/1, F/0
1	1	0	1	A/0, B/0, D/0, X/0, F/1
1	1	1	0	A/0, B/0, C/0, X/0, F/1
1	1	1	1	A/0, B/0, C/0, X/0, F/1

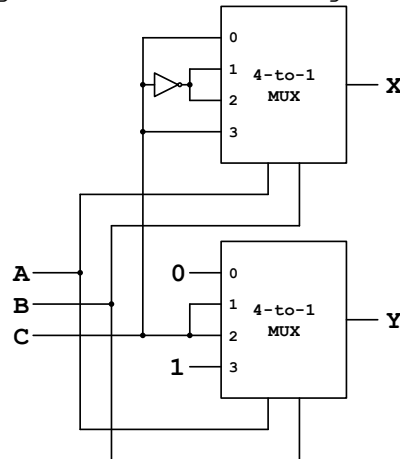Question 3 (40 pts):

Consider the following combinational logic.



- (a) Determine the functions **X** and **Y** as sums of minterms. You may use any process to determine the result, but show your work. **(10 pts)**

A	B	C	X	Y
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$X = \sum (1, 2, 4, 7)$$

$$Y = \sum (3, 5, 6, 7)$$


- (b) What does the circuit do and what are other names for X and Y? **(2.5 pts)**

The circuit implements a FULL ADDER

X is the SUM


Y is the CARRY

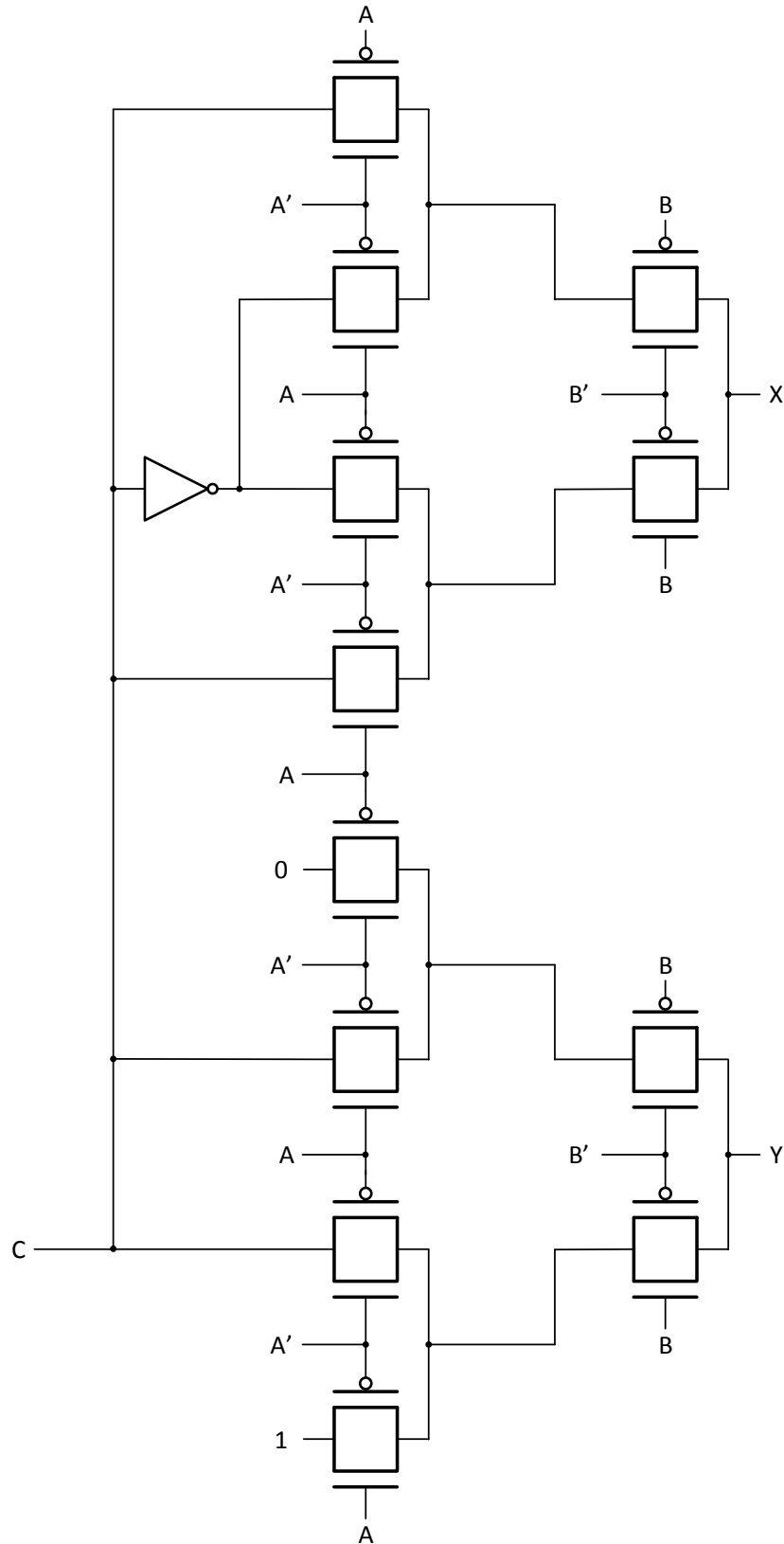(c) Implement the electrically equivalent **transistor-level** schematic for the circuit given. **Label** all the input, outputs and global ports. (7.5 pts)




30 Transistors in total.

 - (d) Implement the given function to **stick diagram** layout. Make sure that the implemented circuit is **area efficient**. Label all the input, outputs and global ports. (10 pts)



 - (e) How many transistors are needed to implement the same circuit **without using multiplexers**? Use **gate-level implementation** and explain how this could be done? (10 pts)



ordinary XOR gate	6 x PMOS + 6 x NMOS	12 transistors
AND gate	3 x PMOS + 3 x NMOS	6 transistors
OR gate	3 x PMOS + 3 x NMOS	6 transistors
Full Adder	2 x XOR + 2 AND + 1x OR 2 x 12 + 2 x 6 + 1 x 6	42 transistors
XOR gate with TG	4 x PMOS + 4 x NMOS	8 transistors
AND gate	3 x PMOS + 3 x NMOS	6 transistors
OR gate	3 x PMOS + 3 x NMOS	6 transistors
Full Adder	2 x XOR + 2 AND + 1x OR 2 x 8 + 2 x 6 + 1 x 6	34 transistors

Question 4 (10 pts):

Please explain the reason, why we usually implement the **Pull-up network** with **PMOS** and **Pull-Down network** with **NMOS**.

(Hint: You can show it by drawing the figure of the CMOS inverter.)

(10 pts)

Answer:

PMOS transistors can pass a strong "1" but a weak "0", and **NMOS** transistors can pass a strong "0" but a weak "1".