



Eastern Mediterranean University

"For Your International Career"

Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EENG223 – Circuit Theory I

**Midterm Exam
Spring 2014-15**

29 April 2015

Duration: 100 minutes

Instructor: M. K. Uyguroğlu

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO.	

Problem		Points
1		20
2		40
3		20
4		20
TOTAL		100

Problem 1

Find i and R_{eq} if $v_{ab} = 40$ V in the circuit of Fig. P1

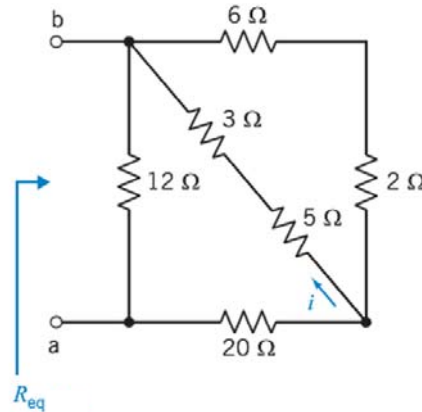


Figure P1

$$R_{eq} = 12 // (20 + \underbrace{(3+5)}_8) // \underbrace{(6+2)}_8 = 8\Omega$$

$$\underbrace{\quad\quad\quad}_4$$


$$\underbrace{\quad\quad\quad}_8$$

Using voltage division principle

$$v = 40 \frac{4}{24} = \frac{40}{6} \text{V}$$

Therefore

$$i = \frac{v}{8} = \frac{40}{48} = \frac{5}{6} \text{ A}$$

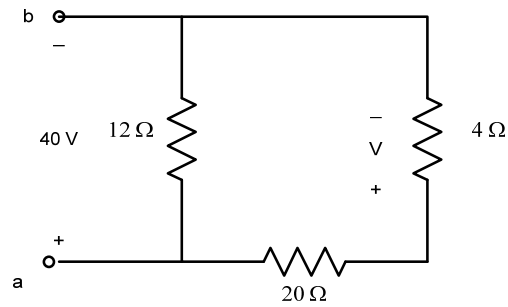

Problem 2

Find the voltage v_a in the circuit of Fig.P2 by using

- Nodal analysis
- Mesh analysis
- Source transformation
- Superposition
- Thevenin's and Norton's theorem.

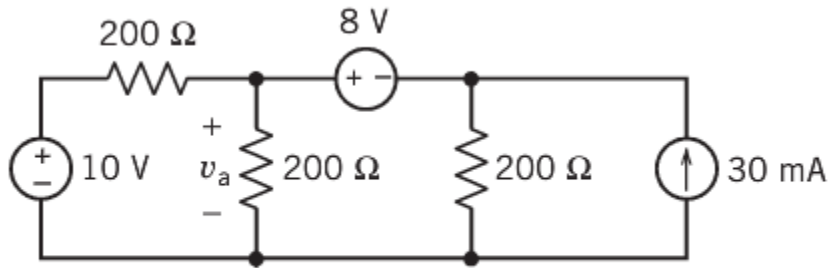
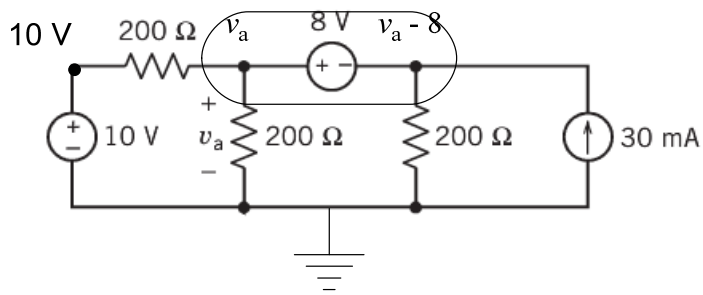


Figure P2

Nodal analysis


KCL at SUPERNODE:

$$\left(\frac{1}{200} + \frac{1}{200}\right)v_a + \frac{1}{200}(v_a - 8) - \frac{1}{200}10 = 30m$$

Multiply both sides by 200 yields:

$$3v_a = 6 + 8 + 10 = 24$$

$$\boxed{v_a = 8 \text{ V}}$$

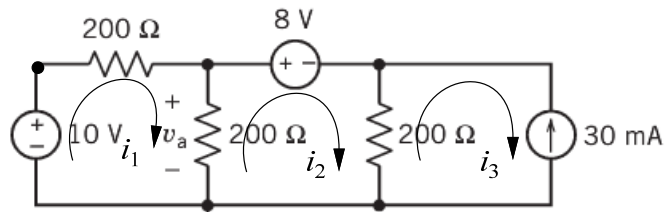Mesh Analysis

$$v_a = 200(i_1 - i_2)$$

$$i_3 = -30\text{mA}$$

KVL around i_1

$$400i_1 - 200i_2 = 10 \dots\dots(1)$$

KVL around i_2

$$-200i_1 + 400i_2 - 200(-30\text{m}) = -8$$

$$-200i_1 + 400i_2 = -14 \dots\dots(2)$$

Multiply Eq.(2) by 2 and sum up Eqs.(1) and (2) gives:

$$600i_2 = -18$$




$$i_2 = -\frac{18}{600} = -0.03 \text{ A}$$

Therefore

$$i_1 = \frac{400i_2 + 14}{200} = \frac{-12 + 14}{200} = \frac{2}{200} = 0.01 \text{ A}$$

$$v_a = 200(0.01 + 0.03) = 8 \text{ V}$$


SOURCE TRANSFORMATION

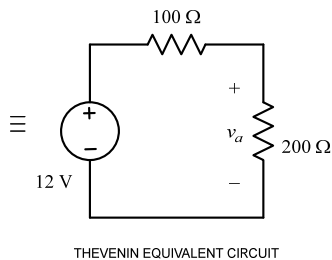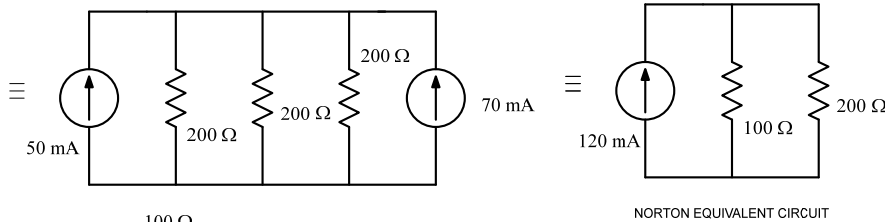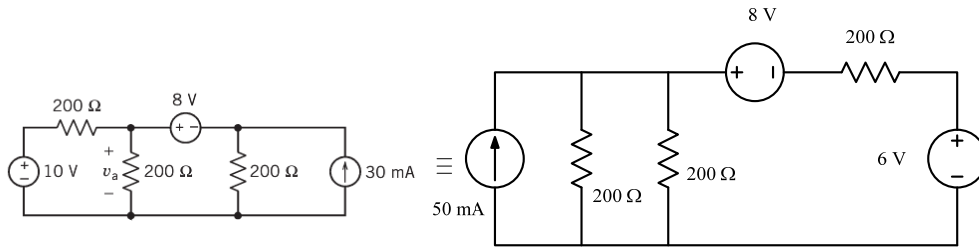

$$v_a = 12 \frac{200}{300} = 8 \text{ V}$$

SUPERPOSITION

10 V Voltage source is active

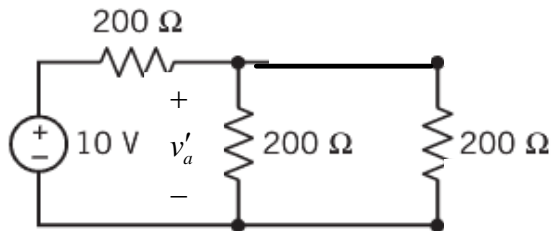


$$200\Omega / / 200\Omega = 100\Omega$$

Then using voltage division principle

$$v'_a = 10 \frac{100}{300} = \frac{10}{3} \text{ V}$$

8 V voltage source is active

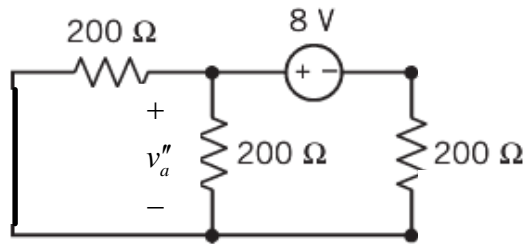


$$200\Omega // 200\Omega = 100\Omega$$

Then using voltage division principle

$$v''_a = 8 \frac{100}{300} = \frac{8}{3} \text{ V}$$

30 mA current source is active

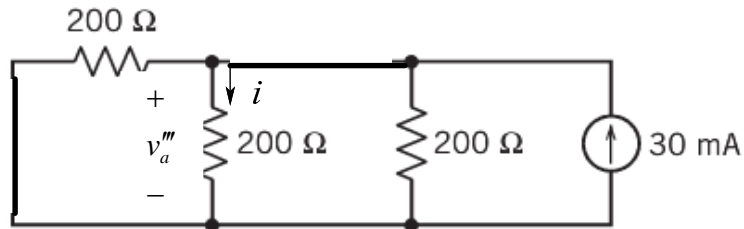

Since all the resistors are in parallel and having the same resistance value:

$$i = \frac{30m}{3} = 10mA$$

$$v'''_a = 200 \times 10m = 2 \text{ V}$$

Therefore

$$v_a = v'_a + v''_a + v'''_a = 8 \text{ V}$$

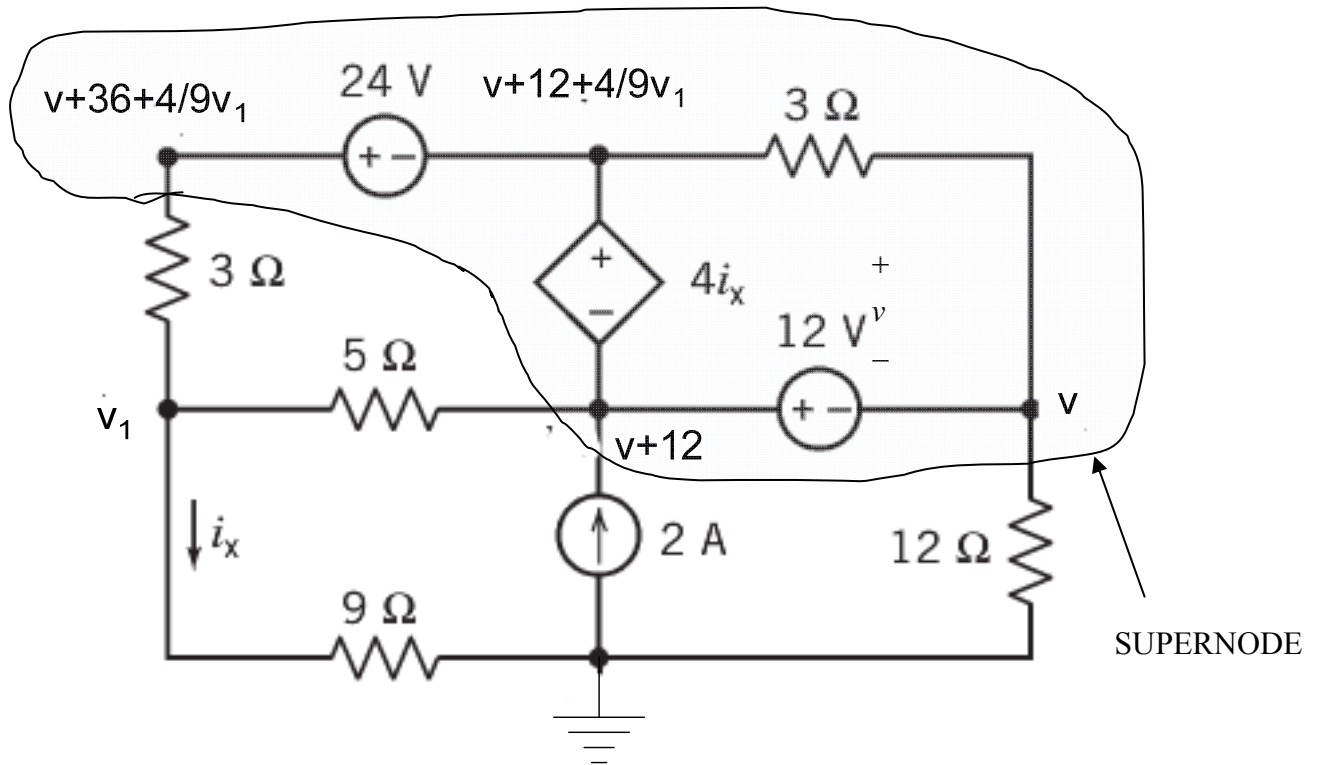
Problem 3Find v in the circuit of Fig.P3.

Figure P3

KCL at v_1 ;

$$\left(\frac{1}{3} + \frac{1}{5} + \frac{1}{9}\right)v_1 - \frac{1}{3}\left(v + 36 + \frac{4}{9}v_1\right) - \frac{1}{5}(v + 12) = 0$$

KCL at SUPERNODE

$$-\left(\frac{1}{3} + \frac{1}{5}\right)v_1 + \frac{1}{3}\left(v + 36 + \frac{4}{9}v_1\right) + \frac{1}{5}(v + 12) + \frac{1}{12}v = 2$$

$$-\frac{8}{15}v + \frac{67}{135}v_1 = \frac{72}{5}$$

$$\frac{37}{60}v - \frac{52}{135}v_1 = -\frac{62}{5}$$

$$\boxed{v = -6.037 \text{ V}}$$

Problem 4

The variable resistor R in the circuit of Fig.P4 is adjusted until it absorbs the maximum power from the circuit.

- (a) Calculate the value of R for maximum power
- (b) Determine the maximum power absorbed by R .


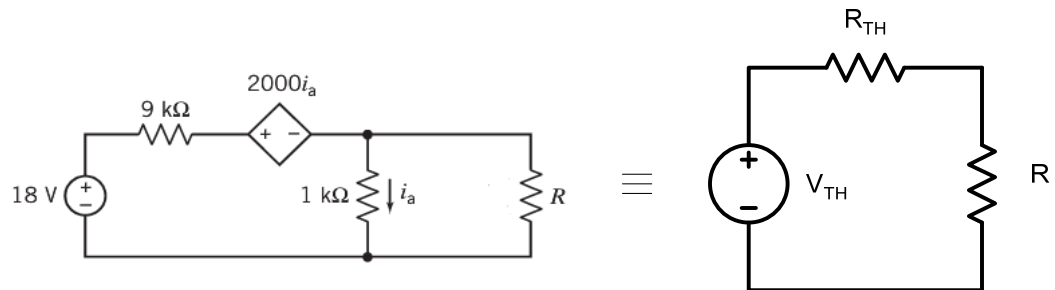


Figure P4

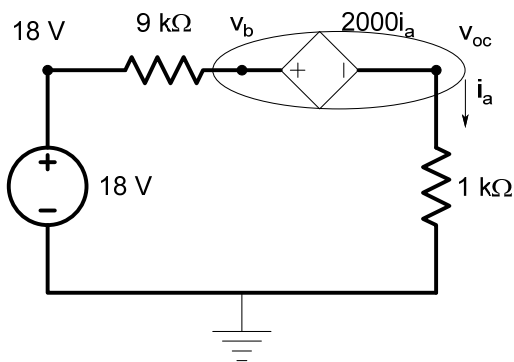In order to find V_{TH} and R_{TH} , we will find open circuit voltage and short circuit current between the terminals where R is connected.



Where

$$v_b = v_{oc} + 2000i_a$$

$$i_a = \frac{v_{oc}}{1k}$$

$$v_b = v_{oc} + 2v_{oc} = 3v_{oc}$$

KCL at SUPERNODE:


$$\frac{1}{9k} 3v_{oc} + \frac{1}{1k} v_{oc} - \frac{1}{9k} 18 = 0$$

Multiply both sides by 9k yields:

$$12v_{oc} = 18$$

$$v_{oc} = 1.5 \text{ V}$$

EENG223 Circuit Theory I – Midterm Exam

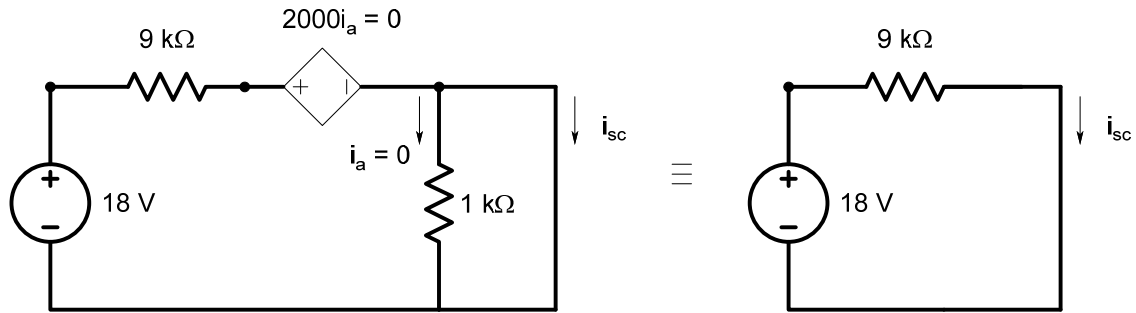

$$i_{sc} = \frac{18}{9k} = 2mA$$

$$R_{TH} = \frac{1.5}{2m} = 0.75k\Omega$$

Therefore when $R = R_{TH}$ it will absorb maximum power and the maximum power is:

$$p_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{\frac{9}{4}}{4 \times \frac{3}{4}k} = \frac{9}{12}mW$$

EENG223 Circuit Theory I – Midterm Exam

EENG223 Circuit Theory I – Midterm Exam