



## Faculty of Engineering

### ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

*EENG223 Circuit Theory I*

**Fall 2006-07**

**Instructor:**

**M. K. Uyguroğlu**

*Final EXAMINATION*

Jan 19, 2007

*Duration : 150 minutes*


Number of Problems: 4

*Good Luck*

STUDENT'S	
NUMBER	
NAME	
SURNAME	<b>SOLUTIONS</b>
GROUP NO	


Problem		Points
1		25
2		25
3		25
4		25
<b>TOTAL</b>		100

1. Find  $i$  in the circuit in Fig.P1 using Superposition.

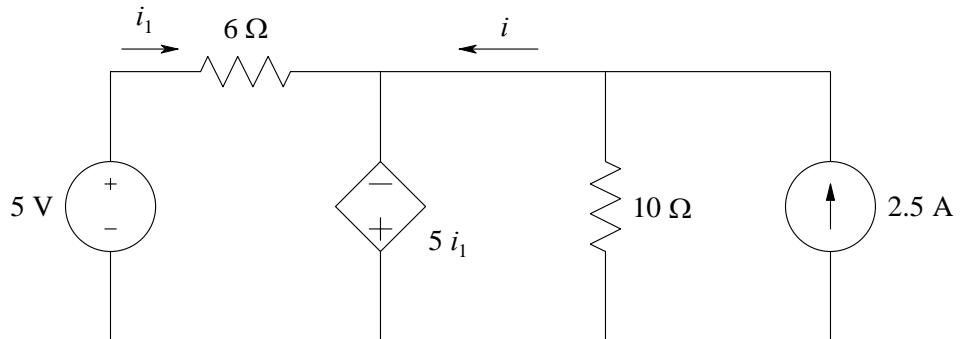

**Figure P1**

5 V Voltage source is active:

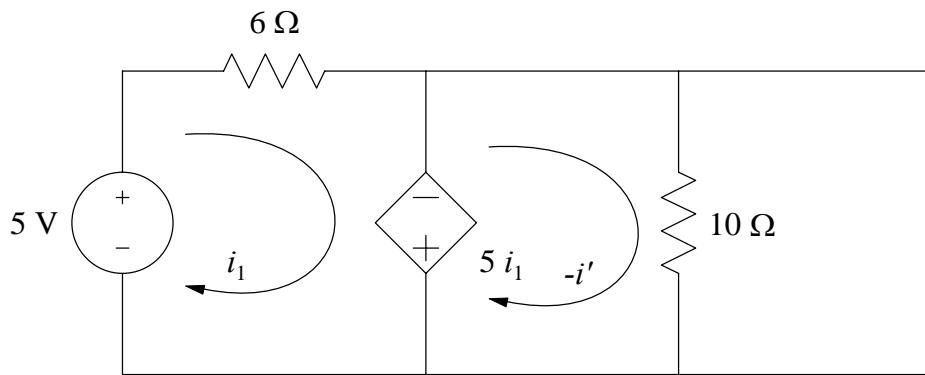

KVL around  $i_1$ :

$$6i_1 = 5 + 5i_1$$


$$i_1 = 5 \text{ A}$$

KVL around  $-i'$ :

$$10(-i') = -5i_1$$

$$i' = 0.5i_1 = 0.1(5) = 2.5 \text{ A}$$

2.5 A Current Source is active:

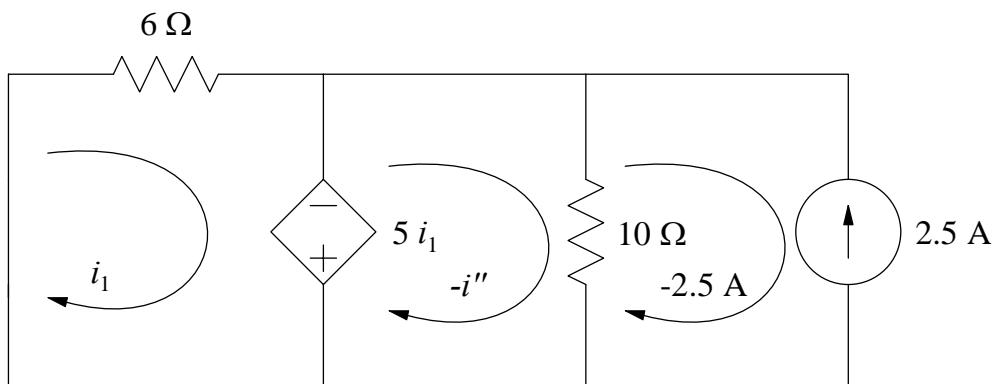

KVL around  $i_1$ :


$$\begin{aligned}6i_1 &= 5i_1 \\i_1 &= 0\end{aligned}$$

KVL around  $-i''$ :


$$\begin{aligned}10(-i'') - 10(-2.5) &= -5i_1 = 0 \\i'' &= 2.5 \text{ A}\end{aligned}$$

$$i = i' + i'' = 2.5 + 2.5 = 5 \text{ A}$$

2. Find the value of  $R$  that will draw the maximum power from the rest of the circuit in Fig. P2. Also find the maximum power.

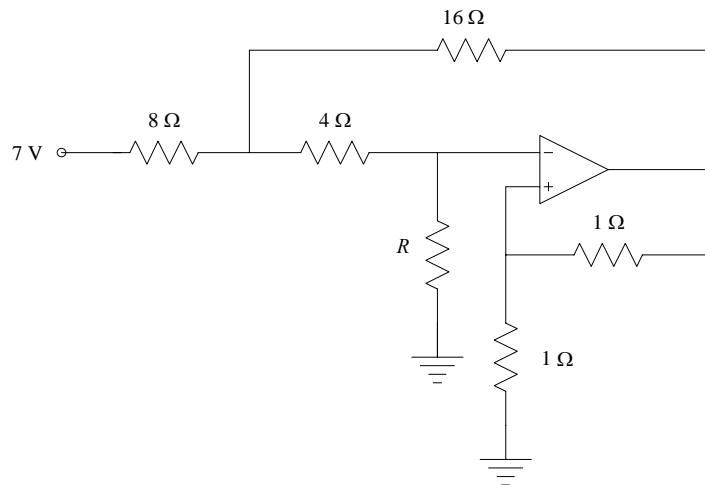


**Figure P2**

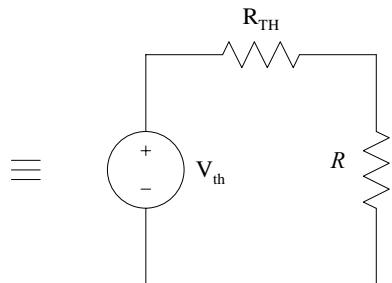

When  $R = R_{TH}$  it will draw maximum power.

$$P_{\max} = \frac{V_{TH}^2}{4R_{TH}}$$

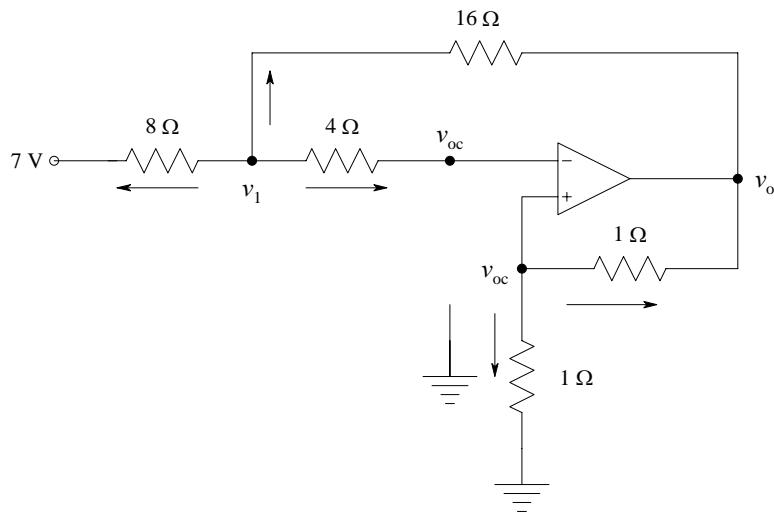In order to find  $V_{TH}$  we will find open circuit voltage.



KCL at the non-inverting input terminal:

$$\frac{v_{oc}}{1} + \frac{v_{oc} - v_o}{1} = 0$$

$$v_o = 2v_{oc}$$

KCL at the inverting input terminal:

$$\frac{v_1 - v_{oc}}{4} = 0 \Rightarrow v_1 = v_{oc}$$

KCL at  $v_1$ :


$$\frac{v_1 - 7}{8} + \frac{v_1 - v_{oc}}{4} + \frac{v_1 - v_o}{16} = 0$$

multiply both sides by 16 yields:

$$2v_1 - 14 + 4v_1 - 4v_{oc} + v_1 - v_o = 0$$

$$v_{oc} = 14 \text{ V}$$

In order to find  $R_{TH}$ :

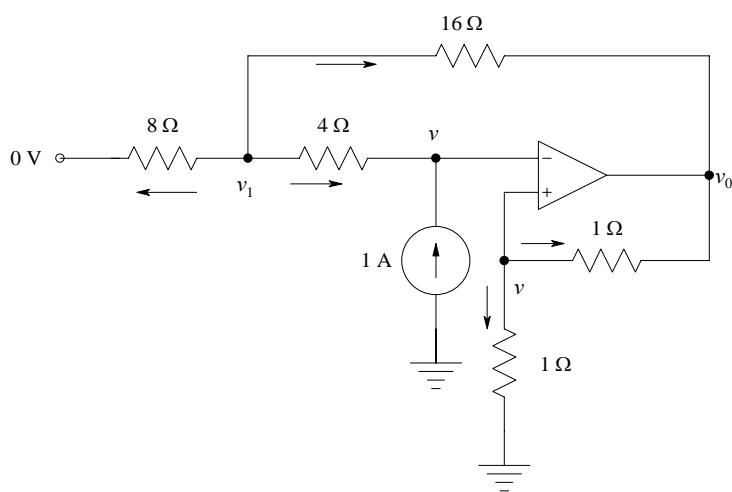

KCL at the non-inverting input terminal:

$$\frac{v - v_0}{1} + \frac{v}{1} = 0$$

$$v_0 = 2v$$

KCL at the inverting input terminal:

$$\frac{v - v_1}{4} = 1 \Rightarrow v_1 = v - 4$$

KCL at  $v_1$ :

$$\frac{v_1}{8} + \frac{v_1 - v}{4} + \frac{v_1 - v_0}{16} = 0$$

multiply both sides by 16:

$$2v_1 + 4v_1 - 4v + v_1 - v_0 = 0$$

$$7(v - 4) - 4v - 2v = 0$$

$$v = 28 \text{ V}$$

$$R_{TH} = \frac{v}{1} = 28\Omega$$

When  $R = 28\Omega$  it will draw maximum power.

$$P_{\max} = \frac{14^2}{4 \times 28} = 7/4 \text{ W}$$



3. Find  $v(t)$  for  $t \geq 0$  in the circuit in Fig.P3 if  $i(0) = 1 \text{ A}$ . (25 pts.)

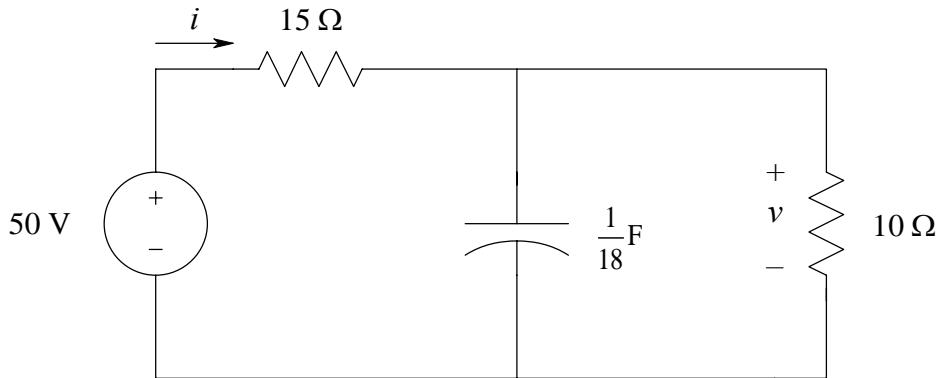


Figure P3

Since  $10\Omega$  resistor and the capacitor are in parallel, the same voltage is present across the capacitor as well. Therefore

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-\frac{t}{\tau}} \quad \text{for } t \geq 0$$

In order to find  $v(t)$  we need to determine  $v(0)$ ,  $v(\infty)$  and the time constant  $\tau$ .



KVL around the outer loop gives:

$$50 = 15i + v$$

At  $t = 0$ :

$$50 = 15i(0) + v(0) \Rightarrow v(0) = 50 - 15(1) = 35 \text{ V}$$

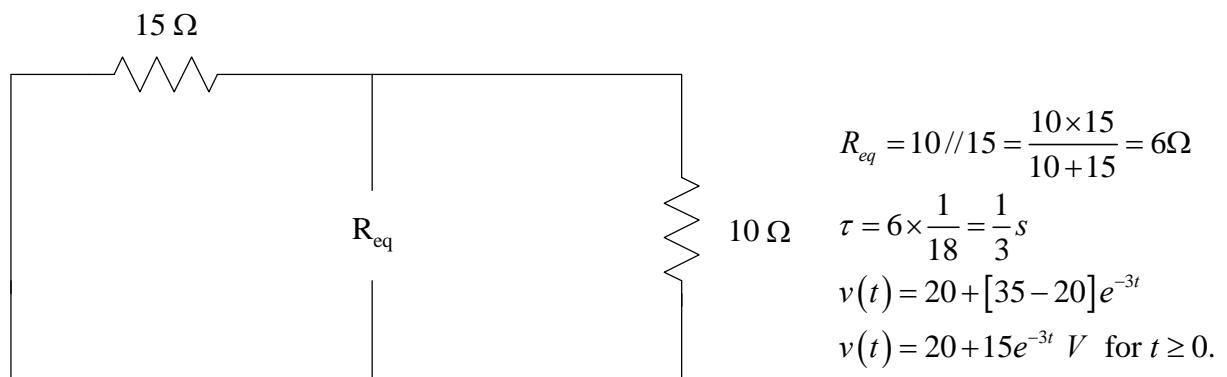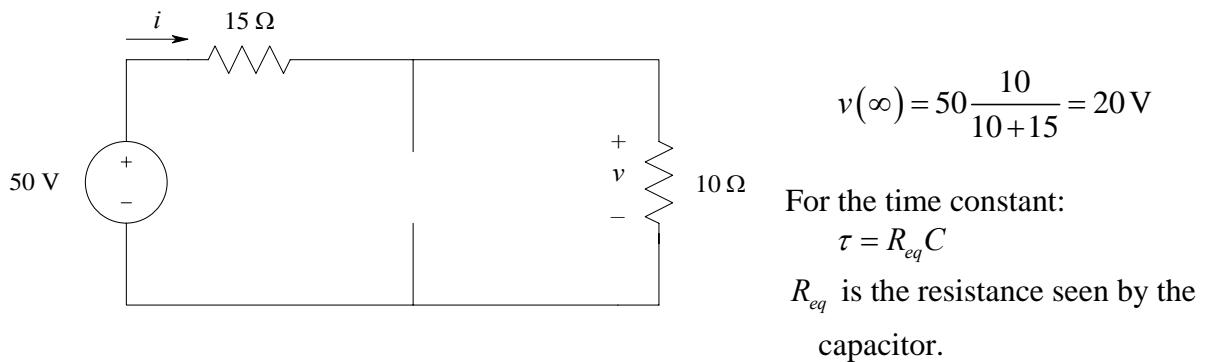At  $t = \infty$ , the circuit is under dc conditions:



4. Find  $i(t)$  for  $t \geq 0$  in the circuit in Fig. P4 if  $i(0) = 4 \text{ A}$  and  $v(0) = 8$ . (25 pts.)


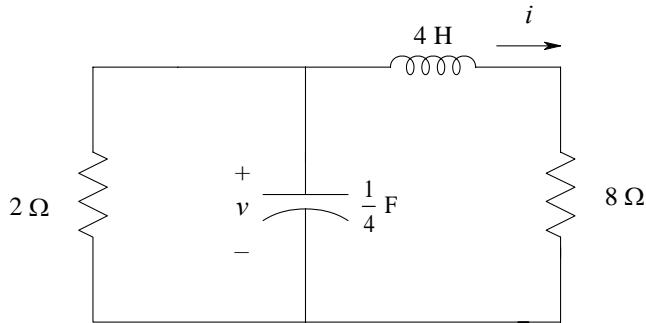


Figure P4

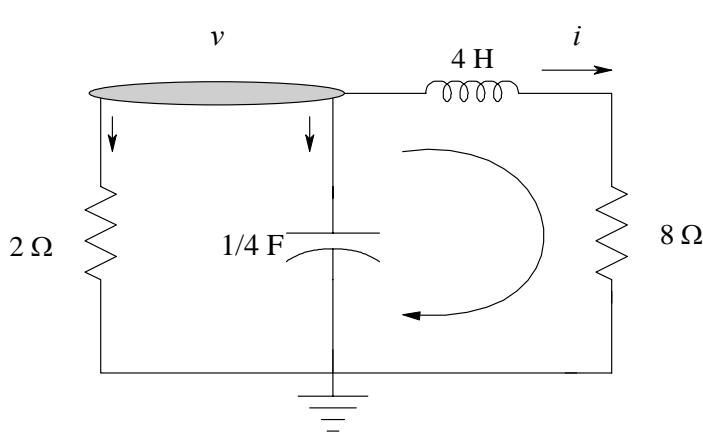

KCL at  $v$ :

$$\frac{v}{2} + \frac{1}{4} \frac{dv}{dt} + i = 0 \dots\dots\dots (1)$$

KVL around the loop:

$$-v + 4 \frac{di}{dt} + 8i = 0 \dots\dots\dots (2)$$

$$v = 4 \frac{di}{dt} + 8i \dots\dots\dots (3)$$

Subst. Eq.(3) into (1) yields:

$$\frac{1}{2} \left( 4 \frac{di}{dt} + 8i \right) + \frac{1}{4} \frac{d}{dt} \left( 4 \frac{di}{dt} + 8i \right) + i = 0$$

$$2 \frac{di}{dt} + 4i + \frac{d^2i}{dt^2} + 2 \frac{di}{dt} + i = 0$$

$$\boxed{\frac{d^2i}{dt^2} + 4 \frac{di}{dt} + 5i = 0}$$

If we write Eq.(2) at  $t = 0$ :

$$-v(0) + 4 \frac{di(0)}{dt} + 8i(0) = 0$$

$$\frac{di(0)}{dt} = \frac{1}{4} (v(0) - 8i(0)) = \frac{1}{4} (8 - 32) = -6 \text{ A/s}$$

Characteristic equation:

$$s^2 + 4s + 5 = 0$$

$$s_{1,2} = \frac{-4 \mp \sqrt{16 - 20}}{2} = -2 \mp j$$

Therefore

$$\begin{aligned}i(t) &= e^{-2t} (A \cos t + B \sin t) \\i(0) &= 4 = A \\ \frac{d}{dt} i(t) &= -2e^{-2t} (A \cos t + B \sin t) + e^{-2t} (-A \sin t + B \cos t) \\ \frac{d}{dt} i(0) &= -6 = -2(A) + (B) \Rightarrow B = 2 \\ \therefore i(t) &= e^{-2t} (4 \cos t + 2 \sin t) \text{ for } t \geq 0\end{aligned}$$