

# Operational Amplifiers (Op Amps)

---

Dr. Mustafa Kemal Uygurođlu



# Introduction

---

- Op Amp is short for operational amplifier.
- An operational amplifier is modeled as a voltage controlled voltage source.
- An operational amplifier has a very high input impedance and a very high gain.



# Use of Op Amps

---

- Op amps can be configured in many different ways using resistors and other components.
- Most configurations use feedback.



# Applications of Op Amps

---

- Amplifiers provide gains in voltage or current.
- Op amps can convert current to voltage.
- Op amps can provide a buffer between two circuits.
- Op amps can be used to implement integrators and differentiators.




# More Applications


---

- Lowpass and bandpass filters.

# The Op Amp Symbol

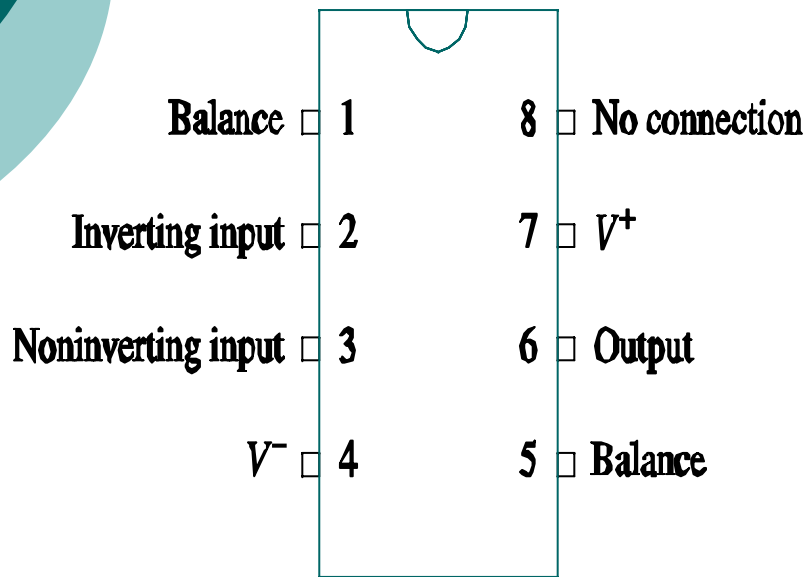


(a)

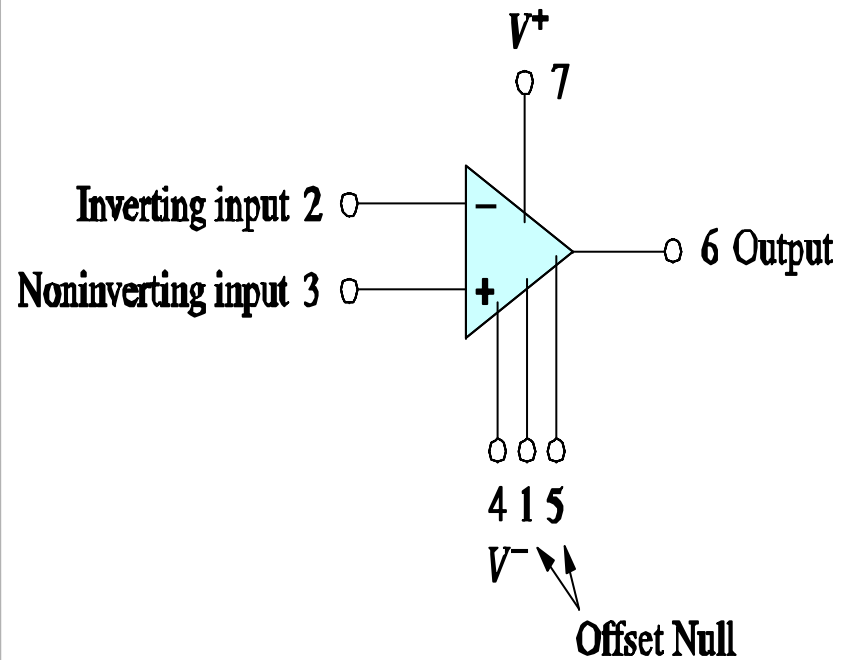


(b)

# Schematic diagram of op amp

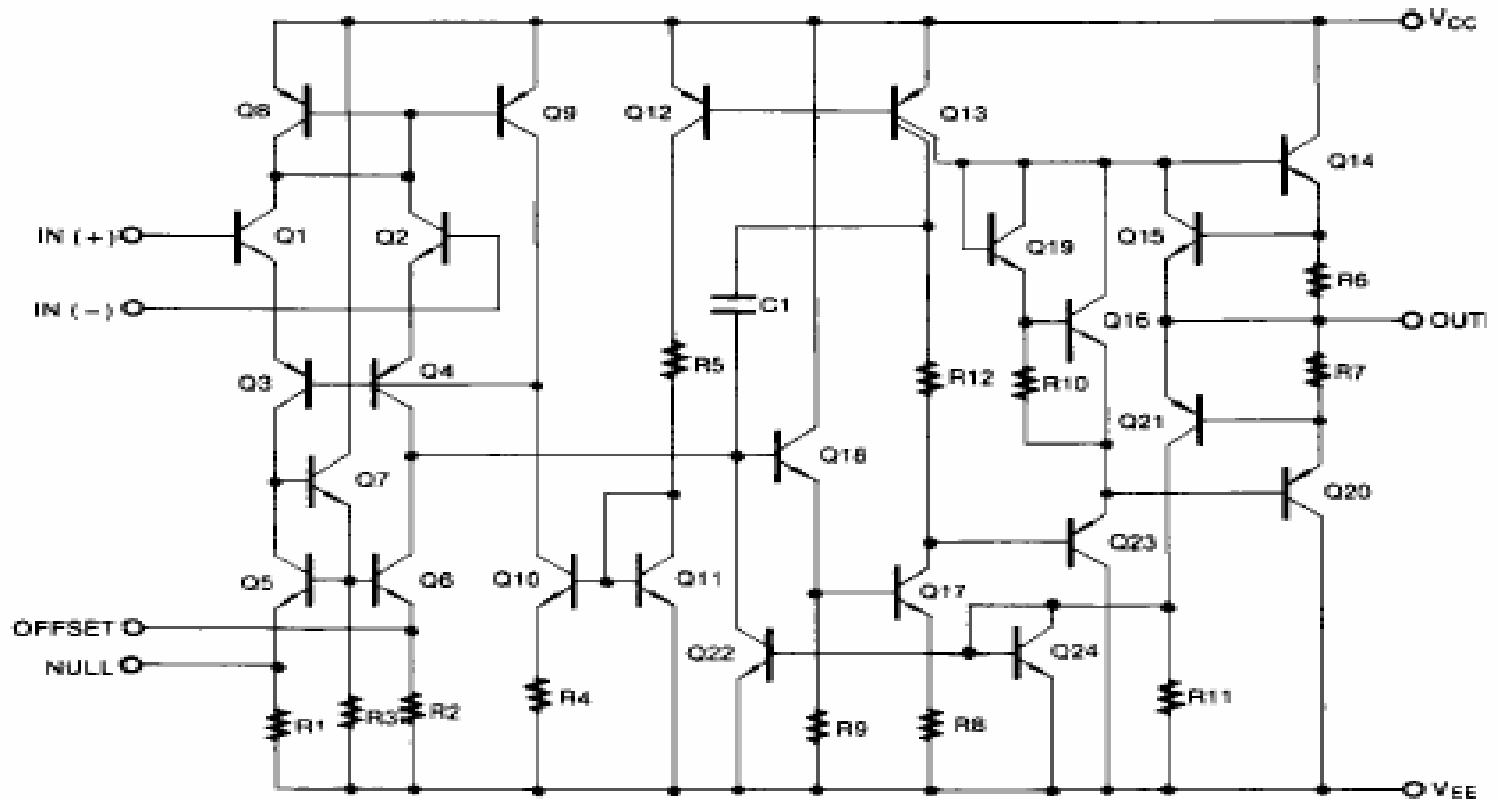

# The Op Amp Model

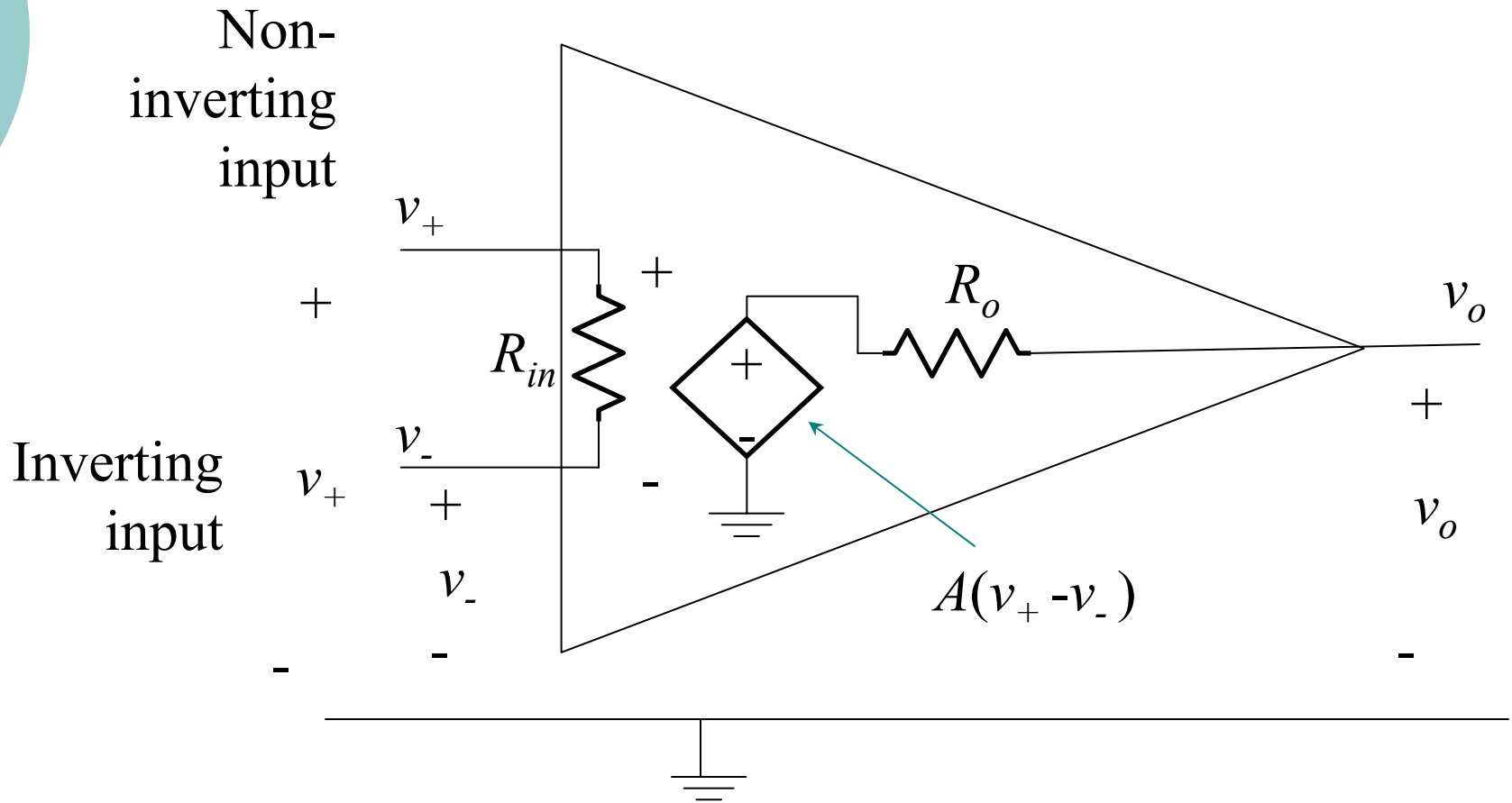




# Typical Op Amp

---

Parameter	Typical Range	Ideal Values
Open-loop gain, $A$	$10^5$ to $10^8$	$\infty$
Input resistance, $R_{in}$	$10^6$ to $10^{13}$	$\infty$
Output resistance, $R_o$	10 to 100	$0 \Omega$
Supply voltage, $v_{cc}$	5 to 24	
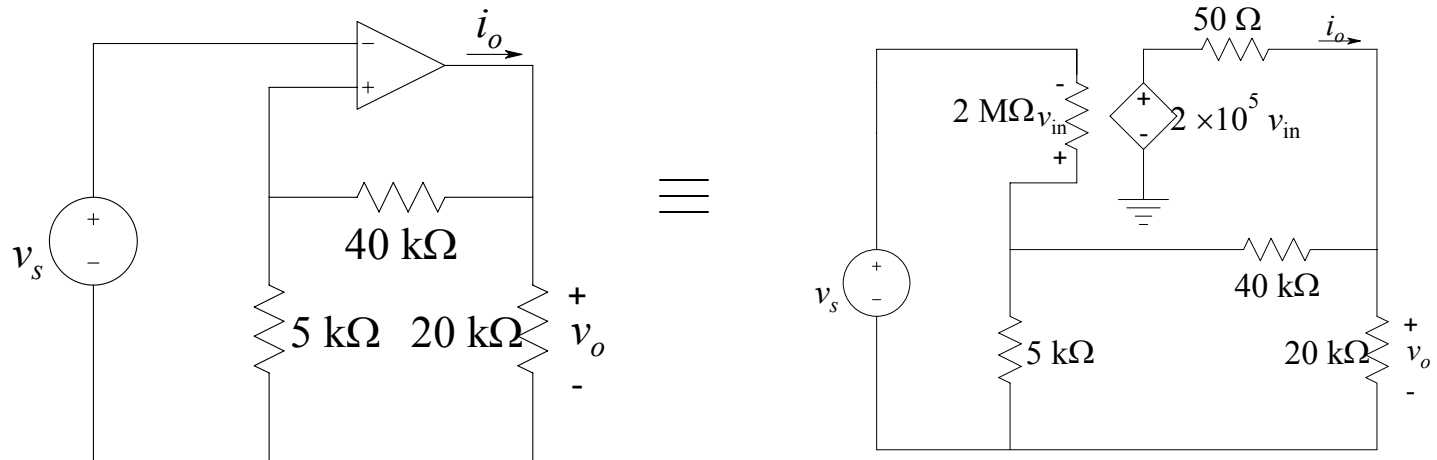
# Example


- A 741 op amp has an open-loop voltage gain of  $2 \times 10^5$ , input resistance of  $2 \text{ M}\Omega$ , and output resistance of  $50 \Omega$ . The op amp is used in the circuit shown below. Find the closed-loop gain  $v_o/v_s$ . Find  $i_o$  when  $v_s = 1 \text{ V}$ .



Equivalent circuit

# Example cont.

- Redrawn for clarity

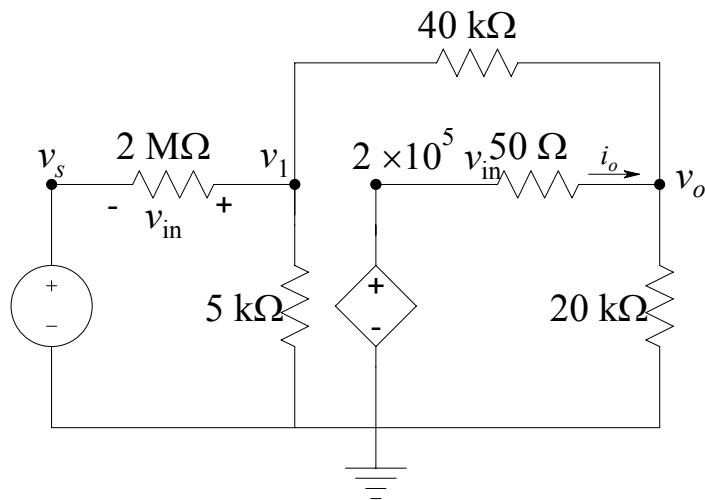

KCL at  $v_1$

$$\frac{v_1 - v_s}{2 \times 10^6} + \frac{v_1}{5 \times 10^3} + \frac{v_1 - v_o}{40 \times 10^3} = 0$$

KCL at  $v_o$

$$\frac{v_o}{20 \times 10^3} + \frac{v_o - v_1}{40 \times 10^3} + \frac{v_o - 2 \times 10^5 (v_1 - v_s)}{50} = 0$$

$$v_o = 9.0004 v_s$$

$$i_o = 0.675 \text{ mA}$$

# “Ideal” Op Amp

---

- The input resistance is infinite,  $R_{in} = \infty$
- The gain is infinite,  $A = \infty$
- Zero output resistance,  $R_o = 0$
- The op amp is in a negative feedback configuration.

# Consequences of the Ideal

---


- Infinite input resistance means the current into the inverting input is zero:

$$i_- = 0 = i_+$$

- Infinite gain means the difference between  $v_+$  and  $v_-$  is zero:

$$v_+ - v_- = 0$$

# Example

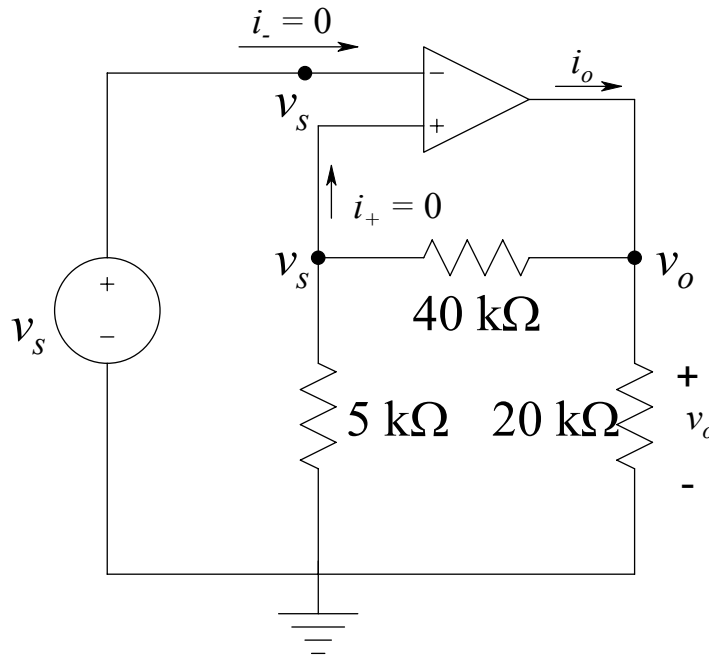

KCL at noninverting terminal:


$$\frac{v_s - v_o}{40} + \frac{v_s}{5} = 0$$
$$9v_s = v_o$$

KCL at  $v_o$ :

$$i_o = \left( \frac{v_o}{20k} + \frac{v_o - v_s}{40k} \right)$$

If  $v_s = 1\text{ V}$  then  $i_o = 0.65\text{ mA}$

# Inverting Amplifier

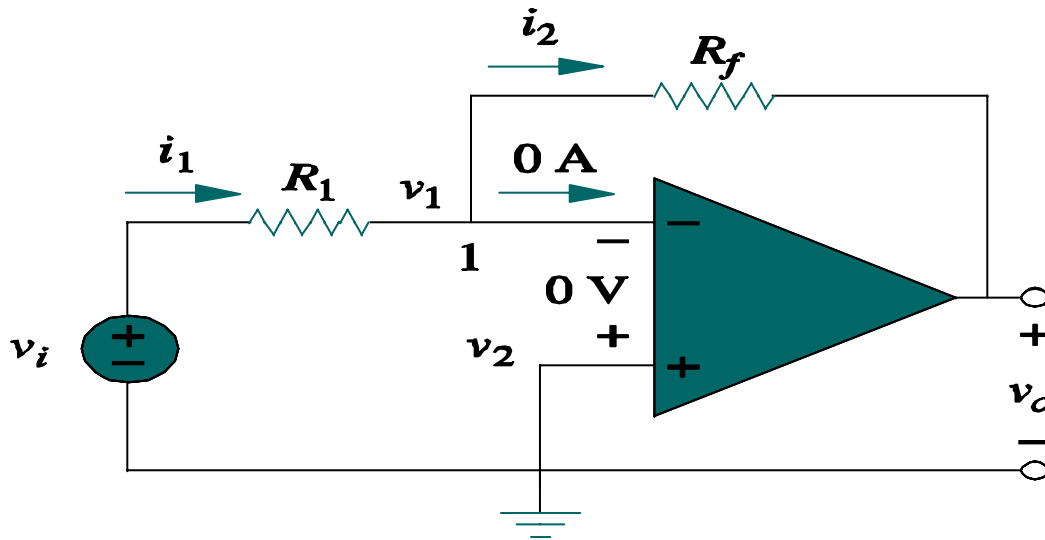

Since the noninverting terminal is grounded


$$v_1 = v_2 = 0$$

$$\text{KCL at } v_1: i_1 = i_2 \Rightarrow \frac{v_i - 0}{R_1} = \frac{0 - v_o}{R_f}$$

$$v_o = -\frac{R_f}{R_1} v_i$$

# Where is the Feedback?

---

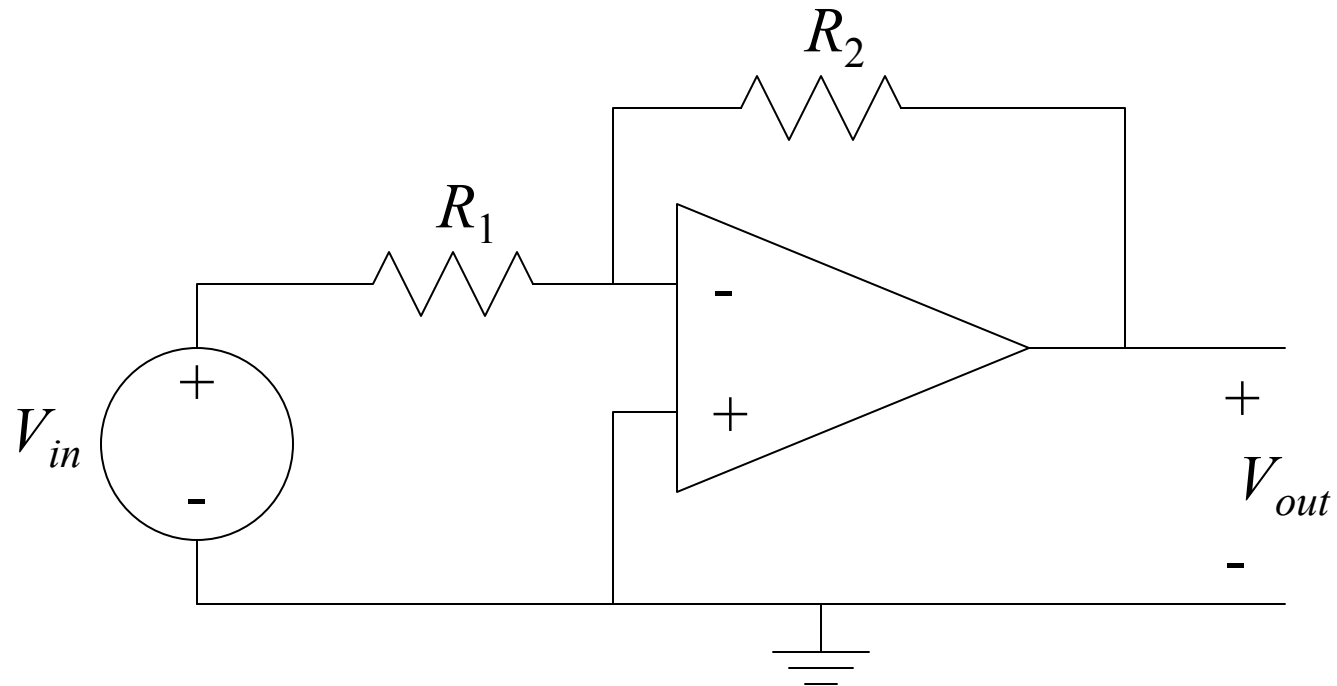



# Review

---

- To solve an op amp circuit, we usually apply KCL at one or both of the inputs.
- We then invoke the consequences of the ideal model.


$$i_- = 0 = i_+$$

$$v_+ - v_- = 0$$


- We solve for the op amp output voltage.

# The Non-Inverting Amplifier

---

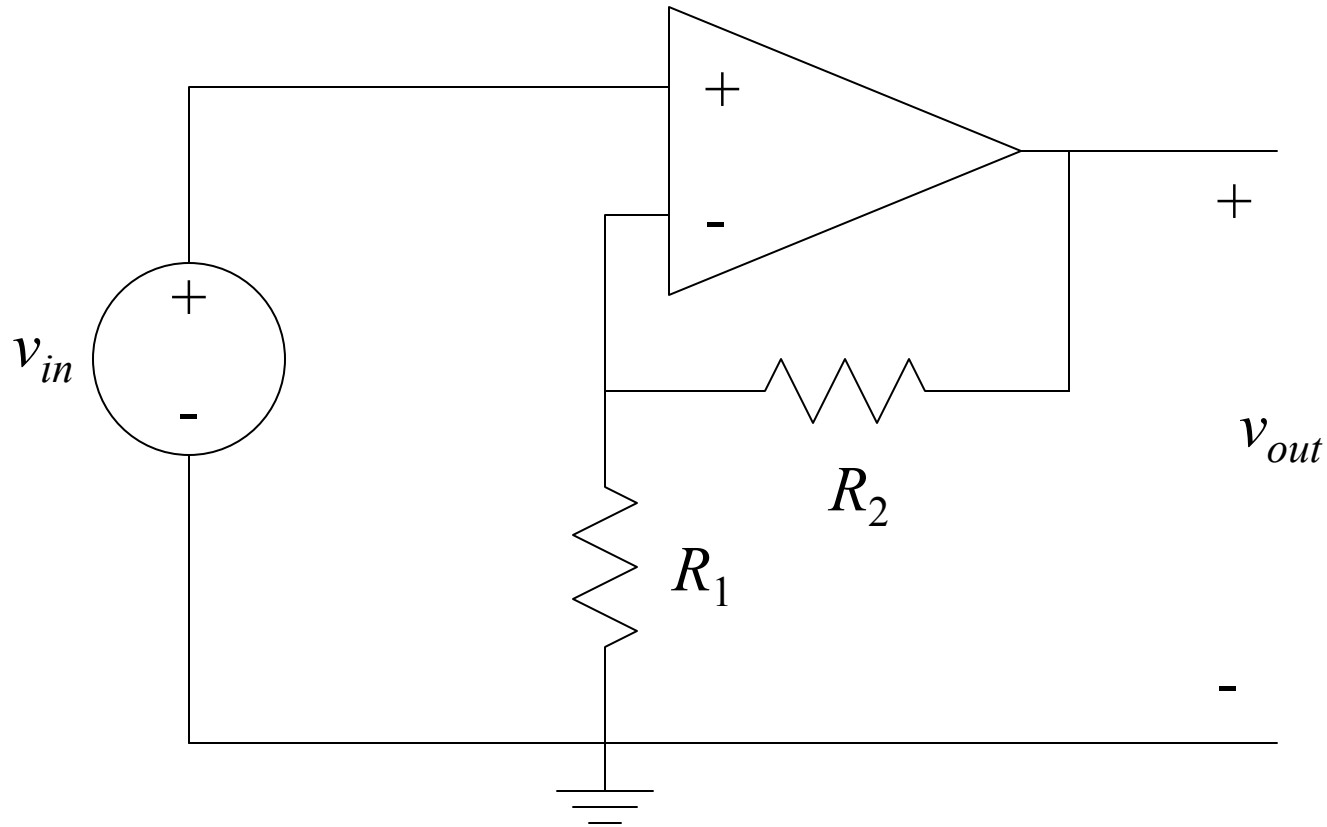

# KCL at the Inverting Input

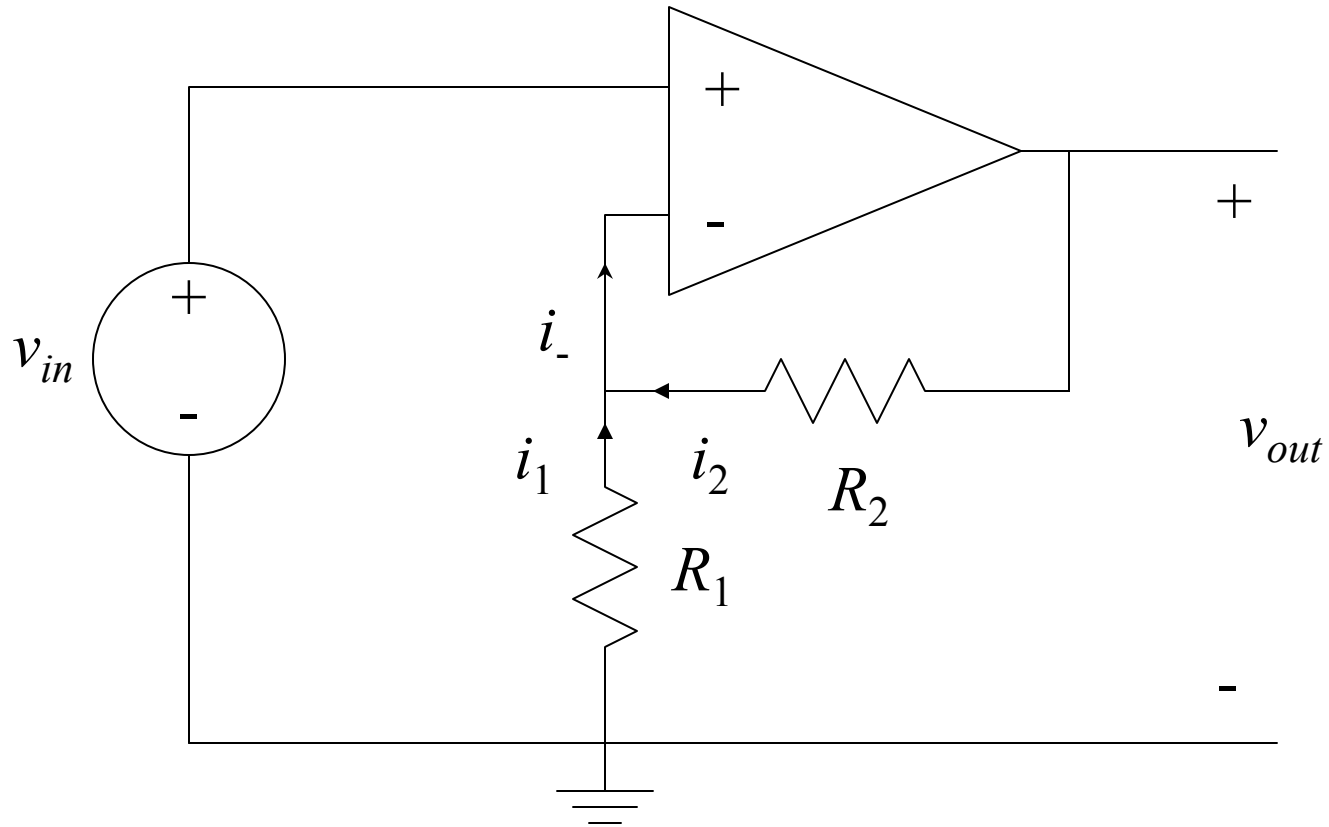

# KCL

---

$$i_- = 0$$

$$i_1 = \frac{-v_-}{R_1} = \frac{-v_{in}}{R_1} \quad \text{Since } v_- = v_+ = v_{in}$$

$$i_2 = \frac{v_{out} - v_-}{R_2} = \frac{v_{out} - v_{in}}{R_2}$$

# Solve for $V_{out}$


---

$$\frac{-v_{in}}{R_1} + \frac{v_{out} - v_{in}}{R_2} = 0$$


$$v_{out} = v_{in} \left( 1 + \frac{R_2}{R_1} \right)$$

# The Voltage Follower


---

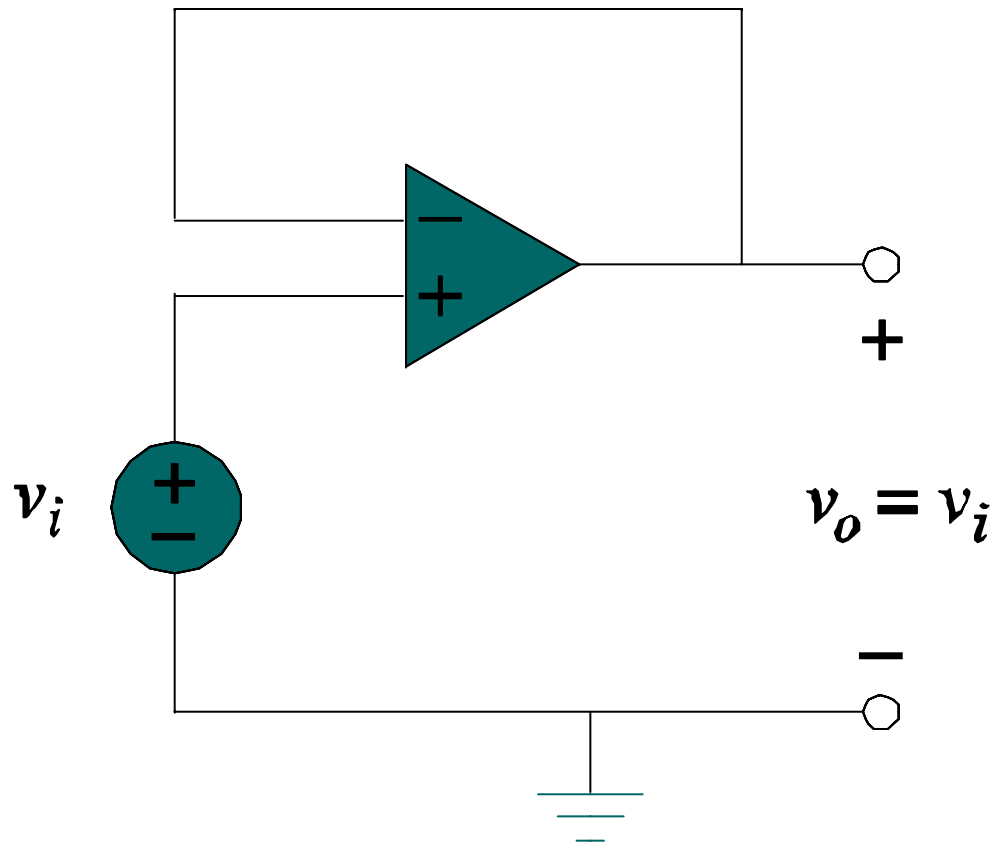

# Inverting Summer

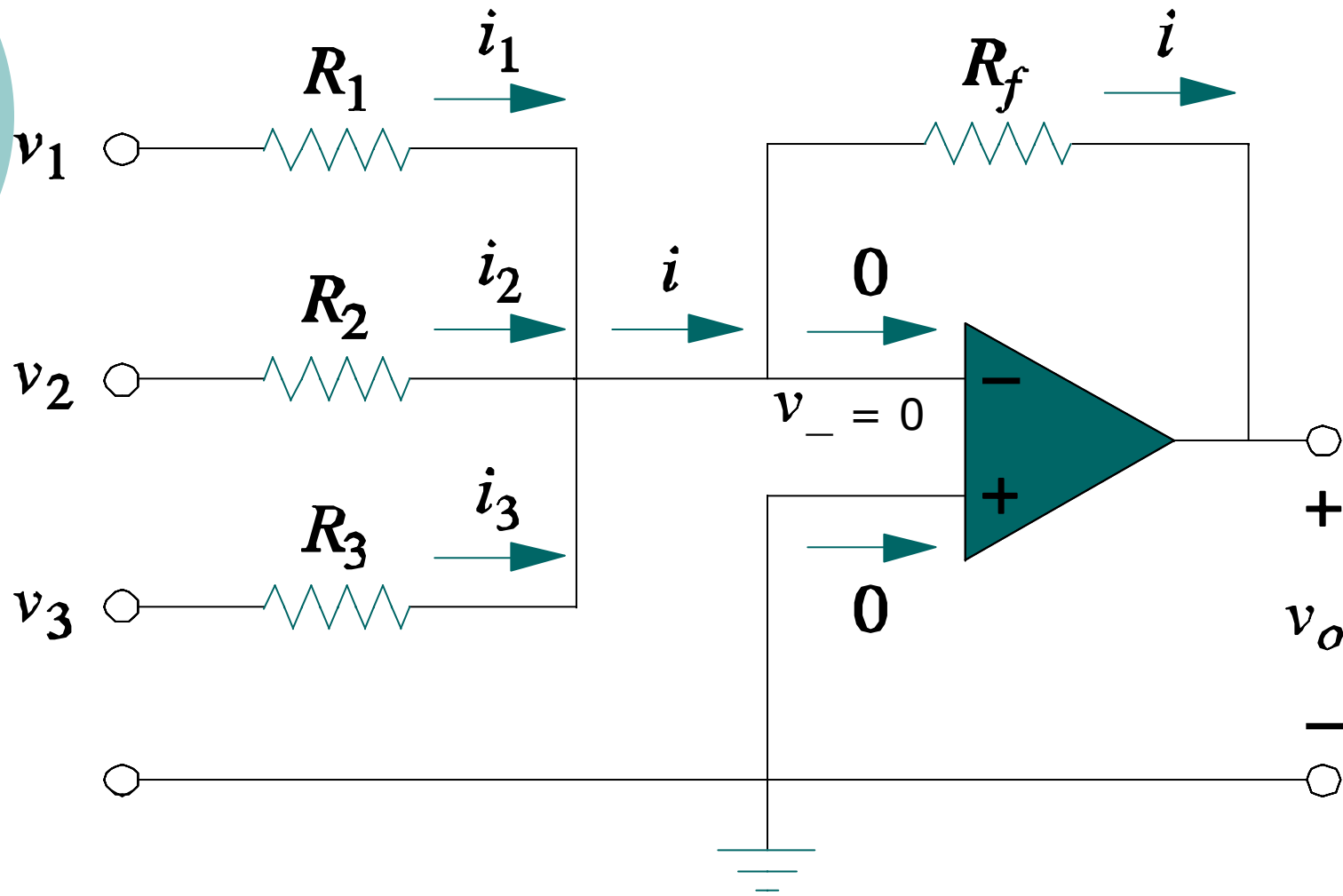

# KCL at the Inverting Input

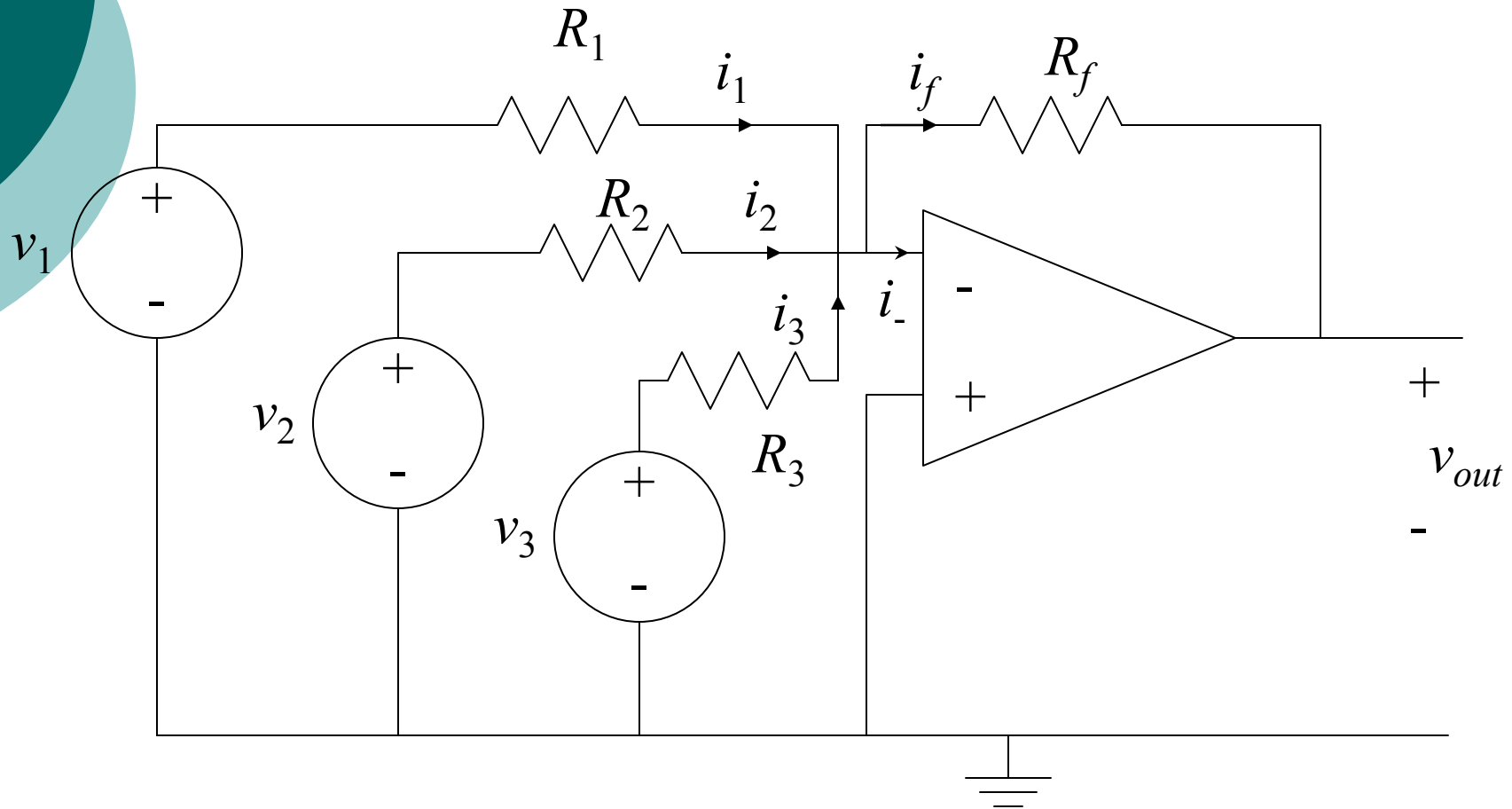



# KCL

---

$$i_1 = \frac{v_1 - v_-}{R_1} = \frac{v_1}{R_1} \quad \text{since } v_- = 0$$

$$i_2 = \frac{v_2 - v_-}{R_2} = \frac{v_2}{R_2}$$

$$i_3 = \frac{v_3 - v_-}{R_3} = \frac{v_3}{R_3}$$

# KCL

---

$$i_- = 0$$

$$i_f = \frac{v_{out} - v_-}{R_f} = \frac{v_{out}}{R_f}$$


# Solve for $V_{out}$

---

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} + \frac{v_{out}}{R_f} = 0$$

$$v_{out} = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2 - \frac{R_f}{R_3} v_3$$

# Noninverting Summer

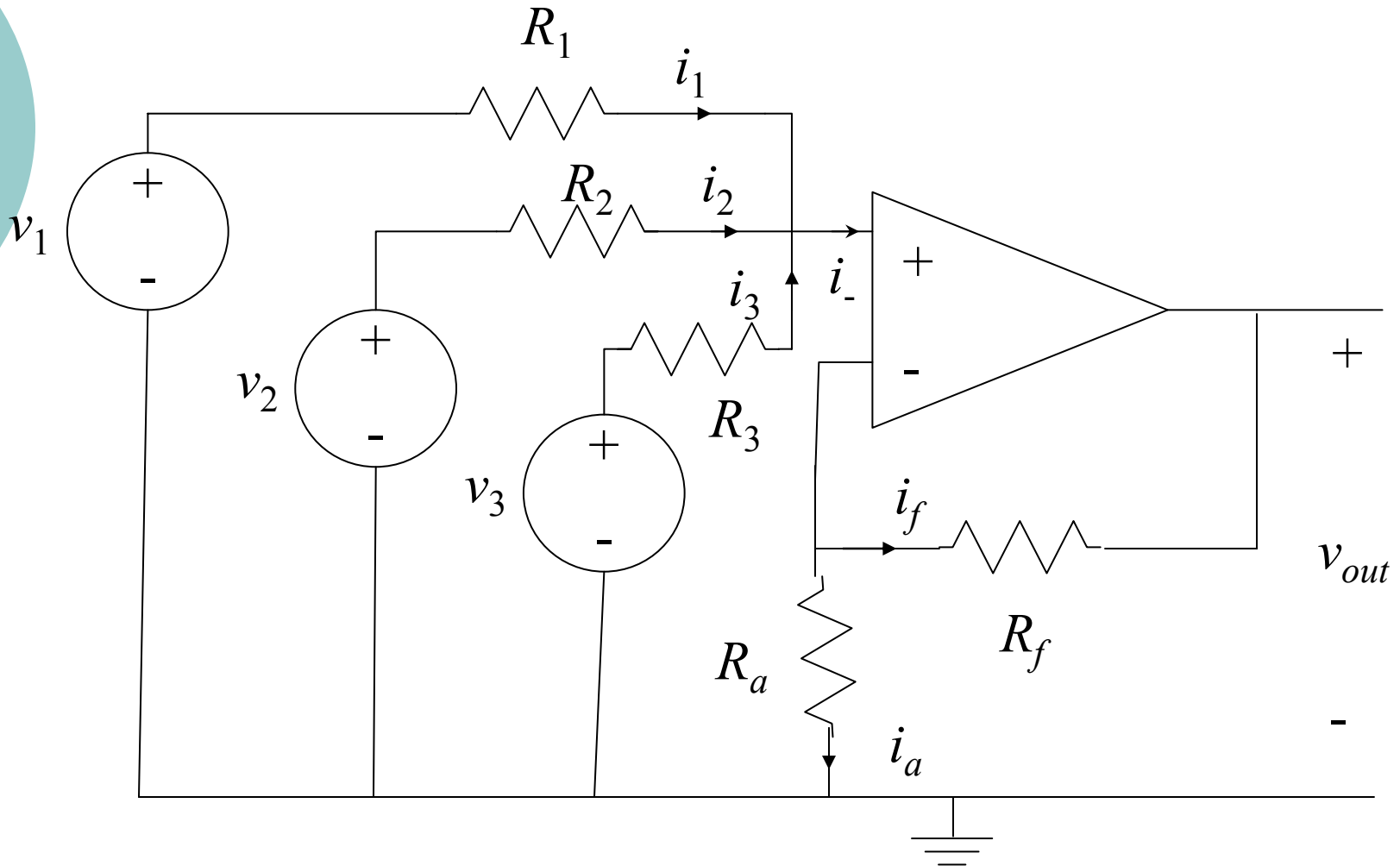

---

KCL at noninverting input:

$$i_1 + i_2 + i_3 = 0$$

$$i_1 = \frac{v_1 - v_+}{R_1}$$

$$i_2 = \frac{v_2 - v_+}{R_2}$$

$$i_3 = \frac{v_3 - v_+}{R_3}$$

KCL at inverting input:

$$i_f + i_a = 0$$

$$i_f = \frac{v_- - v_{out}}{R_f}$$

$$i_a = \frac{v_-}{R_a}$$

$$v_- = \frac{R_a}{R_a + R_f} v_{out}$$

$$v_- = v_+$$

---

$$i_1 + i_2 + i_3 = 0$$


$$\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) v_+$$

$$\frac{1}{R_T} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} = \frac{1}{R_T} \frac{R_a}{R_a + R_f} v_{out}$$

$$v_{out} = \left( 1 + \frac{R_f}{R_a} \right) \left( \frac{R_T}{R_1} v_1 + \frac{R_T}{R_2} v_2 + \frac{R_T}{R_3} v_3 \right)$$


# The difference amplifier

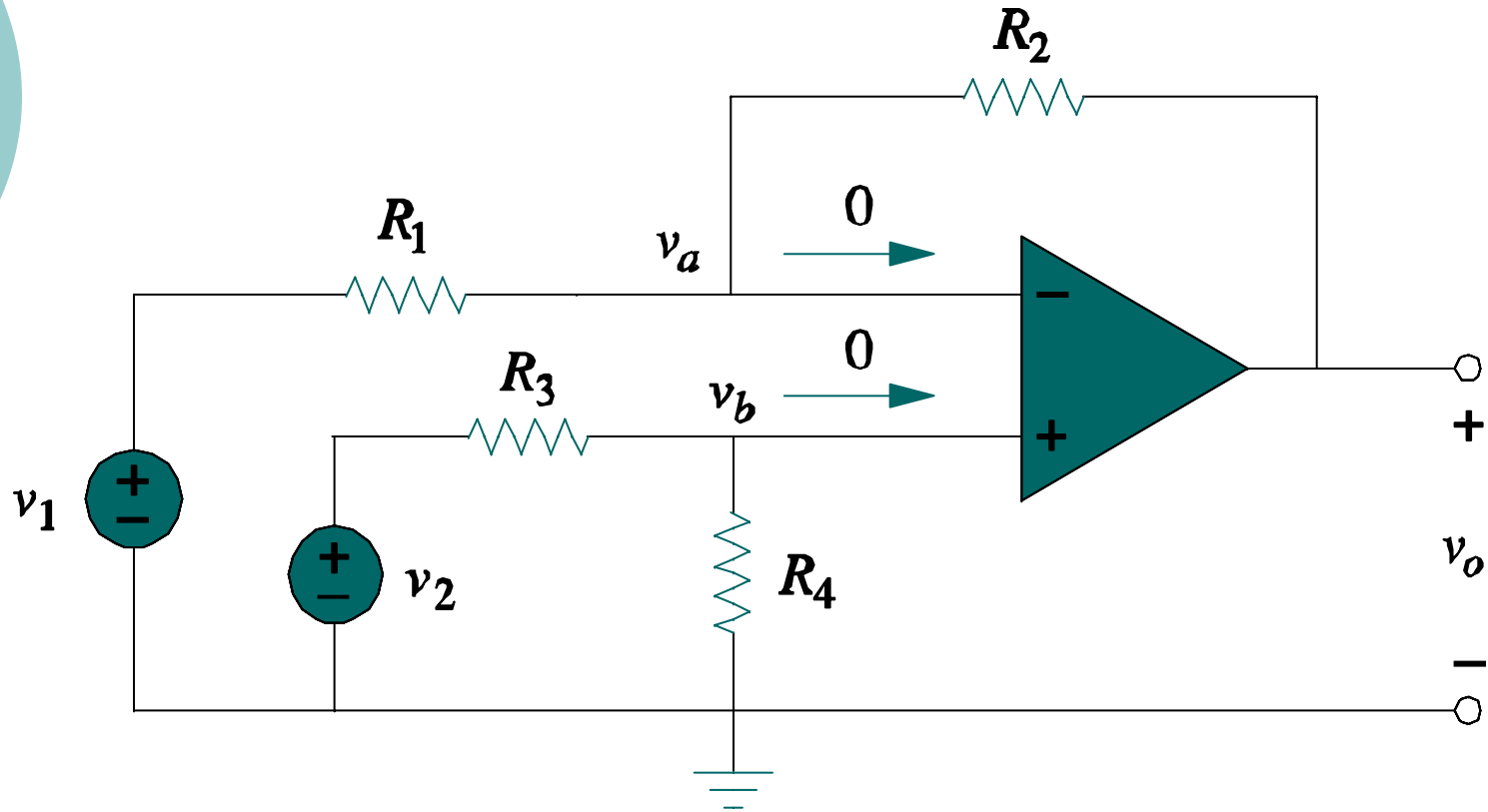

KCL at node  $v_b$  :

$$\frac{v_b - v_2}{R_3} = \frac{v_b}{R_4}$$
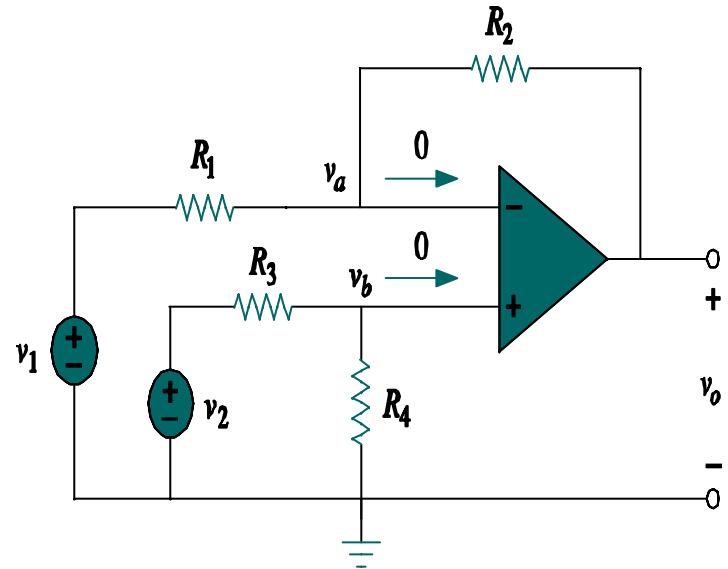
$$v_b = \frac{R_4}{R_3 + R_4} v_2 = v_a$$






KCL at  $v_a$

$$\frac{v_a - v_1}{R_1} + \frac{v_a - v_o}{R_2} = 0$$

$$\frac{1}{R_2} v_o = \left( \frac{1}{R_1} + \frac{1}{R_2} \right) v_a - \frac{1}{R_1} v_1$$

$$v_o = \left( 1 + \frac{R_2}{R_1} \right) v_a - \frac{R_2}{R_1} v_1 = \left( 1 + \frac{R_2}{R_1} \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1$$
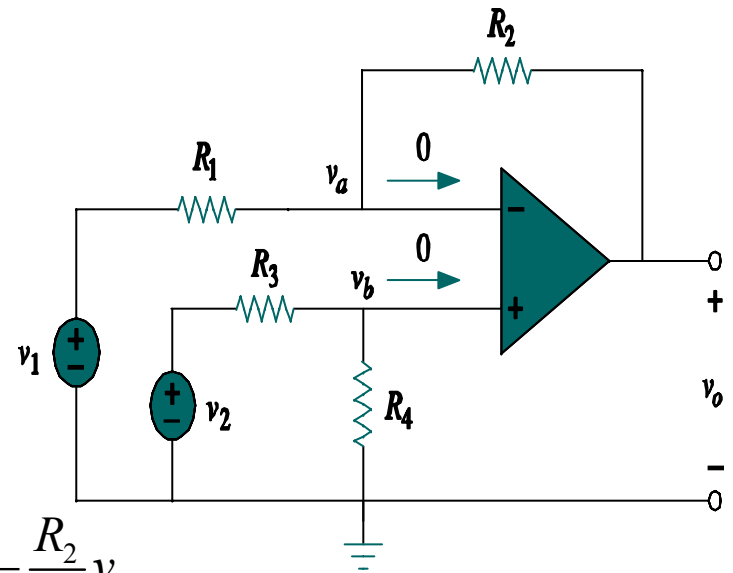
$$v_o = \left( 1 + \frac{R_2}{R_1} \right) \frac{1}{\frac{R_3}{R_4} + 1} v_2 - \frac{R_2}{R_1} v_1 = \frac{R_2}{R_1} \frac{\left( \frac{R_1}{R_2} + 1 \right)}{\frac{R_3}{R_4} + 1} v_2 - \frac{R_2}{R_1} v_1$$



- 
- Since a difference must reject a signal common to the two inputs, the amplifier must have the property that  $v_o = 0$  when  $v_1 = v_2$ . This implies that


$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

When  $R_1 = R_2$  and  $R_3 = R_4$  it acts like a subtractor

$$v_o = v_2 - v_1$$

# Interconnecting of Op Amps

---

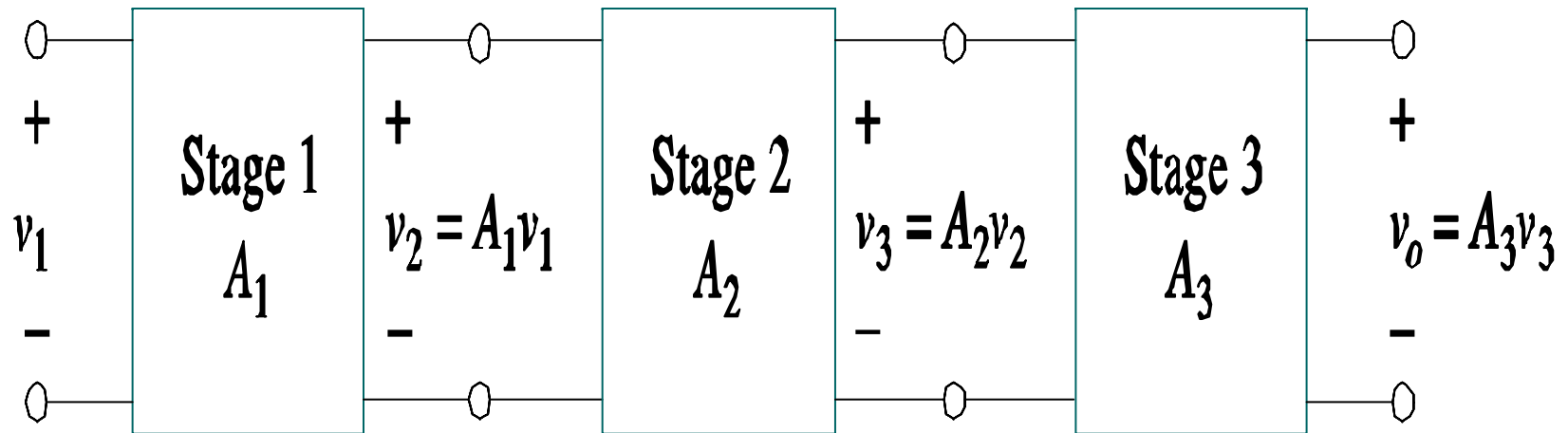

# Example

Find the voltage transfer equation of the following circuit

