



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EEE 223 Circuit Theory I

Fall 2005-06

Instructors:

M. K. Uygurođlu (Gr: 01)

E. Erdil (Gr: 02)

Midterm EXAMINATION

Dec 02, 2005

Duration : 100 minutes

Number of Problems: 4

Good Luck

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

Problem		Points
1		25
2		25
3		25
4		25
<i>TOTAL</i>		100

1. (a) Use nodal analysis to find the branch currents i_1 , i_2 and i_3 in the circuit in Fig.P1.
- (b) Check your solution for i_1 , i_2 and i_3 by showing that the power dissipated in the circuit equals the power developed.

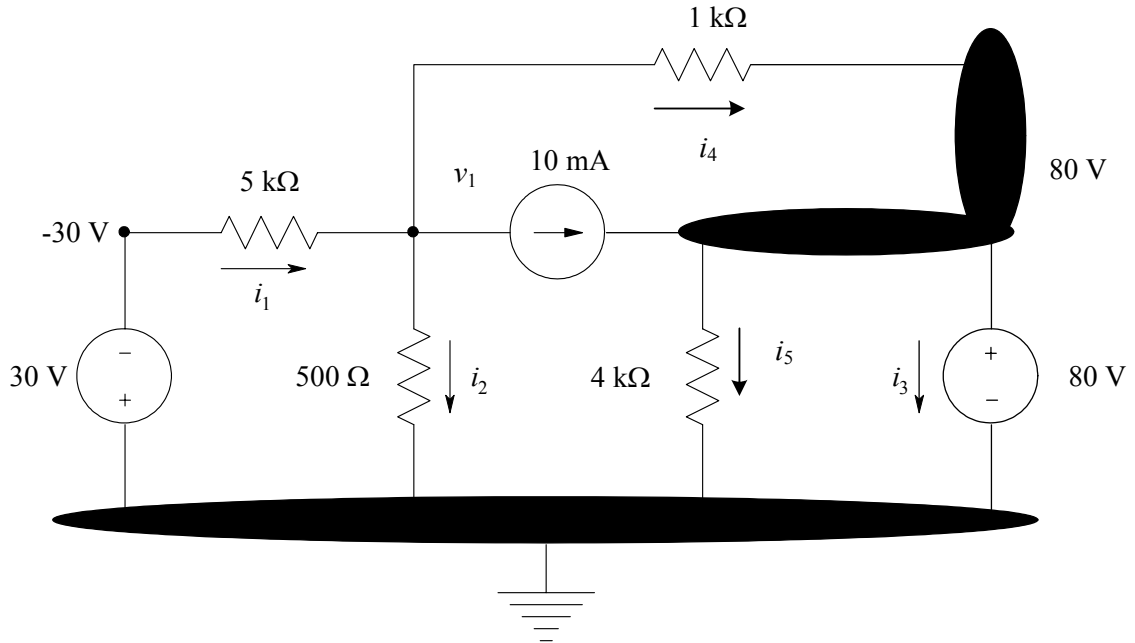


Figure P1

KCL at v_1 :

$$-i_1 + i_2 + i_4 + 10m = 0$$

$$-\frac{-30 - v_1}{5k} + \frac{v_1}{0.5k} + \frac{v_1 - 80}{1k} = -10m$$

multiply both sides by 5k yields

$$30 + v_1 + 10v_1 + 5v_1 - 400 = -50$$

$$16v_1 = 320$$

$$v_1 = \frac{320}{16} = 20 \text{ V}$$

$$i_1 = \frac{-30 - 20}{5k} = -10mA$$

$$i_2 = \frac{20}{0.5k} = 40mA$$

$$i_3 = i_4 + 10m - i_5 = \frac{20 - 80}{1k} + 10m - \frac{80}{4k}$$

$$i_3 = -60m + 10m - 20m = -70mA$$

$$P_{30V} + P_{5k} + P_{0.5k} + P_{10m} + P_{1k} + P_{4k} + P_{80V} = 0$$

$$30(-10m) + (-10m)^2 5k + (40m)^2 0.5k +$$

$$\frac{(20 - 80)^2}{1k} + 10m(20 - 80) + \frac{80^2}{4k} + 80(-70m) = 0$$

$$-300m + 500m + 800m + 3600m - 600m$$

$$+1600m - 5600m = 0$$

2. For the circuit in Fig. P2, find the value of v_0 using mesh analysis.

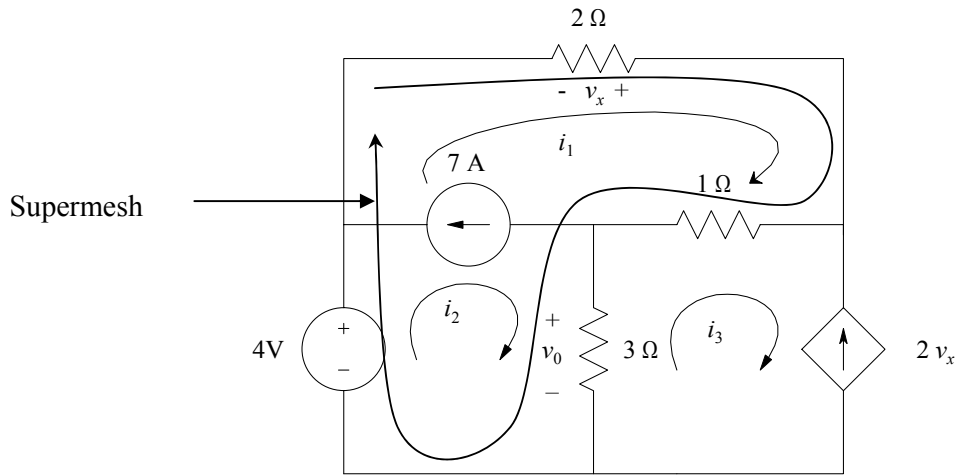


Figure P2

$$v_x = -2i_1$$

$$i_3 = -2v_x = -2(-2i_1) = 4i_1$$

$$i_1 - i_2 = 7$$

$$\boxed{i_2 = i_1 - 7}$$

KVL around the supermesh:

$$2i_1 + 1(i_1 - 4i_1) + 3(i_1 - 7 - 4i_1) - 4 = 0$$

$$(2 + 1 - 4 + 3 - 12)i_1 = 25$$



$$-10i_1 = 25$$

$$\boxed{i_1 = -2.5A}$$

$$v_0 = 3(i_1 - 7 - 4i_1)$$

$$\boxed{v_0 = 1.5V}$$

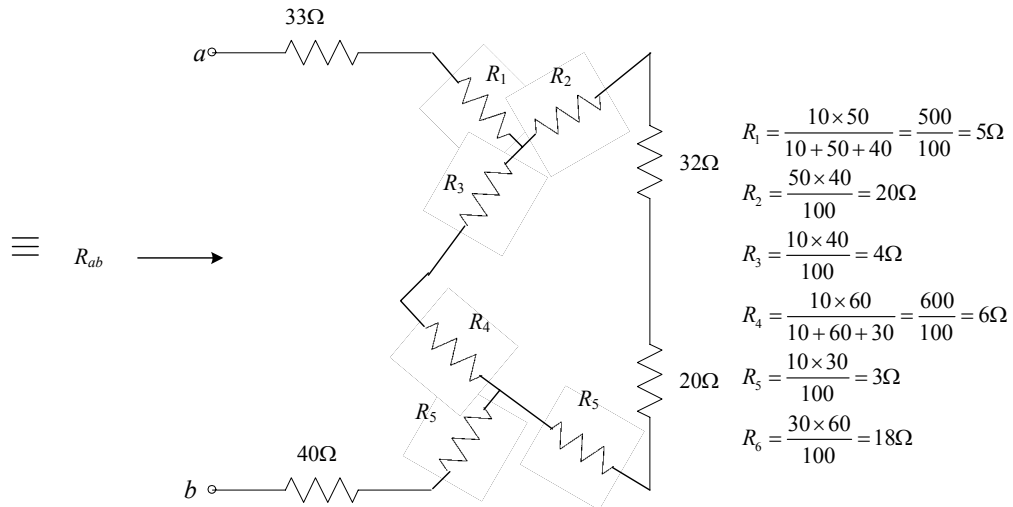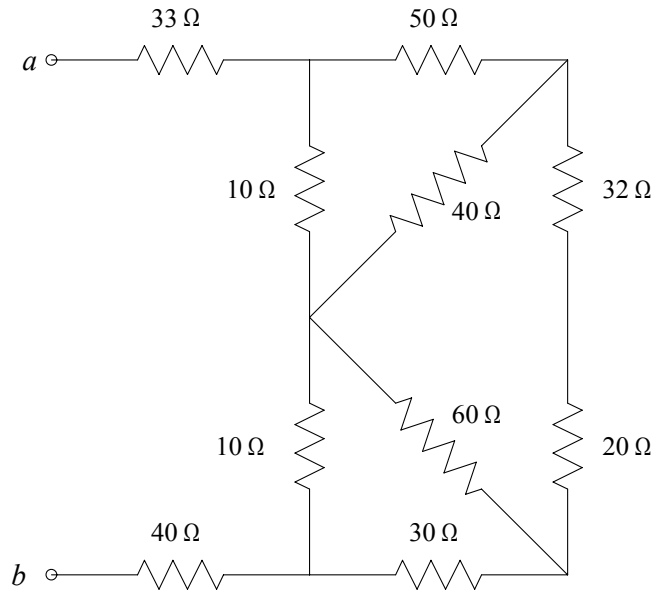3. Find the equivalent resistance R_{ab} in the circuit in Fig. P3.



$$R_{ab} = 33 + R_1 + (R_3 + R_4) // (R_2 + 32 + 20 + R_6) + R_5 + 40$$

$$R_{ab} = 33 + 5 + (4 + 6) // (20 + 32 + 20 + 18) + 3 + 40$$

$$R_{ab} = 33 + 5 + 9 + 3 + 40 = 90\Omega$$

4. The variable resistor in the circuit in Fig. P4 is adjusted for maximum power transfer to R_0 .
- Find the value of R_0 .
 - Find the maximum power that can be delivered to R_0 .


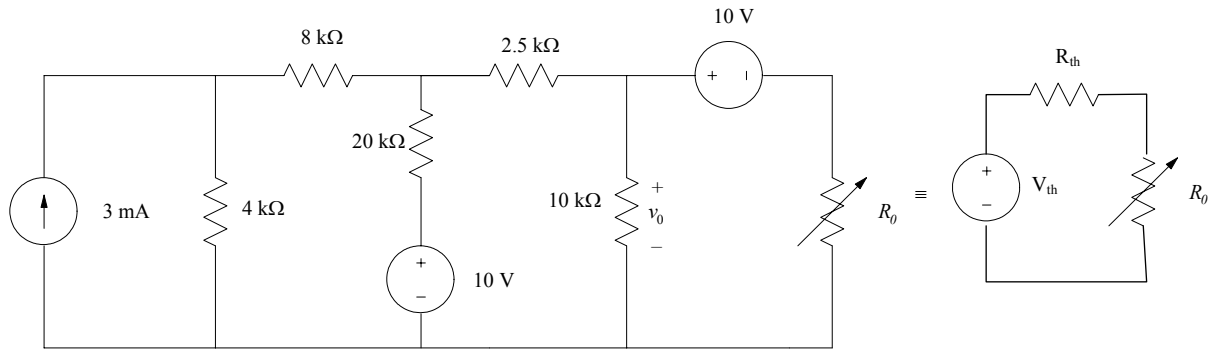


Figure P4

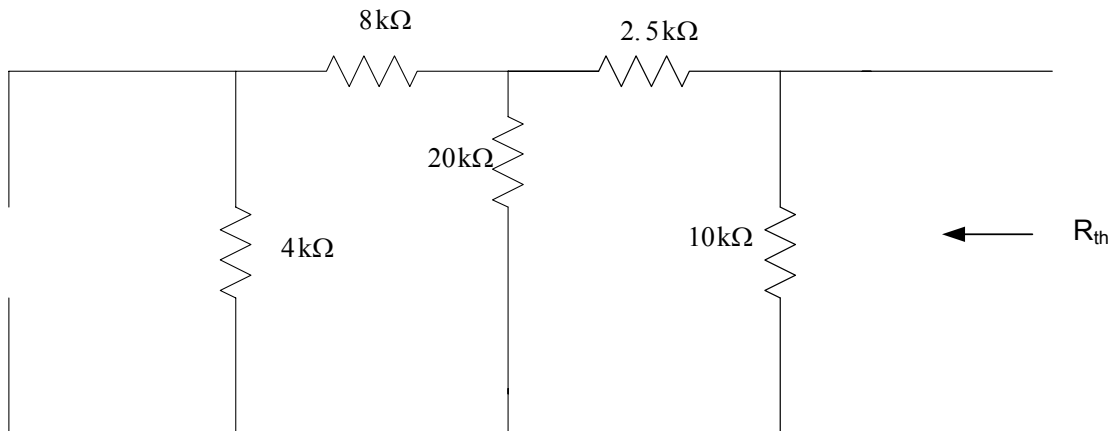
In order to find R_{th} all the independent source values are set to 0.



$$R_{th} = ((8k + 4k) // 20k + 2.5k) // 10k$$

$$R_{th} = (7.5k + 2.5k) // 10k$$

$$\boxed{R_{th} = 5k\Omega}$$

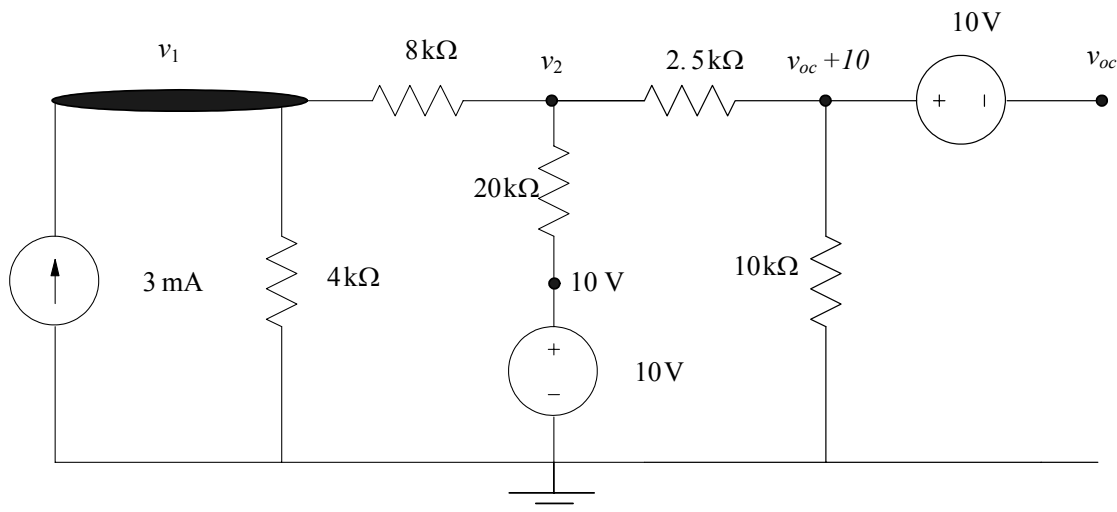

KCL at v_1 :

$$\left(\frac{1}{4k} + \frac{1}{8k}\right)v_1 - \frac{1}{8k}v_2 = 3m$$

multiply both sides by 8k yields:

$$3v_1 - v_2 = 24$$

$$v_1 = 8 + \frac{1}{3}v_2 \dots \dots \dots (1)$$

KCL at v_2 :

$$-\frac{1}{8k}v_1 + \left(\frac{1}{8k} + \frac{1}{20k} + \frac{1}{2.5k}\right)v_2 - \frac{1}{20k}10 - \frac{1}{2.5k}(v_{oc} + 10) = 0$$

multiply both sides by 40k yields:

$$-5v_1 + 23v_2 - 16v_{oc} = 180 \dots \dots \dots (2)$$

KCL at v_3 :

$$-\frac{1}{2.5k}v_2 + \left(\frac{1}{2.5k} + \frac{1}{10k}\right)(v_{oc} + 10) = 0$$

multiply both sides by 10:

$$-4v_2 + 5v_{oc} = -50$$

$$v_{oc} = -10 + \frac{4}{5}v_2 \dots \dots \dots (3)$$

Subst. Eqs. (1) and (3) into (2) gives:

$$-5\left(8 + \frac{1}{3}v_2\right) + 23v_2 - 16\left(-10 + \frac{4}{5}v_2\right) = 180$$

$$\left(-\frac{5}{3} + 23 - \frac{64}{5}\right)v_2 = 180 + 40 - 160 = 60$$

$$(-25 + 345 - 192)v_2 = 900$$

$$128v_2 = 900$$

$$v_2 = 7.03125V$$

$$v_{oc} = -10 + 0.8(7.03125) = -4.375V$$

When $R_0 = R_{th} = 5k\Omega$ it absorbs maximum power.

$$P_{max} = \frac{V_{oc}^2}{4R_{th}} = \frac{(-4.375)^2}{4(5k)} = 0.957mW$$