



**Faculty of Engineering**

**ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT**

***EENG223 Circuit Theory I***

**Fall 2006-07**

**Instructor:**

**M. K. Uyguroğlu**

*Midterm EXAMINATION*

Nov 24, 2006

*Duration : 100 minutes*

Number of Problems: 4

*Good Luck*

<b>STUDENT'S</b>	
NUMBER	
NAME	
SURNAME	
GROUP NO	

<b>Problem</b>		<b>Points</b>
1		25
2		25
3		25
4		25
<i>TOTAL</i>		100


1. (a) The current that enters an element is shown in Fig.P1(a).  
 a) Write the current expression between  $0 < t < 20s$  (5 pts.)  
 b) Find the charge that enters the element in the time interval  $0 < t < 20s$ . (5 pts.)

Figure P1(a)

$$i(t) = \begin{cases} 10 \times 10^{-3} \text{ A} & 0 < t < 10s \\ (-t + 20) \times 10^{-3} & 10 < t < 20s \end{cases}$$

$$q(t) = \int_0^{20} i dt = \int_0^{10} 10 \times 10^{-3} dt + \int_{10}^{20} ((-t + 20) \times 10^{-3}) dt$$
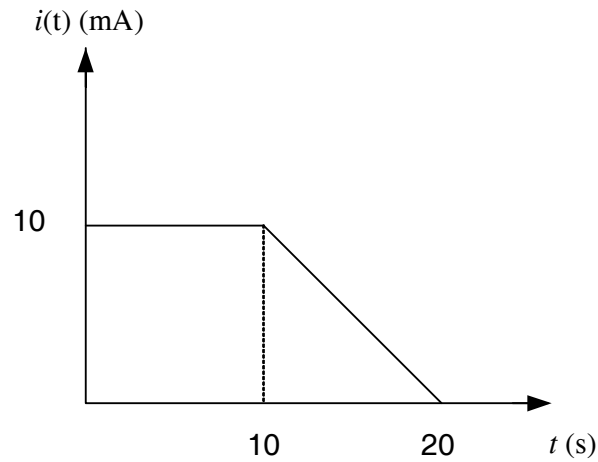
$$q(t) = 100 \times 10^{-3} + 50 \times 10^{-3} = 150 \text{ mC}$$



1. (b) Find  $R_{AB}$  in the circuit in Fig. P1(b). (5 pts.)

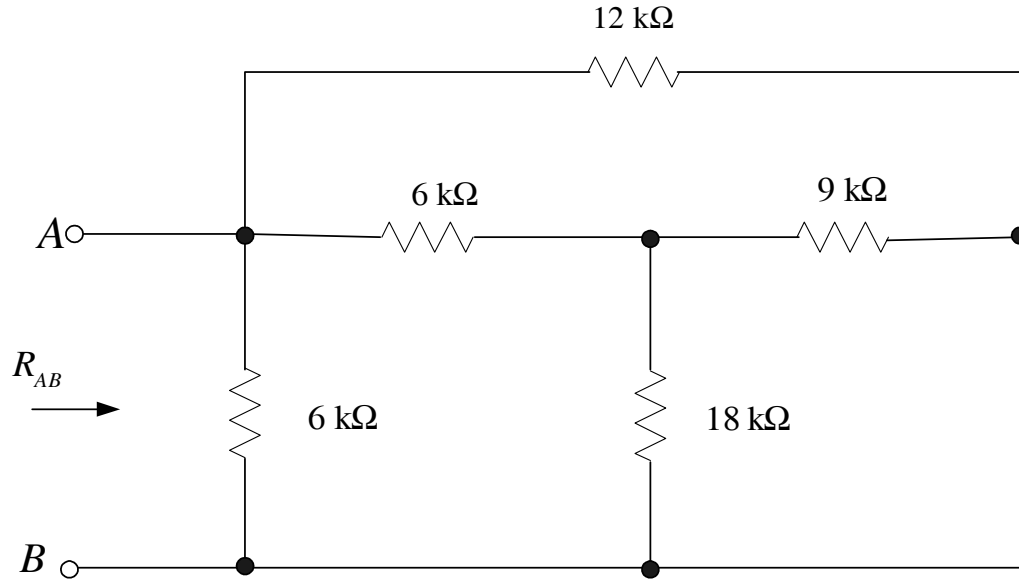


Figure P 1(b)

$$R_{AB} = 6k // (6k + 9k // 18k) // 12k$$

$$R_{AB} = 3k\Omega$$

1. (c) Combine sources and use the voltage division principle to find  $V_{ab}$  in the circuit in Fig.P1(c). (5 pts.)

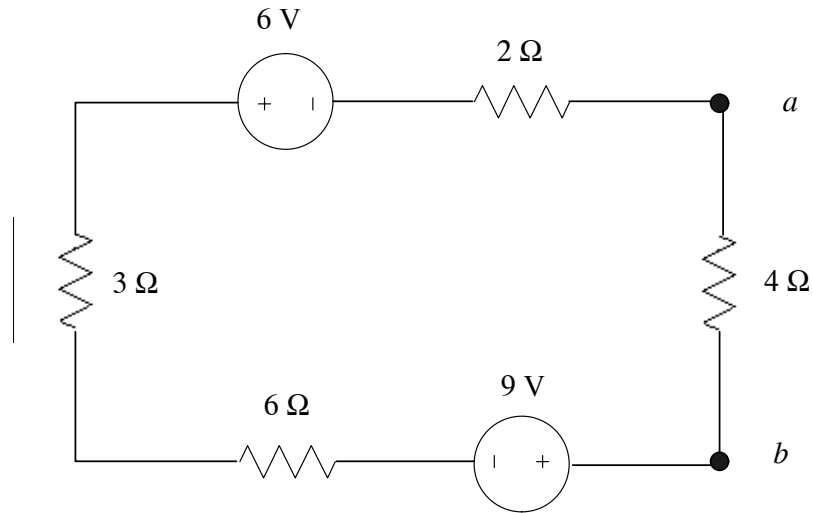


Figure P 1(c)

$$V_{ab} = -15 \frac{4}{15} = -4V$$

1. (d) Use current division principle to find  $I_0$  in the circuit in Fig. P1(d) and the power supplied by 12-mA current source. (5 pts.)

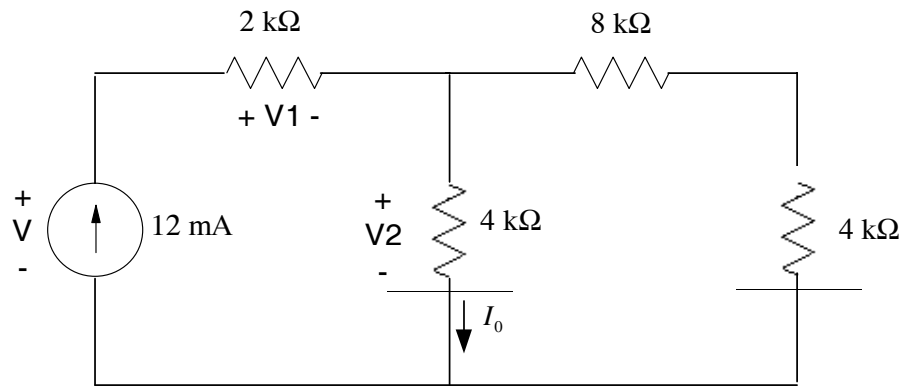


Figure P 1(d)

$$I_0 = 12m \frac{12k}{16k} = 9mA$$

$$V = V1 + V2 = 2k(12m) + 4k(9m) = 60V$$

$$P_{12mA} = -12 \times 10^{-3} (60) = -720mW \text{ supplied}$$

2. Use nodal analysis to find  $I_0$  in the circuit in Fig. P2.


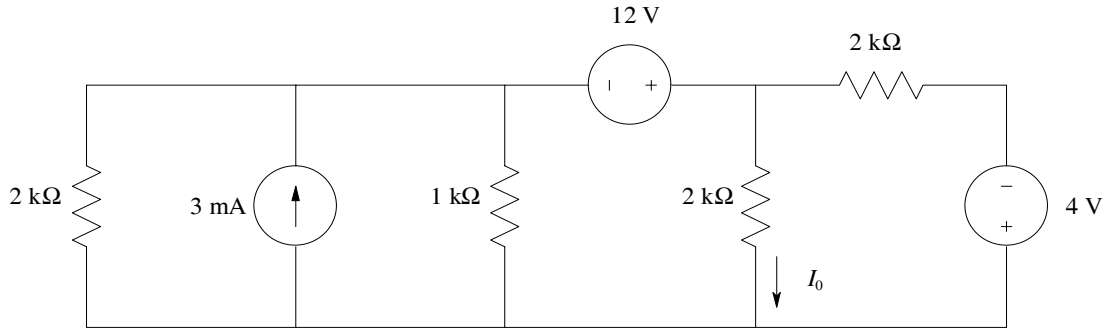


Figure P 2

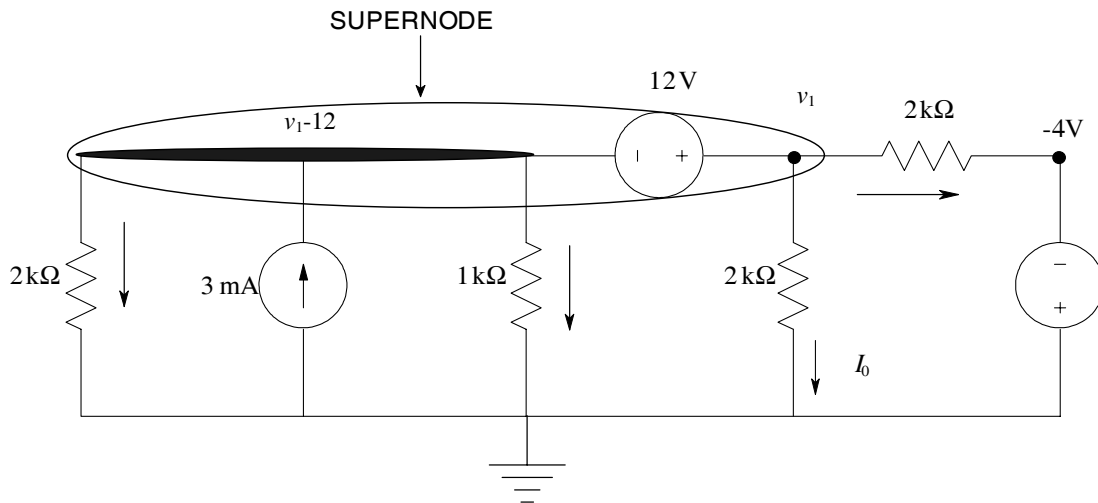

KCL at the supernode:

$$\frac{v_1 - 12}{2k} + \frac{v_1 - 12}{1k} - 3m + \frac{v_1}{2k} + \frac{v_1 + 4}{2k} = 0$$

multiply both sides by 2k yields:

$$v_1 - 12 + 2v_1 - 24 - 6 + v_1 + v_1 + 4 = 0$$

$$5v_1 = 38$$

$$v_1 = \frac{38}{5} = 7.6V$$

$$I_0 = \frac{v_1}{2k} = 3.8mA$$

3. Use mesh analysis to find the power dissipated in the  $1\ \Omega$  resistor in the circuit in Fig.P3.


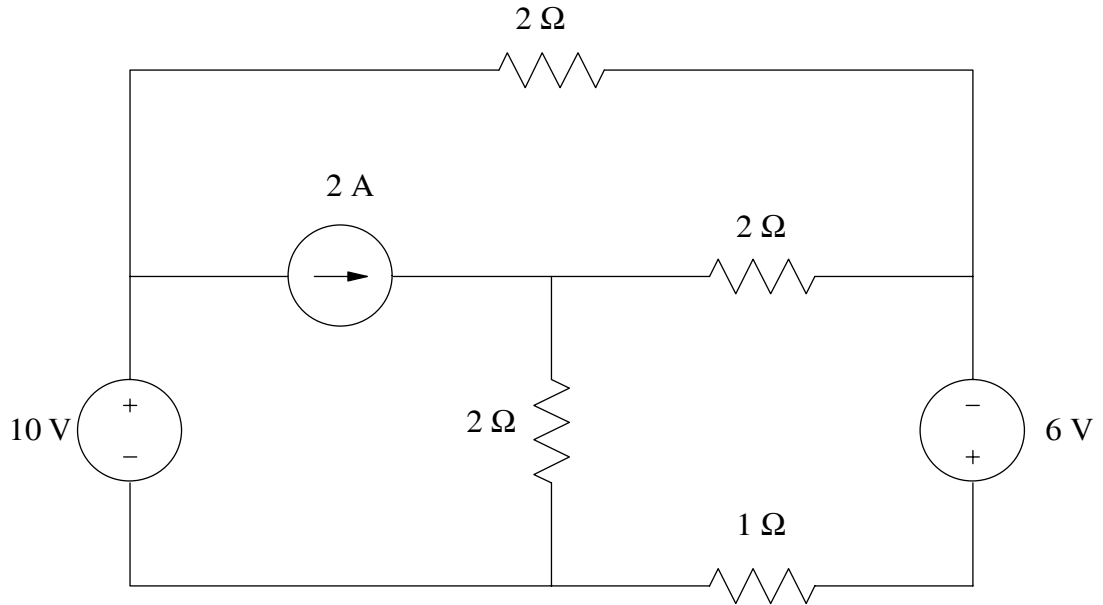


Figure P 3

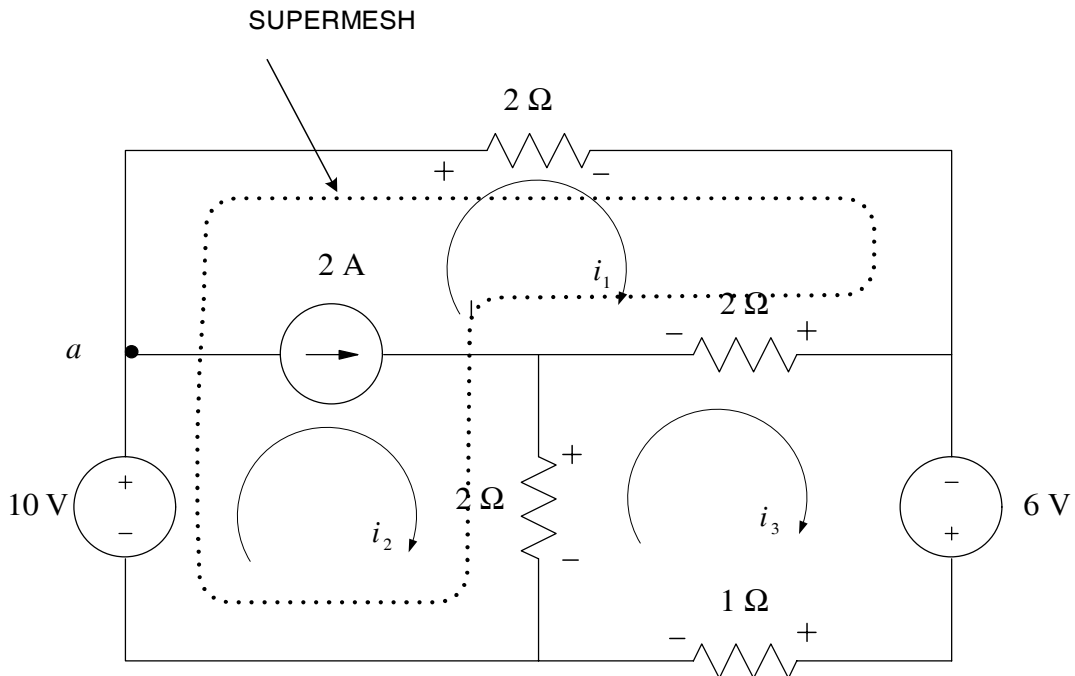

KVL around the supermesh:

$$-10 + 2i_1 + 2(i_1 - i_2) + 2(i_2 - i_3) = 0$$

$$4i_1 + 2i_2 - 4i_3 = 10 \dots\dots\dots(1)$$

KVL around  $i_3$ :

$$\begin{aligned} -2(i_2 - i_3) - 2(i_1 - i_3) - 6 + 1i_3 &= 0 \\ -2i_1 - 2i_2 + 5i_3 &= 6 \dots\dots\dots (2) \end{aligned}$$

KCL at node  $a$ :

$$\begin{aligned} -i_2 + i_1 + 2 &= 0 \\ \text{or} \\ i_2 &= i_1 + 2 \dots\dots\dots (3) \end{aligned}$$

Subst. of Eq.(3) into (1) and (2) and solving for  $i_3$  yields:

$$\begin{aligned} i_3 &= 6A \\ \therefore P_{1\Omega} &= (i_3)^2 1 = 36W \end{aligned}$$



4. Find the value of  $I_0$  in the circuit in Fig. P4 using  
 a) Superposition  
 b) Source transformation

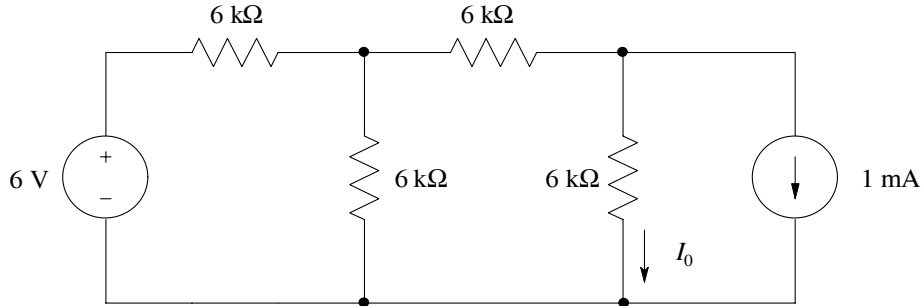


Figure P 4


a) Superposition

6 V voltage source is active:


$$R_T = 6k + 6k \parallel (6k + 6k) = 10k\Omega$$

$$I_T = \frac{6}{10k} = 0.6mA$$
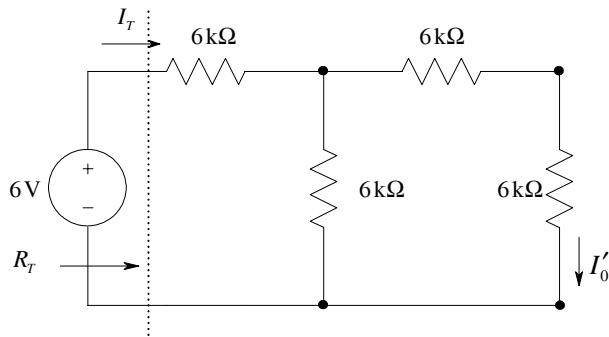
$$I'_0 = 0.6 \times 10^{-3} \frac{6k}{6k + 12k} = 0.2mA$$



1 mA current source is active:





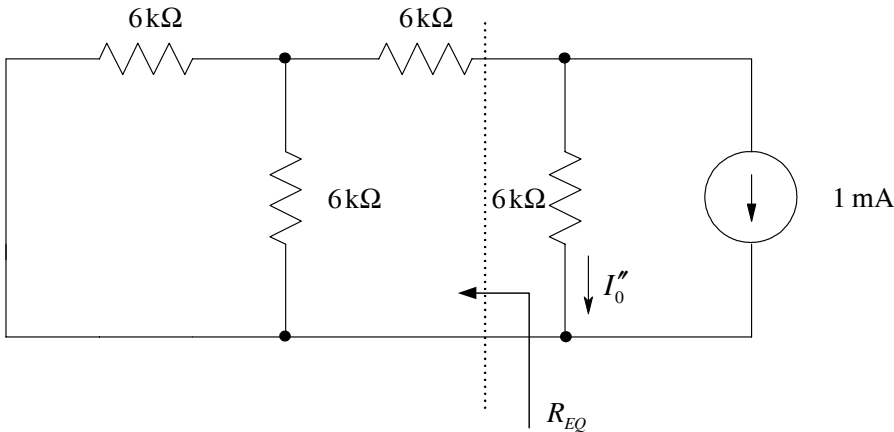


$$R_{EQ} = 6k + 6k \parallel 6k = 9k\Omega$$

$$I''_0 = -1 \times 10^{-3} \frac{R_{EQ}}{R_{EQ} + 6k} = -1 \times 10^{-3} \frac{9k}{15k} = -0.6mA$$

$$\therefore I_0 = I'_0 + I''_0 = 0.2m - 0.6m = -0.4mA$$

B) Source transformation

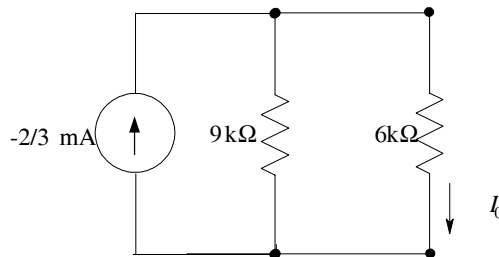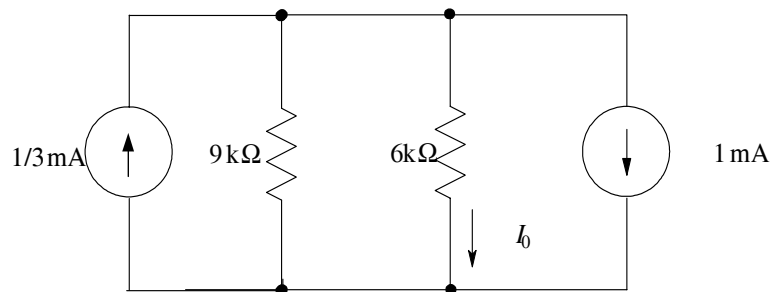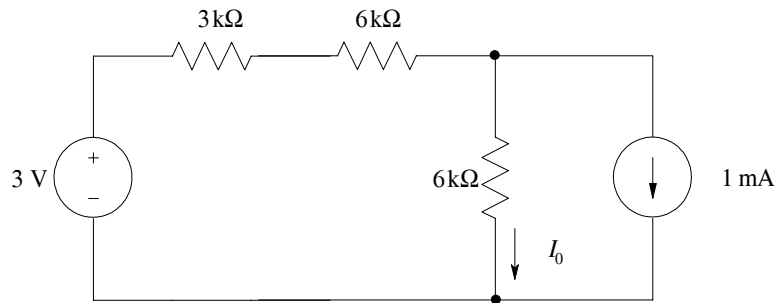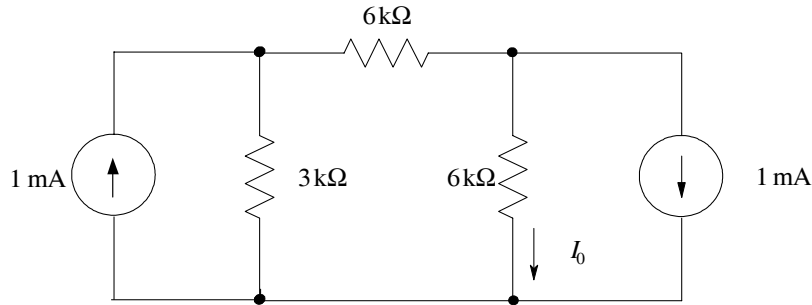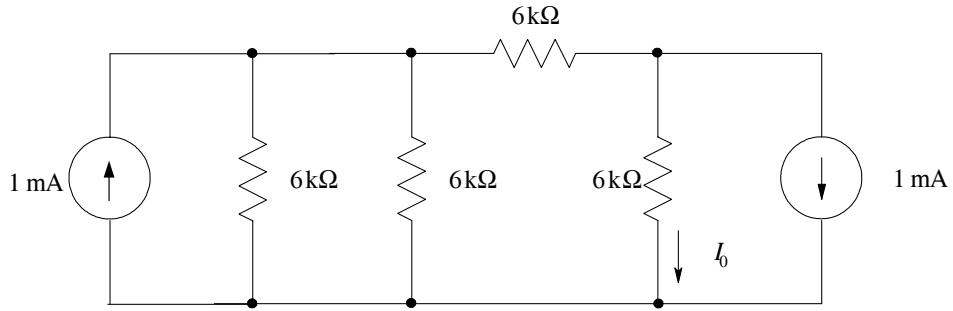

$$I_0 = -\frac{2}{3} \times 10^{-3} \frac{9k}{9k + 6k} = -0.4mA$$