



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EENG223 Circuit Theory I

Fall 2007-08

Instructor:

**M. K. Uygurođlu
E. G. Erdil**

Final EXAMINATION

Jan 15, 2008

Duration : 120 minutes

Number of Problems: 4

Good Luck

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

Problem		Points
1		30
2		20
3		25
4		25
TOTAL		100

1. Find v_0 in the circuit in Fig. P1,
 - a) using nodal analysis. (15 pts.)
 - b) using mesh analysis. (15 pts.)

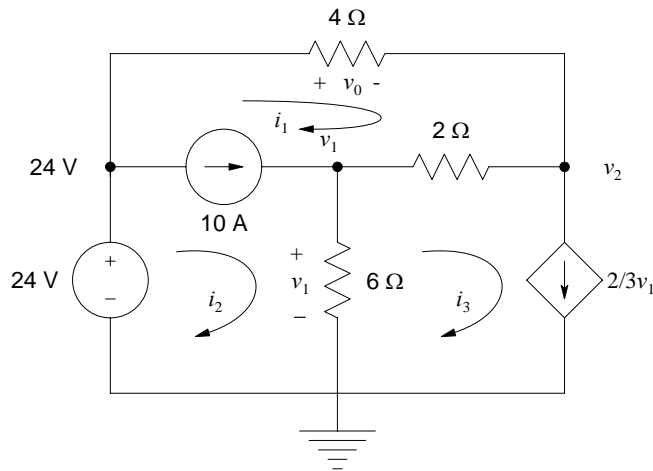


Figure P1

Using Nodal Analysis

KCL at v_1 :

$$\left(\frac{1}{6} + \frac{1}{2}\right)v_1 - \frac{1}{2}v_2 = 10$$

Multiply both sides by 6 yields:

$$4v_1 - 3v_2 = 60 \dots\dots\dots(1)$$

KCL at v_2 :

$$-\frac{1}{2}v_1 + \left(\frac{1}{2} + \frac{1}{4}\right)v_2 - \frac{1}{4}(24) = -\frac{2}{3}v_1$$

Multiply both sides by 12 gives:

$$-6v_1 + 9v_2 - 72 = -8v_1$$

or

$$2v_1 + 9v_2 = 72 \dots\dots\dots(2)$$

Multiply Eq.(2) by -2 and add to Eq.(1) gives:

$$-21v_2 = -84 \Rightarrow v_2 = 4 \text{ V}$$

$$v_0 = 24 - v_2 = 20 \text{ V}$$

Using Mesh Analysis

$$i_3 = \frac{2}{3}v_1 = \frac{2}{3}(6)(i_2 - i_3) = 4i_2 - 4i_3$$

$$i_3 = \frac{4}{5}i_2 \dots\dots\dots(1)$$

$$i_2 - i_1 = 10$$

$$i_1 = i_2 - 10 \dots\dots\dots(2)$$

Mesh 1 and mesh 2 constitute a SUPERMESH.

KVL around the SUPERMESH:

$$4i_1 + 2(i_1 - i_3) + 6(i_2 - i_3) - 24 = 0$$

$$4(i_2 - 10) + 2\left(i_2 - 10 - \frac{4}{5}i_2\right) + 6\left(i_2 - \frac{4}{5}i_2\right) = 24$$

$$\left(4 + 2 - \frac{8}{5} + 6 - \frac{24}{5}\right)i_2 = 24 + 40 + 20$$

$$(12 - 6.4)i_2 = 84$$

$$5.6i_2 = 84$$

$$i_2 = \frac{84}{5.6} = 15 \text{ A}$$

$$v_0 = 4(i_2 - 10) = 20 \text{ V}$$

2. Find the value of R that will draw the maximum power from the rest of the circuit in Fig. P2. Also find the maximum power. (20 pts.)


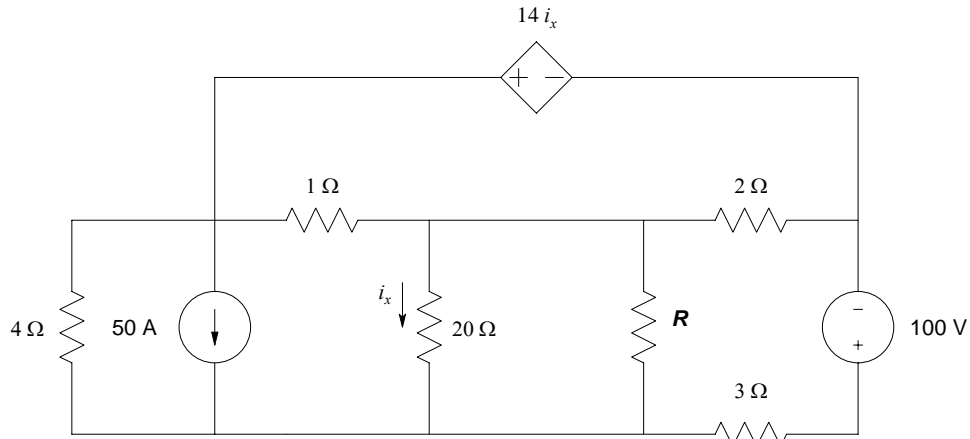


Figure P2

In order to find R_{TH} :

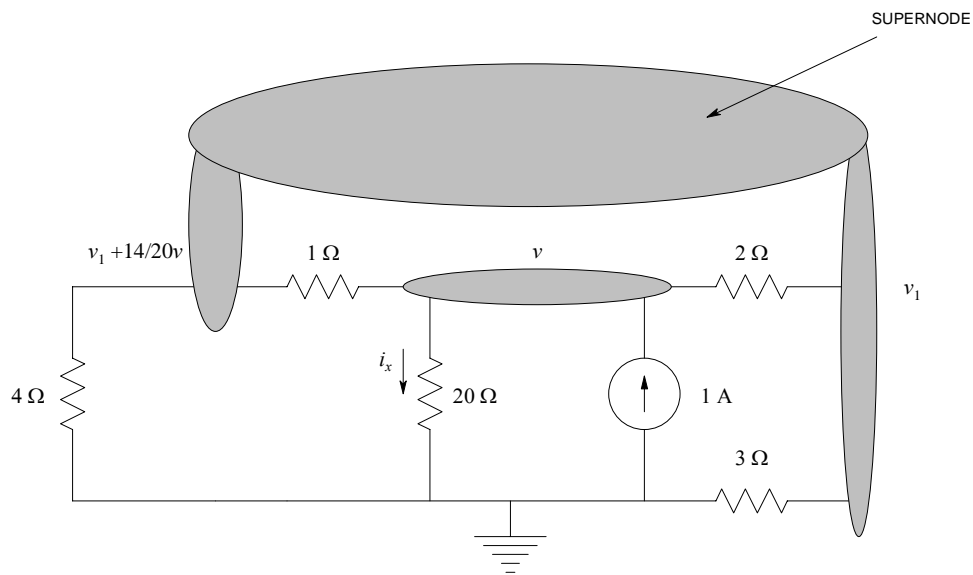

KCL at v :

$$\left(\frac{1}{2} + 1 + \frac{1}{20}\right)v - \frac{1}{2}v_1 - \left(v_1 + \frac{14}{20}v\right) = 1$$

Multiply both sides by 20 yields:

$$(10 + 20 + 1)v - 10v_1 - 20v_1 - 14v = 20$$

$$17v - 30v_1 = 20 \dots \dots \dots (1)$$

KCL at the SUPERNODE:

$$\left(\frac{1}{4}+1\right)\left(v_1+\frac{14}{20}v\right)+\left(\frac{1}{2}+\frac{1}{3}\right)v_1-\left(1+\frac{1}{2}\right)v=0$$

$$\left(\frac{5}{4}v_1+\frac{7}{8}v\right)+\left(\frac{1}{2}+\frac{1}{3}\right)v_1-\left(1+\frac{1}{2}\right)v=0$$

Multiply both sides by 24 yields:

$$30v_1+21v+20v_1-36v=0$$


$$-15v+50v_1=0\text{.....(2)}$$

From Eq. (1) and (2) we can obtain v as:

$$v=2.5V$$

$$R_{TH}=\frac{v}{1}=2.5\Omega$$

For V_{TH} :

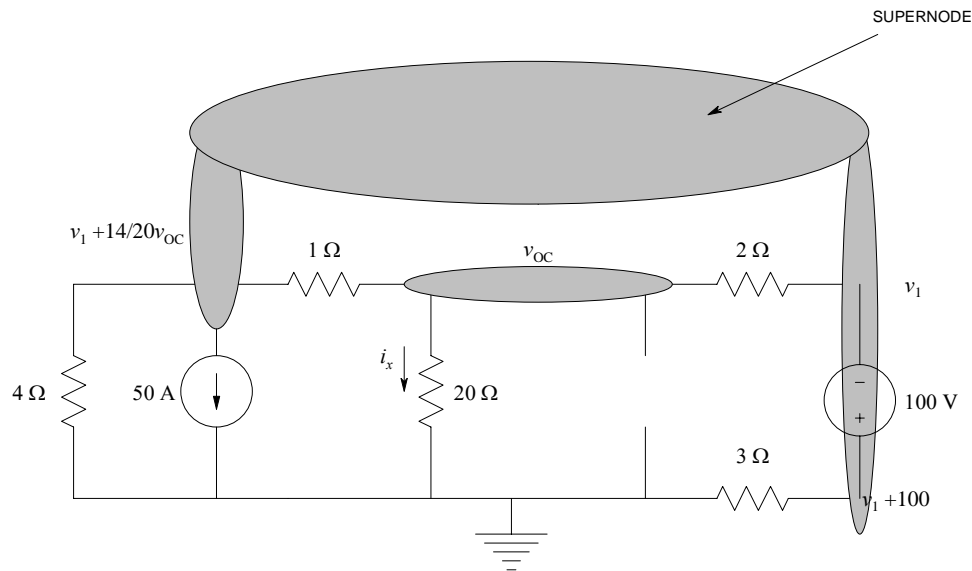

KCL at v_{oc} :

$$\left(\frac{1}{2}+1+\frac{1}{20}\right)v_{oc}-\frac{1}{2}v_1-\left(v_1+\frac{14}{20}v_{oc}\right)=0$$

Multiply both sides by 20 yields:

$$(10+20+1)v_{oc}-10v_1-20v_1-14v_{oc}=0$$

$$17v_{oc}-30v_1=0\text{.....(1)}$$

KCL at the SUPERNODE:

$$\left(\frac{1}{4}+1\right)\left(v_1+\frac{14}{20}v_{oc}\right)+\left(\frac{1}{2}\right)v_1+\left(\frac{1}{3}\right)(v_1+100)-\left(1+\frac{1}{2}\right)v_{oc}=-50$$

$$\left(\frac{5}{4}v_1+\frac{7}{8}v_{oc}\right)+\left(\frac{1}{2}\right)v_1+\left(\frac{1}{3}\right)(v_1+100)-\left(1+\frac{1}{2}\right)v_{oc}=-50$$

Multiply both sides by 24 yields:

$$30v_1+21v_{oc}+12v_1+8v_1+800-36v_{oc}=-1200$$

$$-15v_{oc}+50v_1=-2000\text{.....(2)}$$

From Eq. (1) and (2) v_{oc} is obtained as:

$$v_{oc}=V_{TH}=-150V$$

When the value of $R=R_{TH}$ then it draws maximum power and the maximum power is:

$$P_{\max}=\frac{V_{TH}^2}{4R_{TH}}=\frac{22500}{10}=2250W$$

3. In the circuit given in Fig. P3, label (insert with values) the voltages V_1 , V_2 , V_3 , and resistors (in ohms), so that the output voltage $V_0 = 3V_1 - 2V_2 - V_3$.

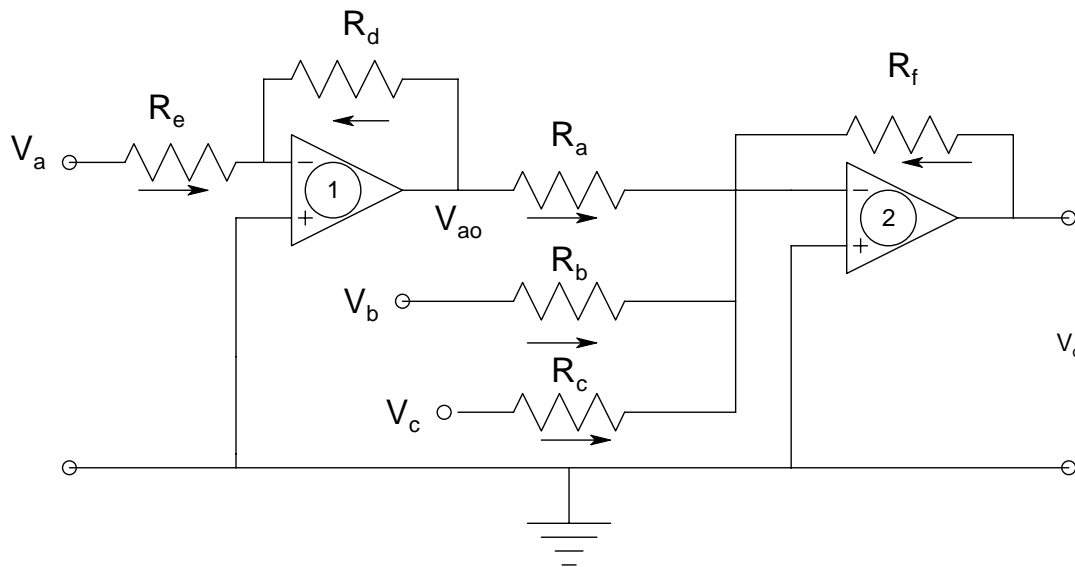


Figure P3

KCL at the inverting input terminal of OP-AMP 1

$$\frac{V_a}{R_e} + \frac{V_{ao}}{R_d} = 0 \Rightarrow V_{ao} = -\frac{R_d}{R_e} V_a$$

KCL at the inverting input terminal of OP-AMP 2

$$\frac{V_{ao}}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} + \frac{V_0}{R_f} = 0 \Rightarrow V_{ao} = -\frac{R_f}{R_a} V_{ao} - \frac{R_f}{R_b} V_b - \frac{R_f}{R_c} V_c = \frac{R_f R_d}{R_a R_e} V_a - \frac{R_f}{R_b} V_b - \frac{R_f}{R_c} V_c$$

Therefore

$$V_1 = V_a$$

$$V_2 = V_b$$

$$V_3 = V_c$$

And

$$\frac{R_f}{R_a} \frac{R_d}{R_e} = 3$$

$$\frac{R_f}{R_b} = 2 = R_f = 2R_b$$

$$\frac{R_f}{R_c} = 1 \Rightarrow R_f = R_c$$

if we choose $R_f = 150\Omega$ then $R_c = 150\Omega$, $R_b = 75\Omega$ and

if we choose $R_d = R_e = 100\Omega$ then $R_a = 50\Omega$

4. In the circuit given in Fig. P4, switches S_1 and S_2 are open for a long time. When $t=0$ switch S_1 is closed while switch S_2 is kept open. After 10 seconds the switch S_2 is ALSO closed.
- Find $i(t)$ flowing through the inductor for $t > 0$
 - The voltage across the $4\text{-}\Omega$ resistor when $t = 2$ seconds
 - The voltage across the $4\text{-}\Omega$ resistor when $t = 12$ seconds.


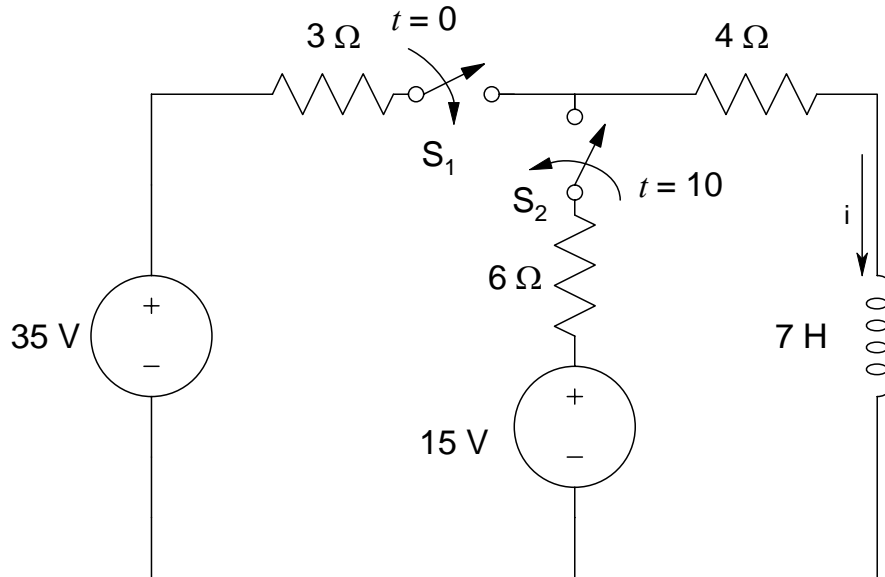


Figure P4

$t < 0$

$$i(t) = 0 \text{ A}$$

$0 < t < 10\text{s}$

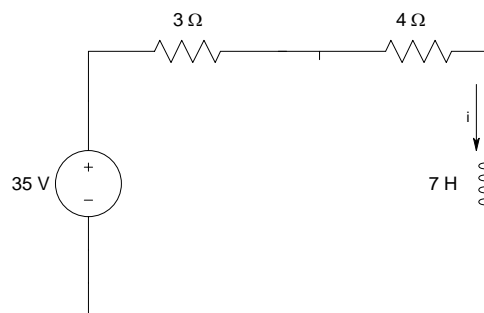

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}}$$

Where $i(\infty) = \frac{35}{7} = 5 \text{ A}$ (since the inductor acts like a short circuit at $t = \infty$)

And


$$\tau = \frac{L}{R_{eq}} = \frac{7}{7} = 1\text{s}$$

Therefore

$$i(t) = 5 + [0 - 5]e^{-t} = 5 - 5e^{-t} \text{ A}$$

$$v(2s) = 4i(2) = 20 - 20e^{-2} \text{ V}$$


For $t > 10s$

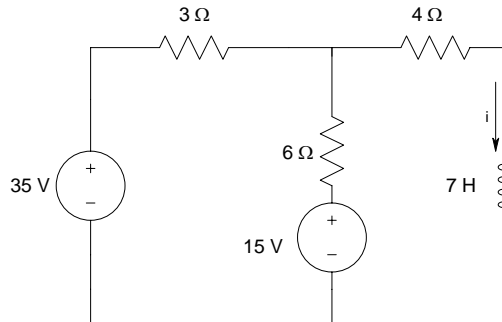

$$i(t) = i(\infty) + [i(10) - i(\infty)]e^{-\frac{(t-10)}{\tau}}$$

where

$$i(10) = 5 - 5e^{-10} \text{ A}$$

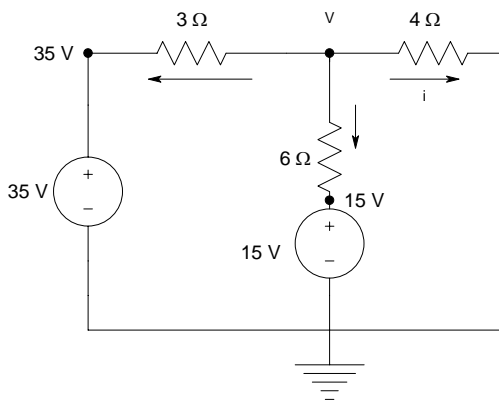

At $t = \infty$, the circuit is under dc conditions. In order to find $i(\infty)$:

KCL at v:

$$\left(\frac{1}{3} + \frac{1}{6} + \frac{1}{4}\right)v - \frac{1}{3}35 - \frac{1}{6}15 = 0$$

Multiply both sides by 12 yields:

$$(9)v = 140 + 30 = 170$$

$$v = \frac{170}{9} \text{ V}$$

$$i(\infty) = \frac{v}{4} = \frac{170}{36} = \frac{85}{18} \text{ A}$$

$$\text{Time constant } \tau = \frac{L}{R_{eq}}$$

$$R_{eq} = 3 // 6 + 4 = 6\Omega$$

$$\tau = \frac{7}{6} \text{ s}$$

$$i(t) = \frac{85}{18} + \left[5 - 5e^{-10} - \frac{85}{18}\right]e^{-\frac{6}{7}(t-10)}$$

$$v(12) = 4i(12) = \frac{340}{18} + \left[20 - 20e^{-10} - \frac{340}{18}\right]e^{-\frac{12}{7}} \text{ V}$$