



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EENG223 Circuit Theory I
INFE221 – Electrical Circuits

FALL 2008-09

Instructor:

M. K. Uygurođlu

Final EXAMINATION

January 29, 2009

Duration : 150 minutes

Number of Problems: 6

Good Luck

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

Problem		Points
1		15
2		15
3		15
4		20
5		15
6		20
<i>TOTAL</i>		100

1. (a) Use superposition to find v_0 in the circuit in Fig.P1(a). (5 pts.)


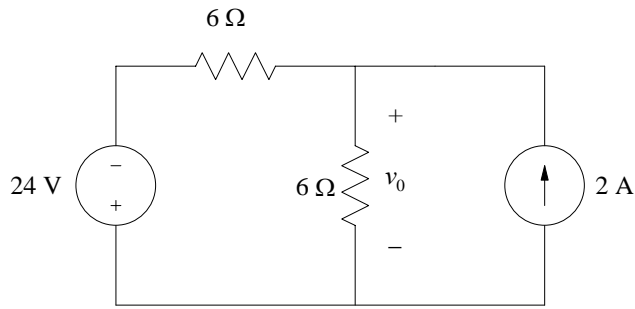


Figure P1(a)

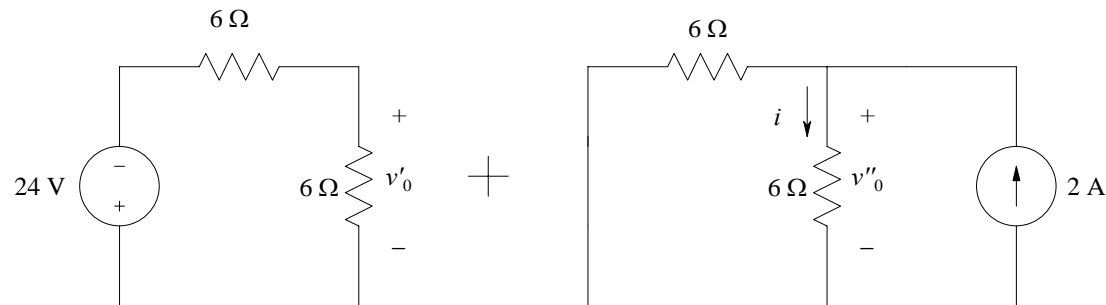

$$v'_0 = -24 \frac{6}{12} = -12 \text{ V}$$

$$v''_0 = 6i = 6 \left(2 \frac{6}{12} \right) = 6 \text{ V}$$

$$v_0 = v'_0 + v''_0 = -12 + 6 = -6 \text{ V}$$

1. (b) Use source transformation to find v_0 in the circuit in Fig.P1(b). (5 pts.)


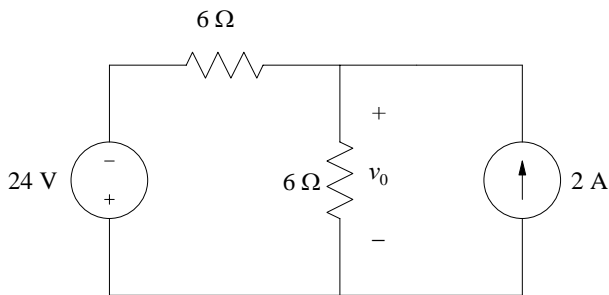


Figure P1(b)

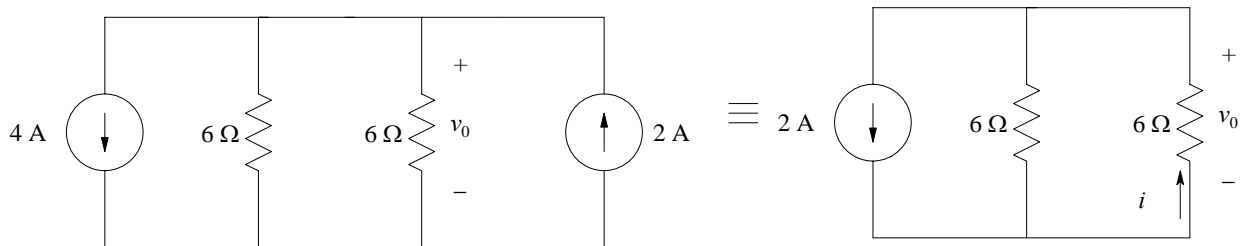

$$v_0 = -6i = -6 \left(2 \frac{6}{12} \right) = -6 \text{ V}$$

1. (c) Determine V_{TH} , R_{TH} , I_N , and R_N at terminals 1-2 of the circuit in Fig.P1c.
(5 pts.)



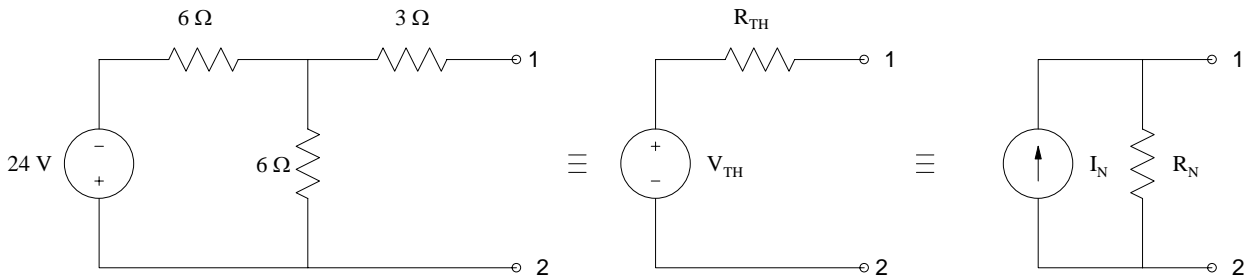


Figure P1(c)

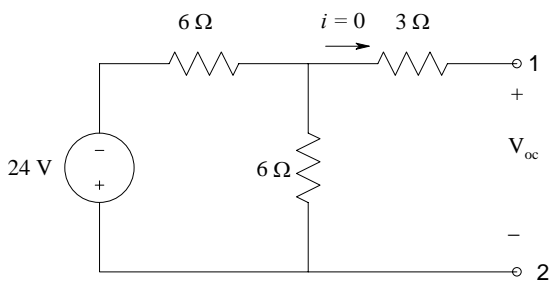
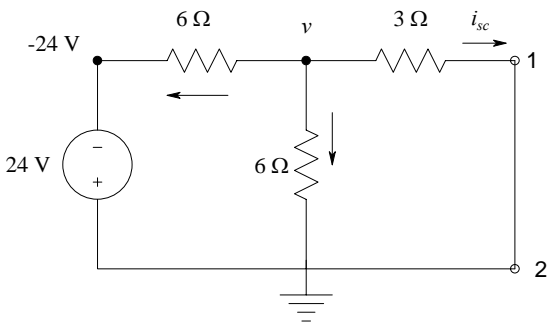
$$V_{oc} = -24 \frac{6}{6+6} = -12 \text{ V} = V_{TH}$$



KCL at v :

$$\frac{v+24}{6} + \frac{v}{6} + \frac{v}{3} = 0 \quad \text{multiply both sides by 6 yields:}$$

$$v+24+v+2v=0$$

$$v = -6 \text{ V}$$

$$i_{sc} = \frac{v}{3} = -2 \text{ A} = I_N$$

$$R_{TH} = R_N = \frac{v_{oc}}{i_{sc}} = \frac{-12}{-2} = 6 \Omega$$

2. Find v in the circuit in Fig.P2 using nodal analysis. (15 pts.)

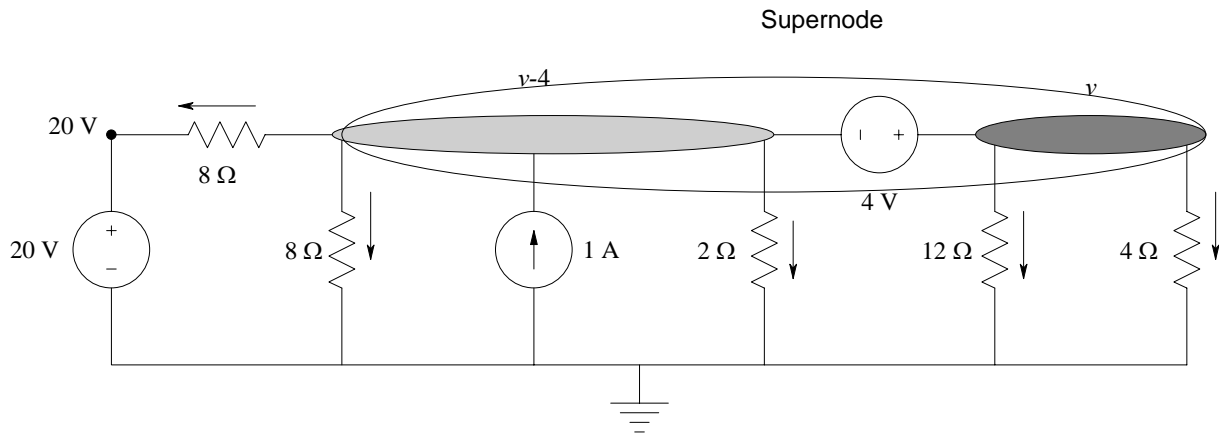


Figure P2

KCL at SUPERNODE:

$$\frac{v-4-20}{8} + \frac{v-4}{8} + \frac{v-4}{2} + \frac{v}{12} + \frac{v}{4} = 1$$

Multiply both sides by 24 yields:

$$\frac{v-4-20}{8} + \frac{v-4}{8} + \frac{v-4}{2} + \frac{v}{12} + \frac{v}{4} = 1$$

$$3v - 72 + 3v - 12 + 12v - 48 + 2v + 6v = 24$$

$$26v = 156$$

$$\boxed{v = 6 \text{ V}}$$

3. Find v in the circuit in Fig.P3 using mesh analysis. (15 pts.)

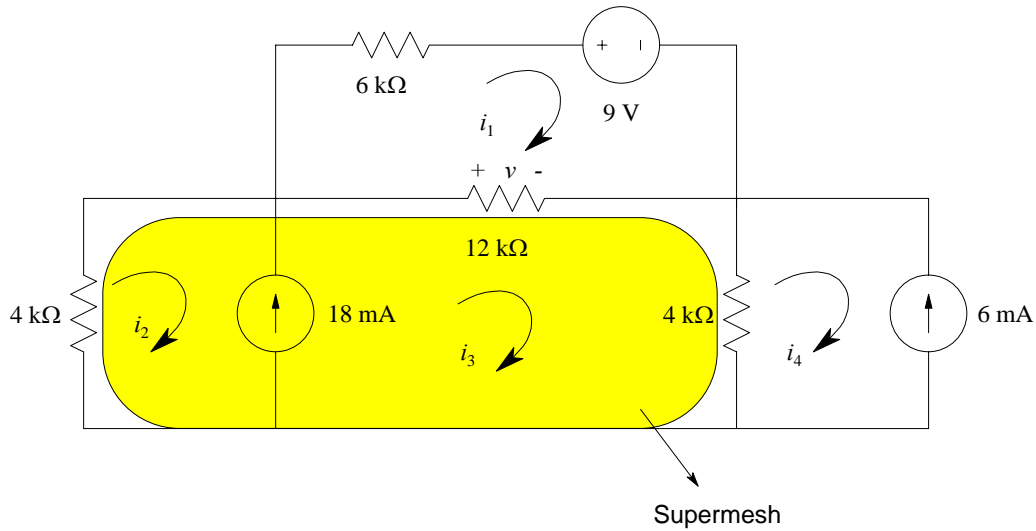


Figure P3

$$i_4 = -6mA$$

$$i_3 - i_2 = 18mA$$

$$i_3 = 18mA + i_2$$

KVL around i_1 :

$$(6k + 12k)i_1 - 12k(i_2 + 18m) = -9$$

$$18ki_1 - 12ki_2 = 207 \dots \dots \dots (1)$$

KVL around the SUPERMESH:

$$4ki_2 + (12k + 4k)(i_2 + 18m) - 12ki_1 - 4k(-6m) = 0$$

$$-12ki_1 + 20ki_2 = -312 \dots \dots \dots (2)$$

$$2 \times (18ki_1 - 12ki_2 = 207) \\ + [3 \times (-12ki_1 + 20ki_2 = -312)]$$

$$36ki_2 = -936 + 414 = -522$$

$$i_2 = -14.5 mA$$

$$i_1 = \frac{11}{6} mA$$

$$v = 12k \left(-14.5m + 18m - \frac{11}{6}m \right) = 20 V$$

4. Find the maximum power transferred to resistor R in the circuit of Fig.P2. (20 pts.)


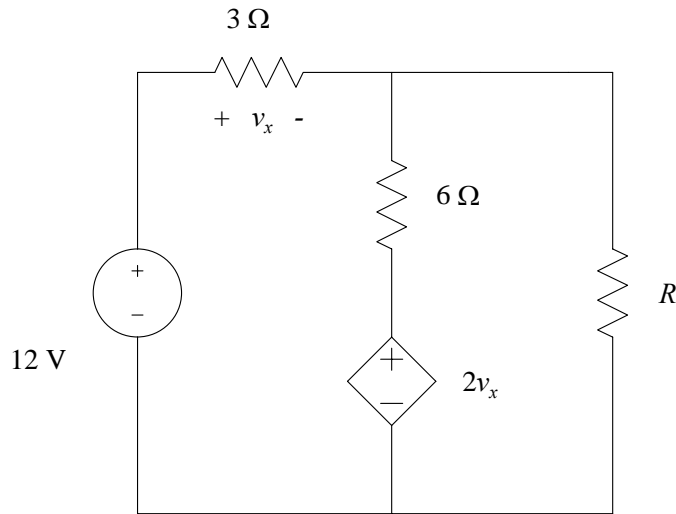


Figure P4

When $R = R_{TH}$, it will absorb maximum power. The maximum power absorbed by the resistor R :

$$P_{\max} = \frac{V_{TH}^2}{4R_{TH}}$$

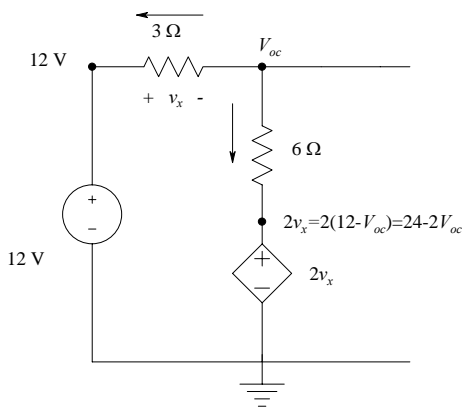In order to find V_{TH} , open circuit voltage is found between the terminals of R .



KCL at V_{oc} :


$$\frac{V_{oc} - 12}{3} + \frac{V_{oc} - 24 + 2V_{oc}}{6} = 0$$

Multiply both sides by 6 yields:

$$2V_{oc} - 24 + 3V_{oc} - 24 = 0$$

$$5V_{oc} = 48$$
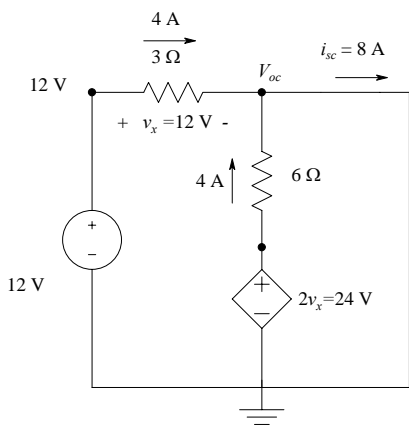
$$V_{oc} = \frac{48}{5} = 9.6 \text{ V}$$



$$R_{TH} = \frac{V_{oc}}{i_{sc}} = \frac{9.6}{8} = 1.2 \Omega$$

$$P_{\max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{9.6^2}{4 \times 1.2} = 19.2 \text{ W}$$

5. In the circuit in Fig. P3, find k in the voltage transfer function $v_0 = kv_s$. (15 pts.)

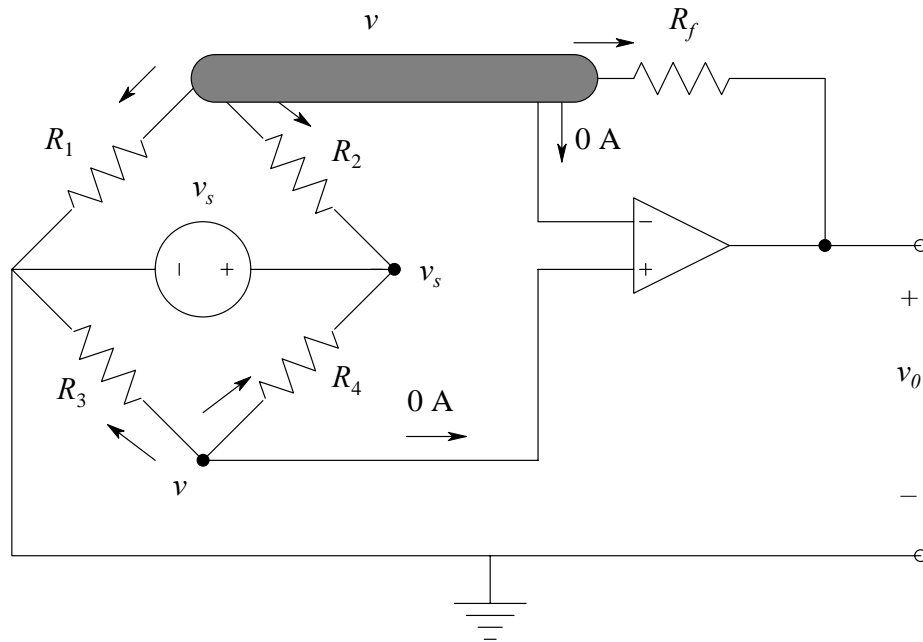


Figure P5

KCL at non-inverting input terminal:

$$\frac{v}{R_3} + \frac{v - v_s}{R_4} = 0$$

$$v = v_s \frac{R_3}{R_3 + R_4}$$

KCL at inverting input terminal:

$$\frac{v}{R_1} + \frac{v - v_s}{R_2} + \frac{v - v_0}{R_f} = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_f} \right) v - \frac{1}{R_2} v_s = \frac{v_0}{R_f}$$

$$v_0 = \underbrace{\left(\left(\frac{R_f}{R_1} + \frac{R_f}{R_2} + 1 \right) \left(\frac{R_3}{R_3 + R_4} \right) - \frac{R_f}{R_2} \right)}_k v_s$$

6. The switch in Fig. P6 has been in position *a* for a long time. At $t = 0$, the switch moves to *b*. Determine $i(t)$ for $t > 0$. (20 pts.)


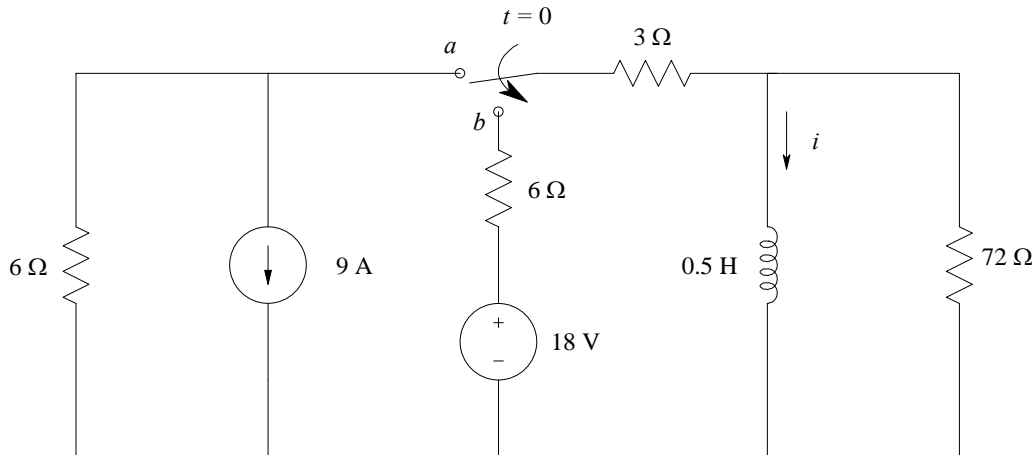


Figure P6

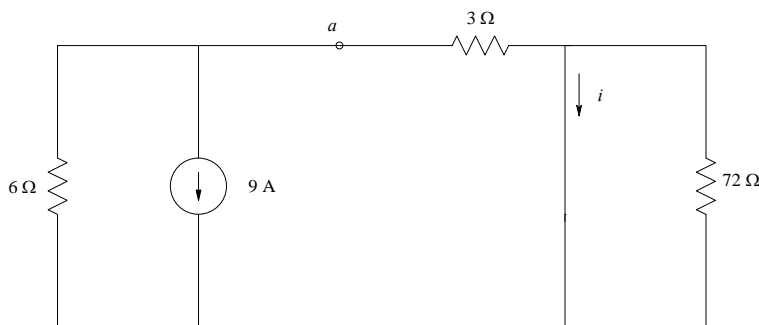
At $t = 0^-$, the circuit is under dc conditions.



$$i(0^-) = -9 \frac{6}{6+3} = -6 \text{ A}$$


Since the inductor current cannot change instantaneously,
 $i(0^-) = i(0^+) = i(0) = -6 \text{ A}$

For $t > 0$

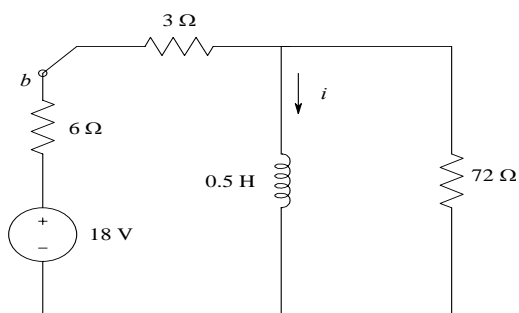


$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-\frac{t}{\tau}} \text{ A}$$

At $t = \infty$

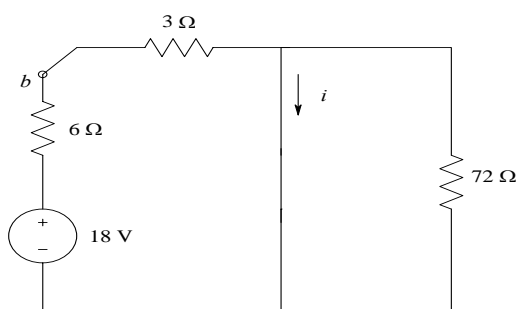

$$i(\infty) = \frac{18}{9} = 2 \text{ A}$$

$$\tau = \frac{L}{R_{eq}}$$

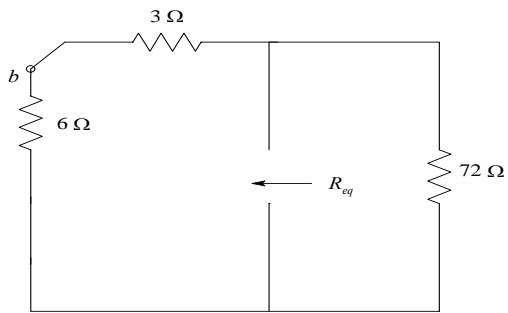

$$R_{eq} = 72 // (6 + 3) = 8 \Omega$$

$$\tau = \frac{0.5}{8} = \frac{1}{16} s$$

$$i(t) = 2 + [-6 - 2]e^{-16t} \text{ A}$$

$$i(t) = 2 - 8e^{-16t} \text{ A for } t > 0$$