



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EEE 223 Circuit Theory I

Instructors:

M. K. Uygurođlu (Gr: 01)

E. Erdil (Gr: 02)

Final EXAMINATION

June 13, 2005

Duration : 120 minutes

Number of Problems: 6

Good Luck

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

Problem		Points
1		15
2		15
3		15
4		15
5		20
6		20
<i>TOTAL</i>		100

1. Find the power delivered by the 4 A current source in the circuit in Fig.P1.

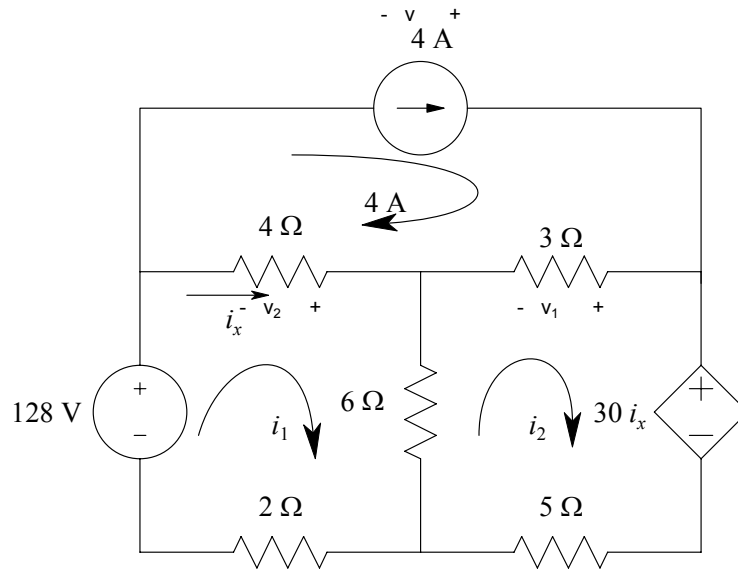


Figure P1

$$i_x = i_1 - 4$$

KVL around i_1 :

$$12i_1 - 6i_2 - 4(4) = 128$$

$$12i_1 - 6i_2 = 144 \dots \dots \dots (1)$$

KVL around i_2 :

$$-6i_1 + 14i_2 - 3(4) = -30i_x = -30(i_1 - 4)$$

$$24i_1 + 14i_2 = 132 \dots \dots \dots (2)$$

Multiplying Eq.(1) by (-2) and adding to Eq.(2) yields:

$$26i_2 = -156$$

$$i_2 = -6 \text{ A}$$

$$i_1 = 9 \text{ A}$$

KVL around the upper mesh:


$$-v + v_1 + v_2 = 0$$

$$v = v_1 + v_2 = (4 - i_2)3 + (4 - i_1)4 = 30 - 20 = 10 \text{ V}$$

Power **delivered** by the 4 A current source

$$p = 4 \times 10 = 40 \text{ W}$$

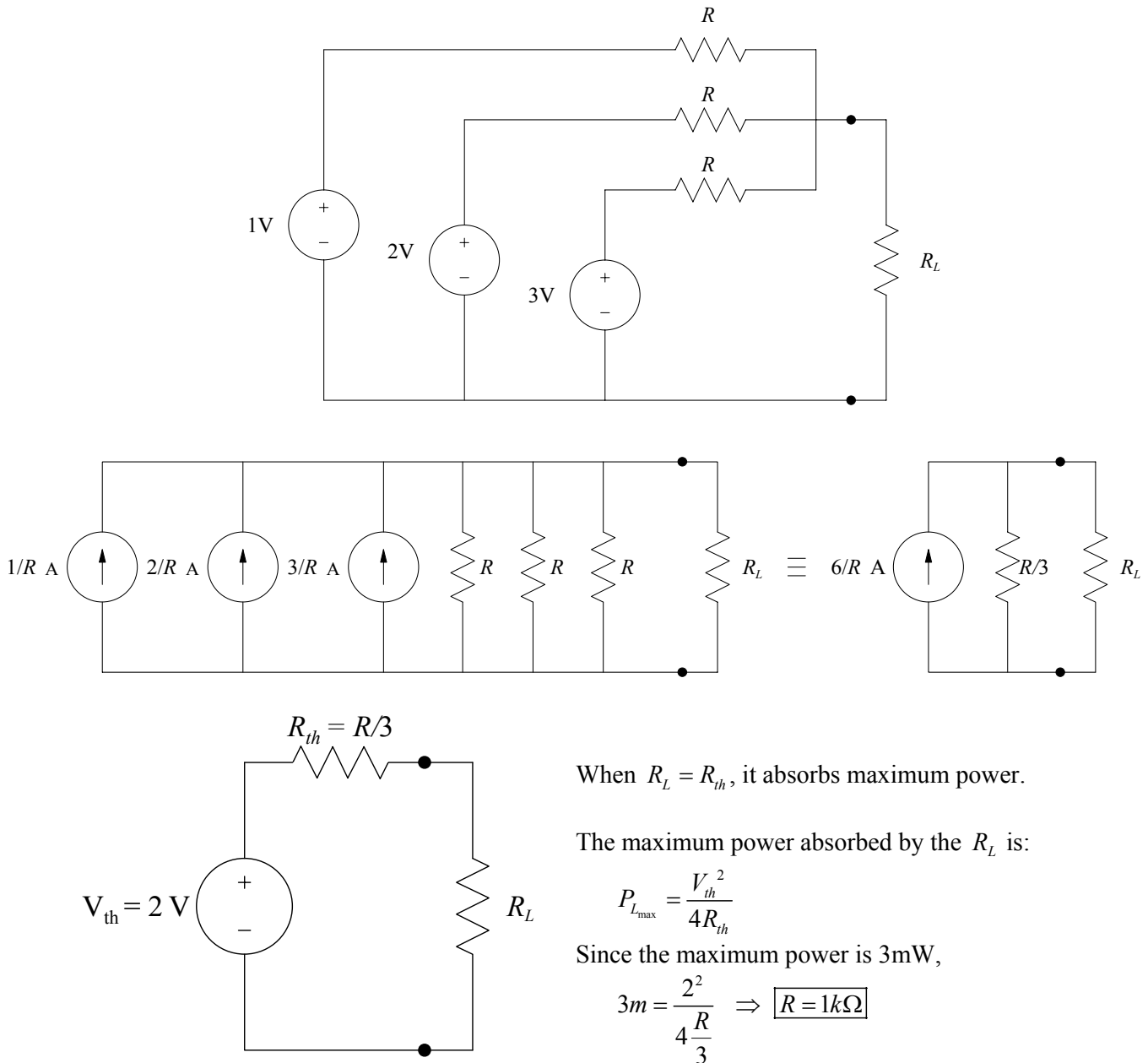2. For the circuit in Fig. P2, determine the value of R such that the maximum power delivered to the load, R_L , is 3 mW.



When $R_L = R_{th}$, it absorbs maximum power.


The maximum power absorbed by the R_L is:

$$P_{L_{max}} = \frac{V_{th}^2}{4R_{th}}$$

Since the maximum power is 3mW,

$$3m = \frac{2^2}{4 \frac{R}{3}} \Rightarrow \boxed{R = 1k\Omega}$$

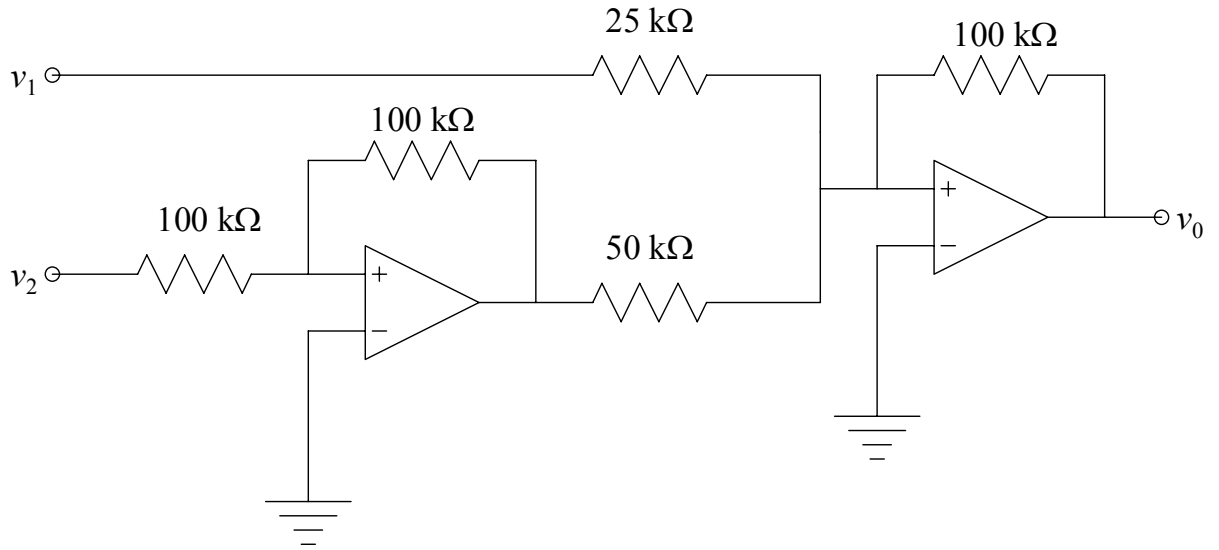3. Design an op-amp circuit with inputs v_1 and v_2 such that the output $v_0 = -4v_1 + 2v_2$. You may use one inverting and one inverting summer op amps to obtain the required output.



4. If the current waveform in Fig. P4 is applied to a $5 \mu\text{F}$ capacitor, find and draw the voltage $v(t)$ across the capacitor. Assume that $v(0) = 12 \text{ V}$.


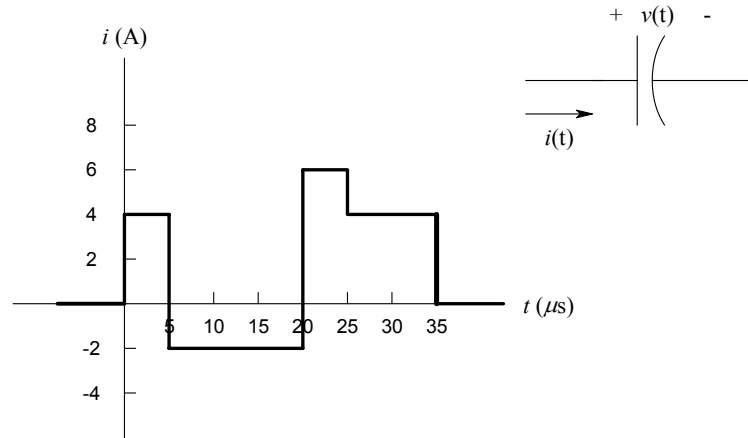


Figure P4

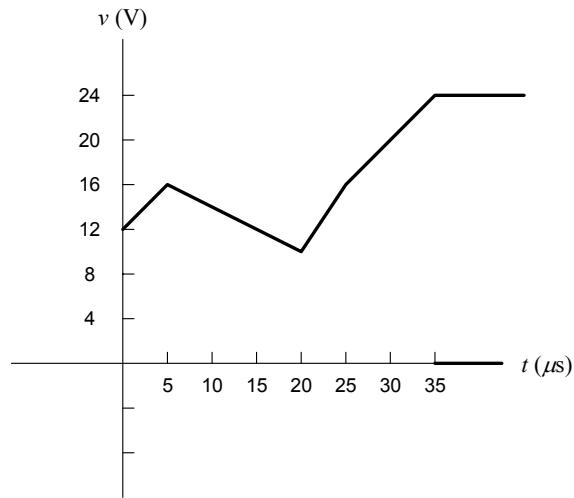

$$i(t) = \begin{cases} 4 \text{ A} & 0 < t < 5 \mu\text{s} \\ -2 \text{ A} & 5 < t < 20 \mu\text{s} \\ 6 \text{ A} & 20 < t < 25 \mu\text{s} \\ 4 \text{ A} & 25 < t < 35 \mu\text{s} \\ 0 & t > 35 \mu\text{s} \end{cases} \quad v(t) = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$$

$$0 < t < 5 \mu\text{s}$$

$$v(t) = \frac{1}{5 \times 10^{-6}} \int_0^t 4 dt + 12 = 0.8 \times 10^6 t + 12$$

$$5\mu s < t < 20\mu s$$

$$v(t) = \frac{1}{5 \times 10^{-6}} \int_{5\mu s}^t -2dt + 16 = -0.4 \times 10^6 t + 2 + 16 = -0.4 \times 10^6 t + 18$$

$$20\mu s < t < 25\mu s$$

$$v(t) = \frac{1}{5 \times 10^{-6}} \int_{20\mu s}^t 6dt + 10 = 1.2 \times 10^6 t - 24 + 10 = 1.2 \times 10^6 t - 14$$

$$25\mu s < t < 35\mu s$$

$$v(t) = \frac{1}{5 \times 10^{-6}} \int_{25\mu s}^t 4dt + 16 = 0.8 \times 10^6 t - 20 + 16 = 0.8 \times 10^6 t - 4$$

$$t > 35\mu s$$

$$v(t) = v(35\mu s) = 24 \text{ V}$$

5. In the circuit in Fig. P5, it is given that $i(0) = 10$ A. Calculate $i(t)$ and $i_x(t)$ for $t \geq 0$.


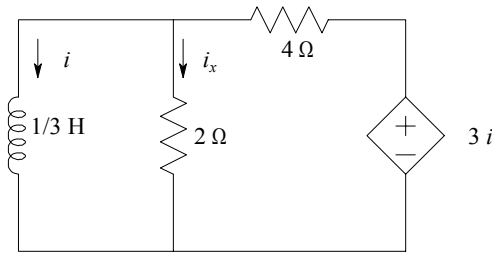


Figure P5

The circuit in Fig. P5 is a source-free RL circuit. Therefore the current flowing through the inductor is

$$i(t) = i(0)e^{-\frac{t}{\tau}}$$

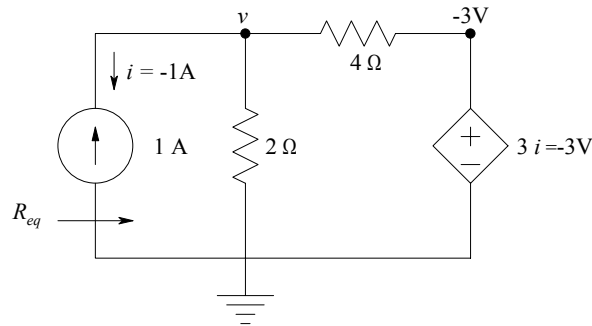where $\tau = \frac{L}{R_{eq}}$. In order to find R_{eq} , a test source is used.



It is obvious that $R_{eq} = \frac{v}{1}$.

KCL at v :

$$\left(\frac{1}{2} + \frac{1}{4}\right)v - \frac{1}{4}(-3) = 1$$

Multiply both sides by (4):

$$3v = 1 \Rightarrow \boxed{v = \frac{1}{3} \text{ V}} \therefore R_{eq} = \frac{1}{3} \Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{1/3}{1/3} = 1 \text{ s} \Rightarrow i(t) = 10e^{-t} \text{ V}$$

Since the 2Ω resistor and the $1/3$ H inductor are in parallel, they have the same voltage

$$v = \frac{1}{3} \frac{di}{dt} = 2i_x \Rightarrow i_x = \frac{1}{6}(-10)e^{-t} = -\frac{10}{6}e^{-t} \text{ A}$$

Consider the circuit shown in Fig. P3.

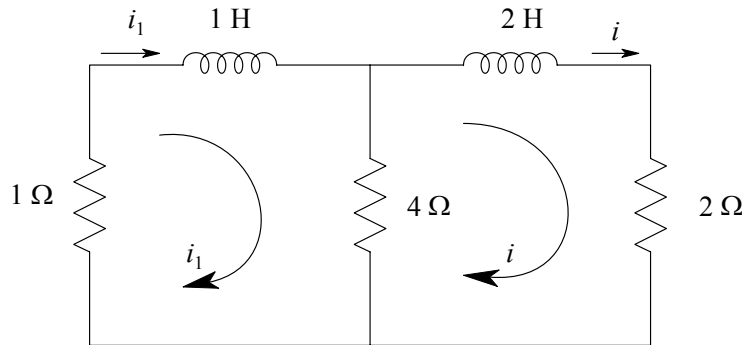


Figure P3

If $i_1(0) = 9 \text{ A}$ and $i(0) = 3 \text{ A}$ then find:

- (a) $\frac{di(0)}{dt}$
- (b) characteristic equation
- (c) $i(t)$ for $t \geq 0$.

KVL around i_1 :

$$5i_1 + \frac{di_1}{dt} - 4i = 0 \dots\dots\dots(1)$$

KVL around i_2 :

$$-4i_1 + 6i + 2\frac{di}{dt} = 0 \Rightarrow i_1 = 1.5i + 0.5\frac{di}{dt} \dots\dots\dots(2)$$

At $t = 0$:

$$i_1(0) = 1.5i(0) + 0.5\frac{di(0)}{dt}$$

$$\boxed{\frac{di(0)}{dt} = 2i_1(0) - 3i(0) = 2(9) - 3(3) = 9 \text{ A/s}}$$

Subst. Eq. (2) into (1) yields:

$$5\left(1.5i + 0.5\frac{di}{dt}\right) + \frac{d\left(1.5i + 0.5\frac{di}{dt}\right)}{dt} - 4i = 0$$

$$7.5i + 2.5\frac{di}{dt} + 1.5\frac{di}{dt} + 0.5\frac{d^2i}{dt^2} - 4i = 0$$

or

$$\boxed{\frac{d^2i}{dt^2} + 8\frac{di}{dt} + 7i = 0}$$

Characteristic equation:

$$s^2 + 8s + 7 = 0$$

Therefore the natural frequencies are

$$s_1 = -7, \text{ and } s_2 = -1 \Rightarrow \text{real and distinct (Overdamped case)}$$

$$i(t) = K_1 e^{-7t} + K_2 e^{-t}$$

In order to find the constants K_1 and K_2 , the initial conditions are used.

$$i(0) = 3 = K_1 + K_2 \dots\dots\dots(3)$$

$$\frac{di(t)}{dt} = -7K_1 e^{-7t} - K_2 e^{-t}$$

$$\frac{di(0)}{dt} = -7K_1 - K_2 = 9 \dots\dots\dots(4)$$

By summing up Eqs.(3) and (4) K_1 can be obtained.

$$-6K_1 = 12$$

$$\boxed{K_1 = -2}$$

$$\boxed{K_2 = 5}$$

$$\boxed{i(t) = -2e^{-7t} + 5e^{-t} \text{ A}}$$