



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EEE 223 Circuit Theory I

Spring 2005-06

Instructor:

M. K. Uyguroğlu

Final EXAMINATION

June 15, 2006

Duration : 120 minutes


Number of Problems: 6

Good Luck

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

Problem		Points
1		15
2		15
3		15
4		15
5		20
6		20
TOTAL		100

- Use nodal analysis to find v .

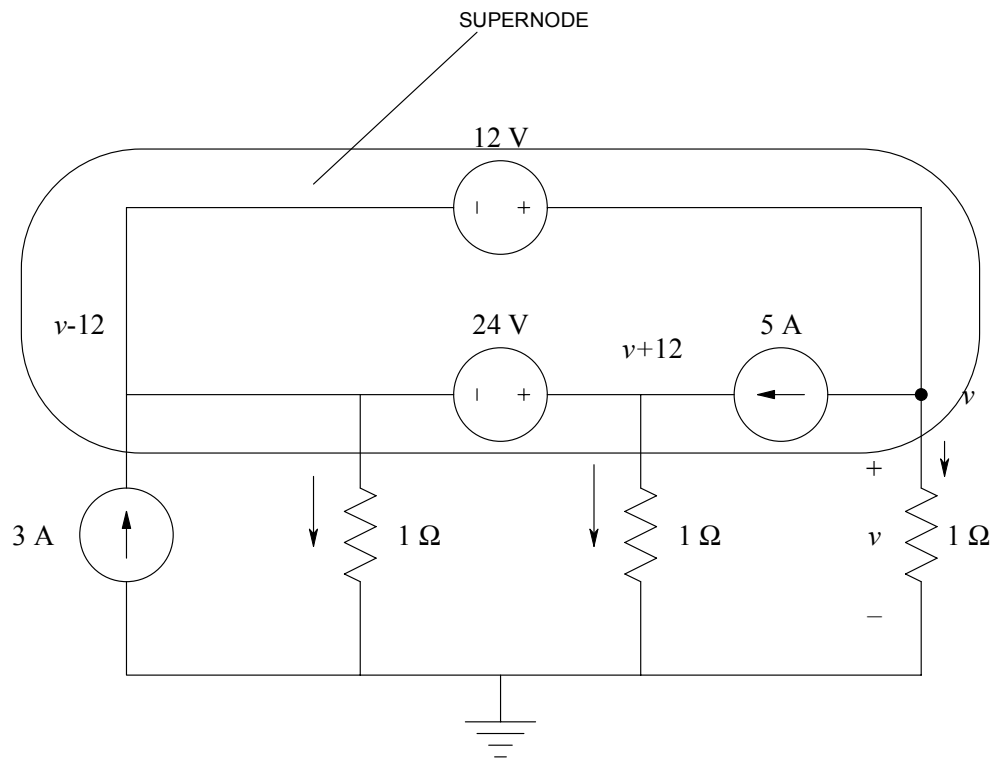


KCL at the supernode:

$$\frac{v-12}{1} + \frac{v+12}{1} + \frac{v}{1} = 3$$

$$3v = 3$$

$$\boxed{v = 1 \text{ V}}$$

2. Use mesh analysis to find v .

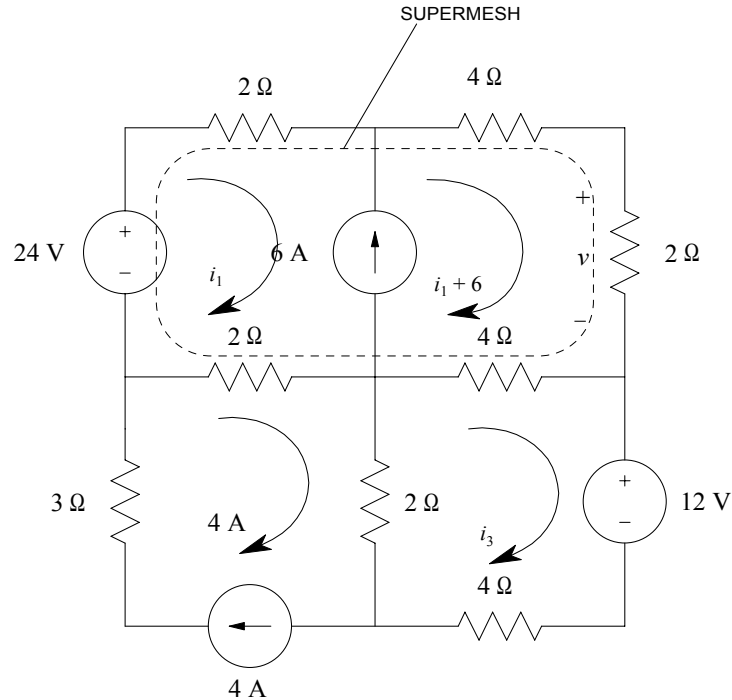

KVL around the supermesh:

$$2i_1 + 4(i_1 + 6) + 2(i_1 + 6) + 4(i_1 + 6 - i_3) + 2(i_1 - 4) = 24$$

$$14i_1 - 4i_3 = 24 - 60 + 8 = -28 \dots \dots (1)$$

KVL around i_3 :

$$2(i_3 - 4) + 4(i_3 - i_1 - 6) + 4i_3 = -12$$


$$10i_3 - 4i_1 = 20 \dots (2)$$

By using Eqns(1) and (2), i_1 is obtained as

$$i_1 = -1.613 \text{ A}$$

$$v = 2(i_1 + 6) = 8.774 \text{ V.}$$

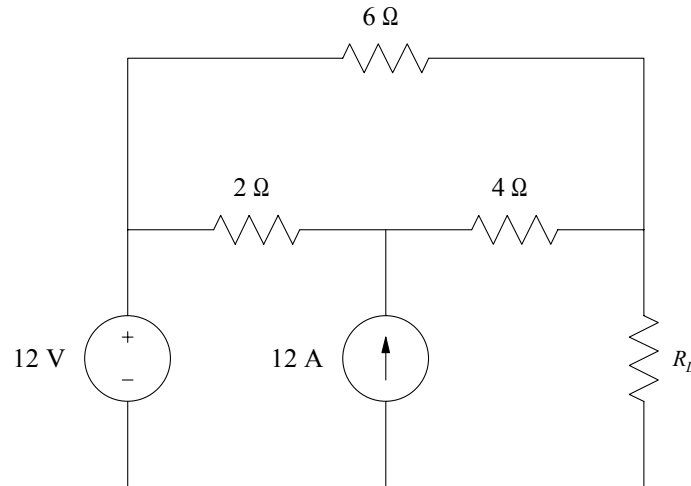3. Find R_L for maximum power transfer and the maximum power absorbed by the load.




When $R_L = R_{TH}$ it will absorb maximum power. The maximum power;


$$P_{\max} = \frac{V_{TH}^2}{4R_{TH}}$$

In order to find R_{TH} :

$$R_{TH} = 6 // (4 + 2) = 3\Omega$$

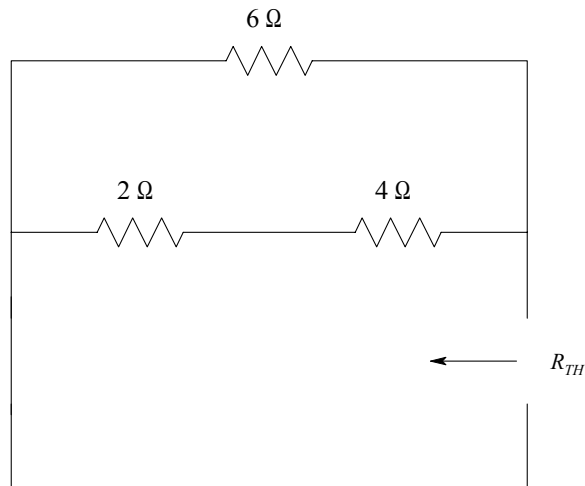

For V_{TH} :

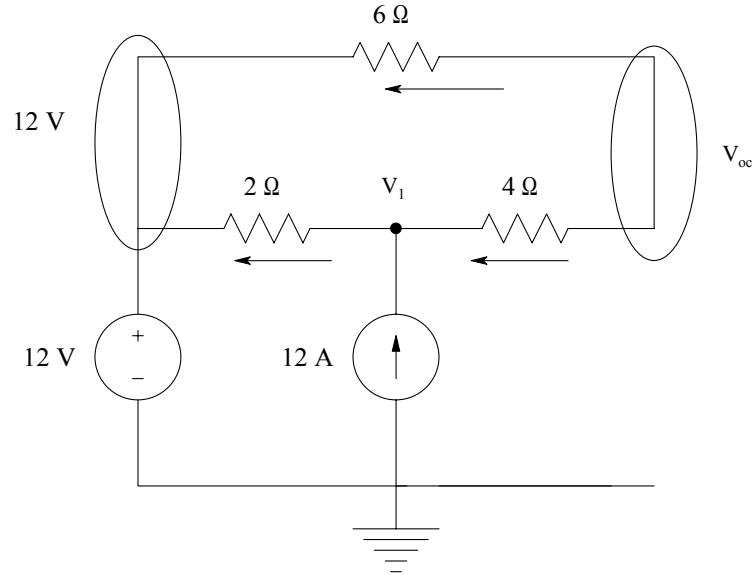

KCL at V_{oc} :

$$\frac{V_{oc} - 12}{6} + \frac{V_{oc} - V_1}{4} = 0$$

$$5V_{oc} - 3V_1 = 24 \dots (1)$$

KCL at V_1 :

$$\frac{V_1 - V_{oc}}{4} + \frac{V_1 - 12}{2} = 12$$

$$-V_{oc} + 3V_1 = 72 \dots (2)$$


From Eqns (1) and (2),

$$\boxed{V_{oc} = 24 \text{ V}}$$

Therefore, when $R_L = 3\Omega$ then it will absorb maximum power.

$$P_{\max} = \frac{24^2}{4 \times 3} = 48 \text{ W}$$

4. Find v_o in the circuit.

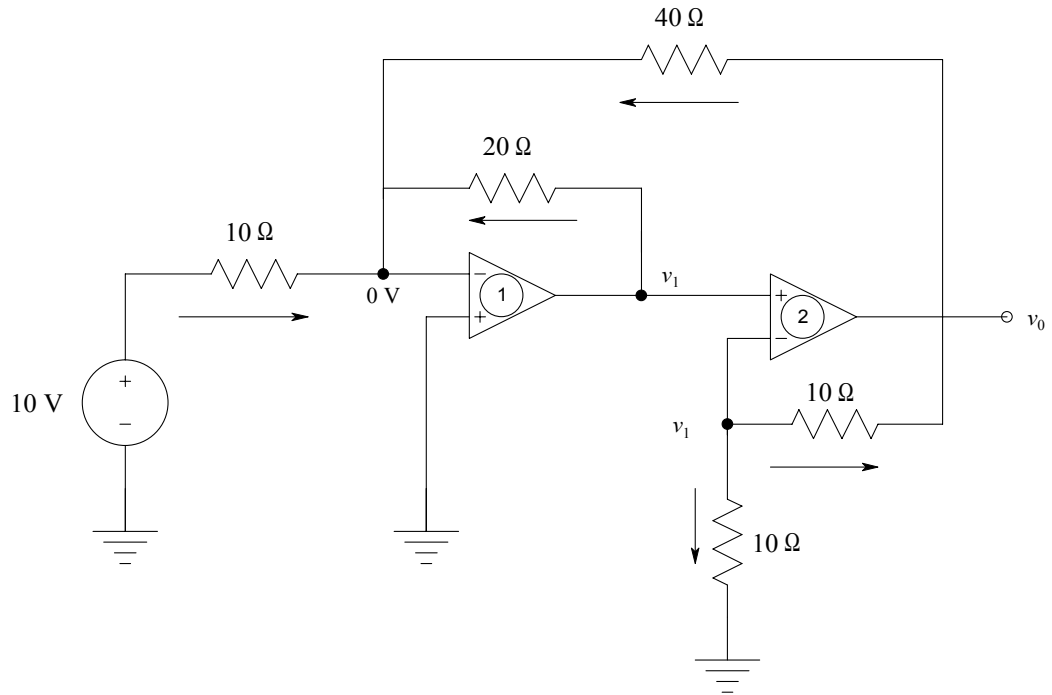

KCL at the inverting input terminal of OPAMP (2):

$$\frac{v_1}{10} + \frac{v_1 - v_o}{10} = 0$$

$$\boxed{v_1 = \frac{v_o}{2}} \dots (1)$$


KCL at the inverting input terminal of OPAMP (1)

$$\frac{10}{10} + \frac{v_o/2}{20} + \frac{v_o}{40} = 0$$

$$2v_o = -40$$

$$\boxed{v_o = -20 \text{ V}}$$

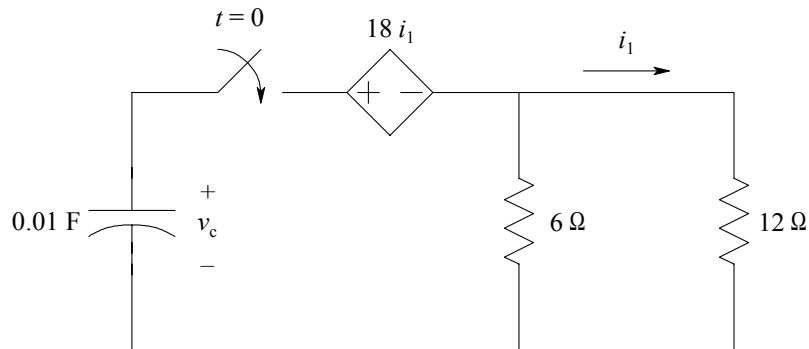
5. If $v_c(0) = 100 \text{ V}$, find $v_c(t)$ for $t \geq 0$.



Since the circuit is a source-free RC circuit, the voltage across the capacitor is

$$v_c(t) = v_c(0)e^{-\frac{t}{\tau}}$$

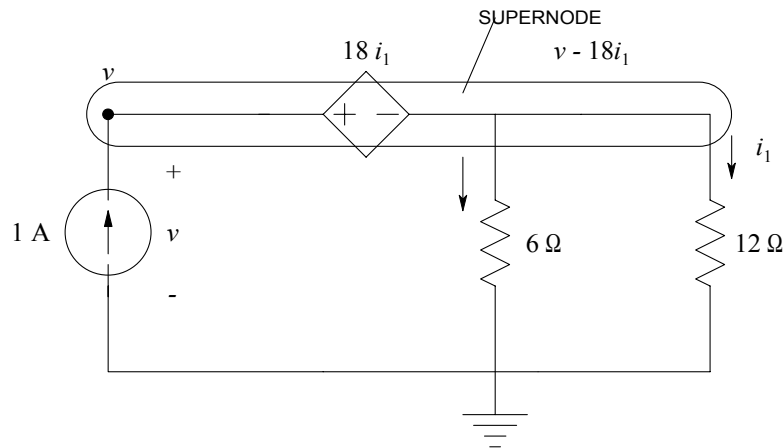Where $\tau = R_{eq}C$ and R_{eq} is the resistance seen by the capacitor.



$$i_1 = \frac{v - 18i_1}{12} \Rightarrow \frac{5}{2}i_1 = \frac{v}{12} \Rightarrow i_1 = \frac{2}{60}v$$

$$v - 18i_1 = v - 18\left(\frac{2}{60}v\right) = v - \frac{36}{60}v = \frac{24}{60}v = 0.4v$$

KCL at the supernode:

$$\frac{0.4v}{6} + \frac{0.4v}{12} = 1$$

$$1.2v = 12$$


$$v = 10 \text{ V}$$

$$R_{eq} = \frac{v}{1} = 10\Omega$$


$$\tau = R_{eq}C = 10 \times 0.01 = 0.1s$$

$$v_c(t) = 100e^{-10t} \text{ V for } t \geq 0$$

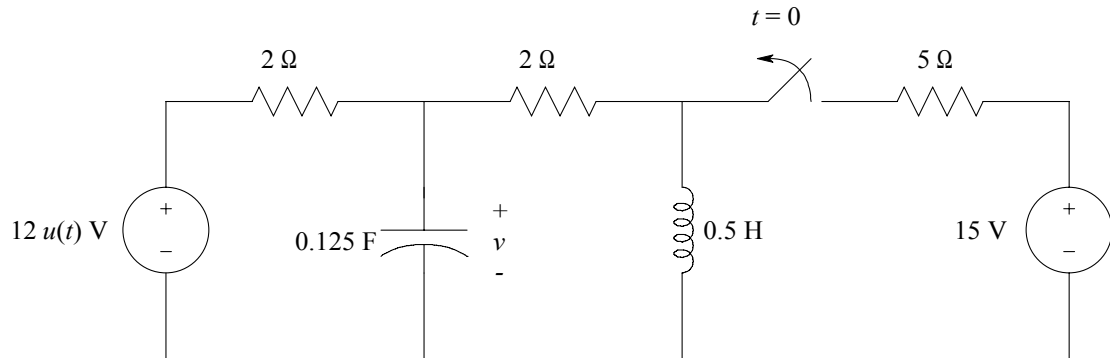6. Suppose that the switch has been closed for a long time and is opened at $t = 0$, determine $v(t)$ for $t \geq 0$.



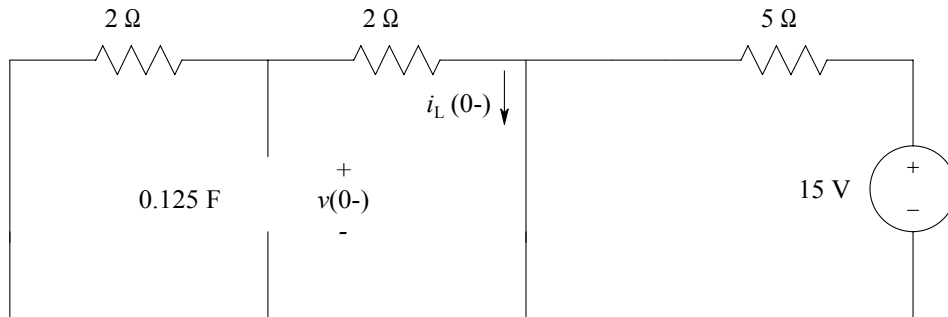At $t = 0^-$ (The circuit is under dc conditions)



$$i_L(0^-) = \frac{15}{5} = 3A$$

$$v_c(0^-) = 0V$$

Since the inductor current and capacitor voltage cannot change instantaneously,

$$i_L(0^-) = i_L(0^+) = 3A$$

$$v_c(0^-) = v_c(0^+) = 0V$$


For $t \geq 0$

KCL at node a :

$$\frac{v-12}{2} + 0.125 \frac{dv}{dt} + i_L = 0 \dots (1)$$

KVL around the loop I:
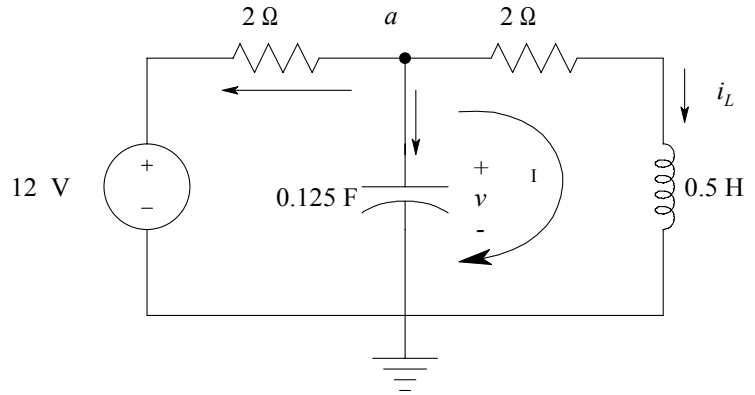
$$-v + 2i_L + 0.5 \frac{di_L}{dt} = 0 \dots (2)$$



From Eqn(1):

$$i_L = -\frac{v-12}{2} - 0.125 \frac{dv}{dt} \dots (3)$$

At $t = 0$

$$i_L(0) = -\frac{v(0)-12}{2} - 0.125 \frac{dv(0)}{dt}$$

$$3 = 6 - 0.125 \frac{dv(0)}{dt}$$

$$\frac{dv(0)}{dt} = 24V/s$$

Subst. Eqn. (3) into (2) gives:

$$-v + 2 \left(-\frac{v-12}{2} - 0.125 \frac{dv}{dt} \right) + 0.5 \frac{d}{dt} \left(-\frac{v-12}{2} - 0.125 \frac{dv}{dt} \right) = 0$$

$$-2v - 0.5 \frac{dv}{dt} - 0.0625 \frac{d^2v}{dt^2} = -12$$

multiply both sides $\frac{-1}{0.0625}$ yields:

$$\boxed{\frac{d^2v}{dt^2} + 8 \frac{dv}{dt} + 32v = 192}$$

The characteristic equation

$$s^2 + 8s + 32 = 0$$

The natural frequencies:

$$s_{1,2} = -4 \mp j4$$

The natural response

$$v_n = e^{-4t} (K_1 \cos 4t + K_2 \sin 4t)$$

The forced response

$$v_f = \frac{192}{32} = 6$$

The complete response

$$v = v_n + v_f$$

$$v = e^{-4t} (K_1 \cos 4t + K_2 \sin 4t) + 6$$

$$v(0) = 0 = e^{-0} (K_1 \cos 0 + K_2 \sin 0) + 6$$

$$K_1 + 6 = 0 \Rightarrow K_1 = -6$$

$$\frac{dv}{dt} = -4e^{-4t} (K_1 \cos 4t + K_2 \sin 4t) + e^{-4t} (-4K_1 \sin 4t + 4K_2 \cos 4t)$$

$$\frac{dv(0)}{dt} = 24 = -4K_1 + 4K_2$$

$$\boxed{K_2 = 0}$$

Therefore

$$v(t) = -6e^{-4t} \cos 4t + 6 \quad \text{for } t \geq 0$$