



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EEE 223 Circuit Theory I

Spring 2005-06

Instructor:

M. K. Uygurođlu

Midterm EXAMINATION

Apr 20, 2006

Duration : 100 minutes

Number of Problems: 6

Good Luck

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

Problem		Points
1		20
2		15
3		15
4		20
5		15
6		15
<i>TOTAL</i>		100

1. Consider the circuit shown below.

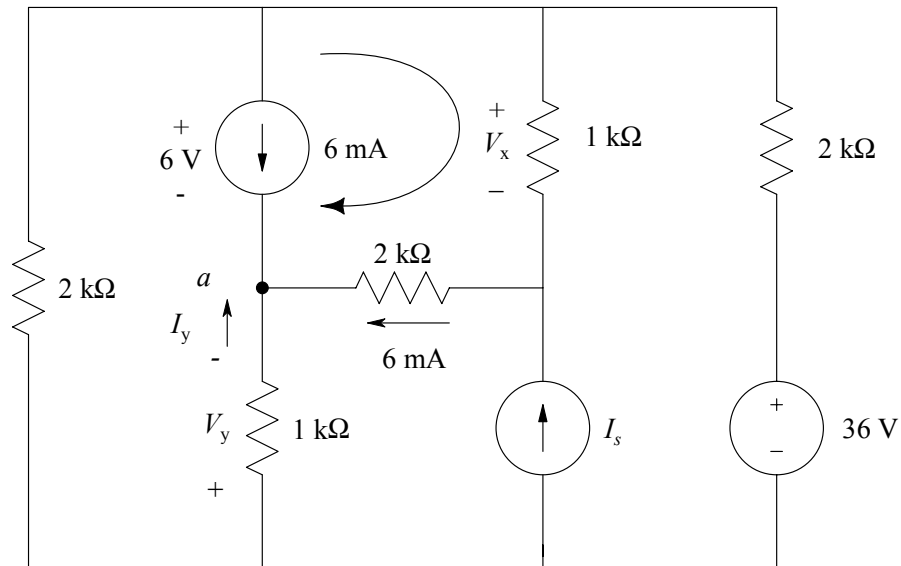


Figure P1

- (a) (5 pts.) How much charge flows through the resistor in the center of the circuit in a 3 second interval of time?

$$q_T = \int_0^3 6 \times 10^{-3} dt = 6 \times 10^{-3} t \Big|_0^3 = 18 mC$$

- (b) (5 pts.) How much energy does the upper-left current source supply in a 5 second interval of time?

$$w = \int_0^5 v i dt = \int_0^5 (6)(6 \times 10^{-3}) dt = 36 \times 10^{-3} t \Big|_0^5 = 180 mJ \text{ Absorbs}$$

$$w_{\text{supply}} = -180 mJ$$

- (c) (5 pts.) Find the voltage V_x .

KVL around the loop:

$$6m \times 2k - 6 + V_x = 0$$

$$V_x = -6V$$

- (d) (5 pts.) Find the voltage V_y .

KCL at node a :

$$I_y + 6mA + 6mA = 0$$

$$I_y = -12mA$$

$$V_y = I_y \times 1k = -12V$$

2. (15 pts.) Use a Δ to Y transform on the $5\text{ k}\Omega$, $3\text{ k}\Omega$, and $7\text{ k}\Omega$ resistors (plus series and parallel combinations) to reduce this circuit to a single resistor connected to the voltage source.

$$R_1 = \frac{3 \times 5 \times 10^6}{(3 + 5 + 7) \times 10^3} = 1\text{ k}\Omega$$


$$R_2 = \frac{21 \times 10^6}{15 \times 10^3} = 1.4\text{ k}\Omega$$

$$R_3 = \frac{35 \times 10^6}{15 \times 10^3} = \frac{7}{3}\text{ k}\Omega$$


$$R_{eq} = (1\text{ k} + R_1) // (9\text{ k} + R_2) + R_3$$

$$R_{eq} = 2\text{ k} // 10.4\text{ k} + \frac{7}{3}\text{ k}$$
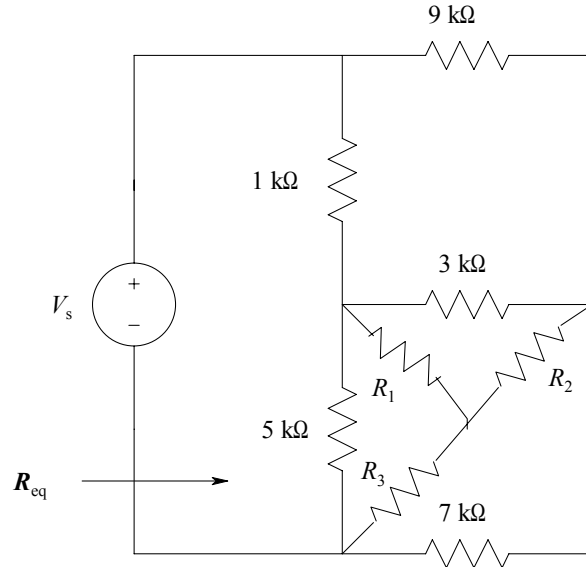
$$R_{eq} = \frac{2 \times 10.4 \times 10^6}{12.4 \times 10^3} + \frac{7}{3}\text{ k} = 4.01\text{ k}\Omega$$



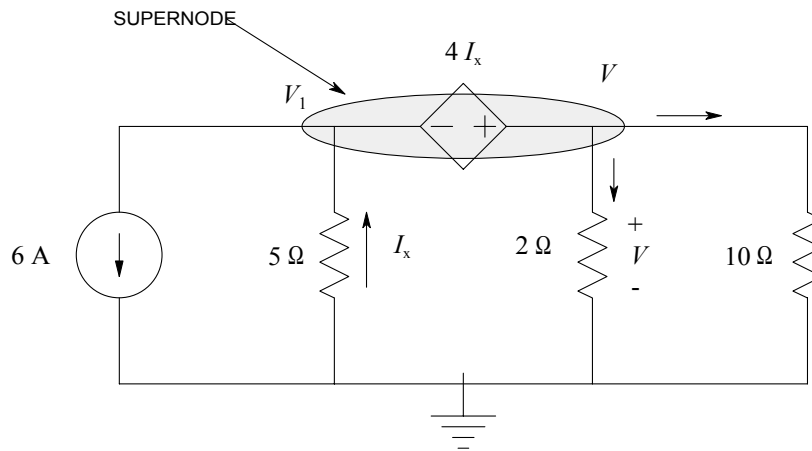3. (15 pts.) Find I_x and V using nodal analysis.



KCL at the supernode:

$$-\left(\frac{-V_1}{5}\right) + 6 + \frac{V}{2} + \frac{V}{10} = 0$$

multiply both sides by 10 gives:

$$2V_1 + 6V = -60 \dots\dots (1)$$

where

$$V - V_1 = 4I_x = 4\left(\frac{-V_1}{5}\right)$$

$$V_1 = 5V \dots\dots (2)$$


Substitute Eq. (2) into (1) yields:

$$2(5V) + 6V = -60$$

$$16V = -60 \Rightarrow \boxed{V = -\frac{60}{16} = -3.75V}$$

$$I_x = -\frac{V_1}{5} = -\frac{5V}{5} = -V = \boxed{3.75A}$$

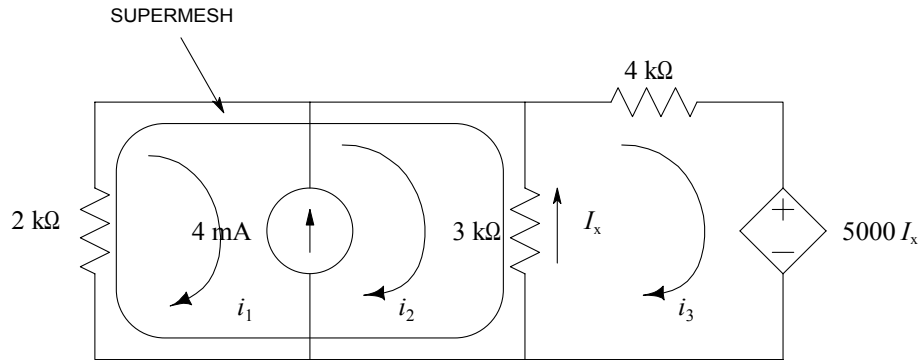4. (15 pts.) Use mesh analysis to find I_x .



$$I_x = i_3 - i_2$$

$$i_2 - i_1 = 4$$

$$i_1 = i_2 - 4$$

KVL around the supermesh:

$$2k(i_2 - 4) + 3k(i_2 - i_3) = 0$$

$$5i_2 - 3i_3 = 8m \dots \dots (1)$$

KVL around i_3 :

$$3k(i_3 - i_2) + 4ki_3 + 5k(i_3 - i_2) = 0$$

$$-8i_2 + 12i_3 = 0 \dots \dots (2)$$


From Eqs. (1) and (2)

$$i_3 = 1.78mA$$

$$i_2 = 2.67mA$$

$$I_x = i_3 - i_2 = -0.89mA$$

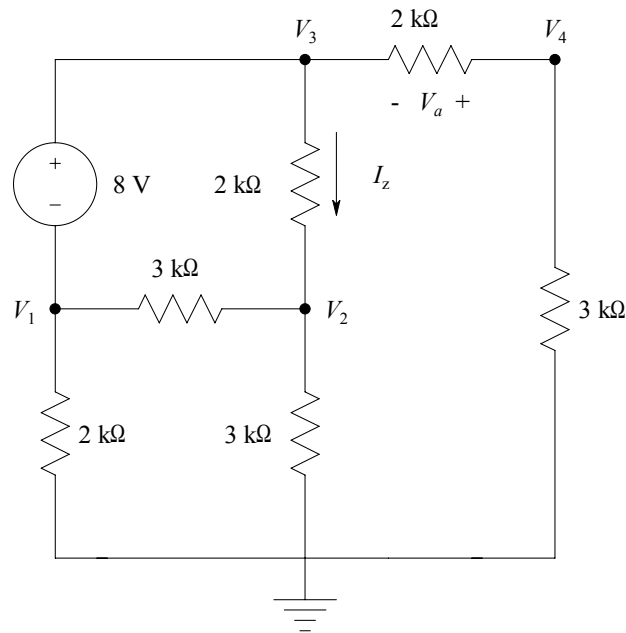In the circuit below, V_1 , V_2 , V_3 , and V_4 are node voltages (relative to the reference node).



In this circuit, two of the node voltages are known: $V_2 = 1.34$ V and $V_3 = 5.08$ V. Using this information, complete the following parts of this problem.

(a) (5 pts.) Find the value of node voltage V_1 .

$$V_3 - V_1 = 8 \Rightarrow V_1 = V_3 - 8 = 5.08 - 8 = -2.92\text{V}$$

(b) (5 pts.) Find the value of current I_z .


$$I_z = \frac{V_3 - V_2}{2k} = \frac{5.08 - 1.34}{2k} = 1.87\text{mA}$$

(c) (5 pts.) Find the value of the voltage V_a .

Using voltage division principle:

$$V_a = -\frac{2k}{2k + 3k}V_3 = (-0.4)(5.08) = -2.03\text{V}$$

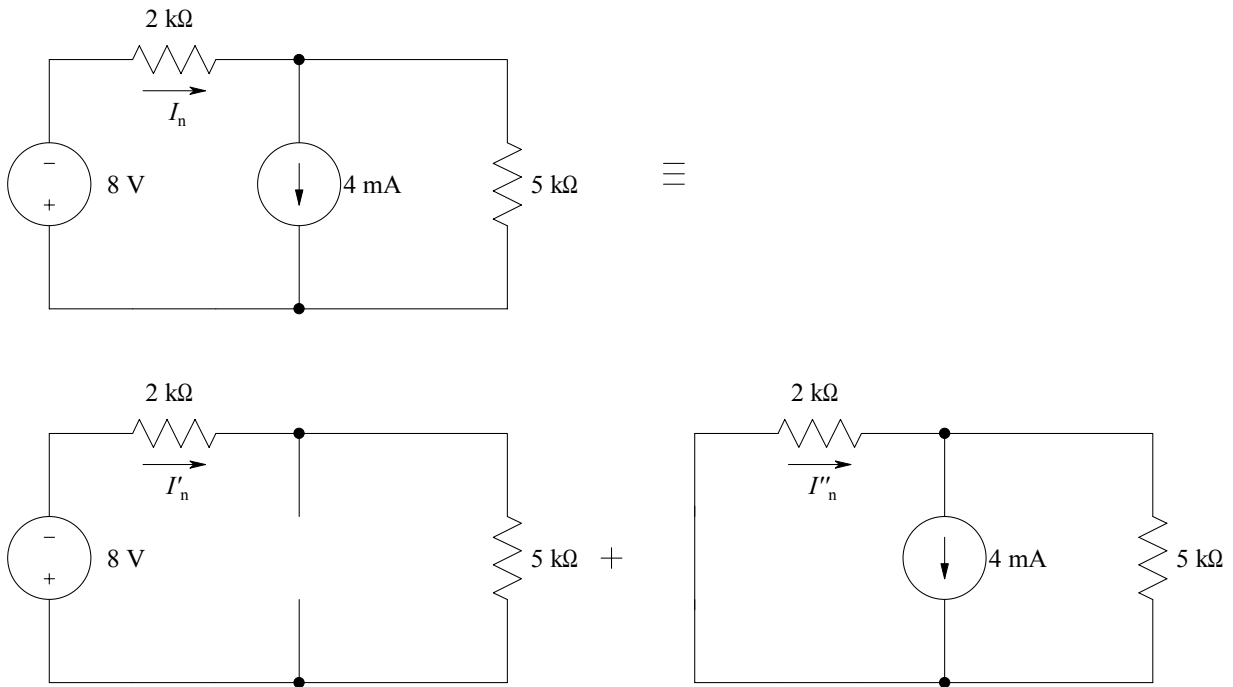5. (15 pts.) Find the value of I_n in the circuit below using *superposition*.



$$I'_n = -\frac{8}{7k} = -\frac{8}{7} \text{ mA}$$

$$I''_n = 4m \frac{5k}{7k} = \frac{20}{7} \text{ mA}$$

$$I_n = I'_n + I''_n = -\frac{8}{7} + \frac{20}{7} = \frac{12}{7} \text{ mA}$$

