



**Faculty of Engineering**

**ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT**

***EENG223 Circuit Theory I***

**Spring 2006-07**

**Instructor:**

**M. K. Uygurođlu**

*Final EXAMINATION*

June 08, 2007

*Duration : 150 minutes*



Number of Problems: 6

*Good Luck*

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

Problem		Points
1		20
2		15
3		15
4		15
5		15
6		20
<b>TOTAL</b>		<b>100</b>

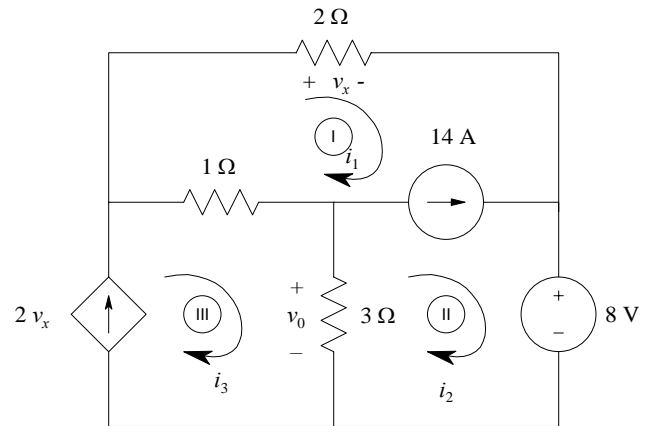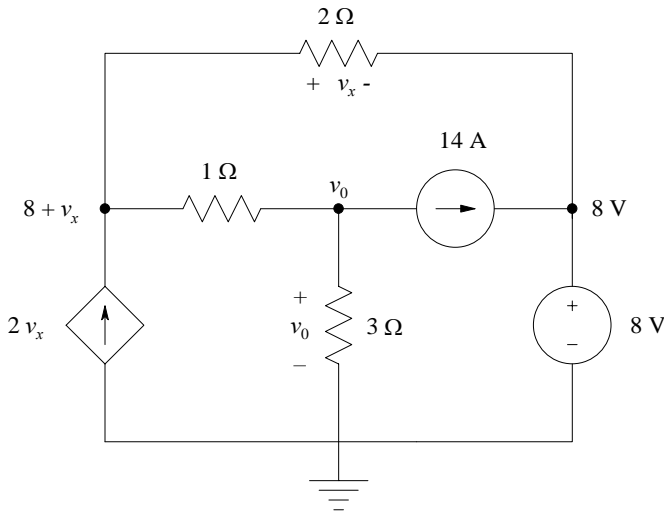1. For the circuit in Fig. P1, find the value of  $v_0$  using  
 a. mesh analysis. (10 pts.)  
 b. nodal analysis. (10 pts.)



KCL at  $v_0$ :

$$\left(1 + \frac{1}{3}\right)v_0 - (1)(8 + v_x) = -14$$

$$\frac{4}{3}v_0 - v_x = -6 \text{ or}$$

$$4v_0 - 3v_x = -18 \dots \dots \dots (1)$$

KCL at  $(8 + v_x)$ :

$$-1v_0 + \left(1 + \frac{1}{2}\right)(8 + v_x) - \frac{8}{2} - 2v_x = 0$$

$$-v_0 - \frac{1}{2}v_x = -8 \text{ or}$$

$$-2v_0 - v_x = -16 \dots \dots \dots (2)$$

Multiply Eq.(2) by (-3) and add to (1) yields:

$$10v_0 = 30 \Rightarrow \boxed{v_0 = 3\text{V}}$$

$$i_3 = 2v_x = 2(2i_1) = 4i_1 \dots \dots \dots (1)$$

$$i_2 - i_1 = 14$$

$$i_2 = 14 + i_1 \dots \dots \dots (2)$$

Mesh (I) and mesh (II) constitute a SUPERMESH.

KVL around the supermesh:

$$2i_1 + 8 + 3(i_2 - i_3) + 1(i_1 - i_3) = 0$$

$$2i_1 + 3(14 + i_1 - 4i_1) + i_1 - 4i_1 = -8$$


$$-10i_1 = -50$$

$$i_1 = 5\text{A}$$

$$v_0 = 3(i_3 - i_2) = 3(4i_1 - 14 - i_1) = 3(15 - 14)$$

$$\boxed{v_0 = 3\text{V}}$$

2. Find  $v_x$ ,  $i_a$ , and  $i_0$  in the circuit in Fig. P2. (15 pts.)

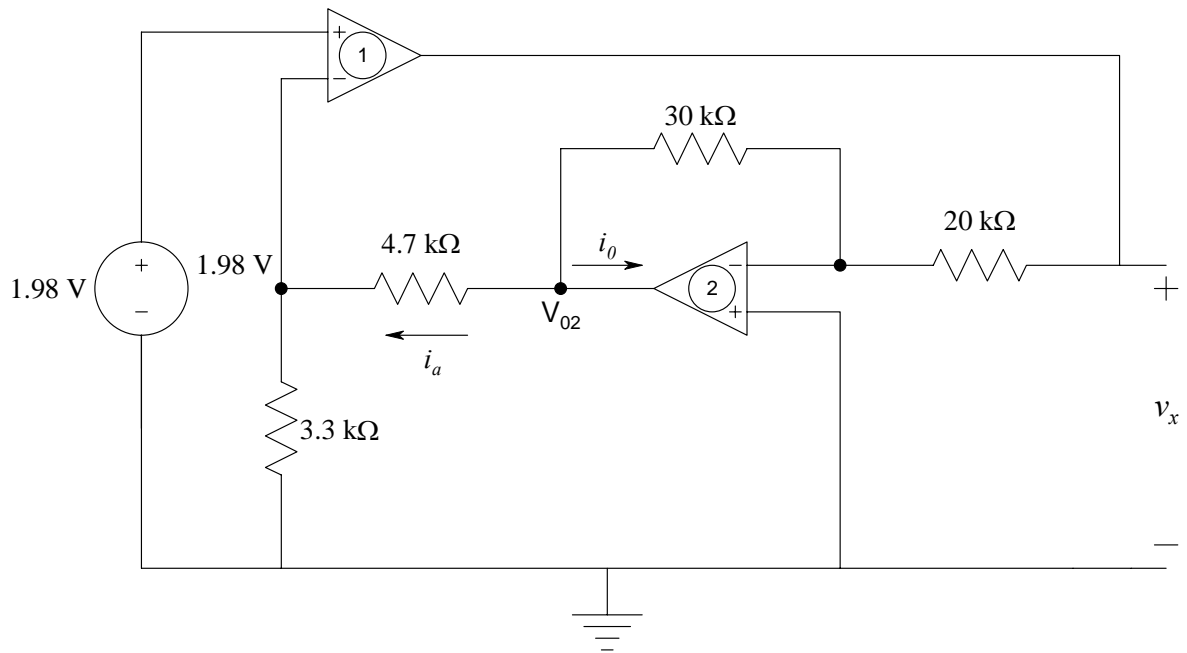

**Figure P2**

KCL at the inverting input terminal of OP AMP (1):

$$1.98 \left( \frac{1}{3.3k} + \frac{1}{4.7k} \right) - \frac{1}{4.7k} v_{01} = 0$$

$$v_{01} = \left( 1 + \frac{4.7}{3.3} \right) 1.98 = 4.8 \text{ V}$$

KCL at the inverting input terminal of OP AMP (2):

$$\frac{v_{01}}{30k} + \frac{v_x}{20k} = 0$$

$$v_x = -\frac{2}{3} v_{01} = -3.2 \text{ V}$$

$$i_a = \frac{4.8 - 1.98}{4.7k} = 0.6 \text{ mA}$$

$$i_0 = -\left( 0.6m + \frac{4.8}{30k} \right) = -0.76 \text{ mA}$$

3. Use the principle of superposition to find  $i$  in the circuit in Fig. P3. (15 pts.)

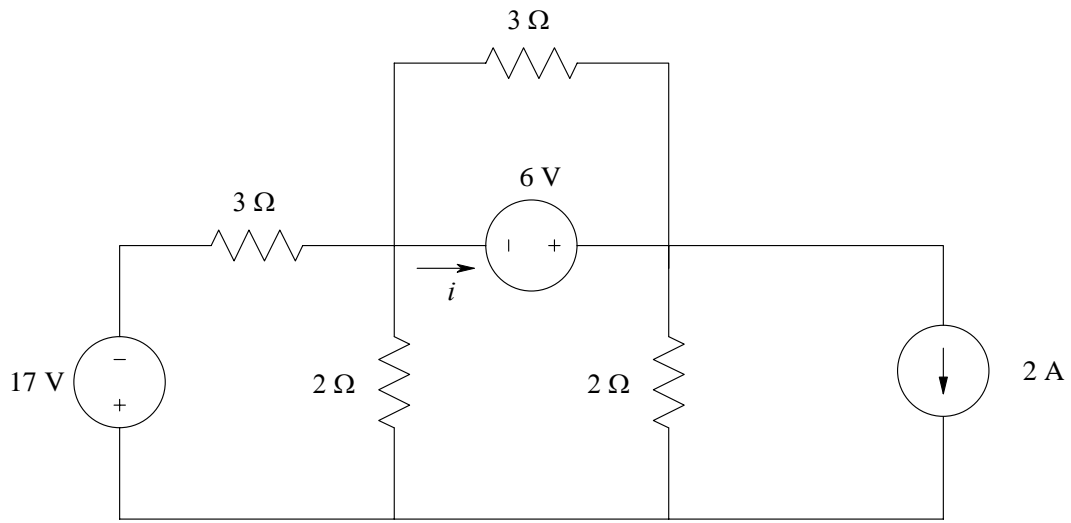



Figure P3

**17 V is active:**

$$i_r = -\frac{17}{R_T} = -\frac{17}{4} A$$


by using current division principle:
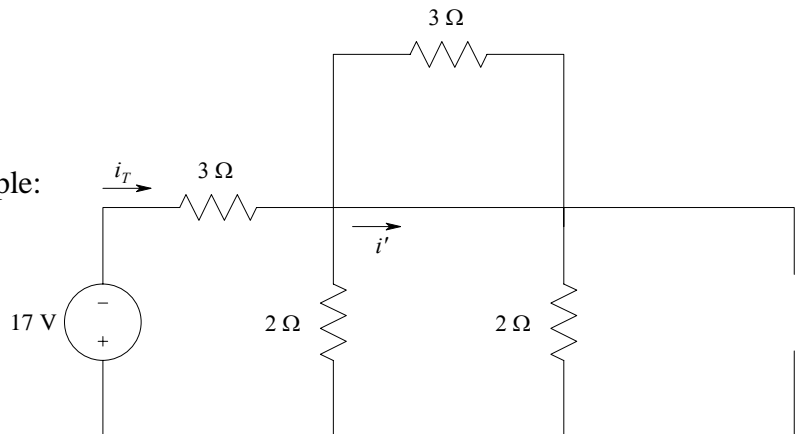
$$i' = i_r \frac{2}{4} = -\frac{17}{8} A$$



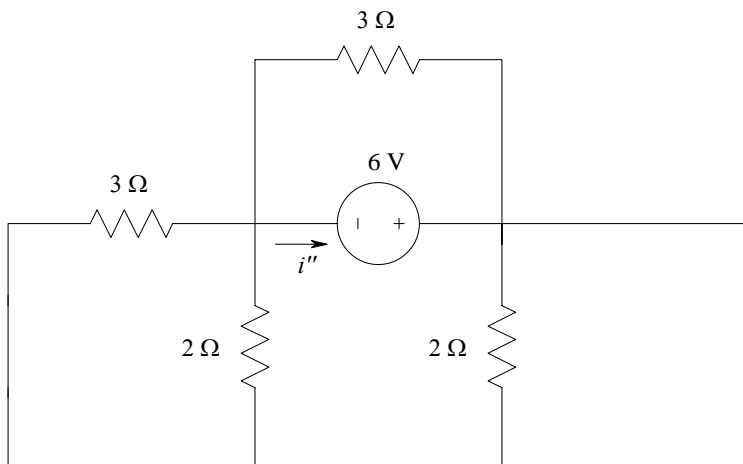**6 V is active:**

$$i'' = \frac{6}{R_T} = \frac{6}{(3//2+2)//3} = \frac{6}{\frac{48}{31}} = \frac{31}{8} A$$




**2 A is active:**

$$i''' = 2 \frac{2}{2 + \frac{6}{5}} = \frac{20}{16} \text{ A}$$

$$i = i' + i'' + i'''$$
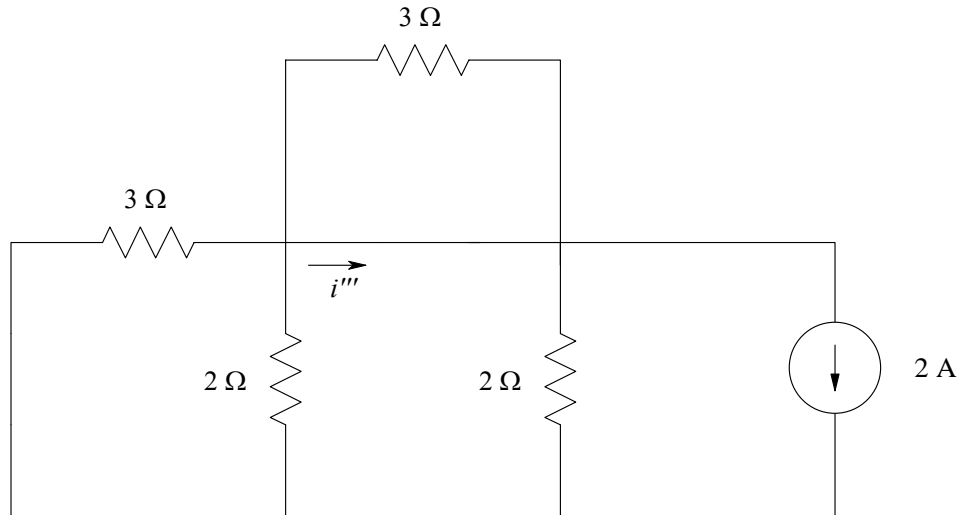
$$i = -\frac{17}{8} + \frac{31}{8} + \frac{20}{16} = 3 \text{ A}$$



4. The variable resistor in the circuit in Fig. P4 is adjusted for maximum power transfer to  $R$ .
- Find the value of  $R$ . (10 pts.)
  - Find the maximum power that can be delivered to  $R$ . (5 pts.)


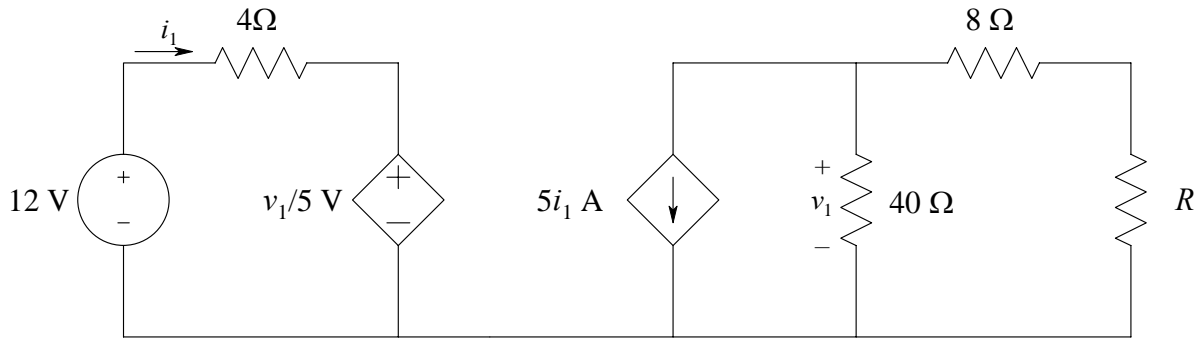


Figure P4

When the value of  $R = R_{TH}$  then it will absorb maximum power. The maximum power is

$$P_{\max} = \frac{V_{TH}^2}{4R_{TH}}$$

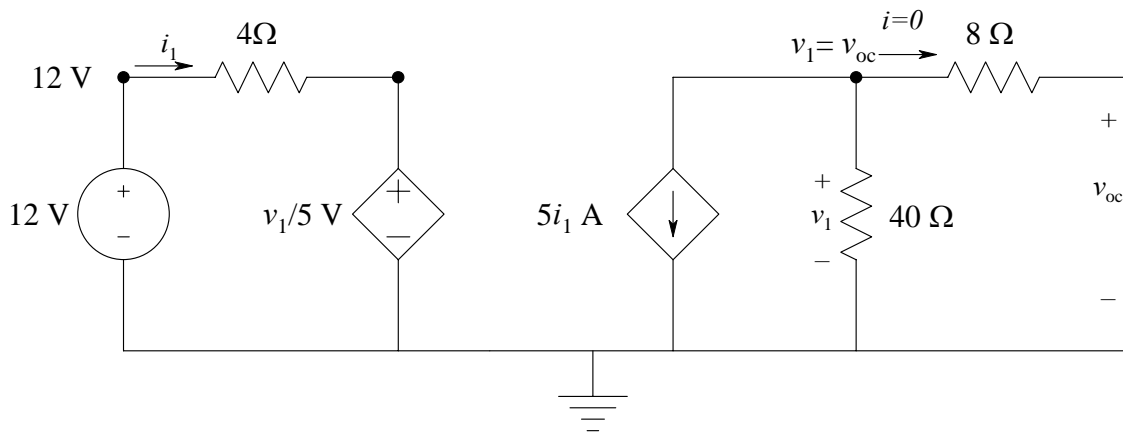In order to find  $V_{TH}$  we will find  $V_{oc}$



$$v_{oc} = -40 \times 5i_1 = -200i_1$$


$$i_1 = \frac{12 - \frac{v_{oc}}{5}}{4} = \frac{60 - v_{oc}}{20}$$

Therefore

$$v_{oc} = -200i_1 = -10(60 - v_{oc})$$

$$-9v_{oc} = -600$$

$$v_{oc} = \frac{600}{9} \text{ V}$$

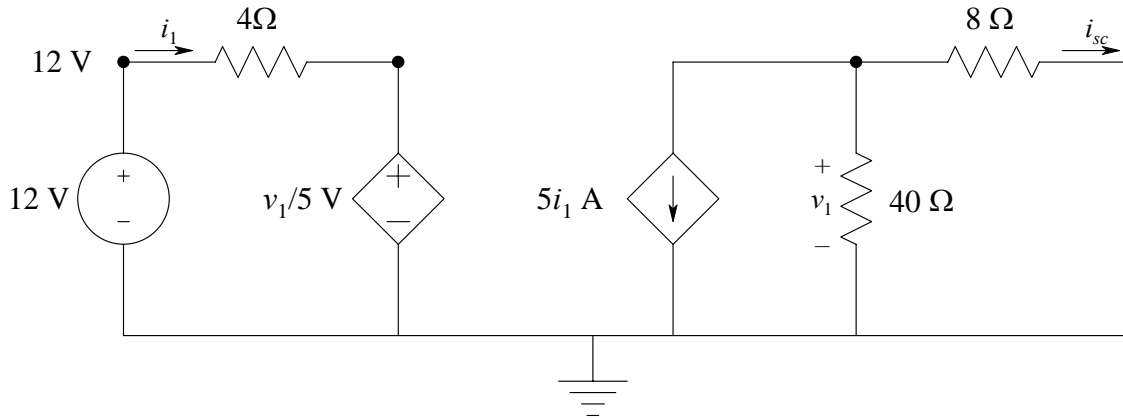

By using current division principle:

$$i_{sc} = -5i_1 \frac{40}{48} = -\frac{25}{6}i_1$$

$$v_1 = -40 \left( 5i_1 \frac{8}{48} \right) = -\frac{200}{6}i_1$$

And

$$i_1 = \frac{12 - \frac{v_1}{5}}{4} = \frac{60 - v_1}{20} = 3 - \frac{1}{20} \left( -\frac{200}{6}i_1 \right)$$

$$i_1 = -\frac{18}{4} A$$

Therefore

$$i_{sc} = -\frac{25}{6} \left( -\frac{18}{4} \right) = \frac{75}{4} A$$

$$R_{TH} = \frac{V_{oc}}{i_{sc}} = \frac{600/9}{75/4} = \frac{32}{9} \Omega$$

When  $R = \frac{32}{9} \Omega$  it will absorb maximum power.

$$P_{\max} = \frac{\left( \frac{600}{9} \right)^2}{4 \left( \frac{32}{9} \right)} = 312.5 W$$

5. Find  $i$  for  $t \geq 0$  if the circuit in Fig.P5 is under dc conditions at  $t = 0^-$ . (15 pts.)


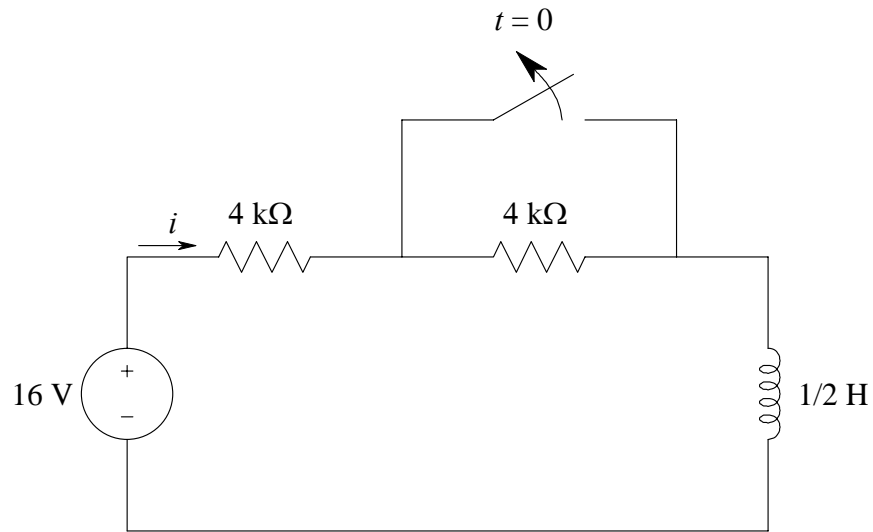



Figure P5

At  $t = 0^-$

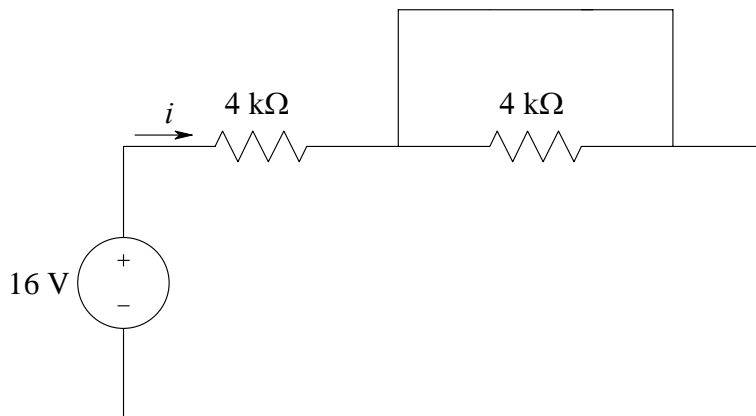

$$i(0^-) = \frac{16}{4k} = 4 \text{ mA} = i(0^+)$$

For  $t \geq 0$

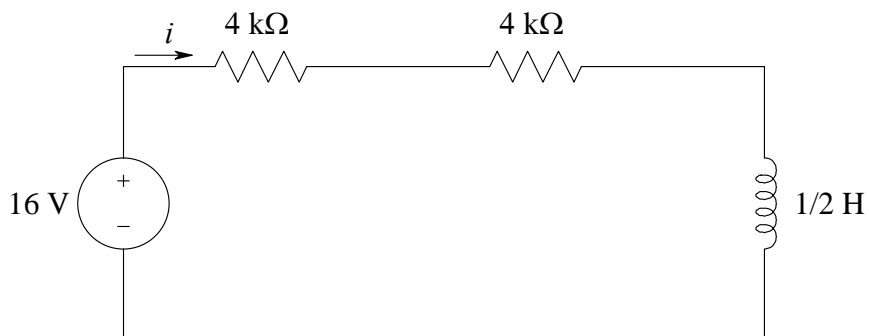




Since the circuit contains a source  $i$  will be:


$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}}$$

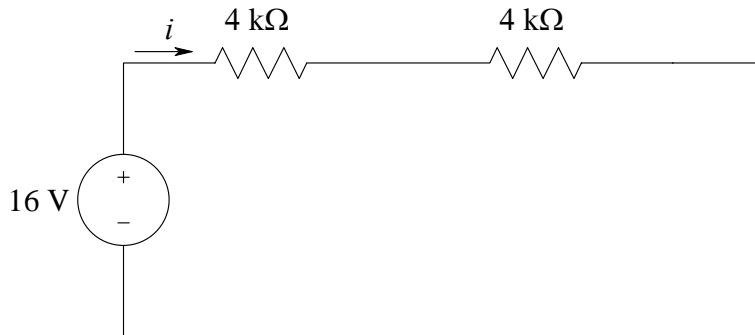At  $t = \infty$ , the circuit is under dc conditions



$$i(\infty) = \frac{16}{8k} = 2 \text{ mA}$$

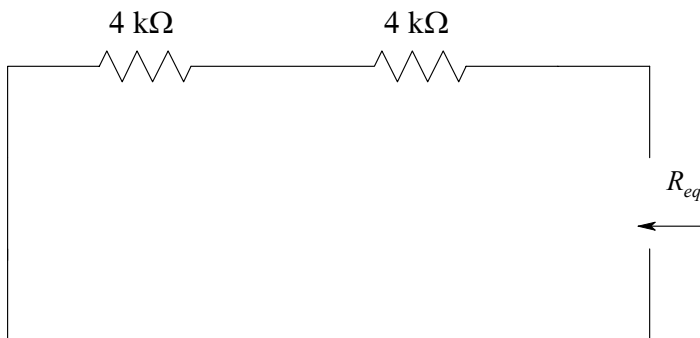$\tau = \frac{L}{R_{eq}}$  where  $R_{eq}$  is the equivalent resistance seen by the inductor.



$$R_{eq} = 8k\Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{1}{16k}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}} = 2 + (4 - 2)e^{-16000t} \text{ mA}$$

$$i(t) = 2 - 2e^{-16000t} \text{ mA}$$

6. Consider the circuit in Fig. P6. Find  $v$  for  $t \geq 0$  if  $v(0) = 4$  V and  $i(0) = 3$  A. (20 pts.)

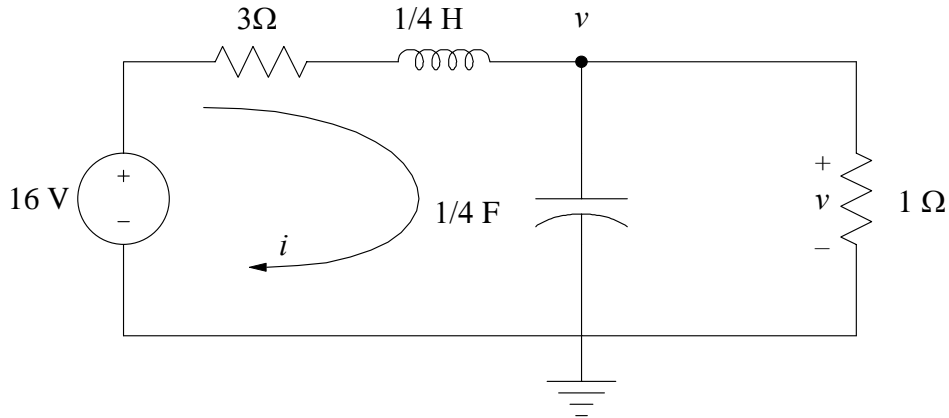


Figure P6

KCL at  $v$ :

$$i = \frac{1}{4} \frac{dv}{dt} + \frac{v}{1} \dots\dots\dots(1)$$

KVL around the loop ( $i$ ):

$$3i + \frac{1}{4} \frac{di}{dt} + v = 16 \dots\dots\dots(2)$$

Subst. Eq.(1) into (2) yields:

$$3\left(\frac{1}{4} \frac{dv}{dt} + \frac{v}{1}\right) + \frac{1}{4} \frac{d}{dt} \left(\frac{1}{4} \frac{dv}{dt} + \frac{v}{1}\right) + v = 16$$

$$\frac{3}{4} \frac{dv}{dt} + 3v + \frac{1}{16} \frac{d^2v}{dt^2} + \frac{1}{4} \frac{dv}{dt} + v = 16$$

Multiply both sides by 16:

$$\frac{d^2v}{dt^2} + 16 \frac{dv}{dt} + 64v = 16^2$$

Characteristic equation:

$$s^2 + 16s + 64 = 0$$

$$\therefore s_{1,2} = -8$$

The natural response  $v_n$ :

$$v_n = (A + Bt)e^{-8t}$$

The force response  $v_f$ :

$v_f = K$  the trial forced response.

$$64K = 16^2$$

$$K = 4$$

$$v_f = 4 \text{ V}$$

The complete response

$$v = v_n + v_f$$

$$v = (A + Bt)e^{-8t} + 4$$

$$v(0) = 4 = A + 4 \Rightarrow \boxed{A = 0}$$

By writing Eq(1) at  $t = 0$

$$i(0) = \frac{1}{4} \frac{dv(0)}{dt} + \frac{v(0)}{1}$$

$$\frac{dv(0)}{dt} = 4(i(0) - v(0)) = 4(3 - 4) = -4 \text{ V/s}$$

$$\frac{dv}{dt} = Be^{-8t} - 8(A + Bt)e^{-8t}$$

$$\frac{dv(0)}{dt} = -4 = B - 8(A) \Rightarrow \boxed{B = -4}$$

$$\therefore \boxed{v(t) = (-4te^{-8t} + 4)V}$$