



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EENG223 Circuit Theory I

Spring 2006-07

Instructor:

M. K. Uygurođlu

Midterm EXAMINATION

April 13, 2007

Duration : 100 minutes

Number of Problems: 4

Good Luck

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

Problem		Points
1		25
2		25
3		25
4		25
<i>TOTAL</i>		100

1. (a) Is the interconnection in Fig.P1 valid? Explain. (10 pts.)
(b) Can you find the total energy developed in the circuit? Explain. (15 pts.)

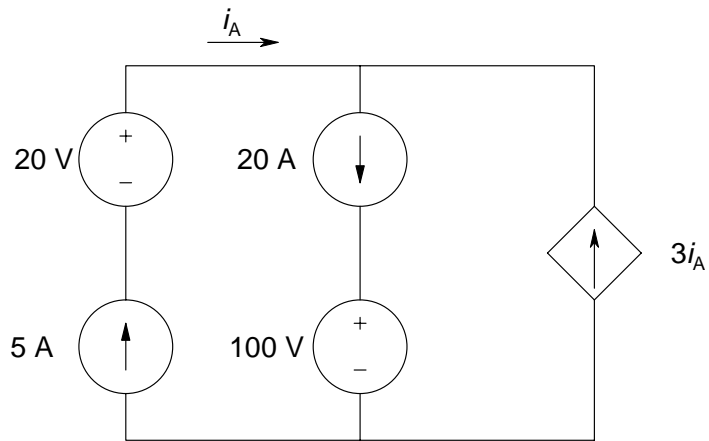


Figure P1

- (a) Yes, no violation of Kirchhoff's Laws.
(b) No, because the voltage across the independent and dependent current sources are indeterminate.

2. Use nodal analysis to find v_0 and i_0 in the circuit in Fig. P2. (25 pts.)

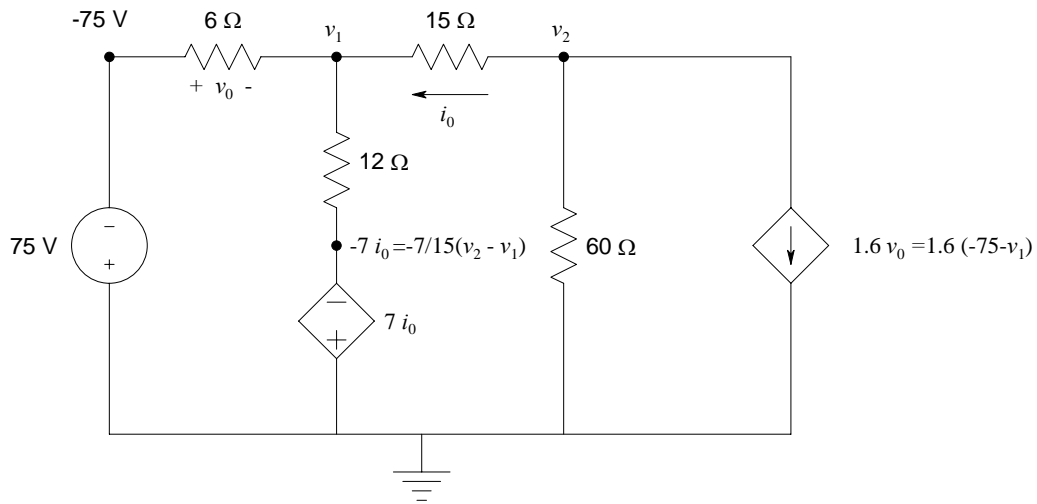


Figure P2

KCL at v_1 :

$$\left(\frac{1}{6} + \frac{1}{12} + \frac{1}{15}\right)v_1 - \frac{1}{15}v_2 - \frac{1}{6}(-75) - \frac{1}{12}\left(-\frac{7}{15}(v_2 - v_1)\right) = 0$$

Multiply both sides by 180 yields:

$$(30 + 15 + 12)v_1 - 12v_2 + (30)(75) + 7(v_2 - v_1) = 0$$

$$50v_1 - 5v_2 = -2250 \dots \dots \dots (1)$$

KCL at v_2 :

$$-\frac{1}{15}v_1 + \left(\frac{1}{15} + \frac{1}{60}\right)v_2 + 1.6(-75 - v_1) = 0$$

Multiply both sides by 60 yields:

$$-4v_1 + 5v_2 + 96(-75 - v_1) = 0$$

$$-100v_1 + 5v_2 = 7200 \dots \dots \dots (2)$$

One can obtain v_1 and v_2 by solving Eqns. (1) and (2) as:

$$v_1 = -99V$$

$$v_2 = -540V$$

Therefore

$$v_0 = -75 - v_1 = 24V$$

And

$$i_0 = \frac{1}{15}(v_2 - v_1) = -29.4A$$

3. Use superposition theorem to find i_0 and v_0 in the circuit in Fig.P3. (25 pts.)


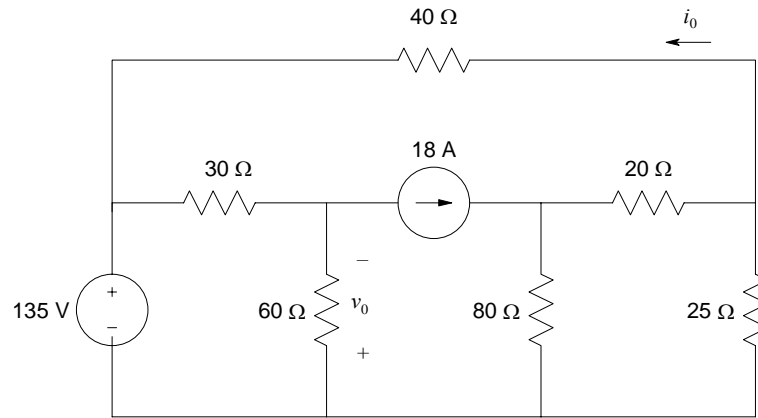


Figure P3

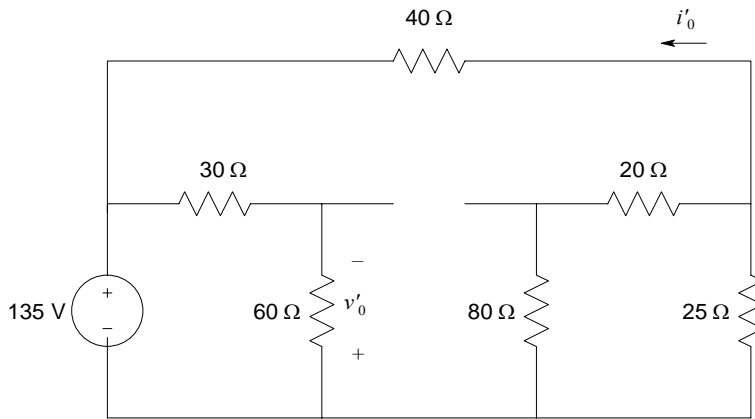

By using voltage division principle:

$$v'_0 = -135 \frac{60}{60+30} = -90V$$


20Ω and 80Ω resistors are in series.

$$20+80 = 100 \Omega$$

100Ω and 25Ω resistor are in parallel.

$$\frac{100 \times 25}{100+25} = 20\Omega$$

$$i'_0 = -\frac{135}{60} = -2.25A$$

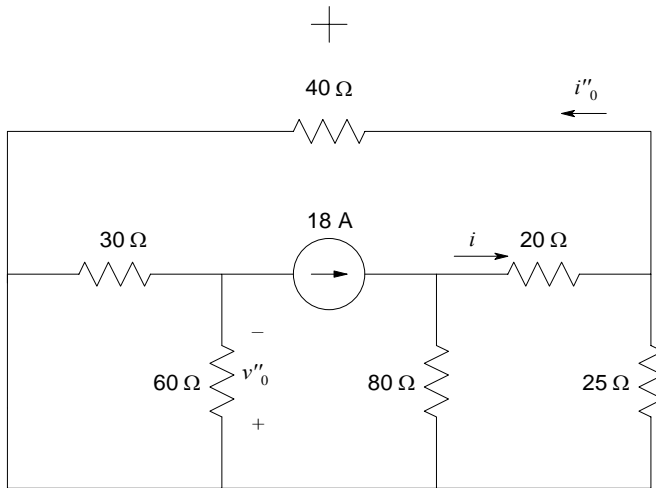

30Ω and 60Ω resistors are in parallel

$$30//60=20\Omega. \text{ Therefore}$$

$$v''_0 = 20 \times 18 = 360V$$

$$40//25=15.3846\Omega$$

By using current division principle:

$$i = 18 \frac{80}{80+20+15.3846} = 12.48A$$

By using current division principle one more:

$$i''_0 = i \frac{25}{25+45} = 4.8A$$

Therefore

$$v_0 = v'_0 + v''_0 = -90 + 360 = 270V$$

$$i_0 = i'_0 + i''_0 = -2.25 + 4.8 = 2.55A$$

4. (a) Use a series of source transformation to find i_0 in the circuit in Fig. P4. (10 pts.)
 (b) Verify your solution by using the mesh analysis method to find i_0 . (15 pts.)


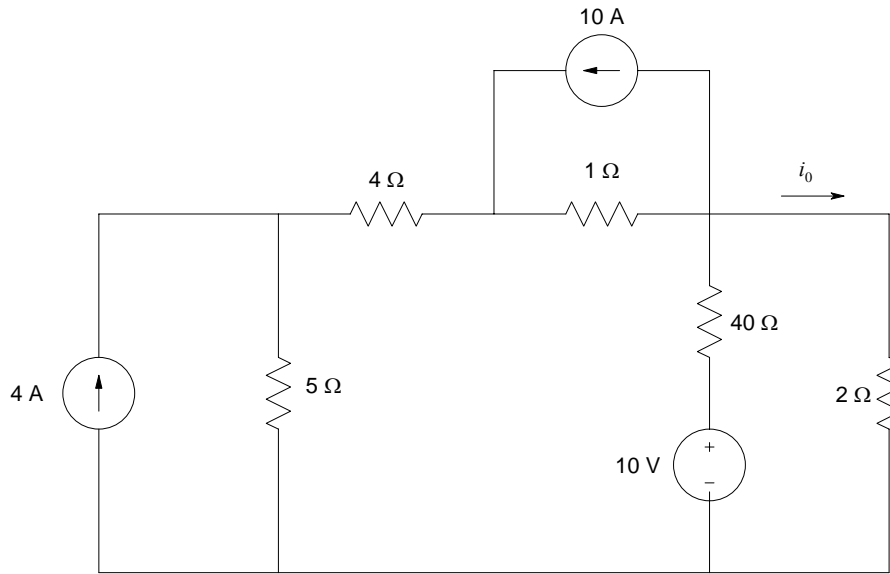


Figure P4


(a)

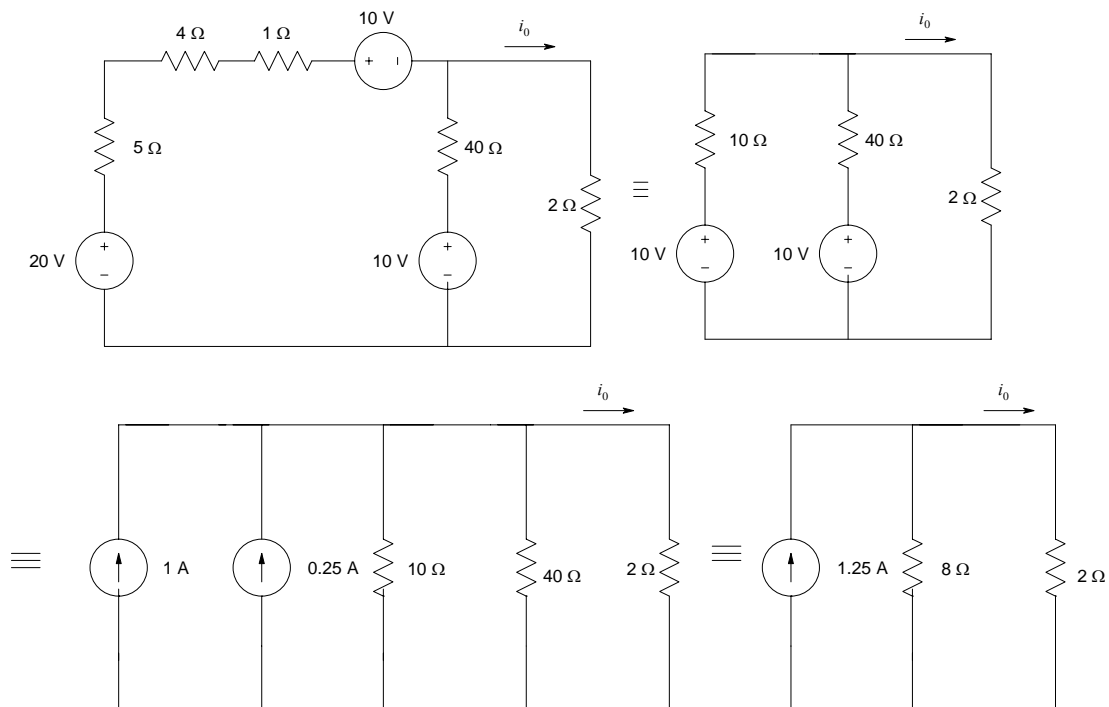

By using voltage division principle

$$i_0 = 1.25 \frac{8}{10} = 1A$$

(b)

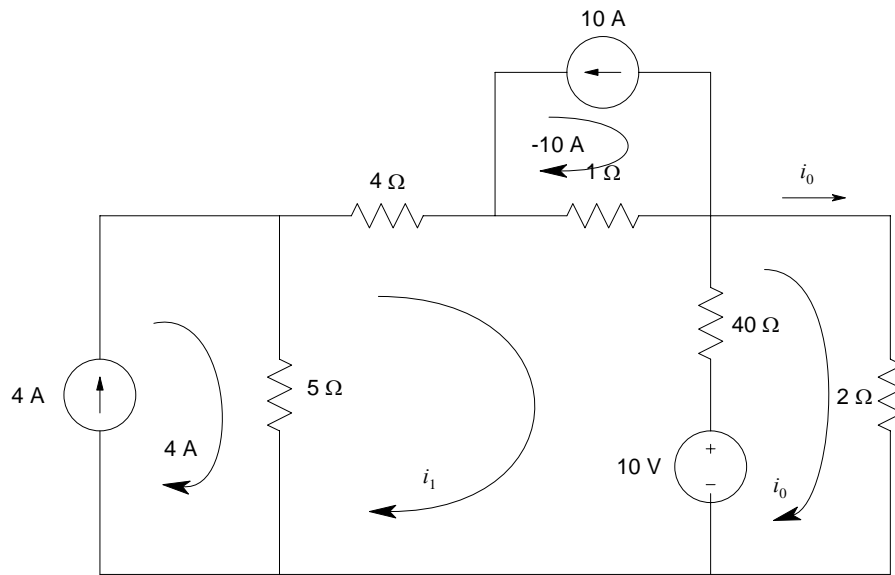

KVL around i_1 :

$$(5 + 4 + 1 + 40)i_1 - 40i_0 - 5(4) - 1(-10) = -10$$

$$50i_1 - 40i_0 = 0 \dots \dots \dots (1)$$

KVL around i_0 :

$$-40i_1 + 42i_0 = 10 \dots \dots \dots (2)$$

Using Eqns.(1) and (2) we can obtain i_0 as:

$$i_0 = 1A$$