



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EENG223 Circuit Theory I *INFE221 – Electrical Circuits*

Spring 2010-11

Instructors:

M. K. Uygurođlu
O. Kükrrer

Final EXAMINATION

June 3, 2011

Duration : 150 minutes


Number of Problems: 5

Good Luck

STUDENT'S	
NUMBER	
NAME	
SURNAME	SOLUTIONS
GROUP NO	


Problem		Points
1		30
2		20
3		15
4		20
5		15
<i>TOTAL</i>		100

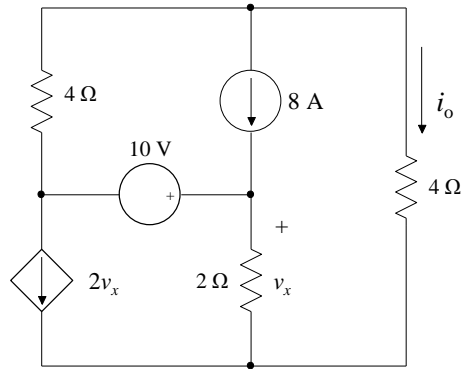1. Find the current i_o in the circuit shown using
 (a) Nodal analysis. (15 pts.)
 (b) Mesh analysis. (15 pts.)



Solution:

- (a) Nodal analysis

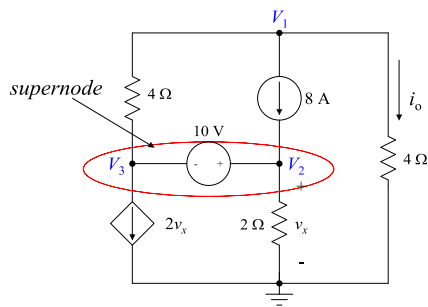

KVL for the 10-V source :

$$V_3 = V_2 - 10$$

$$v_x = V_2$$

KCL for the supernode:


$$2V_2 + \frac{V_2}{2} + \frac{V_2 - 10 - V_1}{4} = 8 \Rightarrow 11V_2 - V_1 = 42 \quad (1)$$

KCL for node 1:

$$\frac{V_1 - V_3}{4} + 8 + \frac{V_1}{4} = 0 \Rightarrow 2V_1 - (V_2 - 10) = -32 \Rightarrow 2V_1 - V_2 = -42 \quad (2)$$

From Eqs. (1) & (2) $\Rightarrow v_x = 2 \text{ V} \Rightarrow V_1 = -20 \text{ V} \therefore i_o = -5 \text{ A}$

- (b) Mesh analysis

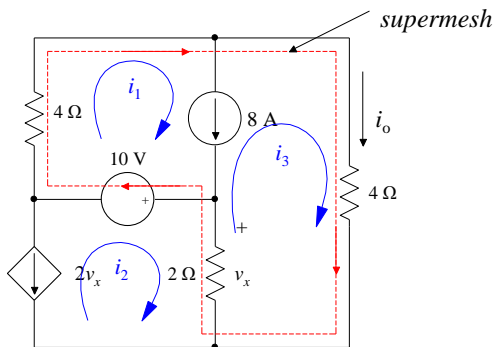

KVL for the supermesh:


$$4i_3 + 2(i_3 - i_2) + 10 + 4i_1 = 0 \quad (1)$$

For the 8-A current source: $i_1 - i_3 = 8 \text{ A} \quad (2)$

$$i_2 = -2v_x \quad v_x = 2(i_2 - i_3) \Rightarrow 5i_2 = 4i_3 \quad (3)$$


$$(1), (2) \text{ \& } (3) \Rightarrow i_3 = i_o = -5 \text{ A}$$

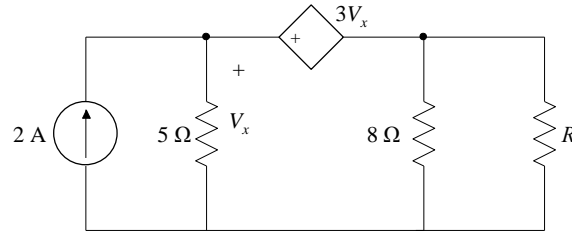2. In the circuit shown, find the value of R that will absorb maximum power from the circuit. Find also the value of this maximum power. (20 pts.)



Solution:


$$R = R_{Th} :$$

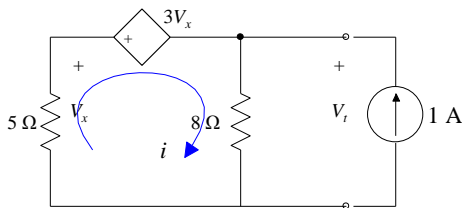

KVL:

$$\begin{aligned} -V_x + 3V_x + 8(i+1) &= 0 & V_x &= -5i \\ \Rightarrow i &= 4 \text{ A} & V_t &= 40 \text{ V} & \therefore R_{Th} &= \frac{V_t}{1 \text{ A}} = 40 \Omega \end{aligned}$$

V_{Th} :

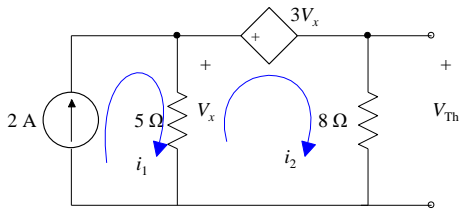


$$\begin{aligned} \text{KVL: } -V_x + 3V_x + 8i_2 &= 0 & \Rightarrow i_2 &= -\frac{1}{4}V_x \\ V_x &= 5(i_1 - i_2) & i_1 &= 2 \text{ A} & \Rightarrow V_x &= 10 + \frac{5}{4}V_x \\ \Rightarrow V_x &= -40 \text{ V}, & V_{Th} &= -2V_x = 80 \text{ V} \end{aligned}$$


$$P_{\max} = \frac{V_{Th}^2}{4R} = \frac{6400}{4 \times 40} = 40 \text{ W}$$

3. The initial capacitor voltage in the circuit shown is $v(0) = 10 \text{ V}$.

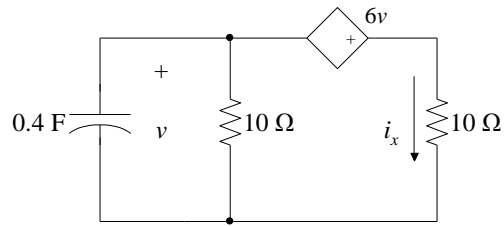- (a) Find the capacitor voltage $v(t)$ for $t > 0$. (10 pts.)
 (b) Find the current i_x at $t = 0.5 \text{ s}$. (5 pts.)



Solution:

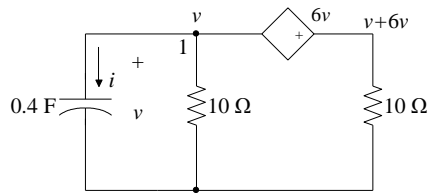


(a) KCL for node 1: $i + \frac{v}{10} + \frac{v+6v}{10} = 0 \Rightarrow i = -0.8v$

$$i = C \frac{dv}{dt} \Rightarrow \frac{dv}{dt} = \frac{i}{0.4} = -2v$$

$$v(t) = v(0) e^{-2t} = 10 e^{-2t} \text{ V}$$

(b) $i_x = \frac{7v}{10} = 0.7 \times 10 e^{-2t} = 7e^{-2t} \text{ A}$ $i_x(t = 0.5) = 7 e^{-1} \text{ A}$

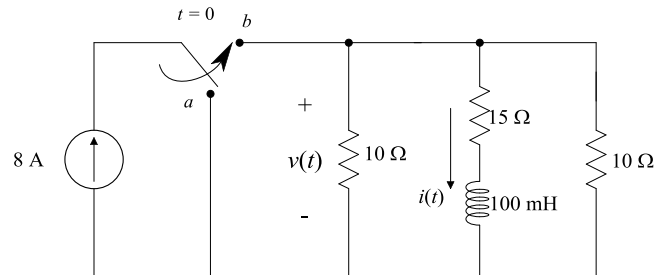
4. In the circuit shown, the switch has been in position *a* for a long time. At $t = 0$, the switch moves to *b*.
- (a) Find the current $i(t)$ for $t \geq 0$ s. (10 pts.)
- (b) Find the voltage $v(t)$ for $t \geq 0$ s. (10 pts.)




Solution:

- (a) $i(0) = 0$ A since for $t < 0$ the source current is zero.

To find $i(\infty)$:

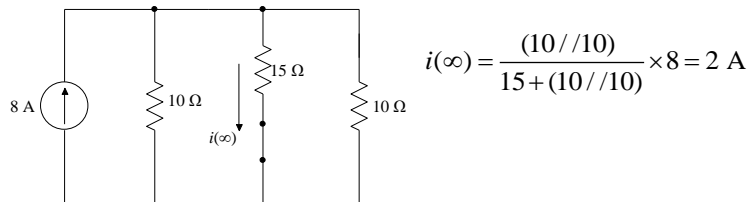


R_{eq} :

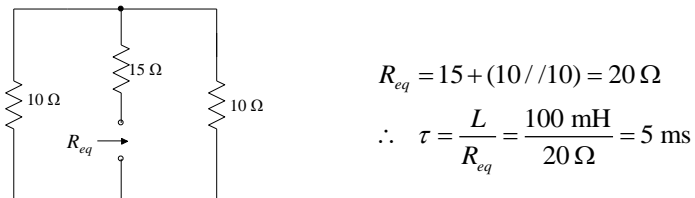


$$\Rightarrow i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau} = 2 + [0 - 2] e^{-t/0.005} = 2(1 - e^{-200t})$$

$$v(t) = 15 i(t) + 0.1 \frac{di(t)}{dt} = 30(1 - e^{-200t}) + 0.2 \times 200 e^{-200t} = 30 + 10 e^{-200t} \text{ V}$$

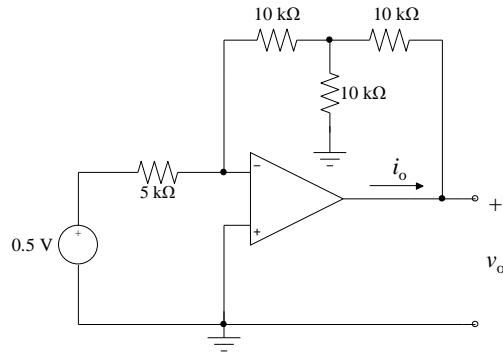5. Find the output voltage v_o and the output current i_o of the op-amp circuit shown. (15 pts.)



Solution:

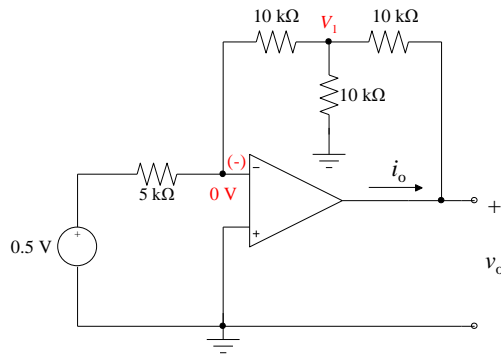

KCL at nodes (-) and V_1 :

$$\frac{0.5 - 0}{5 \text{ k}\Omega} = \frac{0 - V_1}{10 \text{ k}\Omega} \Rightarrow V_1 = -1 \text{ V}$$

$$\frac{V_1}{10 \text{ k}\Omega} + \frac{V_1}{10 \text{ k}\Omega} + \frac{V_1 - v_o}{10 \text{ k}\Omega} = 0 \Rightarrow v_o = 3V_1 = -3 \text{ V}$$

$$i_o = \frac{v_o - V_1}{10 \text{ k}\Omega} = -0.2 \text{ mA}$$