



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EENG223 Circuit Theory I ***INFE221 – Electrical Circuits***

Spring 2010-11

Instructors:

M. K. Uygurođlu

Second Midterm EXAMINATION

May 14, 2011

Duration : 100 minutes


Number of Problems: 4

Good Luck

| STUDENT'S | |
|-----------|--|
| NUMBER | |
| NAME | |
| SURNAME | |
| GROUP NO | |

| Problem | | Points |
|---------------------|--|--------|
| 1 | | 25 |
| 2 | | 25 |
| 3 | | 25 |
| 4 | | 25 |
| <i>TOTAL</i> | | 100 |

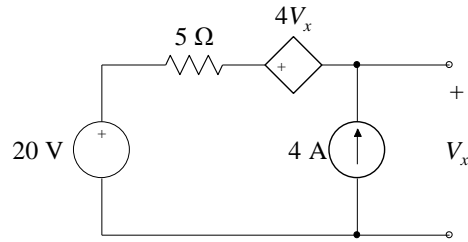
1. Use superposition to find V_x in the following circuit.



Solution

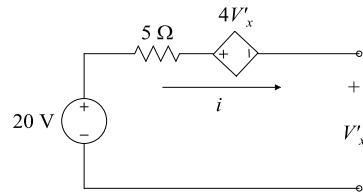(a) Apply 20 V source only:

Since $i = 0$ $5V'_x = 20 \Rightarrow V'_x = 4 \text{ V}$




Apply 4 A source only:

KVL:

$$5i_2 + 4V''_x + V''_x = 0$$

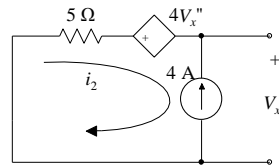
$$i_2 = -4 \text{ A} \Rightarrow V''_x = 4 \text{ V}$$



$$V_x = V'_x + V''_x$$


$$V_x = 4 + 4 = 8 \text{ V}$$

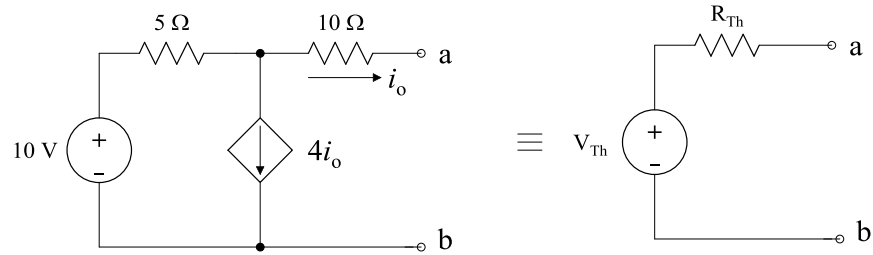2. In the circuit shown, find the Thevenin equivalent with respect to the terminals a-b.




Solution

In order to find V_{Th}

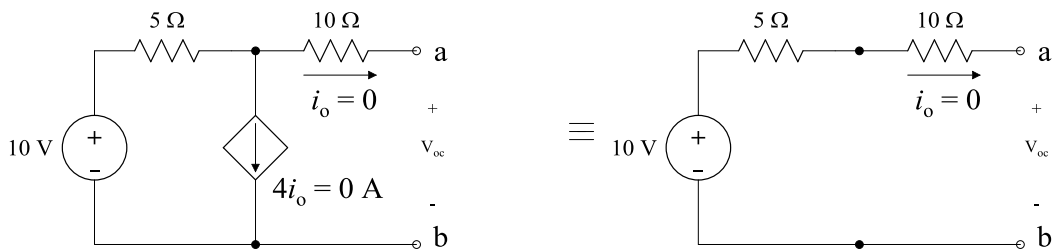


$V_{oc} = 10 \text{ V} = V_{Th}$ since $i_o = 0 \text{ A}$.

R_{Th} : KCL at node V_1 :

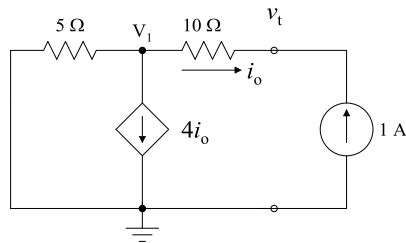


$$\begin{aligned} \frac{V_1}{5} + 4i_o + i_o &= 0 \Rightarrow V_1 = -25i_o \\ v_t = V_1 - 10i_o &= -35i_o \quad i_o = -1 \text{ A} \\ \Rightarrow v_t &= 35 \text{ V} \\ \therefore R_{Th} &= \frac{v_t}{1 \text{ A}} = 35 \Omega \end{aligned}$$

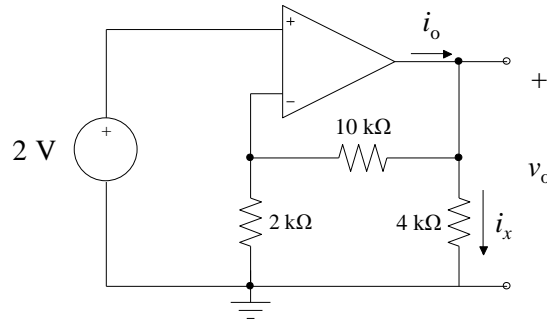3. In the op-amp circuit shown, find the currents i_o and i_x .



Solution

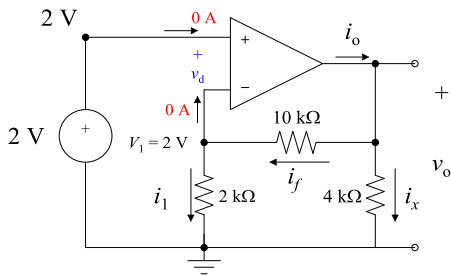

KCL at V_1 :

$$i_1 - i_f = 0$$

$$\frac{V_1}{2k} - \frac{V_0 - V_1}{10k} = 0$$


$$6V_1 - V_0 = 0 \Rightarrow V_0 = 6V_1 = 12 \text{ V}$$

$$i_x = \frac{12}{4k} = 3 \text{ mA}$$

$$i_f = \frac{12 - 2}{10k} = 1 \text{ mA}$$

$$i_o = i_x + i_f = 3 + 1 = 4 \text{ mA}$$

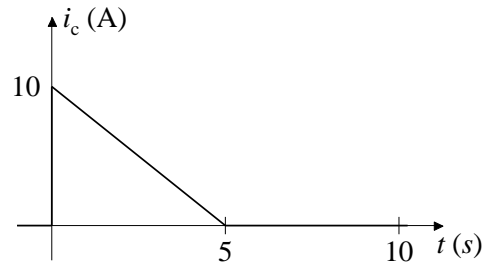4. The current through a capacitor $C = 0.2 \text{ F}$ is shown below. The initial capacitor voltage is $v_c(0) = 0 \text{ V}$. Find the capacitor voltage for $0 \leq t \leq 10 \text{ s}$.



Solution

$$i_c = \begin{cases} 0 & t < 0 \\ 10 - 2t & 0 \leq t < 5 \text{ s} \\ 0 & t > 5 \text{ s} \end{cases} \quad \Rightarrow \quad v_c(t) = v_c(0) + \frac{1}{C} \int_0^t i_c(\tau) d\tau = \begin{cases} 0 & t < 0 \\ 5(10t - t^2) & 0 \leq t < 5 \text{ s} \\ 125 & 5 \leq t \text{ s} \end{cases}$$

