



## Faculty of Engineering

### ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

#### ***EENG223 Circuit Theory I*** ***INFE221 – Electrical Circuits***

**Spring 2010-11**

**Instructors:**

**M. K. Uyguroğlu**

*Midterm EXAMINATION*

March 30, 2011

*Duration : 100 minutes*

Number of Problems: 6


*Good Luck*

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

**SOLUTIONS**


Problem		Points
1		15
2		15
3		15
4		15
5		20
6		20
<i>TOTAL</i>		100

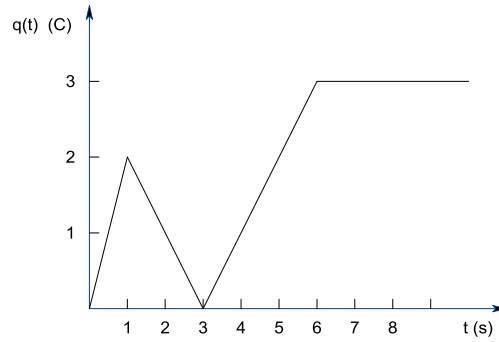1. The charge flowing in a wire is plotted in the following figure. Sketch the corresponding current.




$$q = \begin{cases} 2t \text{ C} & 0 < t < 1 \\ (-t+3) \text{ C} & 1 < t < 3 \\ (t-3) \text{ C} & 3 < t < 6 \\ 3 \text{ C} & t > 6 \end{cases}$$
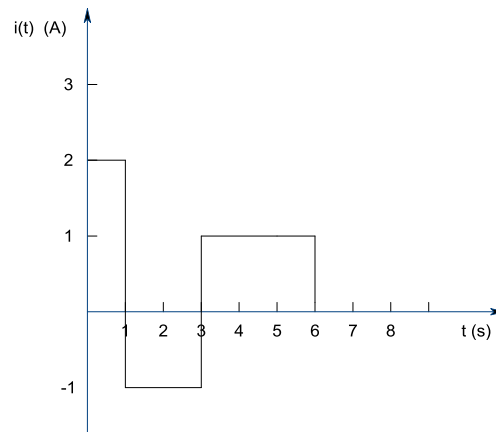
$$i = \frac{dq}{dt} = \begin{cases} 2 \text{ A} & 0 < t < 1 \text{ s} \\ -1 \text{ A} & 1 \text{ s} < t < 3 \text{ s} \\ 1 \text{ A} & 3 \text{ s} < t < 6 \text{ s} \\ 0 & t > 6 \text{ s} \end{cases}$$



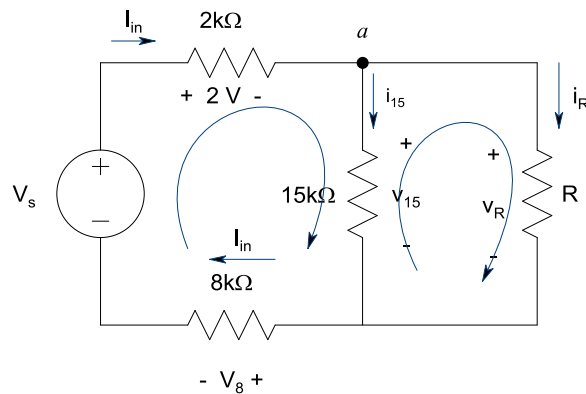2. Consider the following circuit. If the power delivered by the source is 20 mW, find R and  $V_s$ .



$$I_{in} = \frac{2}{2k} = 1mA$$

$$P_{delivered\ by\ the\ source} = V_s I_{in} = 20\ mW$$

$$V_s = \frac{20m}{1m} = 20\ V$$

$$v_8 = I_{in} 8k = 1m \times 8k = 8\ V$$

KVL around the left loop:

$$-V_s + 2 + v_{15} + v_8 = 0$$

$$v_{15} = 20 - 2 - 8 = 10\ V$$

Using Ohm's Law:

$$i_{15} = \frac{v_{15}}{15k} = \frac{10}{15}\ mA$$

KCL at node  $a$  yields:

$$I_{in} = i_{15} + i_R \Rightarrow i_R = I_{in} - i_{15} = 1 - \frac{10}{15} = \frac{5}{15} = \frac{1}{3}\ mA$$



KVL around the right loop:

$$-v_{15} + v_R = 0 \Rightarrow v_R = v_{15} = 10\ V$$


Therefore

$$R = \frac{v_R}{i_R} = \frac{10}{\frac{1}{3}} = 30k\ \Omega$$

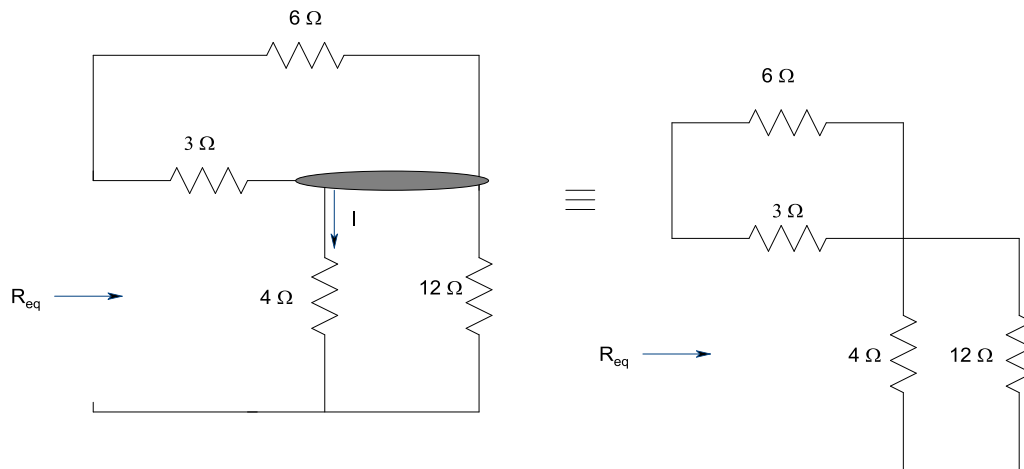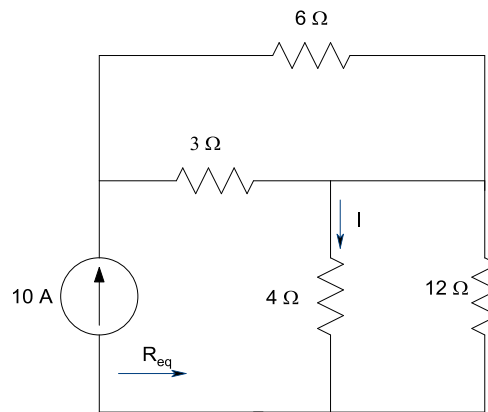3. Find the equivalent resistance ( $R_{eq}$ ) seen by the current source and the current  $I$  shown in the following circuit.



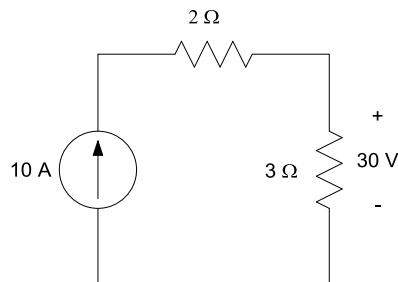
$$R_{eq} = \underbrace{6 // 3}_{\text{parallel}} + \underbrace{4 // 12}_{\text{parallel}} = \frac{6 \times 3}{6 + 3} + \frac{4 \times 12}{4 + 12} = 2 + 3 = 5 \Omega$$




Since the voltage across the  $4 \Omega$  is  $30 \text{ V}$  as well, then

$$I = \frac{30}{4} = 7.5 \text{ A}$$

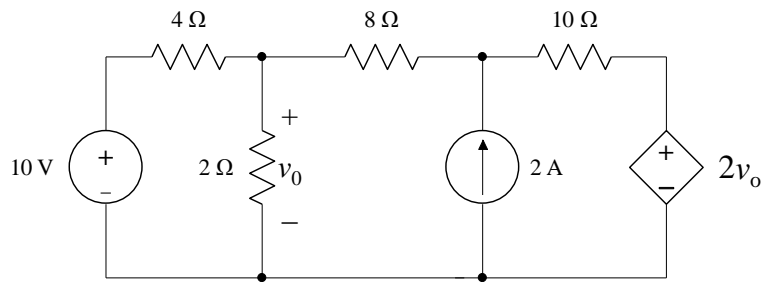4. In the following circuit, find the voltage  $v_o$  using nodal analysis.



SOLUTION:

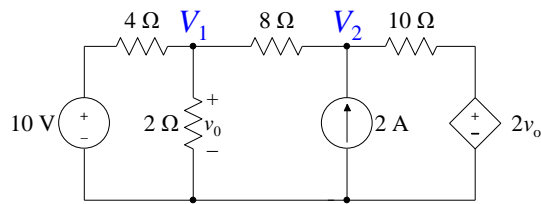


KCL equations:

Node 1: 
$$\frac{V_1 - 10}{4} + \frac{V_1}{2} + \frac{V_1 - V_2}{8} = 0 \Rightarrow 7V_1 - V_2 = 20 \quad (1)$$

Node 2: 
$$\frac{V_2 - V_1}{8} - 2 + \frac{V_2 - 2v_o}{4} = 0, \quad v_o = V_1 \Rightarrow -13V_1 + 9V_2 = 80 \quad (2)$$


Multiply (1) by 9 and add it to (2): 
$$50V_1 = 260 \Rightarrow V_1 = 5.2 \text{ V} \Rightarrow v_o = 5.2 \text{ V}$$

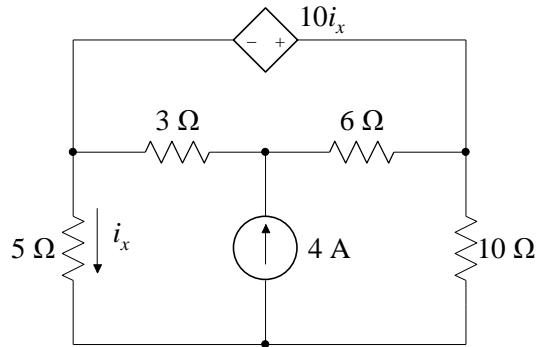5. In the circuit shown below,  
 (a) Find the current  $i_x$  using nodal analysis. (15 pts)  
 (b) Find the power supplied by the 4-A current source. (5 pts)



SOLUTION:

(a)

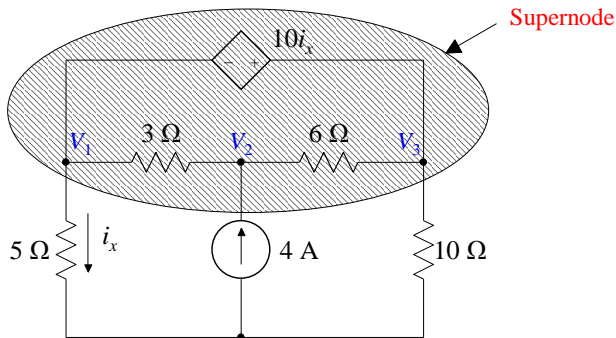

KCL eqn. for the supernode:  $\frac{V_1}{5} - 4 + \frac{V_3}{10} = 0 \Rightarrow 2V_1 + V_3 = 40$  (1)

KCL eqn. for node 2:  $\frac{V_2 - V_1}{3} - 4 + \frac{V_2 - V_3}{6} = 0 \Rightarrow -2V_1 + 3V_2 - V_3 = 24$  (2)

KVL equation for the  $10i_x$  source:


$$V_3 - V_1 = 10i_x = 2V_1 \Rightarrow V_3 = 3V_1$$

$$(1) \Rightarrow V_1 = 8 \text{ V} \Rightarrow i_x = 1.6 \text{ A}$$


(b) Power supplied by the 4-A source:

$$P = 4V_2 \quad \text{From (2)} \quad V_2 = \frac{24 + 2V_1 + V_3}{3} = 21.33 \text{ V} \quad \Rightarrow \quad P = 85.33 \text{ W}$$

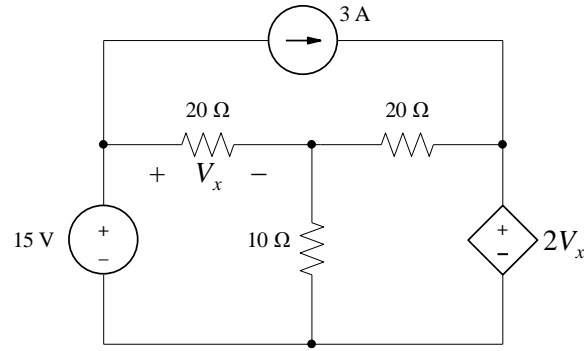6. In the circuit below, find the voltage  $V_x$  using mesh analysis.



SOLUTION:

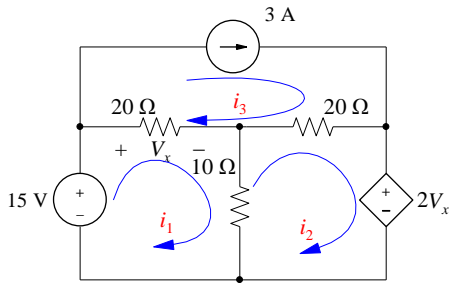

KVL equations:

Mesh 1:

$$\begin{aligned} -15 + 20(i_1 - i_3) + 10(i_1 - i_2) &= 0, \\ i_3 = 3 \text{ A} \Rightarrow 30i_1 - 10i_2 &= 75 \end{aligned} \quad (1)$$

Mesh 2:

$$\begin{aligned} 10(i_2 - i_1) + 20(i_2 - i_3) + 2V_x &= 0 \\ V_x = 20(i_1 - i_3) \Rightarrow 30i_1 + 30i_2 &= 180 \end{aligned} \quad (2)$$

$$\begin{aligned} (2) - (1) \Rightarrow 40i_2 &= 105 \quad i_2 = 2.625 \text{ A} \Rightarrow i_1 = \frac{75 + 26.25}{30} = 3.375 \text{ A} \\ \Rightarrow V_x &= 7.5 \text{ V} \end{aligned}$$

6.