



**Faculty of Engineering**

**ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT**

***EEE 223 Circuit Theory I***

**Instructor:**

**M. K. Uygurođlu**

*Final EXAMINATION*

January 10, 2005

*Duration : 90 minutes*


Number of Problems: 6

*Good Luck*

STUDENT'S	
NUMBER	
NAME	
SURNAME	

Problem		Points
1		20
2		20
3		20
4		20
5		20
<b><i>TOTAL</i></b>		100

1. Find  $i_1$  and  $v$ .

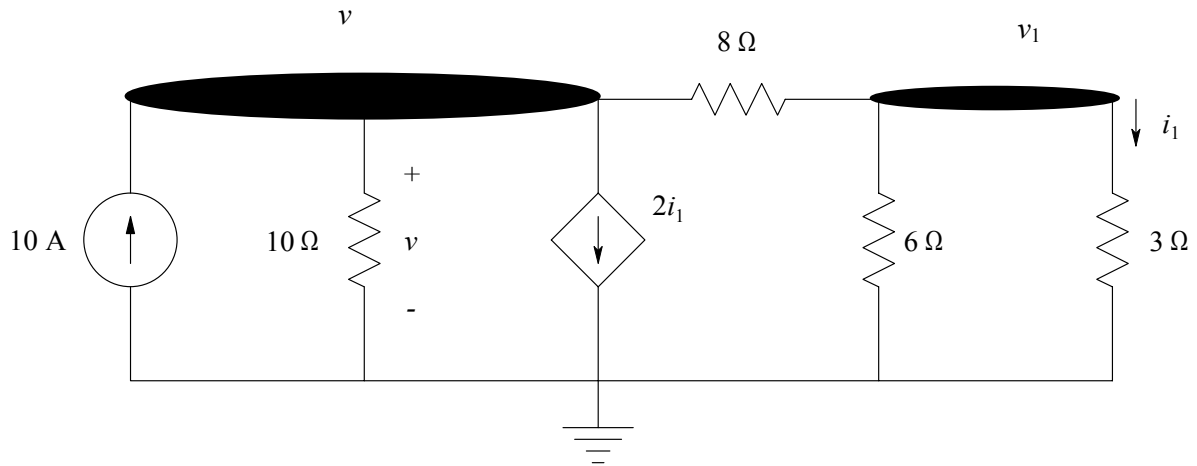

KCL at  $v$ :

$$\left(\frac{1}{10} + \frac{1}{8}\right)v - \frac{1}{8}v_1 = 10 - 2i_1$$

where  $i_1 = \frac{v_1}{3}$ .

Multiply both sides by 240 yields:

$$54v + 130v_1 = 2400 \quad (1.1)$$

KCL at  $v_1$ :

$$-\frac{1}{8}v + \left(\frac{1}{8} + \frac{1}{6} + \frac{1}{3}\right)v_1 = 0$$

Multiply both sides by 24:


$$-3v + 15v_1 = 0 \Rightarrow v = 5v_1 \quad (1.2)$$

Subst. Eqn.(1.2) into (1.1) yields:

$$\begin{aligned} 400v_1 &= 2400 \\ v_1 &= 6 \text{ V} \\ v &= 5v_1 = 30 \text{ V} \end{aligned} \quad (1.3)$$

$$i_1 = \frac{v_1}{3} = 2 \text{ A}$$

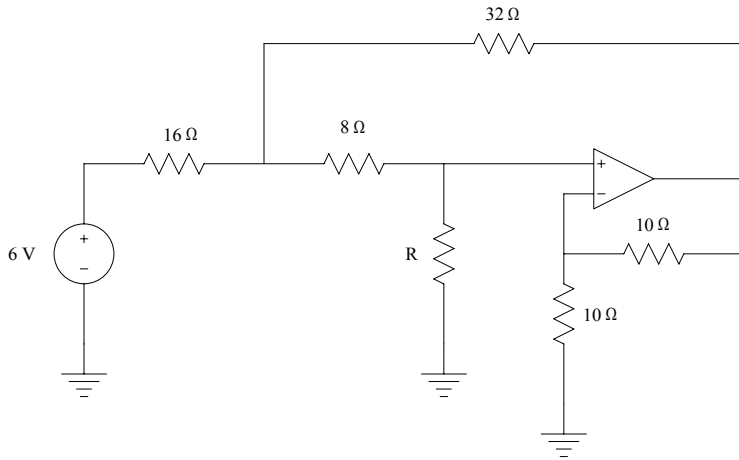
2. Find the maximum power that can be delivered to resistor  $R$  and the value of  $R$  for maximum power in the circuit shown below.



When  $R = R_{th}$ , it absorbs maximum power.

$$\text{And } P_{\max} = \frac{(V_{th})^2}{4R_{th}}$$

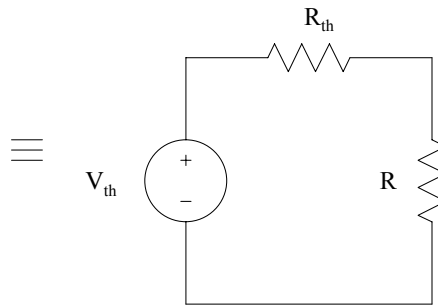In order to find  $V_{th}$ , open circuit voltage is found.



KCL at the inverting terminal:

$$\left(\frac{1}{10} + \frac{1}{10}\right)v_{oc} - \frac{1}{10}v_o = 0$$

$$v_o = 2v_{oc} \dots \dots \dots (1)$$

KCL at the non-inverting terminal:

$$\frac{v_{oc} - v_1}{8} = 0 \Rightarrow v_1 = v_{oc} \dots \dots \dots (2)$$

KCL at  $v_1$ :


$$\left(\frac{1}{8} + \frac{1}{16} + \frac{1}{32}\right)v_1 - \frac{1}{8}v_{oc} - \frac{1}{32}v_o - \frac{1}{16}6 = 0$$

or

$$7v_1 - 4v_{oc} - v_o = 12 \dots \dots \dots (3)$$

Subst. Eqns. (1) and (2) into (3) yields:

$$v_{oc} = 12 \text{ V}$$

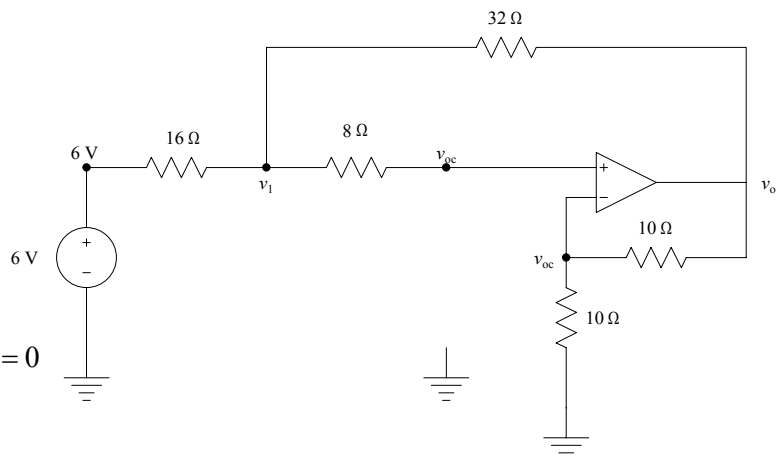

In order to find  $R_{th}$ , 1 A test source can be used.

KCL at the inverting terminal:

$$\left(\frac{1}{10} + \frac{1}{10}\right)v - \frac{1}{10}v_o = 0$$

$$v_o = 2v \dots \dots \dots (4)$$

KCL at the non-inverting terminal:

$$\frac{v - v_1}{8} = 1 \Rightarrow v_1 = v - 8 \dots \dots \dots (5)$$

KCL at  $v_1$ :

$$\left(\frac{1}{8} + \frac{1}{16} + \frac{1}{32}\right)v_1 - \frac{1}{8}v - \frac{1}{32}v_o = 0$$


or

$$7v_1 - 4v - v_o = 0 \dots \dots \dots (6)$$

Subst. Eqns. (4) and (5) into (6) yields:

$$v = 56 \text{ V}$$



$$R_{th} = \frac{v}{1} = 56 \Omega$$

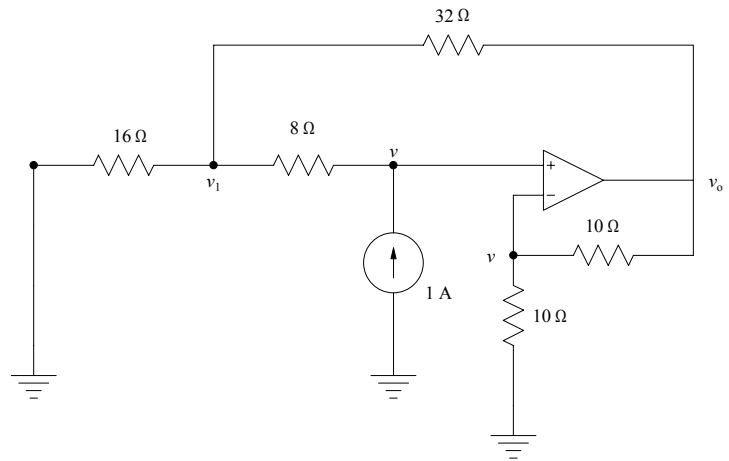

Therefore when  $R = 56 \Omega$  it absorbs maximum power and the maximum power is:

$$P_{\max} = \frac{12^2}{4(56)} = \frac{144}{224} = \frac{9}{14} \text{ W}$$

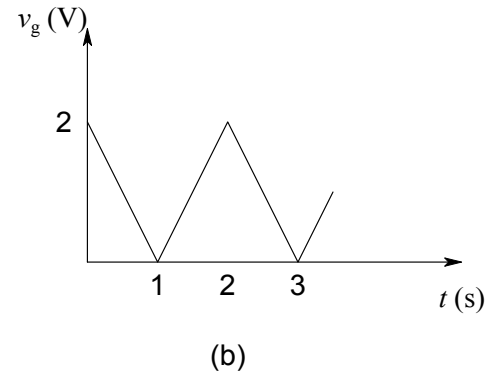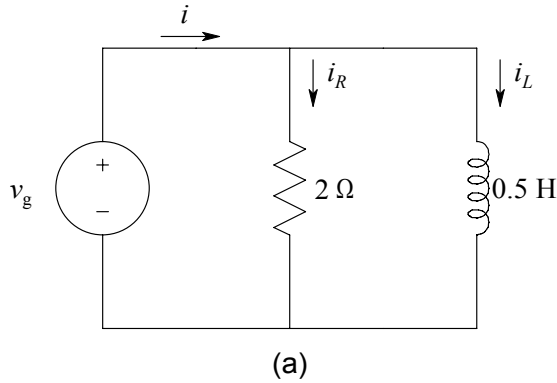3. For the circuit shown in (a), the source voltage is given in (b). Find the current  $i$  if  $i_L(0) = -1$  A for (a)  $0 < t < 1$  s and (b)  $1 < t < 2$  s.



$$i = i_R + i_L = \frac{v_g}{2} + \frac{1}{0.5} \int_0^t v_g dt + i_L(0)$$

where

$$v_g(t) = \begin{cases} -2t+2 & 0 < t < 1 \\ 2t-2 & 1 < t < 2 \\ -2t+6 & 2 < t < 3 \end{cases}$$

$0 < t < 1$ :

$$i = i_R + i_L = \frac{-2t+2}{2} + \frac{1}{0.5} \int_0^t (-2t+2) dt - 1 = -t+1+2[-t^2+2t]-1$$

$$i = -2t^2 + 3t \text{ A}$$


$1 < t < 2$ :

$$i = i_R + i_L = \frac{2t-2}{2} + \frac{1}{0.5} \int_1^t (2t-2) dt + i_L(1) = t-1+2[t^2-2t-1+2]+1$$

$$\text{where } i_L(1) = -2(1)^2 + 3(1) = 1$$

$$i = 2t^2 - 3t + 2 \text{ A}$$

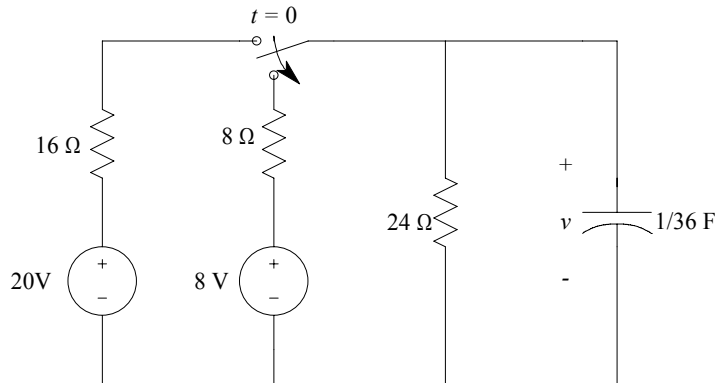
4. Find  $v$  for  $t > 0$  if the circuit is under dc condition at  $t = 0^-$ .



At  $t = 0^-$

Using voltage division principle:

$$v(0) = 20 \frac{24}{24+16} = 12V$$

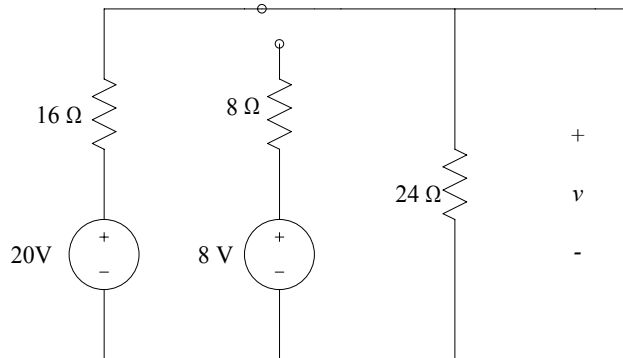


For  $t > 0$ :

It is known that

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-\frac{t}{\tau}}$$

$$\tau = R_{eq} C = 6 \frac{1}{36} = \frac{1}{6} s$$
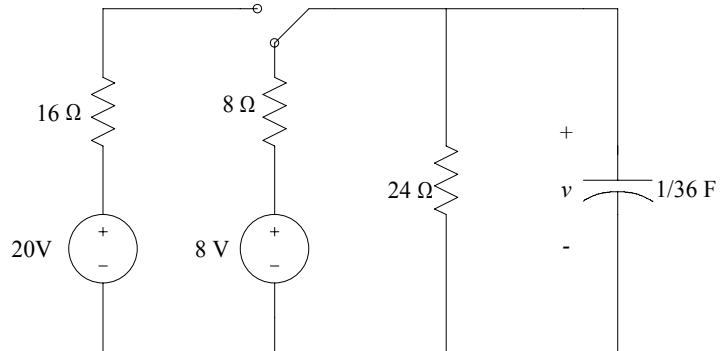
$$R_{eq} = 8 // 24 = \frac{8 \times 24}{8 + 24} = 6 \Omega$$




At  $t = \infty$  the circuit is under dc conditions.


$$v(\infty) = 8 \times \frac{24}{32} = 6V$$

Therefore
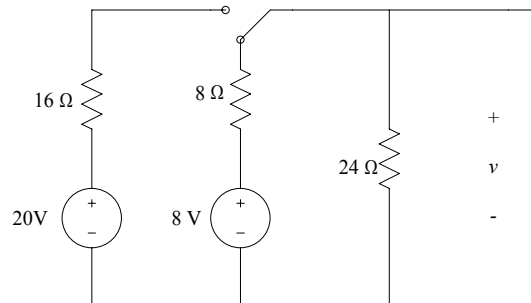
$$v(t) = 6 + [12 - 6] e^{-6t} = 6(1 + e^{-6t}) V$$



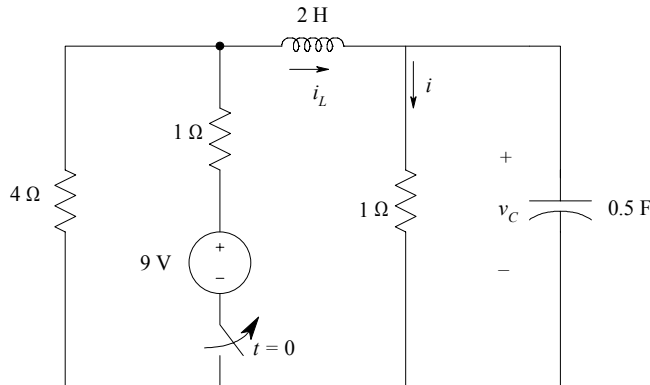5. Find  $i$  for  $t > 0$  if the circuit is under dc conditions at  $t = 0^-$ .



At  $t = 0^-$ .


$$i_T = \frac{9}{R_T} = 5 \text{ A}$$

$$R_T = 1 + 1 // 4 = \frac{9}{5} \Omega$$

Using current division principle:

$$i_L(0) = i(0) = 5 \times \frac{4}{4+1} = 4 \text{ A}$$

$$v_C(0) = 4(1) = 4 \text{ V}$$

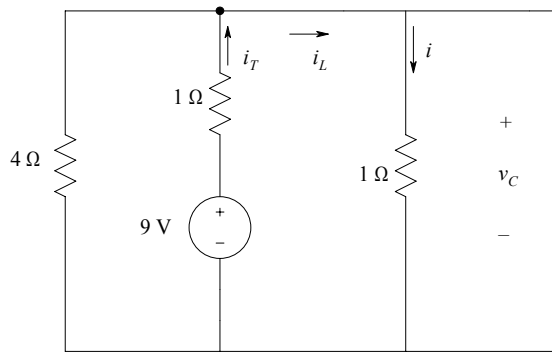

For  $t > 0$ :

$$i = \frac{v_C}{1}$$

KCL at node a:

$$i_L = v_C + 0.5 \frac{dv_C}{dt} \dots\dots(1)$$

At  $t=0$

$$i_L(0) = v_C(0) + 0.5 \frac{dv_C}{dt}(0) \Rightarrow \frac{dv_C}{dt}(0) = 0$$


KVL around the outer loop:

$$4i_L + 2 \frac{di_L}{dt} + v_C = 0 \dots\dots(2)$$

Subst. Eqn(1) into (2) yields:

$$4 \left( v_C + 0.5 \frac{dv_C}{dt} \right) + 2 \frac{d}{dt} \left( v_C + 0.5 \frac{dv_C}{dt} \right) + v_C = 0$$
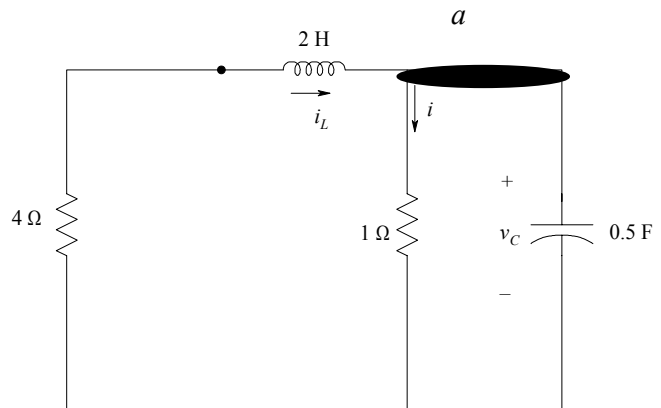
$$\frac{d^2 v_C}{dt^2} + 4 \frac{dv_C}{dt} + 5v_C = 0$$



Characteristic equation

$$s^2 + 4s + 5 = 0$$

$$s_{1,2} = \frac{-4 \mp \sqrt{16 - 20}}{2} = -2 \mp j1 \quad \text{Complex conjugate natural frequencies}$$

Therefore

$$v_C(t) = e^{-2t} (A_1 \cos t + A_2 \sin t)$$

In order to find  $A_1$  and  $A_2$  initial conditions will be used.

$$v_C(0) = 4 = A_1$$

$$\frac{dv_C}{dt} = -2e^{-2t} (A_1 \cos t + A_2 \sin t) + e^{-2t} (-A_1 \sin t + A_2 \cos t)$$

$$\frac{dv_C}{dt}(0) = -2A_1 + A_2 = 0$$

$$A_2 = 8$$

$$\therefore v_C(t) = e^{-2t} (4 \cos t + 8 \sin t) \text{ V}$$