



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EENG223 Circuit Theory I

Fall 07-08

Instructors:

M. K. Uygurođlu
E.G. Erdil

Midterm EXAMINATION

Nov. 20, 2007

Duration : 100 minutes

Number of Problems: 4

Good Luck

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

Problem		Points
1		25
2		25
3		25
4		25
<i>TOTAL</i>		100

1. Find v_o in the circuit in Fig. P1 using nodal analysis. (25 pts.)

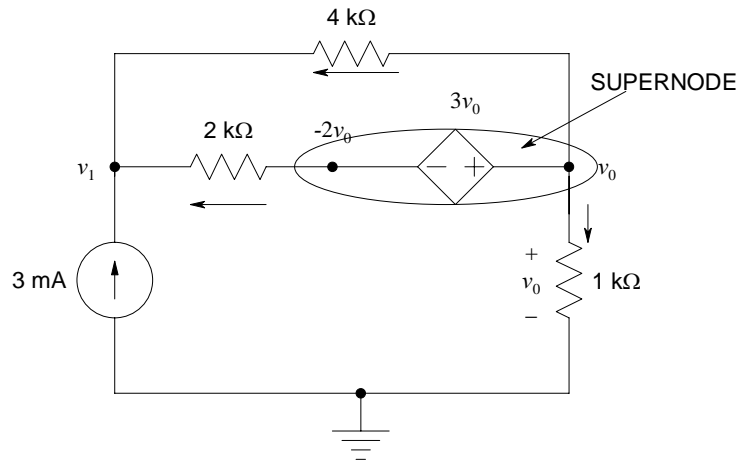


Figure P1

KCL at v_1 :

$$-\frac{v_o - v_1}{4k} - \frac{-2v_o - v_1}{2k} - 3m = 0$$

Multiply both sides by $4k$ yields:

$$-v_o + v_1 + 4v_o + 2v_1 = 12$$

$$3v_1 + 3v_o = 12 \dots \dots \dots (1)$$

KCL at the SUPERNODE:

$$\frac{v_o}{1k} + \frac{v_o - v_1}{4k} + \frac{-2v_o - v_1}{2k} = 0$$

Multiply both sides by $4k$ yields:

$$4v_o + v_o - v_1 - 4v_o - 2v_1 = 0$$

$$-3v_1 + v_o = 0 \dots \dots \dots (2)$$

By summing up Eq.(1) and (2) gives:

$$\boxed{v_o = 3 \text{ V}}$$

2. Use mesh analysis to find v in the circuit in Fig.P2. (25 pts.)

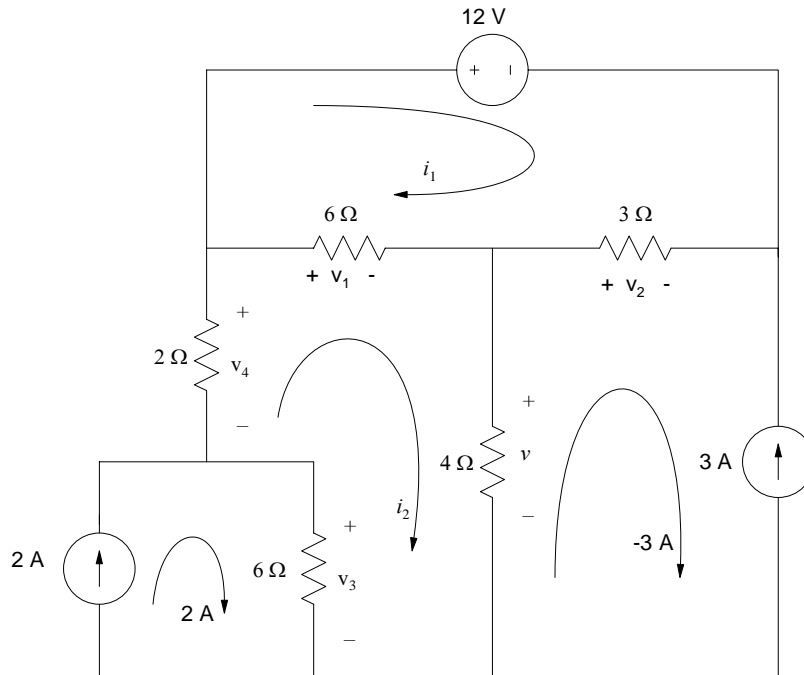


Figure P2

KVL around i_1 :

$$\begin{aligned}
 12 - v_2 - v_1 &= 0 \\
 -3(-3 - i_1) - 6(i_2 - i_1) &= -12 \\
 9i_1 - 6i_2 &= -21 \dots\dots\dots(1)
 \end{aligned}$$


KVL around i_2 :

$$\begin{aligned}
 v_1 + v - v_3 - v_4 &= 0 \\
 6(i_2 - i_1) + 4(i_2 + 3) - 6(2 - i_2) - 2(-i_2) &= 0 \\
 -6i_1 + 18i_2 &= 0 \dots\dots\dots(2)
 \end{aligned}$$


Multiplying Eq.(1) by 3 and summing up with (2) gives:

$$\begin{aligned}
 21i_1 &= -63 \\
 \boxed{i_1 = -3 \text{ A}} \quad \therefore \quad \boxed{i_2 = -1 \text{ A}} \\
 v &= 4(i_2 + 3) \\
 \boxed{v = 8 \text{ V}}
 \end{aligned}$$

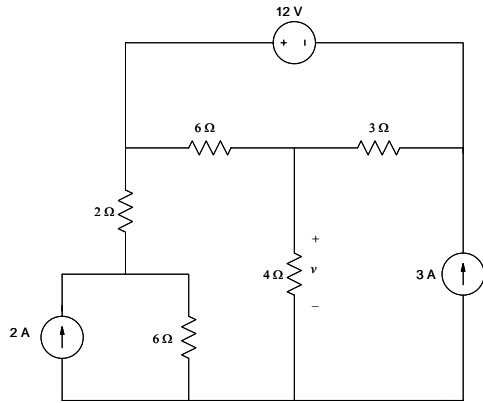3. Solve Problem 2 using superposition. (25 pts.)



|||

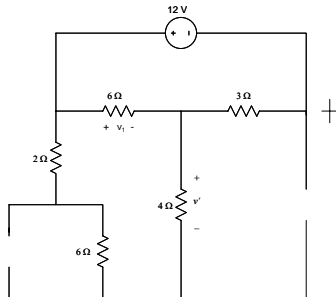

2, 6, and 4Ω resistors are in series and the series combination of these resistors is in parallel with 6Ω resistor. $(2+6+4)//6 = 4\Omega$
By using voltage division principle

v_1 can be calculated as

$$v_1 = 12 \frac{4}{7} = \frac{48}{7} \text{ V}$$

and

$$v' = -v_1 \frac{4}{4+8} = -\frac{16}{7} \text{ V}$$


6Ω and 3Ω resistors are in parallel

$$6//3 = 2\Omega$$

By using current division principle, the current flowing through 4Ω resistor is

$$i = 2 \frac{6}{6+8} = \frac{12}{14} \text{ A}$$

$$v'' = 4i = \frac{24}{7} \text{ V}$$

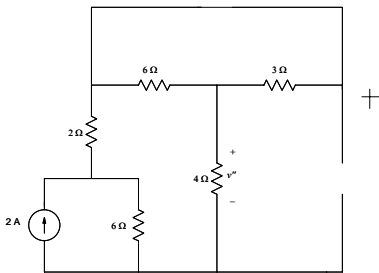

6Ω and 3Ω resistors are in parallel

$$6//3 = 2\Omega$$

By using current division principle we can calculate the current flowing through 4Ω resistor.

$$i = 3 \frac{8}{8+6} = \frac{24}{14} \text{ A}$$

$$\therefore v''' = 4i = \frac{48}{7} \text{ V}$$

$$v = v' + v'' + v''' = -\frac{16}{7} + \frac{24}{7} + \frac{48}{7} = 8\text{V}$$

Find the Thevenin equivalent looking into terminals a - b of the circuit in Fig. P4 and solve for i_x . (25 pts.)


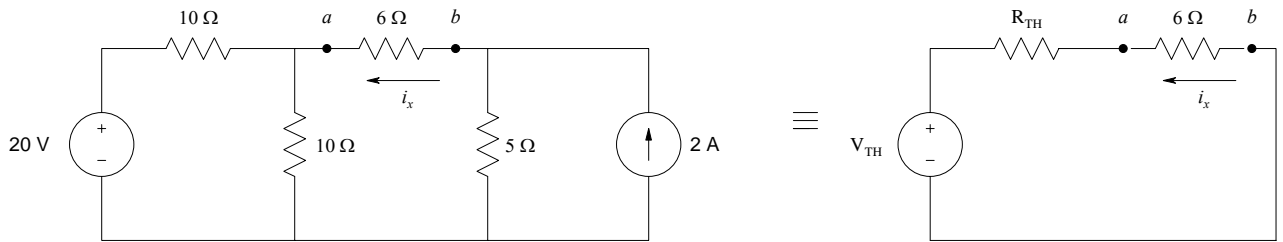


Figure P4


In order to find R_{TH} , all independent source values are set to zero.

⇒ All independent voltage sources are replaced by short circuits.

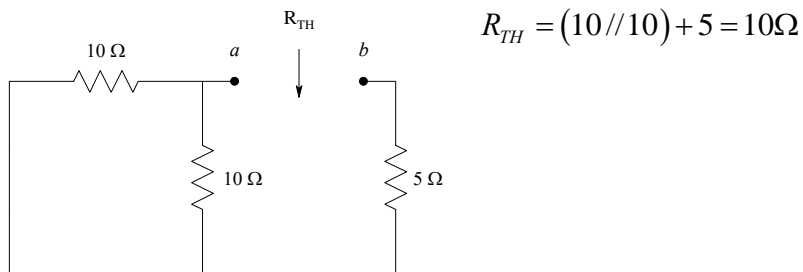⇒ All independent current sources are replaced by open circuits.



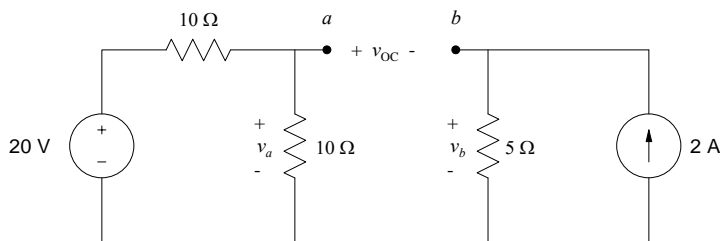For V_{TH} , open circuit voltage v_{OC} will be found between terminals a - b .



$$v_{OC} = v_a - v_b$$

where

$$v_a = 20 \frac{10}{10+10} = 10 \text{ V}$$

(using voltage division principle)

and

$$v_b = 2 \times 5 = 10 \text{ V}$$

$$v_{OC} = 0 \text{ V} = V_{TH}$$

$$i_x = \frac{V_{TH}}{R_{TH} + 6} = \frac{0}{16} = 0 \text{ A}$$