



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EENG223 Circuit Theory I ***INFE221 – Electrical Circuits***

Spring 2007-08

Instructor:

M. K. Uyguroğlu

Final EXAMINATION

May 27, 2008

Duration : 120 minutes

Number of Problems: 4

Good Luck

STUDENT'S	
NUMBER	
NAME	SOLUTIONS
SURNAME	
GROUP NO	

Problem		Points
1		25
2		25
3		25
4		25
TOTAL		100

1. Find v_0 in the circuit in Fig. P1 using
 - a) Superposition. (15 pts.)
 - b) Source transformation. (10 pts.)


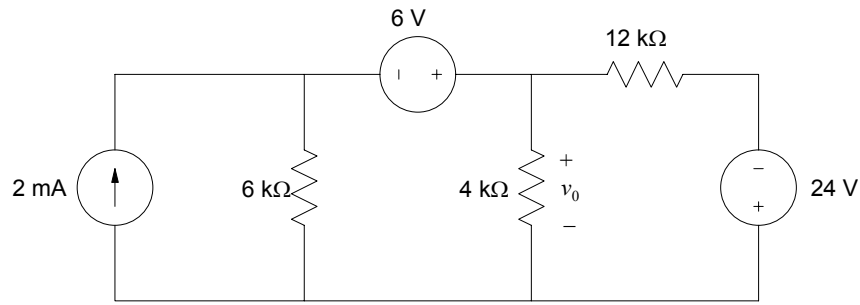


Figure P1

2 mA Current Source is active

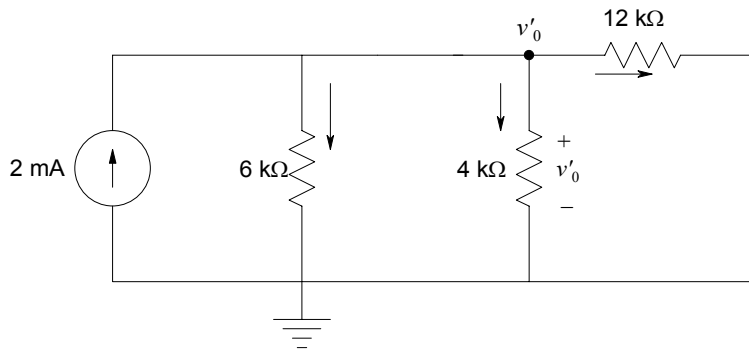

KCL at v_0 :

$$\frac{v'_0}{6k} + \frac{v'_0}{4k} + \frac{v'_0}{12k} = 2m$$


Multiply both sides by 12k yields:

$$2v'_0 + 3v'_0 + v'_0 = 24$$

$$6v'_0 = 24$$

$$v'_0 = 4V$$

6 V Voltage Source is active

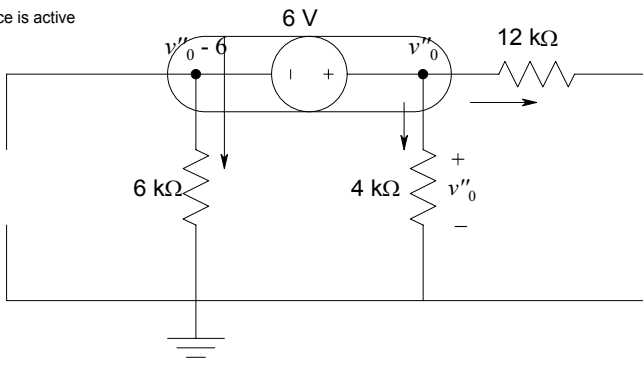

KCL at supernode:

$$\frac{v''_0 - 6}{6k} + \frac{v''_0}{4k} + \frac{v''_0}{12k} = 0$$


Multiply both sides by 12k yields:

$$2v''_0 - 12 + 3v''_0 + v''_0 = 0$$

$$6v''_0 = 12$$

$$v''_0 = 2V$$

24V Voltage Source is active

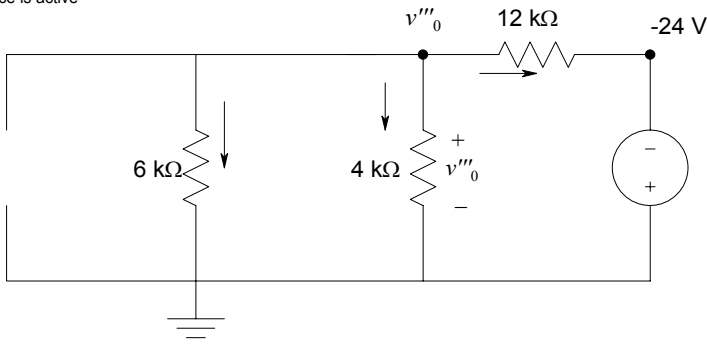

KCL at v_0 :

$$\frac{v'''_0}{6k} + \frac{v'''_0}{4k} + \frac{v'''_0 + 24}{12k} = 0$$




Multiply both sides by 12k yields:

$$2v'''_0 + 3v'''_0 + v'''_0 + 24 = 0$$

$$6v'''_0 = -24$$

$$v'''_0 = -4V$$
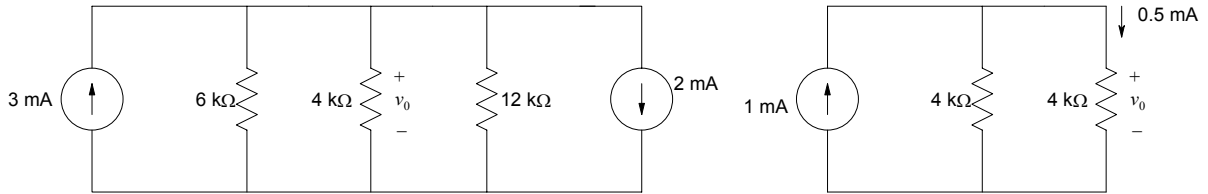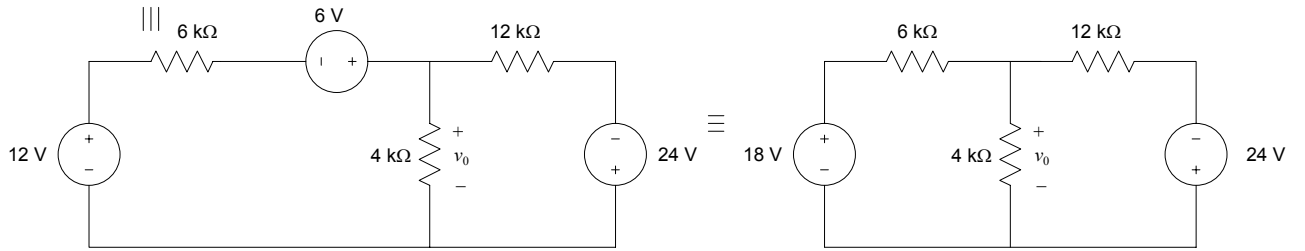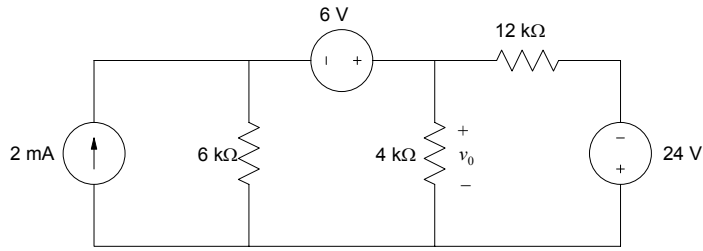
$$v_0 = v'_0 + v''_0 + v'''_0 = 4 + 2 - 4 = 2V$$



$$v_0 = 4k \times 0.5m = 2V$$

2. Find R_L for maximum power transfer and the maximum power that can be transferred to the load in Fig. P2. (20 pts.)


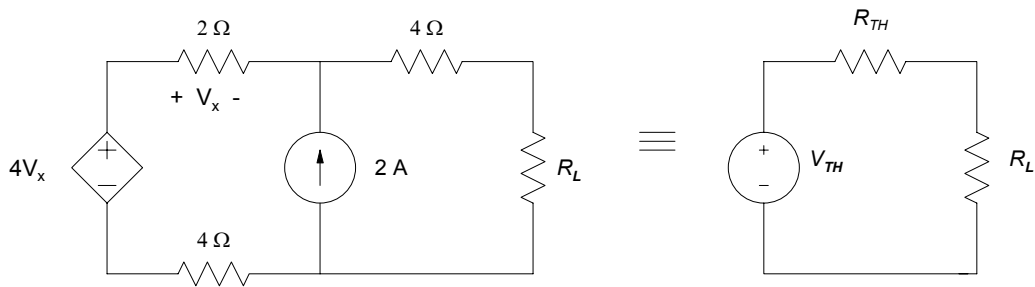


Figure P2

When $R_L = R_{TH}$ it absorbs maximum power.

$$P_{\max} = \frac{V_{TH}^2}{4R_{TH}}$$

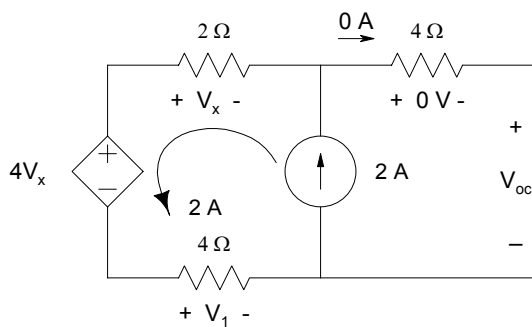In order to find V_{TH} , open circuit voltage V_{oc} is found.



KVL around the outer loop:

$$-4V_x + V_x + V_{OC} - V_1 = 0$$

$$V_{OC} = 3V_x + V_1$$


where

$$V_1 = 2 \times 4 = 8V$$

$$V_x = -2 \times 2 = -4V$$

$$\therefore V_{OC} = -12_x + 8 = -4V$$

In order to find R_{TH} :

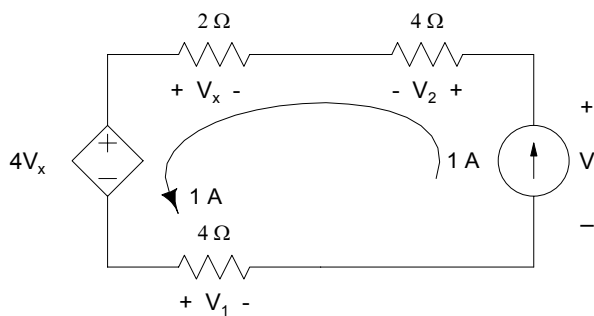

KVL around the loop:

$$-4V_x + V_x - V_2 + V - V_1 = 0$$

$$V = 3V_x + V_2 + V_1$$

where

$$V_x = -1 \times 2 = -2V$$

$$V_1 = 4 \times 1 = 4V$$

$$V_2 = 4 \times 1 = 4V$$

$$\therefore V = -6 + 4 + 4 = 2V$$


$$R_{TH} = \frac{V}{1} = 2\Omega$$

When $R_L = 2\Omega$ it absorbs maximum power.

$$P_{\max} = \frac{(-4)^2}{4 \times 2} = \frac{16}{8} = 2W$$

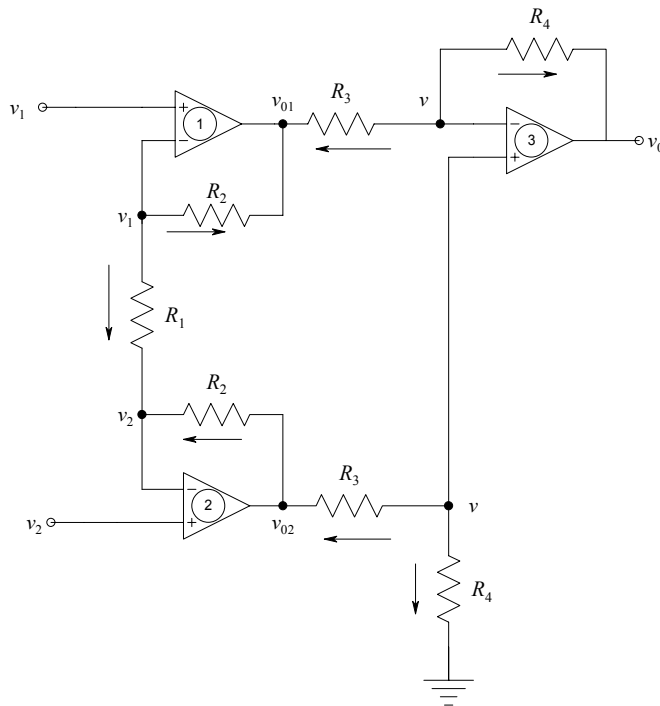3. Show that the output of the circuit in Fig.P3 is

$$v_0 = \frac{R_4}{R_3} \left(1 + 2 \frac{R_2}{R_1} \right) (v_2 - v_1)$$



KCL at the inverting input terminal of OP-AMP (3):

$$\frac{v - v_{01}}{R_3} + \frac{v - v_0}{R_4} = 0$$

$$\left(\frac{1}{R_3} + \frac{1}{R_4} \right) v - \frac{1}{R_3} v_{01} = \frac{v_0}{R_4}$$

$$v_0 = \left(\frac{R_4 + R_3}{R_3} \right) v - \frac{R_4}{R_3} v_{01} \dots \dots (1)$$

KCL at the inverting input terminal of OP-AMP (2):

$$\frac{v - v_{02}}{R_3} + \frac{v}{R_4} = 0$$

$$\left(\frac{1}{R_3} + \frac{1}{R_4} \right) v = \frac{v_{02}}{R_4}$$

$$v = \left(\frac{R_4}{R_3 + R_4} \right) v_{02} \dots \dots (2)$$

Subst. of Eq.(2) into (1) gives:

$$v_0 = \frac{R_4}{R_3} (v_{02} - v_{01}) \dots \dots (3)$$

KCL at the inverting input terminal of OP-AMP (1):

$$\frac{v_1 - v_{01}}{R_2} + \frac{v_1 - v_2}{R_1} = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} \right) v_1 - \frac{1}{R_1} v_2 = \frac{v_{01}}{R_2}$$

$$v_{01} = \left(\frac{R_2 + R_1}{R_1} \right) v_1 - \frac{R_2}{R_1} v_2 \dots \dots (4)$$

KCL at the inverting input terminal of OP-AMP (2):

$$\frac{v_2 - v_{02}}{R_2} + \frac{v_2 - v_1}{R_1} = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} \right) v_2 - \frac{1}{R_1} v_1 = \frac{v_{02}}{R_2}$$

$$v_{02} = \left(\frac{R_2 + R_1}{R_1} \right) v_2 - \frac{R_2}{R_1} v_1 \dots \dots (5)$$

Subst. of Eqns.(4) and (5) into (3) yields:

$$v_{01} = \frac{R_4}{R_3} \left(\left(\frac{R_2 + R_1}{R_1} \right) v_2 - \frac{R_2}{R_1} v_1 - \left(\frac{R_2 + R_1}{R_1} \right) v_1 + \frac{R_2}{R_1} v_2 \right)$$
$$v_{01} = \frac{R_4}{R_3} \left(\left(2 \frac{R_2}{R_1} + 1 \right) (v_2 - v_1) \right)$$

4. Suppose that the switch in Fig.P4 has been closed for a long time and is opened at $t = 0$. Find $i_0(t)$ for $t > 0$.


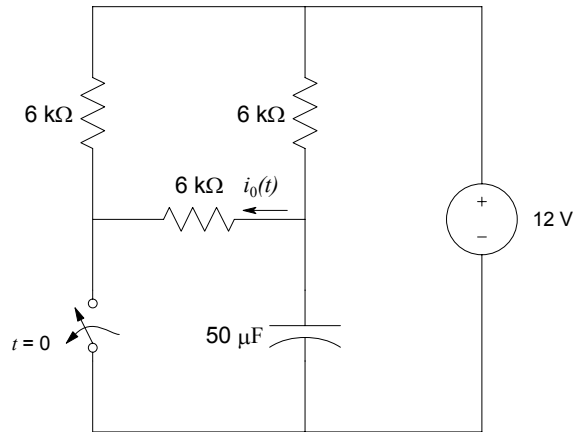


Figure P4

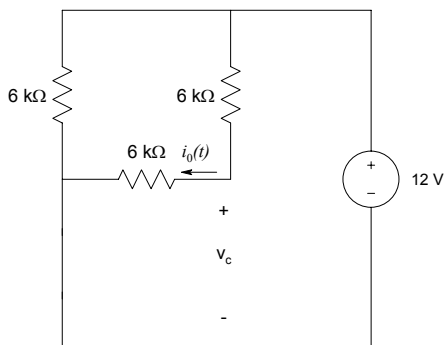
At $t = 0^-$, the circuit is under dc conditions. (Capacitor acts like an open circuit.)



Using voltage division principle:

$$v_c(0^-) = 12 \frac{6}{6+6} = 6 \text{ V}$$

For $t \geq 0$

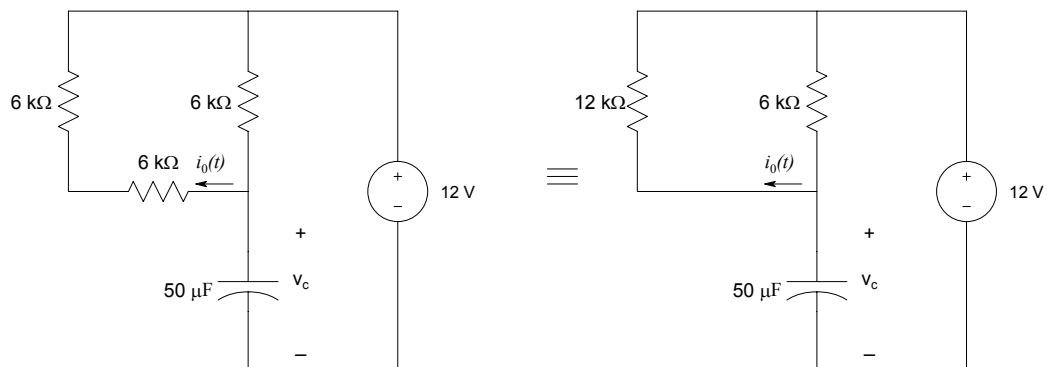


Since the circuit contains an independent source for $t \geq 0$, the voltage across the capacitor is:

$$v_c(t) = v_c(\infty) + [v_c(0) - v_c(\infty)] e^{-\frac{t}{\tau}}$$

Where $v_c(0) = v_c(0^-) = 6 \text{ V}$.

In order to find $v_c(\infty)$, let us consider the circuit at $t = \infty$. At $t = \infty$ the circuit is under dc conditions.

$$v_c(\infty) = 12 \text{ V}$$

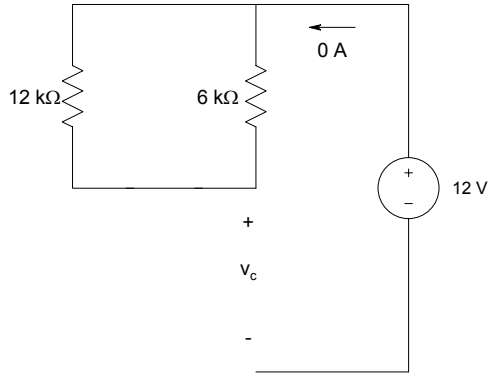


$$\tau = R_{eq} C$$

Where R_{eq} is the resistance seen by the capacitor.

$$R_{eq} = 12k // 6k = 4k \Omega$$
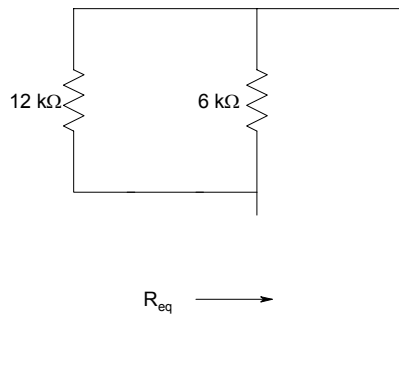
$$\tau = R_{eq} C = 4 \times 10^3 \times 50 \times 10^{-6} = 200 \times 10^{-3} = \frac{1}{5} \text{ s}$$



$$v_c(t) = 12 + [6 - 12]e^{-5t} \text{ V}$$

$$i_0(t) = \frac{v_c(t) - 12}{12} = \frac{12 + [6 - 12]e^{-5t} - 12}{12} = -0.5e^{-5t} \text{ A}$$