



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

**INFE221 – Electrical Circuits**

**Midterm Examination  
Fall 2018-19**

26 November 2018  
Duration: 105 minutes

**Instructor:** M. K. Uyguroğlu

STUDENT'S	
NUMBER	
NAME	SOLUTIONS
SURNAME	

Problem		Points
1		15
2		15
3		15
4		15
5		20
6		20
7		20
TOTAL		120

**Problem 1**

The current through an element is shown in Fig.P1. Determine the total charge that passes through the element.

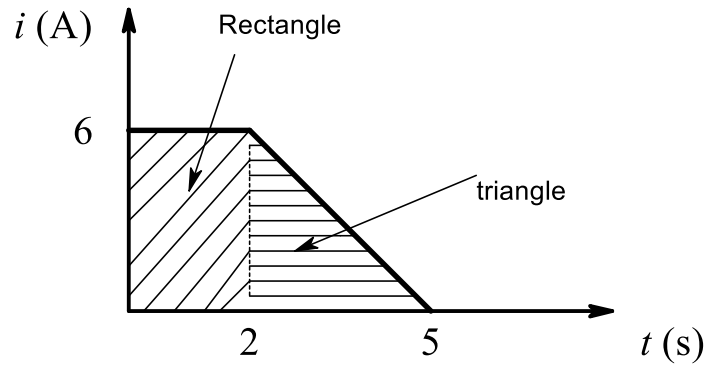


Figure P1

$$q_T = \int_0^5 i dt = \int_0^2 6 dt + \int_2^5 (-2t + 10) dt = 6t \Big|_0^2 + (-t^2 + 10t) \Big|_2^5$$

$$q_T = 12 - 25 + 50 + 4 - 20 = 66 - 45 = 21 \text{ C}$$

OR

By finding the area under the curve:

$$q_T = \underbrace{2 \times 6}_{\text{area of the rectangle}} + \underbrace{\frac{3 \times 6}{2}}_{\text{area of the triangle}} = 12 + 9 = 21 \text{ C}$$

**Problem 2**

Find the equivalent resistance  $R_{ab}$  in the circuit of Fig. P2.

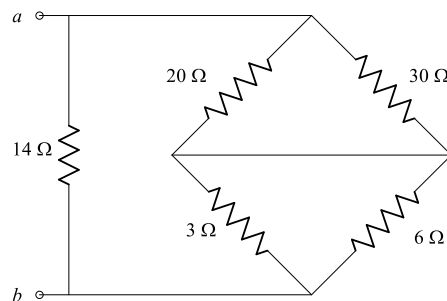


Figure P2

$$R_{ab} = 14 // \left( \underbrace{\left( \frac{20 // 30}{12} + \frac{3 // 6}{2} \right)}_{14} \right) = 7 \Omega$$

**Problem 3**

Use nodal analysis to obtain  $v_a$  in the circuit of Fig.P3.

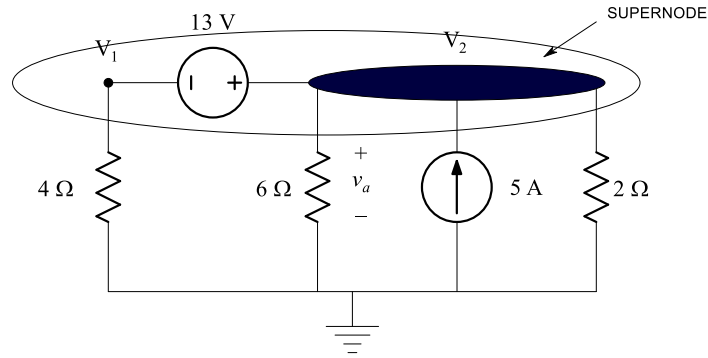


Figure P3

$$v_a = V_2$$

$$V_2 - V_1 = 13$$

$$\boxed{V_1 = V_2 - 13}$$

**KCL at the SUPERNODE:**

$$\frac{V_2 - 13}{4} + \frac{V_2}{6} + \frac{V_2}{2} = 5$$

**Multiply both sides by 12 yields:**

$$\frac{V_2 - 13}{4} + \frac{V_2}{6} + \frac{V_2}{2} = 5$$

$$3V_2 - 39 + 2V_2 + 6V_2 = 60$$

$$11V_2 = 99$$

$$\boxed{V_2 = 9 \text{ V} = v_a}$$

**Problem 4**

Use mesh analysis to obtain  $v_a$  in the circuit of Fig.P4.

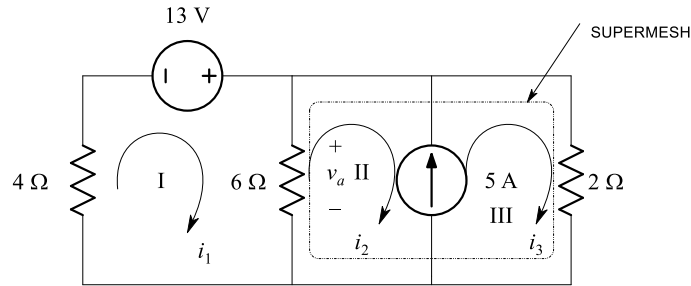


Figure P4

$$i_3 - i_2 = 5$$

$$i_3 = 5 + i_2$$

$$v_a = 6(i_1 - i_2)$$

KVL around mesh I:

$$4i_1 - 13 + 6(i_1 - i_2) = 0$$

$$10i_1 - 6i_2 = 13 \dots \dots (1)$$

KVL around the SUPERMESH:

$$6(i_2 - i_1) + 2(5 + i_2) = 0$$

$$-6i_1 + 8i_2 = -10 \dots \dots (2)$$

Multiply Eq.(1) by 4 and Eq.(2) by 3 and then add the equations:

$$(40 - 18)i_1 = 22$$

$$i_1 = 1 \text{ A}$$

Then using Eq. (1):

$$i_2 = \frac{1}{6}(10(1) - 13) = -0.5 \text{ A}$$

$$v_a = 6(1 + 0.5) = 9 \text{ V}$$

**Problem 5**

Use superposition to obtain  $v_a$  in the circuit of Fig.P5.


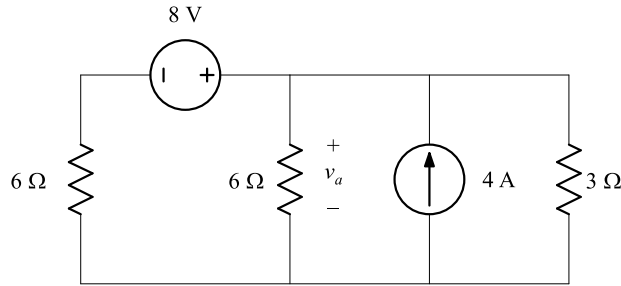


Figure P5

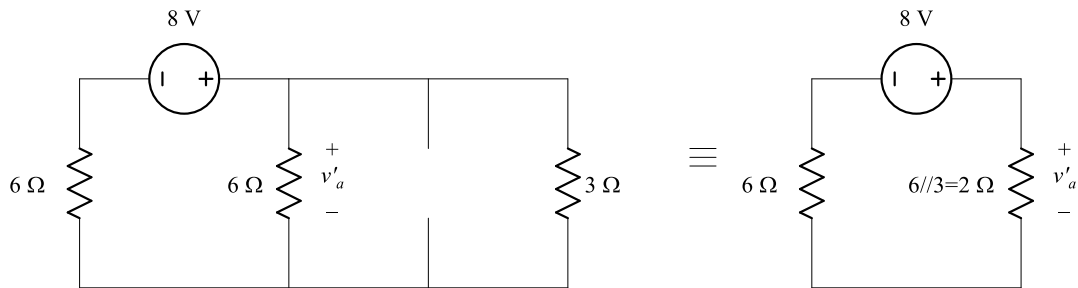
8 V voltage source is active: (Replace the current source with open circuit)



Using voltage division principle:

$$v'_a = 8 \times \frac{2}{8} = 2 \text{ V}$$

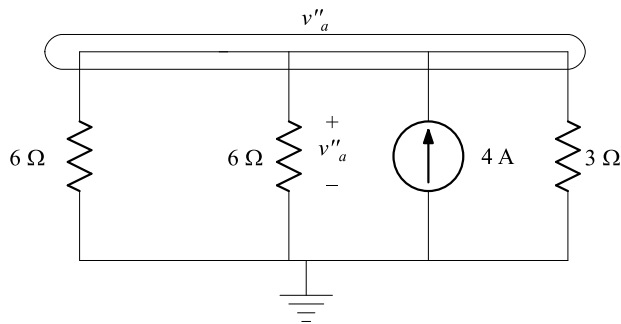4 A Current Source is active: (Replace the voltage source with short circuit)



KCL at  $v''_a$ :

$$\frac{v''_a}{6} + \frac{v''_a}{6} + \frac{v''_a}{3} = 4$$

$$\frac{4}{6} v''_a = 4 \Rightarrow v''_a = 6 \text{ V}$$

$$v_a = v'_a + v''_a = 2 + 6 = 8 \text{ V}$$

**Problem 6**

Compute the value of  $R$  that results in **maximum power transfer** in the circuit of Fig.P6. Find the **maximum power**.


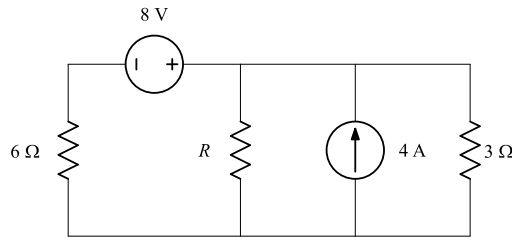


Figure P6


When the value of  $R = R_{TH}$  it will absorb maximum power. Maximum power is

$$P_{\max} = \frac{V_{TH}^2}{4R_{TH}}$$

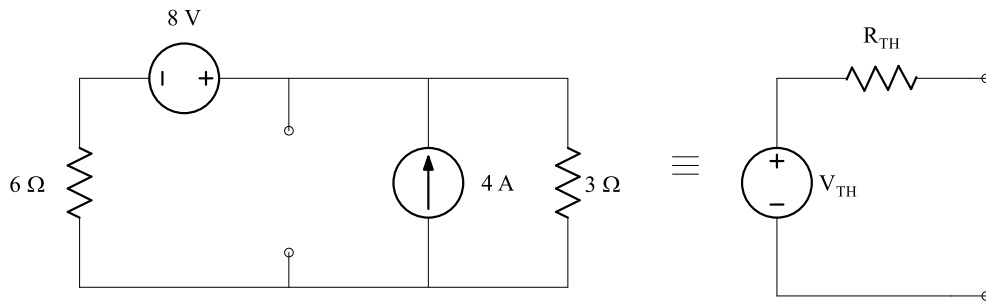In order to find the value of  $R$  and  $P_{\max}$  we need to find the Thevenin Equivalent of the circuit seen by  $R$ .




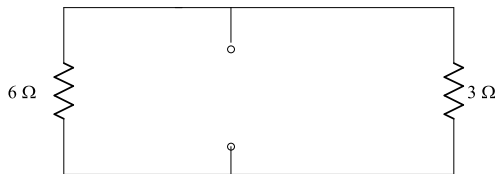In order to find  $R_{TH}$  set all independent source values to 0.



$$R_{TH} = 6 / / 3 = 2 \Omega$$

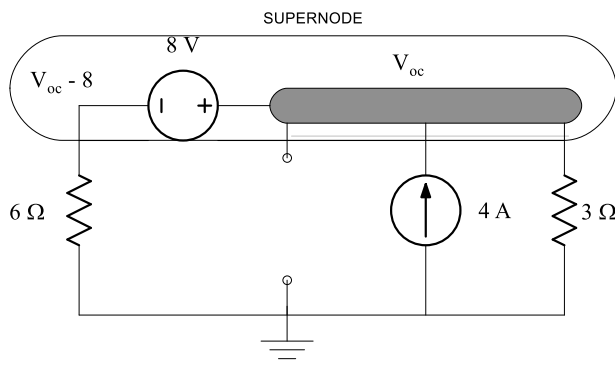In order to find  $V_{TH}$  we need to find open circuit voltage  $V_{oc}$  between the terminals.



KCL at  $V_{oc}$  :

$$\frac{V_{oc} - 8}{6} + \frac{V_{oc}}{3} = 4 \quad \text{Multiply both sides by 6:}$$

$$V_{oc} - 8 + 2V_{oc} = 24$$

$$3V_{oc} = 32 \Rightarrow V_{oc} = \frac{32}{3} \text{ V}$$

$$\therefore P_{\max} = \frac{\left(\frac{32}{3}\right)^2}{4 \times 2} = 14.22 \text{ W}$$

**Problem 7**

Determine the output voltage in the op amp circuit of Fig. P7.

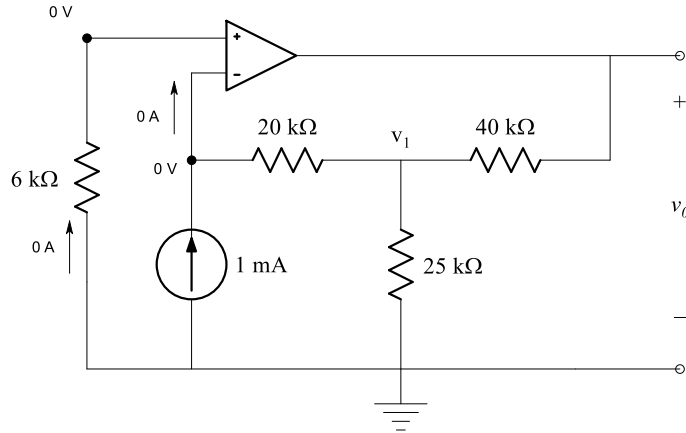


Figure P7

KCL at inverting input terminal:

$$1m + \frac{v_1}{20k} = 0 \Rightarrow \boxed{v_1 = -20 \text{ V}}$$

KCL at  $v_1$ :

$$\frac{v_1}{20k} + \frac{v_1}{25k} + \frac{v_1 - v_0}{40k} = 0 \text{ Multiply both sides by } 200k$$

$$10v_1 + 8v_1 + 5v_1 - 5v_0 = 0$$

$$v_0 = \frac{23}{5}v_1 = -\frac{23}{5} \times 20 = -92 \text{ V}$$