



Eastern Mediterranean University

"For Your International Career"

Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

INFE221 – Electrical Circuits

**Midterm Exam
Fall 2016-17**

16 November 2016
Duration: 90 minutes

Instructor: M. K. Uygurođlu

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO.	

Problem		Points
1		20
2		60
3		20
TOTAL		100

Problem 1

A current source and a voltage source are connected in series with a resistor as shown in Figure P1. Suppose that $V_s = 10\text{ V}$, $I_s = 2\text{ A}$, and $R = 5\ \Omega$.

- Calculate the voltage v across the resistor and the power absorbed by the resistor.
- Calculate the voltage v_1 across the current source and the power supplied by the sources.
- Change the voltage source voltage to $V_s = 5\text{ V}$ and recalculate the voltage, v , across the resistor and the power absorbed by the resistor.

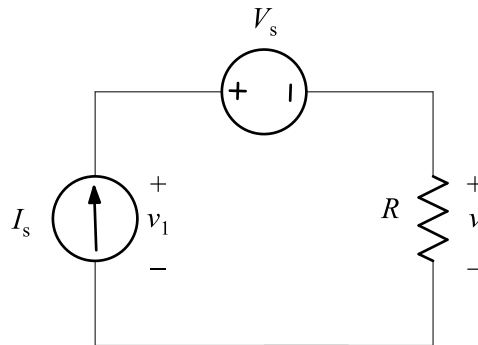


Figure P1

(a)

$$v = I_s R = 2 \times 5 = 10\text{ V}$$

$$P_{5\Omega} = I_s v = 2 \times 10 = 20\text{ W}$$

(b) KVL around the loop:

$$-v_1 + V_s + v = 0$$

$$v_1 = V_s + v = 10 + 10 = 20\text{ V}$$

$$P_{I_s} = -2 \times 20 = -40\text{ W absorbs} \Rightarrow 40\text{ W supplies}$$

$$P_{V_s} = I_s V_s = 2 \times 10 = 20\text{ W absorbs} \Rightarrow -20\text{ W supplies}$$

(c)

$$v = I_s R = 2 \times 5 = 10\text{ V}$$

$$P_{5\Omega} = I_s v = 2 \times 10 = 20\text{ W}$$

Problem 2

The circuit shown in Figure P2 has two inputs, v_s and i_s , and one output v_o . The output is related to the inputs by the equation

$$v_o = ai_s + bv_s$$

where a and b are constants to be determined. Determine the values a and b by

- (a) writing and solving mesh equations (20 pts.)
- (b) writing and solving node equations. (20 pts.)
- (c) using superposition. (20 pts.)


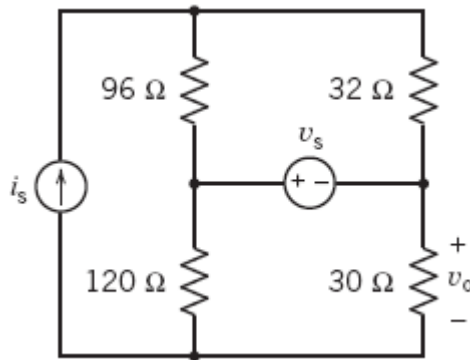


Figure P2

(a)

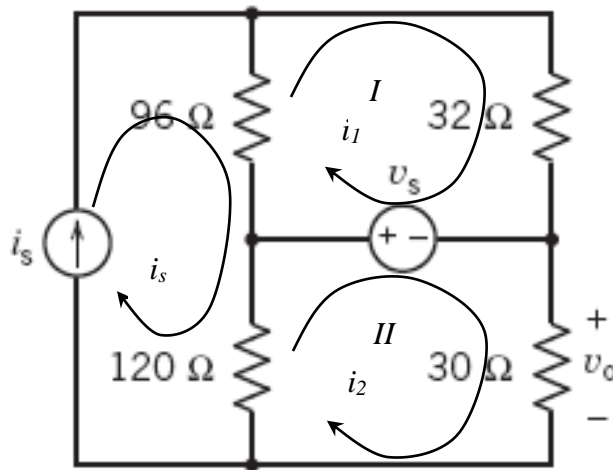

Since there is no resistor between mesh I and II, only one mesh equation is sufficient to find v_0 .

$$v_o = 30i_2$$

KVL around mesh II:

$$120(i_2 - i_s) + v_s + 30i_2 = 0$$


$$150i_2 = 120i_s - v_s$$

$$i_2 = \frac{120}{150}i_s - \frac{1}{150}v_s$$

$$v_o = 30i_2 = 24i_s - 0.2v_s$$

$$\therefore \boxed{a = 24, b = -0.2}$$

(b) Nodal Analysis

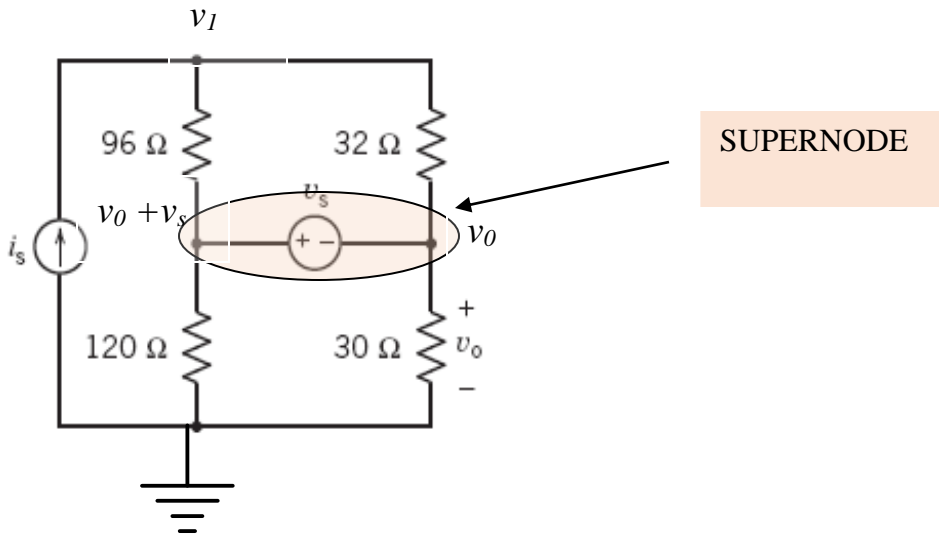

KCL at v_1 :

$$\frac{v_1 - v_0 - v_s}{96} + \frac{v_1 - v_0}{32} = i_s$$

Multiply both sides by 96 yields:

$$v_1 - v_0 - v_s + 3v_1 - 3v_0 = 96i_s$$

$$4v_1 - 4v_0 = 96i_s + v_s \dots\dots\dots(1)$$

KCL at the SUPERNODE:

$$\frac{v_0 + v_s}{120} + \frac{v_0 + v_s - v_1}{96} + \frac{v_0}{30} + \frac{v_0 - v_1}{32} = 0$$

Multiply both sides by 480 yields:

$$4v_0 + 4v_s + 5v_0 + 5v_s - 5v_1 + 16v_0 + 15v_0 - 15v_1 = 0$$

$$40v_0 - 20v_1 = -9v_s \dots\dots\dots(2)$$


Multiply Eq.(1) by 5 and add to Eq. (2) gives:

$$20v_0 = 480i_s - 4v_s$$

$$v_0 = 24i_s - 0.2v_s$$

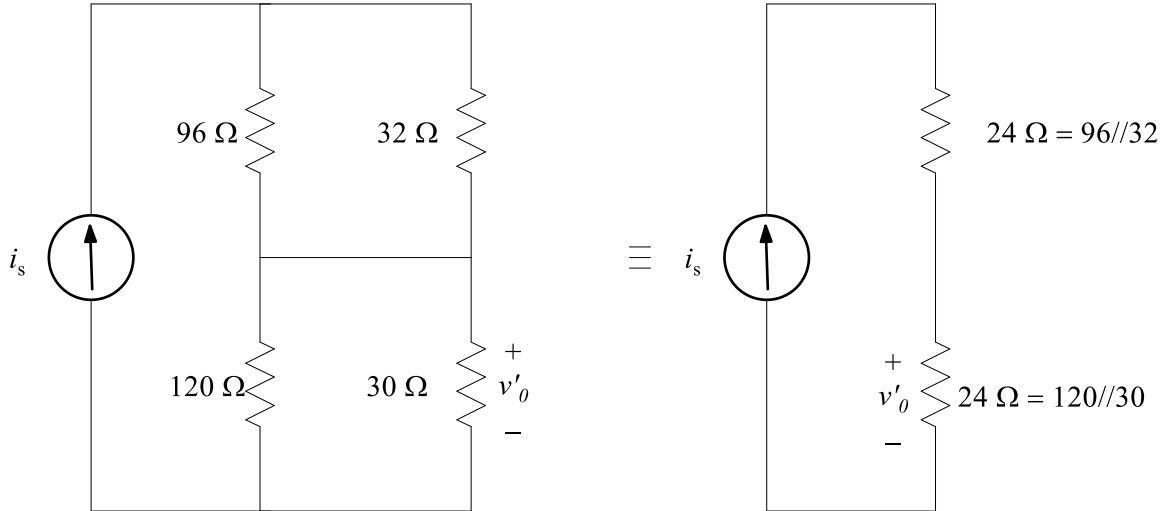
c) SUPERPOSITION

In order to find the contribution of i_s , set the voltage source value to zero. (**Replace the voltage source with short circuit**)



$$v'_0 = 24i_s$$

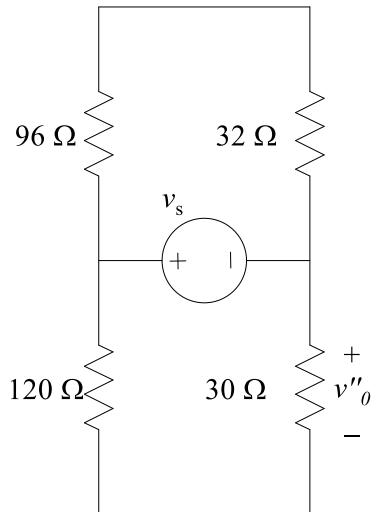In order to find the contribution of v_s , set the current source value to zero. (**Replace the current source with open circuit**)



Using voltage division principle:

$$v''_0 = -v_s \frac{30}{30+120} = -0.2v_s$$

Since

$$v_0 = v'_0 + v''_0$$

then

$$v_0 = 24i_s - 0.2v_s$$

Problem 3

Find the Thévenin equivalent circuit for the circuit shown in Figure P3.


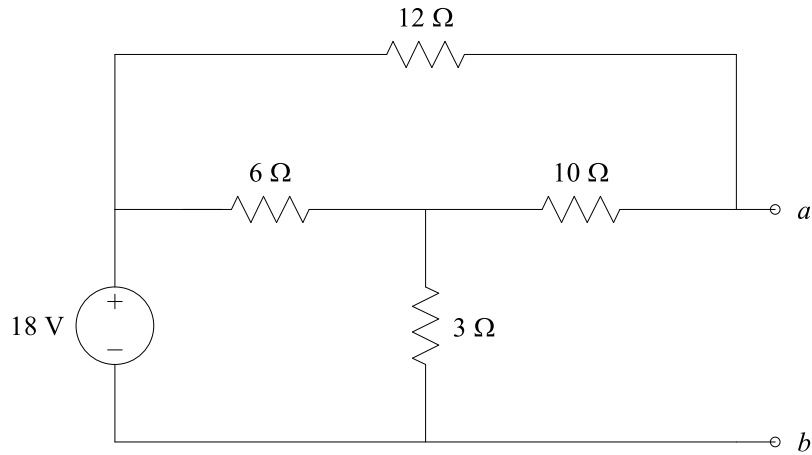


Figure P3

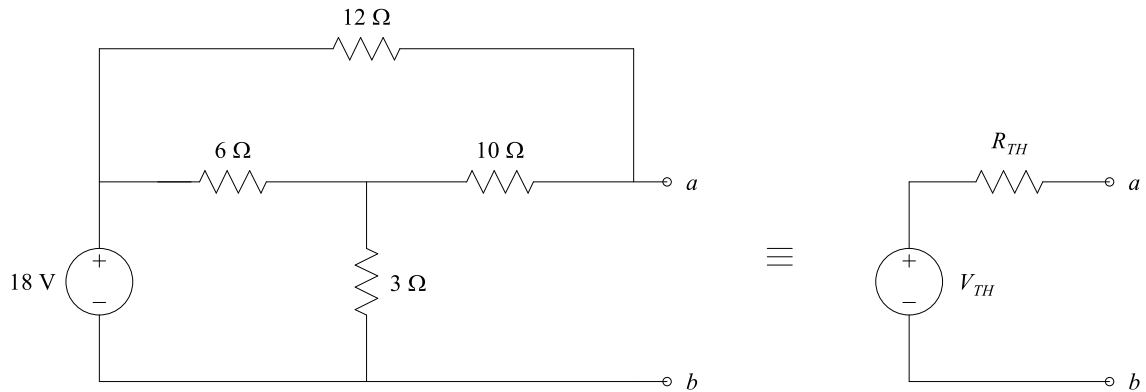


In order to find R_{TH} set all independent source values to zero. (Replace current sources with open circuits and voltage sources with short circuits.)

INFE221 Electric Circuits – Midterm Exam


$$30v_{oc} = 360$$
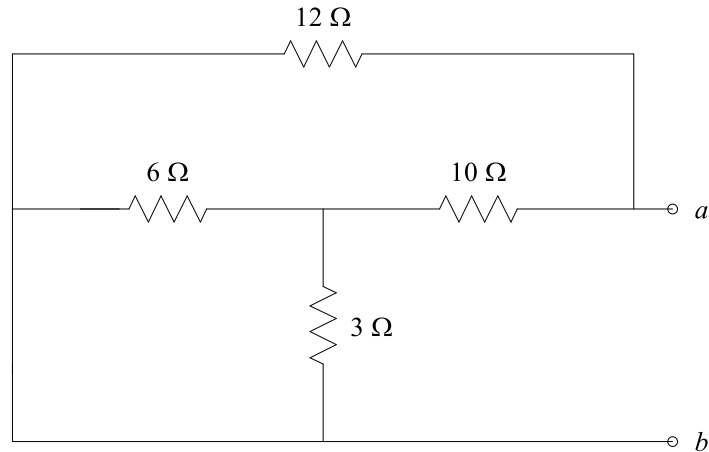
$$v_{oc} = \frac{360}{30} = 12 \text{ V}$$



$$R_{TH} = (6 // 3 + 10) // 12 = \left(\frac{6 \times 3}{6 + 3} + 10 \right) // 12 = 12 // 12 = \frac{12 \times 12}{12 + 12} = 6 \Omega$$

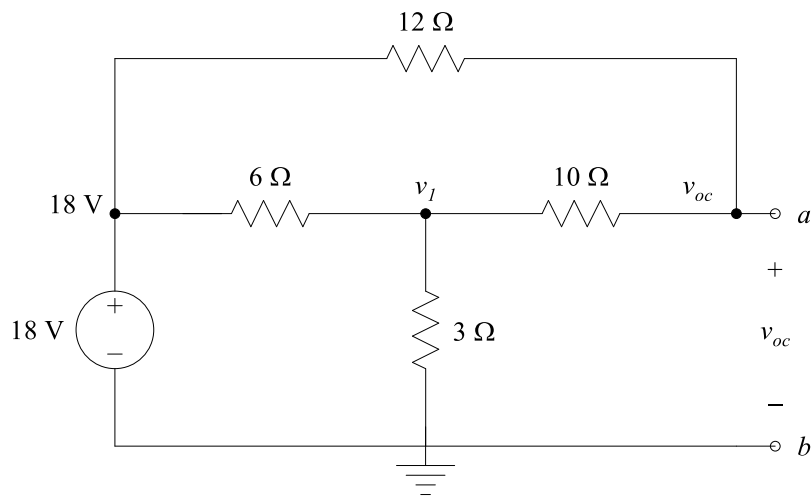In order to find V_{TH} , we will find the open circuit voltage v_{oc} between the terminals *a* and *b*.



KCL at v_{oc}

$$\frac{v_{oc} - v_1}{10} + \frac{v_{oc} - 18}{12} = 0$$

Multiply both sides by 60 yields:

$$6v_{oc} - 6v_1 + 5v_{oc} - 90 = 0$$

$$11v_{oc} - 6v_1 = 90 \dots \dots \dots (1)$$

KCL at v_1

$$\frac{v_1 - 18}{6} + \frac{v_1}{3} + \frac{v_1 - v_{oc}}{10} = 0$$

Multiply both sides by 30 yields:

$$5v_1 - 90 + 10v_1 + 3v_1 - 3v_{oc} = 0$$

$$-3v_{oc} + 18v_1 = 90 \dots \dots \dots (2)$$

Multiply Eq. (1) by 3 and add to Eq. (2) gives:

$$30v_{oc} = 360$$

$$\boxed{v_{oc} = 12 \text{ V} = V_{TH}}$$