



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

Eeng223 Circuit Theory I

**Midterm Exam
Fall 2019-20**

18 November 2019
Duration: 100 minutes

Instructor: M. K. Uyguroğlu

STUDENT'S	
NUMBER	
NAME	SOLUTIONS
SURNAME	

Problem		Points
1		15
2		10
3		15
4		60
TOTAL		100

Problem 1

For the circuit shown in Fig.P1, Calculate the power absorbed or supplied by each element and using conservation of power determine V_s .

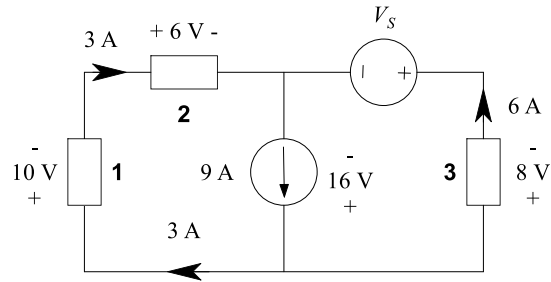


Figure P 1

$$P_1 = 10 \times 3 = 30 \text{ W absorbs}$$

$$P_2 = 6 \times 3 = 18 \text{ W absorbs}$$

$$P_{9A} = -9 \times 16 = -144 \text{ W} \Rightarrow 144 \text{ W Supplies}$$

$$P_{V_s} = V_s \times 6$$

$$P_3 = 8 \times 6 = 48 \text{ W absorbs}$$

$$\sum P_i = 0 = 30 + 18 - 144 + 6V_s + 48$$

$$6V_s = 144 - 30 - 18 - 48 = 48 \text{ W absorbs}$$

$$\Rightarrow \boxed{V_s = \frac{48}{6} = 8 \text{ V}}$$

Problem 2

Find R_{AB} in the circuit in Fig.P2.

12Ω and 6Ω are in parallel. $\frac{12 \times 6}{12 + 6} = 4\Omega$

4Ω and 2Ω are in series $4 + 2 = 6\Omega$


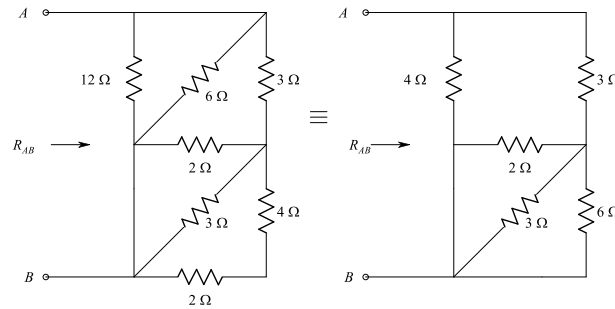


Figure P 2

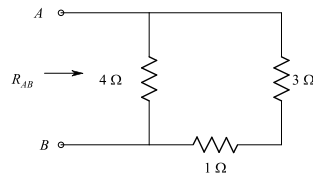6Ω , 3Ω , and 2Ω are in parallel $\frac{1}{R} = \frac{1}{2} + \frac{1}{3} + \frac{1}{6} = 1 \Rightarrow R = 1\Omega$



$$R_{AB} = 4 // (1 + 3) = 2\Omega$$

Problem 3

The 3-A current source in Fig. P3 is absorbing 12 W. Determine R .

$$P=VI$$

$$V=P/I=12/3=4 \text{ V}$$

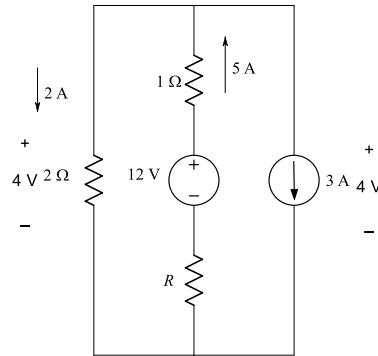


Figure P 3

KVL around the right mesh:

$$5(1+R) - 12 + 4 = 0$$

$$5R = 3$$

$$R = \frac{3}{5} = 0.6 \Omega$$

Problem 4

Find V_0 in the circuit in Fig. P4 using

- a) Nodal analysis. (15 pts.)
- b) Mesh analysis. (20 pts.)
- c) Superposition principle. (25 pts.)


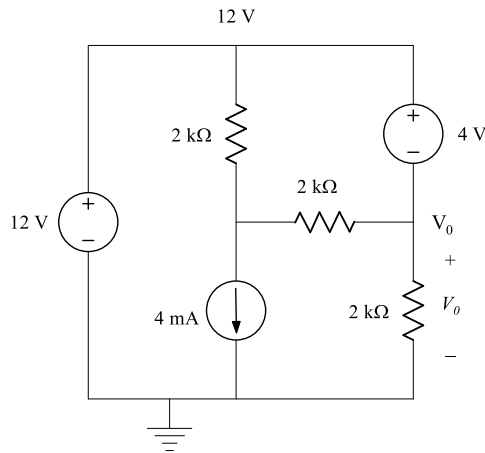


Figure P 4

$$12 - V_0 = 4 \Rightarrow \boxed{V_0 = 8 \text{ V}}$$

MESH ANALYSIS

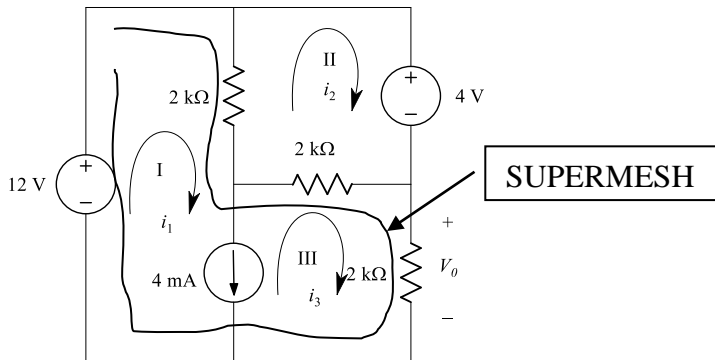

$$i_1 - i_3 = 4mA$$

$$i_1 = i_3 + 4m$$

$$V_0 = 2k \times i_3$$

KVL around mesh II:

$$2k(i_2 - i_3 - 4m) + 4 + 2k(i_2 - i_3) = 0$$

$$4ki_2 - 4ki_3 = 4 \dots (1)$$

KVL around the supermesh:

$$-12 + 2k(4m + i_3 - i_2) + 2k(i_3 - i_2) + 2ki_3 = 0$$

$$-4ki_2 + 6ki_3 = 4 \dots (2)$$

Addition of Eqns. (1) and (2) gives:


$$2ki_3 = 8$$

$$i_3 = 4mA$$

$$\therefore V_0 = 8V$$

SUPERPOSITION:

12 V is active

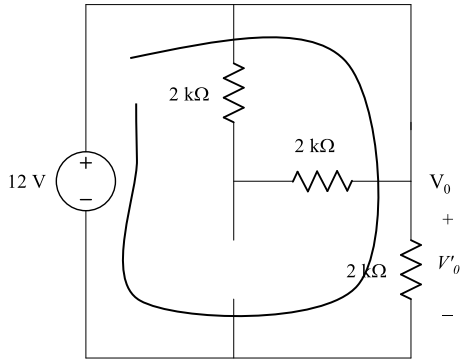


KVL around the loop gives:

$$-12 + V'_0 = 0$$

$$V'_0 = 12 \text{ V}$$

4 V is active

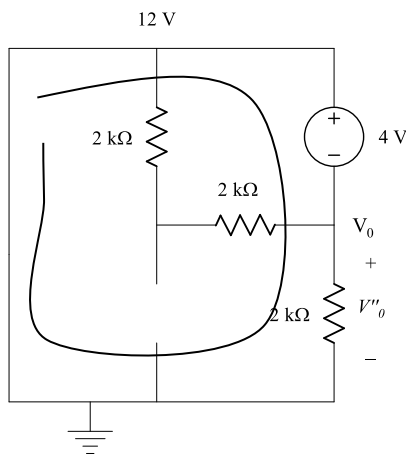


KVL around the loop gives:

$$-V''_0 - 4 = 0$$

$$V''_0 = -4 \text{ V}$$

4mA is active:

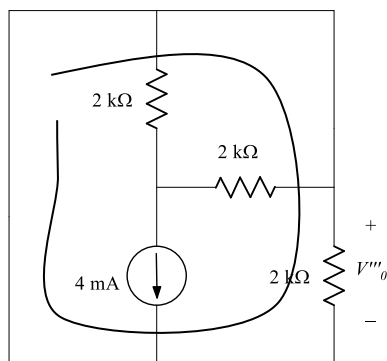

KVL around the loop gives:

$$V'''_0 = 0$$

$$\therefore V_0 = V'_0 + V''_0 + V'''_0 = 12 - 4 + 0 = 8 \text{ V}$$