



## Faculty of Engineering

### DEPARTMENT of ELECTRICAL AND ELECTRONIC ENGINEERING

#### EENG (INFE)115 Introduction to Logic Design

#### Instructors:

**M. K. Uygurođlu**  
**G. Yemiřciođlu**

*Final EXAMINATION*

January 05, 2017

*Duration : 120 minutes*

Number of Questions: 4

*Good Luck*

STUDENT'S	
NUMBER	
NAME	SOLUTIONS
SURNAME	
GROUP NO	

Question		Points
1		30
2		30
3		30
4		30
<i>TOTAL</i>		<b>120</b>

#### **Read the following instructions carefully:**


1. **Calculators** are not allowed.
2. Switch off **mobile phones** and **do not borrow** any stationery from your friends.
3. In your solutions, **show all details** you claim credit for.

### Question 1

Design a combinational circuit that accepts a **three** bit number and generates an **output** binary number equal to the **square of the input**.

Inputs			Outputs						
x	y	z	F1	F2	F3	F4	F5	F6	
0	0	0	0	0	0	0	0	0	
0	0	1	0	0	0	0	0	1	
0	1	0	0	0	0	1	0	0	
0	1	1	0	0	1	0	0	1	
1	0	0	0	1	0	0	0	0	
1	0	1	0	1	1	0	0	1	
1	1	0	1	0	0	1	0	0	
1	1	1	1	1	0	0	0	1	

$F6=z$   
 $F5=0$   
 $F4=x'yz'+xyz'=yz'$   
 $F3=x'yz+xy'z=(x\oplus y)z$   
 $F2=xy'+xz$   
 $F1=xy$

 


**Question 2**

Implement the following Boolean function with a  $8 \times 1$  **multiplexer**, a **2-to-4-line decoder** and two **2-input OR** gates. Note that the complement inputs are not available.

$$F(A, B, C, D, E) = \sum(0, 7, 10, 13, 16, 17, 18, 19, 21, 22, 28, 30)$$


S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Inputs		Output	
A	B	C	D	E	F	
0	0	0	0	0	1	I <sub>0</sub> = D'E'
0	0	0	0	1	0	
0	0	0	1	0	0	
0	0	0	1	1	0	
0	0	1	0	0	0	I <sub>1</sub> = DE
0	0	1	0	1	0	
0	0	1	1	0	0	
0	0	1	1	1	1	
0	1	0	0	0	0	I <sub>2</sub> = DE'
0	1	0	0	1	0	
0	1	0	1	0	1	
0	1	0	1	1	0	
0	1	1	0	0	0	I <sub>3</sub> = D'E
0	1	1	0	1	1	
0	1	1	1	0	0	
0	1	1	1	1	0	
1	0	0	0	0	1	I <sub>4</sub> = 1
1	0	0	0	1	1	
1	0	0	1	0	1	
1	0	0	1	1	1	
1	0	1	0	0	0	I <sub>5</sub> = D'E+DE'
1	0	1	0	1	1	
1	0	1	1	0	1	
1	0	1	1	1	0	
1	1	0	0	0	0	I <sub>6</sub> = 0
1	1	0	0	1	0	
1	1	0	1	0	0	
1	1	0	1	1	0	
1	1	1	0	0	1	I <sub>7</sub> = C'D'+CD'
1	1	1	0	1	0	
1	1	1	1	0	1	
1	1	1	1	1	0	

 
 
### Question 3

Mod-4 counter is a sequential circuit that has two flip-flops A and B and one input x. It consists of a combinatorial logic connected to the D flip-flops, as shown in Figure below. Analyze the circuit:


- Derive the next state and output equations.
- Derive the state table of the sequential circuit.
- Draw the corresponding state diagram.



$$\underbrace{A(t+1)}_{\text{next state}} = D_A = \underbrace{A(t)}_{\text{present state}} \oplus x$$

$$B(t+1) = D_B = (B(t)x') \oplus (A'(t)B(t)x) \oplus (A(t)B'(t)x)$$

Present State		Input	Next State	
A	B	x	A	B
0	0	0	0	0
0	0	1	1	0
0	1	0	0	1
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	1
1	1	1	0	0

 


### Question 4

The state diagram of a sequence detector which allows overlap is shown below. A sequence detector accepts as input a string of bits: either 0 or 1. Its output goes to 1 when a target sequence has been detected. In a sequence detector that allows overlap, the final bits of one sequence can be the start of another sequence. Using the state diagram given below and an input sequence **10110**:

- Assign binary values to the states and derive the state table.
- Derive the **simplified** state equations.
- Use **JK flip-flops** and design a synchronous sequence detector circuit.
- Is this a **Mealy** or **Moore** model?

 Treat unused states as don't care conditions.



State	Assignment
A	000
B	001
C	010
D	011
E	100

Present State			Input	Next State			Output	Flip-flops Inputs					
A	B	C	x	A	B	C	y	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>
0	0	0	0	0	0	0	0	0	X	0	X	0	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X
0	0	1	0	0	1	0	0	0	X	1	X	X	1
0	0	1	1	0	0	1	0	0	X	0	X	X	0
0	1	0	0	0	0	0	0	0	X	X	1	0	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X
0	1	1	0	0	1	0	0	0	X	X	0	X	1
0	1	1	1	1	0	0	0	1	X	X	1	X	1
1	0	0	0	0	0	0	1	X	1	0	X	0	X
1	0	0	1	0	0	1	0	X	1	0	X	1	X
1	0	1	0				X	X	X	X	X	X	X
1	0	1	1				X	X	X	X	X	X	X
1	1	0	0				X	X	X	X	X	X	X
1	1	0	1				X	X	X	X	X	X	X
1	1	1	0				X	X	X	X	X	X	X
1	1	1	1				X	X	X	X	X	X	X

		C <sub>x</sub>			
		00	01	11	10
A\B	00				
	01			1	
	11	x	x	x	x
	10	x	x	x	x

$J_A = BCx$

		C <sub>x</sub>			
		00	01	11	10
A\B	00	x	x	x	x
	01	x	x	x	x
	11	x	x	x	x
	10	1	1	x	x

$K_A = 1$

		C <sub>x</sub>			
		00	01	11	10
A\B	00				1
	01	x	x	x	x
	11	x	x	x	x
	10	0	0	x	x

$J_B = Cx'$

		Cx			
		00	01	11	10
AB	00	x	x	x	x
	01	1	0	1	0
	11	x	x	x	x
	10	x	x	x	x

$$K_B = C'x' + Cx$$

		Cx			
		00	01	11	10
AB	00		1	x	x
	01		1	x	x
	11	x	x	x	x
	10	0	1	x	x

$$J_C = x$$

		Cx			
		00	01	11	10
AB	00	x	x		1
	01	x	x	1	1
	11	x	x	x	x
	10	x	x	x	x

$$K_C = B + x'$$

		Cx			
		00	01	11	10
AB	00				1
	01			1	
	11	x	x	x	x
	10	1	0	x	x

$$Y = Ax'$$



