



## Faculty of Engineering

### DEPARTMENT of ELECTRICAL AND ELECTRONIC ENGINEERING

#### EENG (INFE)115 Introduction to Logic Design

#### Instructors:

**M. K. Uygurođlu**  
**G. Yemiřciođlu**

*Midterm EXAMINATION*

November 17, 2016

*Duration : 90 minutes*

Number of Questions: 4

*Good Luck*

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

Question		Points
1		25
2		25
3		25
4		25
<i>TOTAL</i>		100

#### **Read the following instructions carefully:**

1. **Calculators** are not allowed.
2. Switch off **mobile phones** and **do not borrow** any stationery from your friends.
3. In your solutions, **show all details** you claim credit for.

**Question 1**

a) Convert the binary number 11011.0101 to decimal. Show your steps. Show only the first two digits after the decimal point. **(3 pts.)**

$$1 \times 2^4 + 1 \times 2^3 + 1 \times 2^1 + 1 + 1 \times 2^{-2} + 1 \times 2^{-4} = 16 + 8 + 2 + 1 + \frac{1}{4} + \frac{1}{16}$$

$$= 27.31$$

b) Convert the following decimal numbers to binary: (Show your steps.) **(8 pts.)**

i. 37

	Remainder
37/2 = 18	1
18/2 = 9	0
9/2 = 4	1
4/2 = 2	0
2/2 = 1	0
1/2 = 0	1

$\uparrow$

$$(37)_{10} = (100101)_2$$

ii. 0.9

0.9 × 2 = 1.8	1
0.8 × 2 = 1.6	1
0.6 × 2 = 1.2	1
0.2 × 2 = 0.4	0
0.4 × 2 = 0.8	0
0.8 × 2 = 1.6	1

·  
·

$$(0.9)_{10} = (0.\overline{1100})_2 \quad (1100 \text{ is repeated})$$

c) Convert (10100101010.11)<sub>2</sub> to hexadecimal and to octal. **(4 pts.)**

$$\left( \begin{matrix} 010100101010.1100 \\ \phantom{01} \phantom{01} \phantom{01} \phantom{01} \\ \phantom{01} \phantom{01} \phantom{01} \phantom{01} \\ \phantom{01} \phantom{01} \phantom{01} \phantom{01} \end{matrix} \right) = (52A.C)_{16}$$

$$\left( \begin{matrix} 010100101010.110 \\ \phantom{01} \phantom{01} \phantom{01} \phantom{01} \\ \phantom{01} \phantom{01} \phantom{01} \phantom{01} \\ \phantom{01} \phantom{01} \phantom{01} \phantom{01} \end{matrix} \right) = (2452.6)_8$$

d) Convert +20 and +45 to binary, using the signed-2's complement representation and **enough digit to accommodate** the numbers. Then perform the binary equivalent of  $(-20) - (+45)$ . (10 pts.)

$$(20)_{10} = (10100)_2 \Rightarrow (+20) = (00010100) \quad (-20) = (11101100)$$

$$(45)_{10} = (101101)_2 \Rightarrow (+45) = (00101101) \quad (-45) = (11010011)$$

$$(65)_{10} = (1000001)_2 \Rightarrow (+65) = (01000001) \text{ 8bits are required.}$$

$$(-20) - (+45) = (-20) + (-45)$$

$$\begin{array}{r} 11101100 \\ + 11010011 \\ \hline \end{array}$$

$$\cancel{1}1011111 \Rightarrow -(01000001) = (-65)$$

**Question 2**

- a) Simplify the Boolean function  $F(x, y, z) = \prod(1,3,6,7)$  in sum of products using **algebraic manipulation** and implement it
- with AND and inverter gates
  - with OR and inverter gates



**(15 pts.)**

$$F(x, y, z) = \prod(1,3,6,7) = \sum(0,2,4,5)$$

$$F(x, y, z) = x'y'z' + x'yz' + xy'z' + xy'z = x'z' \underbrace{(y + y')} + xy' \underbrace{(z + z')} = x'z' + xy'$$

$F(x, y, z) = ((x'z')'(xy'))'$  implementation with AND and inverters

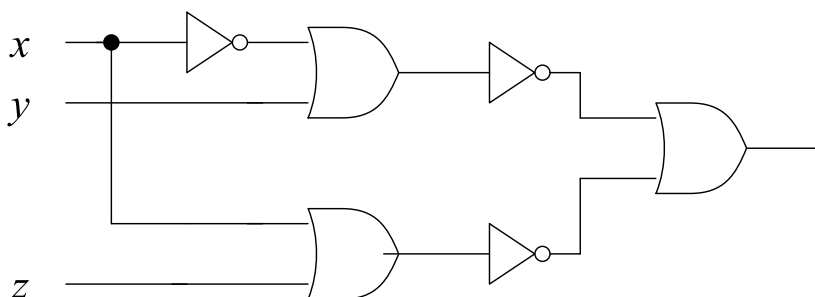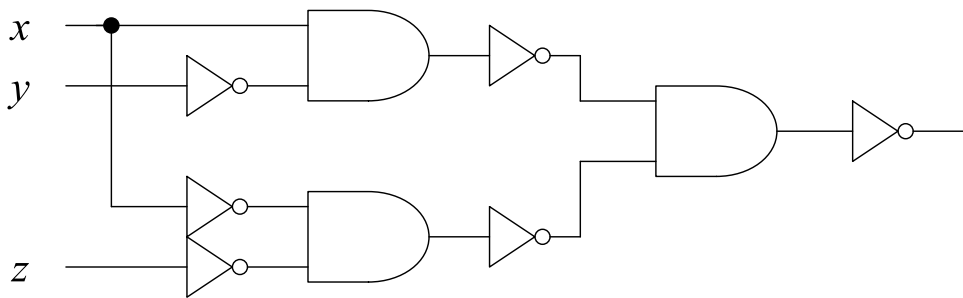$F(x, y, z) = (x+z)' + (x'+y)'$  implementation with OR and inverters.



- b) Express the following function as a sum of minterms and as a product of maxterms (10 pts.)

$$F(a,b,c,d) = a'(b'+d) + acd' = a'b' + a'd + acd'$$

<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>a'b'</i>	<i>a'd</i>	<i>acd'</i>	<i>F</i>	min term
0	0	0	0	1	0	0	1	0
0	0	0	1	1	1	0	1	1
0	0	1	0	1	0	0	1	2
0	0	1	1	1	1	0	1	3
0	1	0	0	0	0	0	0	4
0	1	0	1	0	1	0	1	5
0	1	1	0	0	0	0	0	6
0	1	1	1	0	1	0	1	7
1	0	0	0	0	0	0	0	8
1	0	0	1	0	0	0	0	9
1	0	1	0	0	0	1	1	10
1	0	1	1	0	0	0	0	11
1	1	0	0	0	0	0	0	12
1	1	0	1	0	0	0	0	13
1	1	1	0	0	0	1	1	14
1	1	1	1	0	0	0	0	15

$$F(a,b,c,d) = \sum(0,1,2,3,5,7,10,14)$$

$$F(a,b,c,d) = \prod(4,6,8,9,11,12,13,15)$$

**Question 3**

For a given Boolean function  $F(w, x, y, z) = \sum(1,4,5,6,12,14,15)$  which has the don't care conditions  $d(w, x, y, z) = \sum(3,7,11)$

- a) Determine the sum of products (SOP).
- b) Implement F with only NAND gates.
- c) Determine the product of sums (POS).
- d) Implement F with only NOR gates.



(25 pts.)

	$y'z'$	$y'z$	$yz$	$yz'$
$w'x'$	0	1	×	0
$w'x$	1	1	×	1
$wx$	1	0	1	1
$wx'$	0	0	×	0

$$F(w, x, y, z) = w'z + xy + xz'$$

$$F'(w, x, y, z) = x'z' + wy'z$$

$$F(w, x, y, z) = (x+z)(w' + y + z')$$

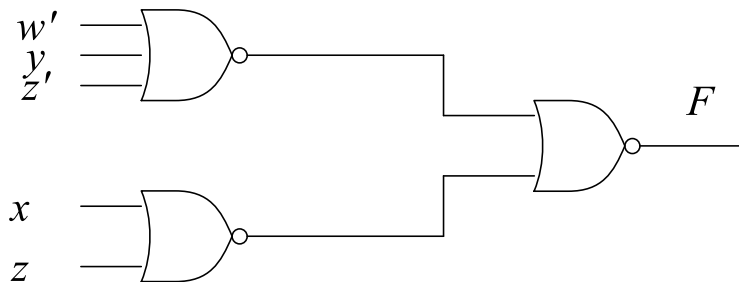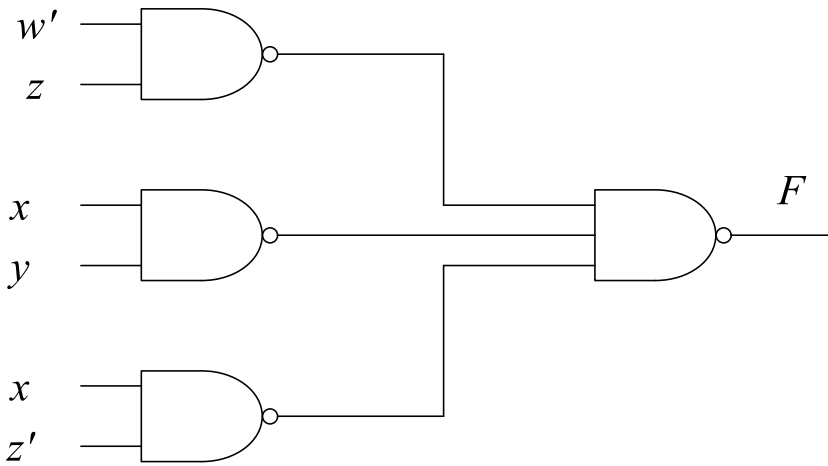

### Question 4

Implement the following Boolean function  $F'(x, y, z) = y' + x'z'$  using the two-level forms.

- Karnaugh map of  $F'$
- NAND-AND for sum of products (SOP)
- AND-NOR for sum of products (SOP)
- OR-NAND for product of sums (POS)
- NOR-OR for product of sums (POS)



(25 pts.)

a)

	$y'z'$	$y'z$	$yz$	$yz'$
$x'$	0	0	1	0
$x$	0	0	1	1

$$F'(x, y, z) = y' + x'z'$$

$$F(x, y, z) = (y' + x'z')'$$

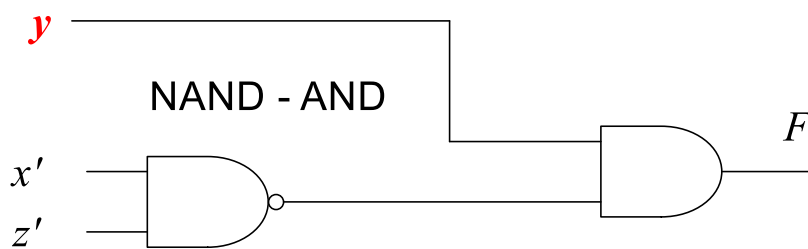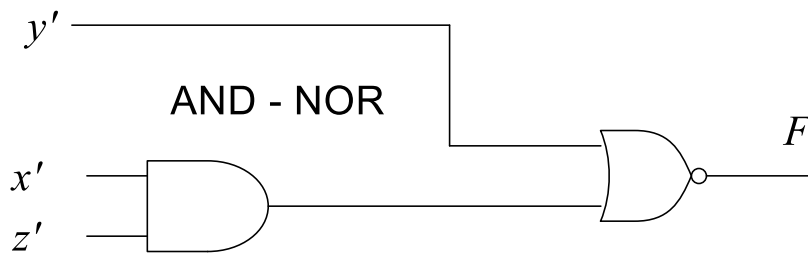

$$F(x, y, z) = yz + xy$$

$$F'(x, y, z) = (y' + z')(x' + y')$$

$$F(x, y, z) = ((y' + z')(x' + y'))'$$

