



Faculty of Engineering
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
EENG115/INFE115 Introduction to Logic Design
EENG211/INFE211 Digital Logic Design I

Fall 2012-13

Instructors:
M. K. Uygurođlu
H. Abou Rajab

Midterm EXAMINATION

Nov. 12, 2012

Duration: 100 minutes

Number of Problems: 5

Good Luck

STUDENT'S	
NUMBER	
NAME	
SURNAME	
GROUP NO	

Problem	Achieved	Maximum
1		20
2		20
3		20
4		20
5		20
TOTAL		100

Question 1 (20 points)

Convert decimal 53 and 34 to binary, using the signed 2's complement representation and enough digits to accommodate the numbers. Then perform the binary equivalent of $(+53) + (-34)$, $(-53) + (+34)$, and $(-53) + (-34)$.

	R		R	
53/2	1	34/2	0	53 110101
26/2	0	17/2	1	34 100010
13/2	1	8/2	0	87 1010111
6/2	0	4/2	0	
3/2	1	2/2	0	
1/2	1	1/2	1	
0		0		

Therefore for sign 2's complement representation of

$$+53=00110101 \quad -53=11001011$$

$$+34=00100010 \quad -34=11011110$$

$$(+53) + (-34)=00110101+11011110=100010011 \text{ most significant bit is discarded. (19)}$$

$$(-53) + (+34)=11001011+00100010=11101101 \text{ (signed 2's complement of -19)}$$

$$(-53) + (-34)=11001011+11011110=110101001 \text{ most significant bit is discarded. The rest signed}$$

2's complement of -87

Question 2 (20 points):

a) How many bit errors can be corrected by an odd parity code?

None

b) Express $(527)_{10}$ in (i) BCD, (ii) Excess-3 and (iii) 2421 codes

	5	2	7
BCD	0101	0010	0111

	5	2	7
Excess-3	1000	0101	1010

	5	2	7
2421	1011	0010	1101

c) Without simplification, write the expressions for F^D (dual) and F' (complement) corresponding to the Boolean function

$$F = A + 0.B'(C' + 1.D)$$

$$F^D = A.(1+B'+(C'(0+D)))$$

$$F' = A'.(1+B+(C(0+D)))$$

d) Minimize $F(A, B, C) = A' + ABC + A(B \oplus C) + AB'C'$ by algebraic manipulations

$$A' + ABC + A(B \oplus C) + AB'C' = A' + ABC + AB'C + ABC' + AB'C' = A' + AB(C + C') + AB'(C + C')$$

$$= A' + A(B + B') = A' + A = 1$$

e) Given

$$F_1(w, x, y, z) = \sum(0, 1, 3, 5, 9, 13) \text{ and}$$

$$F_2(w, x, y, z) = \sum(0, 3, 6, 14)$$

i. Express $G(w, x, y, z) = F_1.F_2$ in sum of minterms = $\sum(0, 3)$

ii. Express $H(w, x, y, z) = F_1 + F_2$ in product of maxterms = $\Pi(2, 4, 7, 8, 10, 11, 12, 15)$

Question 3 (20 points):

Given the Boolean function

$$F(A, B, C, D) = \sum (1, 3, 8, 11, 12, 14)$$

$$d(A, B, C, D) = \sum (0, 2, 6, 9, 10, 13, 15) \text{ don't care conditions}$$

- Simplify F in sum of products (SOP)
- Implement F with the minimum number of NAND gates
- Simplify F in product of sums (POS)
- Implement F with the minimum number of NOR gates


AB\CD	00	01	11	10
00	x	1	1	x
01				x
11	1	x	x	1
10	1	x	1	x

$$F = A + B'$$



$$F' = A'B$$

$$F = A + B'$$

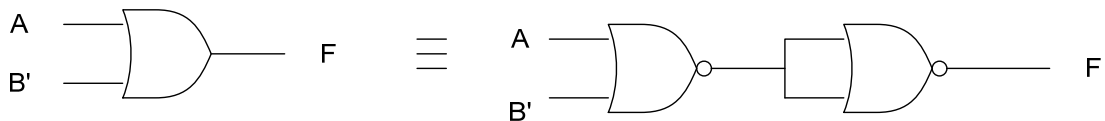

Question 4 (20 points):

Simplify and then implement the following Boolean function F using two-level forms of logic by using

- (a) OR-NAND,
- (b) AND-NOR.


$$F(A, B, C, D) = \prod(1, 3, 6, 9, 11, 12, 14) = \sum(0, 2, 4, 5, 7, 8, 10, 13, 15)$$

AB\CD	00	01	11	10
00	1	0	0	1
01	1	1	1	0
11	0	1	1	0
10	1	0	0	1

$$F = BD + B'D' + A'BC' \text{ or } BD + B'D' + A'C'D'$$


$$F' = (B' + D')(B + D)(A + B' + C) \text{ or } (B' + D')(B + D)(A + C + D)$$
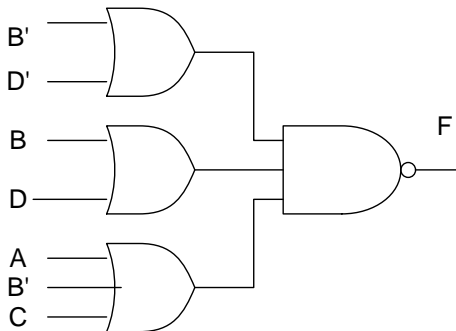
$$F = F' = ((B' + D')(B + D)(A + B' + C))' \text{ or } ((B' + D')(B + D)(A + C + D))'$$




$$F' = B'D + BCD' + ABD'$$

$$F = F' = (B'D + BCD' + ABD')'$$

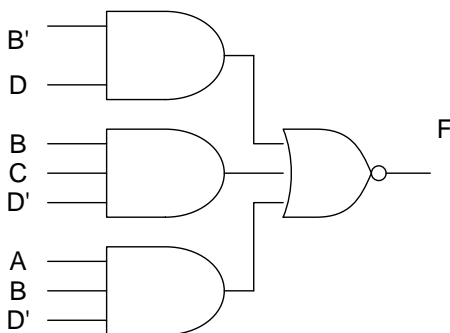

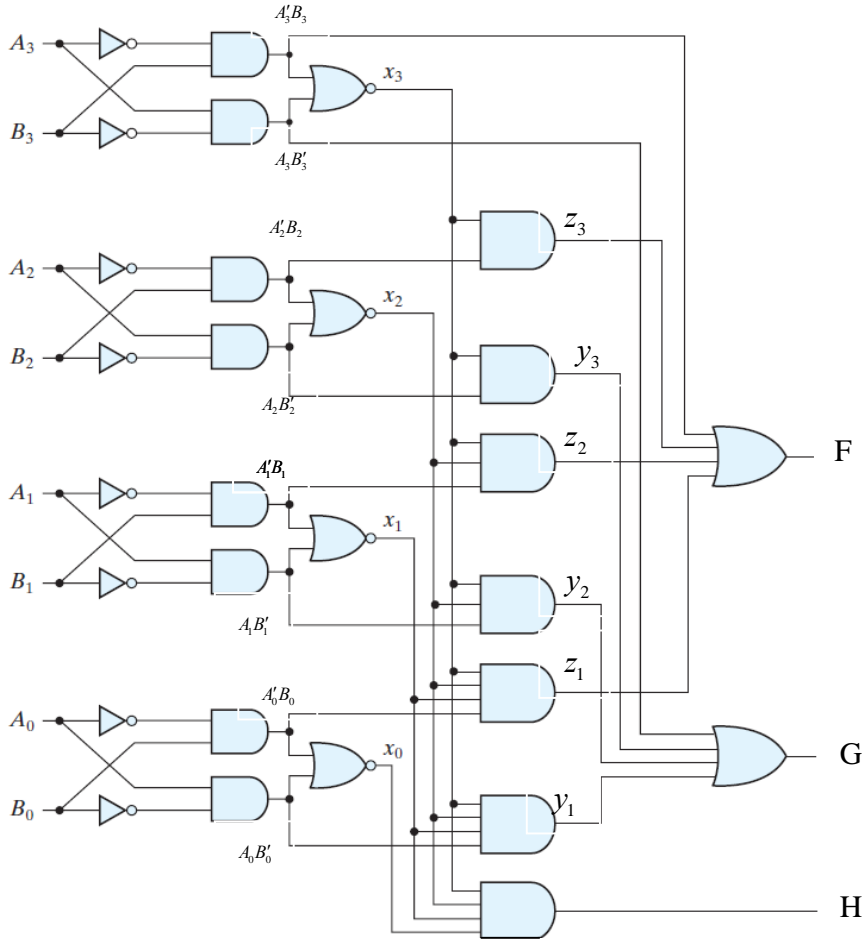Question 5 (20 points):

Obtain the simplified Boolean expressions for output variables F, G, and H in terms of input variables in the circuit shown below:



$$x_0 = (A'_0B_0 + A_0B'_0)' = A'_0B'_0 + A_0B_0$$

$$x_1 = (A'_1B_1 + A_1B'_1)' = A'_1B'_1 + A_1B_1$$

$$x_2 = (A'_2B_2 + A_2B'_2)' = A'_2B'_2 + A_2B_2$$

$$x_3 = (A'_3B_3 + A_3B'_3)' = A'_3B'_3 + A_3B_3$$

$$z_3 = x_3A'_2B_2$$

$$y_3 = x_3A_2B'_2$$

$$z_2 = x_3x_2A'_1B_1$$

$$y_2 = x_3x_2A_1B'_1$$

$$z_1 = x_3x_2x_1A'_0B_0$$

$$y_1 = x_3x_2x_1A_0B'_0$$

$$F = A'_3B_3 + z_3 + z_2 + z_1 = A'_3B_3 + x_3A'_2B_2 + x_3x_2A'_1B_1 + x_3x_2x_1A'_0B_0$$

$$G = A_3B'_3 + y_3 + y_2 + y_1 = A_3B'_3 + x_3A_2B'_2 + x_3x_2A_1B'_1 + x_3x_2x_1A_0B'_0$$

$$H = x_3x_2x_1x_0$$