



Faculty of Engineering

ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT

EENG115/INFE115 Introduction to Logic Design
EENG211/INFE211 - Digital Logic Design I

Fall 2009-10

Instructors:

M. K. Uyguroğlu – H. Demirel

Midterm EXAMINATION

Nov 24, 2009

Duration : 90 minutes

Number of Problems: 10

Good Luck

ST. NUMBER	
ST. NAME AND SURNAME	SOLUTIONS
ST. GROUP NO	

Problem	Score	Points
1		
2		
3		
4		
5		
6		
7		
8		
9		
10		
TOTAL		

Digital Logic Design I - Midterm Examination

5. Given the Boolean expression $F = x'y + xyz'$:
- Derive an algebraic expression for the complement F' . (**? pts.**)
 - Show that $F \cdot F' = 0$. (**? pts.**)
 - Show that $F + F' = 1$. (**? pts.**)

$$F' = (x+y')(x'+y'+z)$$

$$F \cdot F' = (x'y + xyz')(x+y')(x'+y'+z) = (x'y + xyz')(xy' + xz + x'y' + y' + y'z) = 0$$

$$F = x'y + xyz' + xy' + xz + x'y' + y' + y'z$$

$$F = x'(y+y') + y'(1+x+z) + x(yz'+z)$$

$$= x'y + x(y+z) = x'y + xy + xz = (x'+x)(x'+y) + y' + xz = 1 + x' + xz = 1$$

6. Simplify the following Boolean function, using 3-variable **Karnaugh** map:
 $F(x,y,z) = \sum(0,2,6,7)$ (**? pts.**)

x\yz	00	01	11	10
0	1			1
1			1	1

$$F = x'z' + xy$$

7. Simplify the following Boolean function, using 4-variable **Karnaugh** map:
 $F(x,y,z,w) = w'z + xz + x'y + wx'z$ (**? pts.**)

xy\zw	00	01	11	10
00			1	1
01	1	1	1	1
11			1	1
10			1	1

$$F = z + x'y$$

Digital Logic Design I - Midterm Examination

8. Simplify the following Boolean function F , together with the don't-care conditions d , and then express the simplified function in
- sum of products and (? pts.)
 - product of sums. (? pts.)

$$F(A,B,C,D) = \sum(1,3,5,7,9,15), d(A,B,C,D) = \sum(4,6,12,13)$$

AB\CD	00	01	11	10
00		1	1	
01	x	1	1	x
11	x	1	1	
10				

$$F = A'D + BD + C'D$$

$$F' = D' + AB'C$$

$$F = D(A' + B + C')$$

9. Given the Boolean function $F = xy'z + x'y'z + xyz$
- List the truth table (? pts.)
 - Draw the logic diagram of the original function using 2-input gates (? pts.)
 - Simplify the function
 - Draw the logic diagram of the simplified function (using 2-input gates) (? pts.)
 - Draw the logic diagram of the simplified function using only 2-input NAND gates. (? pts.)

$$x \quad y \quad z \quad xy'z + x'y'z + xyz$$

0 0 0 0

0 0 1 1

0 1 0 0

0 1 1 0


1 0 0 0

1 0 1 1

1 1 0 0


1 1 1 1

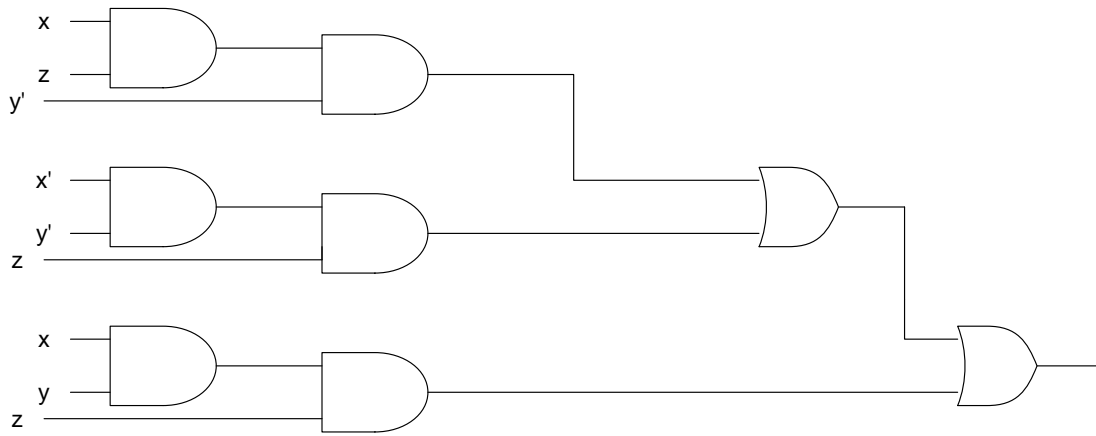Digital Logic Design I - Midterm Examination



x\yz	00	01	11	10
0	0	1	0	0
1	0	1	1	0

$F = y'z + xz$

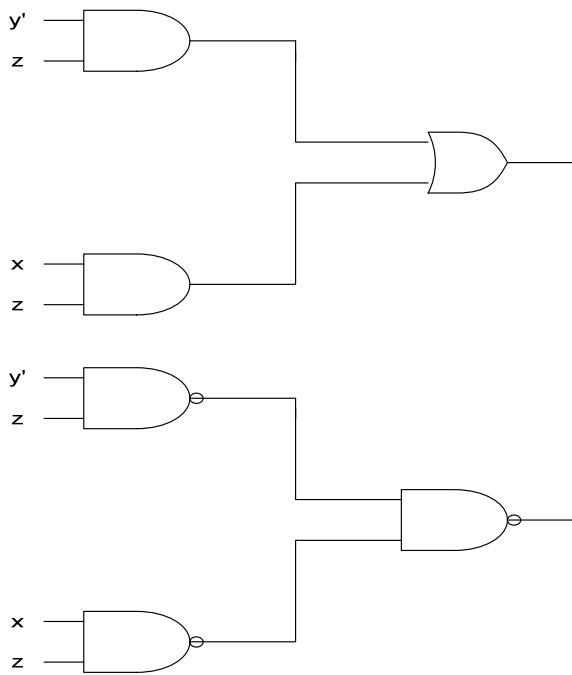

10. Implement the following Boolean function together with the don't-care conditions d , using no more than three NOR gates:

- a. $F(A,B,C,D) = \sum(0,1,9,11)$
- b. $d(A,B,C,D) = \sum(2,8,10,14,15)$

AB\CD	00	01	11	10
00	1	1	0	x
01	0	0	0	0
11	0	0	x	x
10	x	1	1	x

$$F = BC' + A'C$$

$$F = (B' + C)(A + C')$$

