



Faculty of Engineering
ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT
EENG115/INFE115 Introduction to Logic Design
EENG211/INFE211 Digital Logic Design I

Spring 2009-10

Instructors:
M. K. Uygurođlu
H. Demirel

Final EXAMINATION

June 08, 2010

Duration : 120 minutes

Number of Problems: 7

Good Luck

| STUDENT'S | |
|-----------|-----------|
| NUMBER | |
| NAME | SOLUTIONS |
| SURNAME | |
| GROUP NO | |

| Problem | Achieved | Maximum |
|--------------|----------|---------|
| 1 | | 10 |
| 2 | | 10 |
| 3 | | 10 |
| 4 | | 10 |
| 5 | | 20 |
| 6 | | 20 |
| 7 | | 20 |
| <i>TOTAL</i> | | 100 |

Question 1 (10 points)

A. Converting $(153)_{10}$ to base 8 yields which of the following results?

- (a) 107
- (b) 132
- (c) 701
- (d) 231
- (e) 153

B. Converting $(0111011.100)_2$ to base 16 yields which of the following results?

- (a) 73.8
- (b) 3C.4
- (c) 3B.8
- (d) 73.4
- (e) 3B.4

C. 10100 is the two's complement representation of:

- (a) -11
- (b) +12
- (c) -12
- (d) -20
- (e) +20

D. Simplification of the Boolean expression $AB + ABC + ABCD + ABCDE + ABCDEF$ yields which of the following results?

- (a) ABCDEF
- (b) AB
- (c) $AB + CD + EF$
- (d) $A + B + C + D + E + F$
- (e) $A + B(C+D(E+F))$

E. Given that $F = (A + B' + C)(D + E)$, which of the following represents the only correct expression for F' ?

- (a) $F' = A'BC' + D' + E'$
- (b) $F' = AB'C + DE$
- (c) $F' = (A' + B + C')(D' + E')$
- (d) $F' = A'BC' + D'E'$
- (e) $F' = (A + B' + C)(D' + E')$

Question 2 (10 points):

A. Identify the function which generates the K-map shown

- (a) $F(A,B,C) = \Sigma(1,3,4,7)$
- (b) $F(A,B,C) = \Sigma(1,3,5,6)$
- (c) $F(A,B,C) = \Sigma(3,4,5,6)$
- (d) $F(A,B,C) = \Pi(1,3,4,7)$
- (e) $F(A,B,C) = \Pi(1,3,5,6)$

| | | | | | |
|---|---|----|----|----|----|
| | | AB | | | |
| | | 00 | 01 | 11 | 10 |
| C | 0 | 0 | 0 | 1 | 0 |
| | 1 | 1 | 1 | 0 | 1 |

B. Identify the most simple expression from the K-map shown.

- (a) $F(A,B,C,D) = B'C + AD + CD$
- (b) $F(A,B,C,D) = BC' + BCD' + AC'D'$
- (c) $F(A,B,C,D) = BC' + BCD' + AB'C'D'$
- (d) $F(A,B,C,D) = AD + BCD' + CD$
- (e) $F(A,B,C,D) = BC' + BD' + AC'D'$

| | | | | | |
|----|----|----|----|----|----|
| | | AB | | | |
| | | 00 | 01 | 11 | 10 |
| CD | 00 | | 1 | 1 | 1 |
| | 01 | | 1 | 1 | |
| | 11 | | | | |
| | 10 | | 1 | 1 | |

C. Identify the most simple Product of Sums (POS) expression which generates the K-map shown.

- (a) $F(A,B,C)=(A+C')(A+B+C)$
- (b) $F(A,B,C)=(A+B)(A+C')(B+C')$
- (c) $F(A,B,C)=(A'+B')(A'+C)(B'+C)$
- (d) $F(A,B,C)=(A'+C)(A'+B'+C')$
- (e) $F(A,B,C)=(A+B)(A'+C)(B'+C)$

| | | | | | |
|---|---|----|----|----|----|
| | | AB | | | |
| | | 00 | 01 | 11 | 10 |
| C | 0 | 1 | 0 | 0 | 0 |
| | 1 | 1 | 1 | 0 | 1 |


D. The most reduced expression which can be obtained from the K-map illustrated is:

- (a) $F(A,B,C,D)=A + D$
- (b) $F(A,B,C,D)=C$
- (c) $F(A,B,C,D)=A + B$
- (d) $F(A,B,C,D)=A$
- (e) $F(A,B,C,D)=A + B + D$


| | | | | | |
|----|----|----|----|----|----|
| | | AB | | | |
| | | 00 | 01 | 11 | 10 |
| CD | 00 | | x | 1 | 1 |
| | 01 | x | x | 1 | 1 |
| | 11 | x | x | 1 | 1 |
| | 10 | | x | 1 | 1 |

Question 3 (10 points):

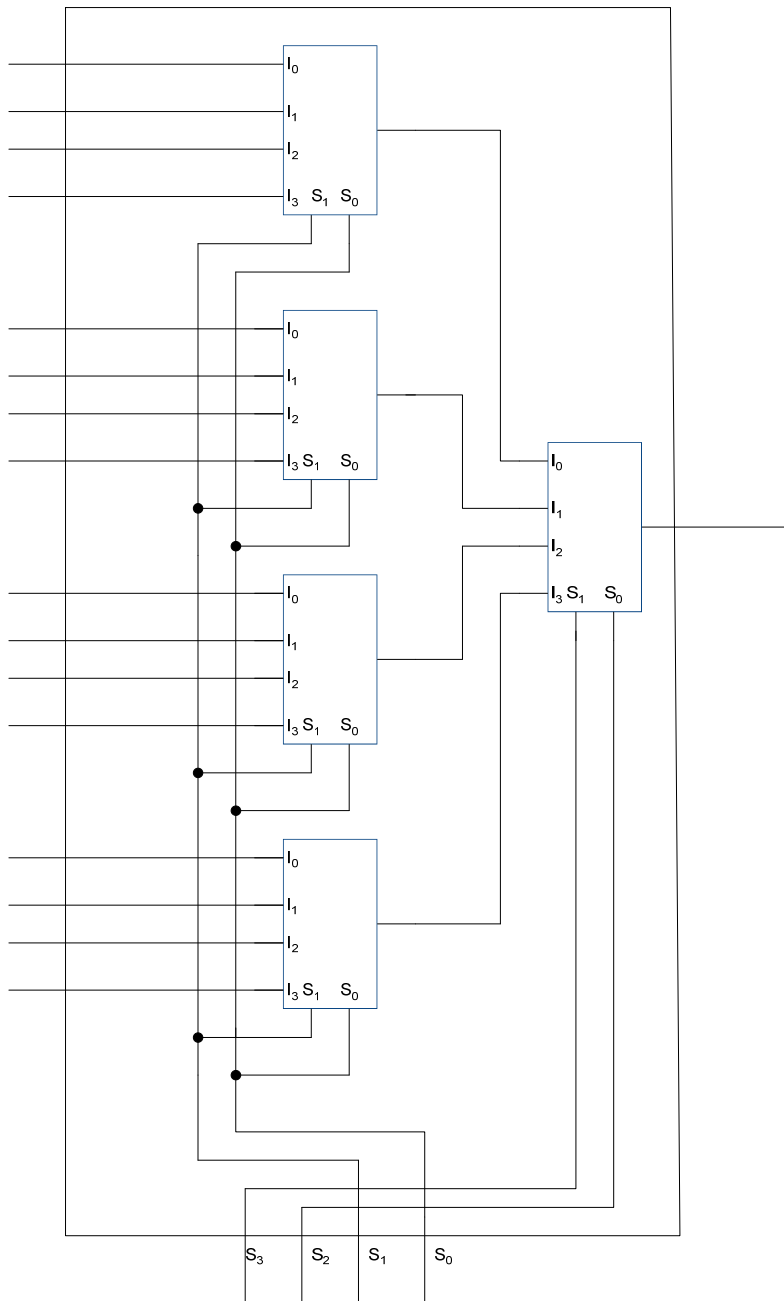- a) Construct a 16 X 1 multiplexer by using 5 4x 1 multiplexers. Use block diagrams.



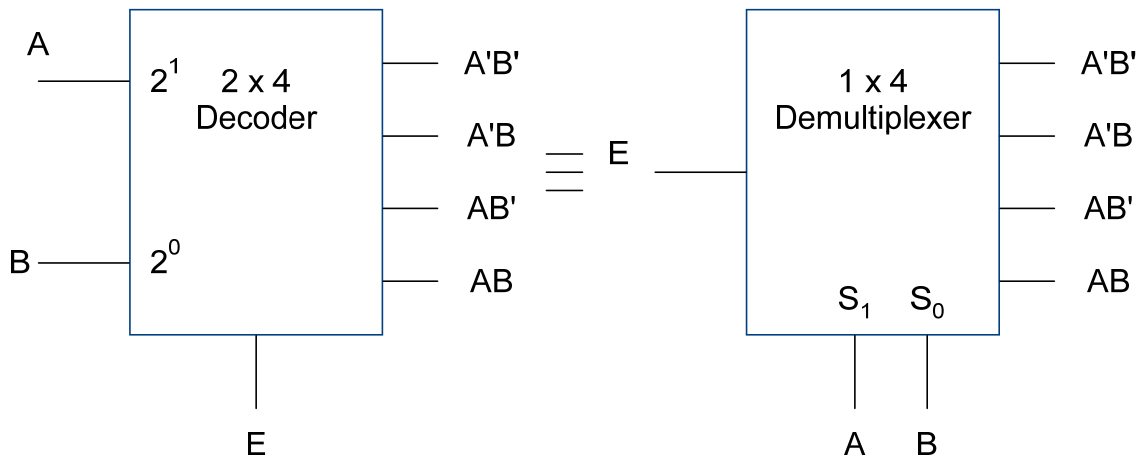b) Construct a 2-to-4-line decoder by using a 1-to-4 Demultiplexer. Use block diagrams.




Question 4 (10 points):

Implement the following Boolean function with a 4 x 1 multiplexer:

$$F(A, B, C, D) = \Sigma (0, 1, 3, 4, 8, 9, 15)$$

| Minterm | A | B | C | D | F |
|---------|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 2 | 0 | 0 | 1 | 0 | 0 |
| 3 | 0 | 0 | 1 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 | 1 |
| 5 | 0 | 1 | 0 | 1 | 0 |
| 6 | 0 | 1 | 1 | 0 | 0 |
| 7 | 0 | 1 | 1 | 1 | 0 |
| 8 | 1 | 0 | 0 | 0 | 1 |
| 9 | 1 | 0 | 0 | 1 | 1 |
| 10 | 1 | 0 | 1 | 0 | 0 |
| 11 | 1 | 0 | 1 | 1 | 0 |
| 12 | 1 | 1 | 0 | 0 | 0 |
| 13 | 1 | 1 | 0 | 1 | 0 |
| 14 | 1 | 1 | 1 | 0 | 0 |
| 15 | 1 | 1 | 1 | 1 | 1 |

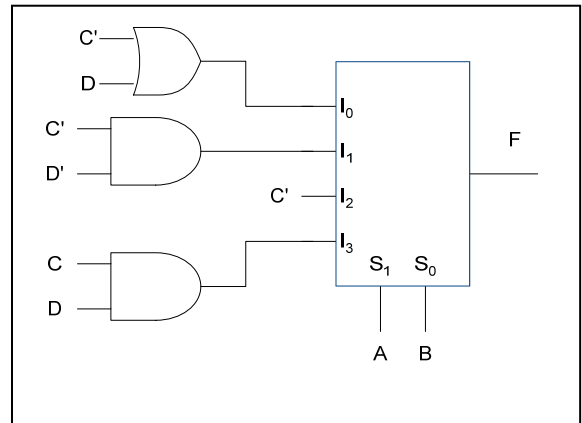$I_0 = C' + D$
 $I_1 = C'D'$
 $I_2 = C'$
 $I_3 = CD$



Question 5 (20 points):

Design a combinational circuit that converts a 4-bit gray code to a 4-bit binary number. Implement the circuit using exclusive-OR gates.

| Decimal | | Gray Code | | | | BINARY | | | |
|---------|------|-----------|---|---|---|--------|---|---|---|
| | | A | B | C | D | W | X | Y | Z |
| 0 | 0000 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0001 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 2 | 0011 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 3 | 0010 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 4 | 0110 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 5 | 0111 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 1 |
| 6 | 0101 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 7 | 0100 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 8 | 1100 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 9 | 1101 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 10 | 1111 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 11 | 1110 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 1 |
| 12 | 1010 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 |
| 13 | 1011 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 |
| 14 | 1001 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 |
| 15 | 1000 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

W = A

| | | CD | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| AB | 00 | | | | |
| | 01 | 1 | 1 | 1 | 1 |
| | 11 | | | | |
| | 10 | 1 | 1 | 1 | 1 |


$$X = A'B + AB' = A \oplus B$$

| | | CD | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| AB | 00 | | | 1 | 1 |
| | 01 | 1 | 1 | | |
| | 11 | | | 1 | 1 |
| | 10 | 1 | 1 | | |

$$Y = A'B'C + A'BC' + ABC + AB'C' = A \oplus B \oplus C$$

| | | CD | | | |
|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| AB | 00 | | 1 | | 1 |
| | 01 | 1 | | 1 | |
| | 11 | | 1 | | 1 |
| | 10 | 1 | | 1 | |

$$Z = A \oplus B \oplus C \oplus D$$

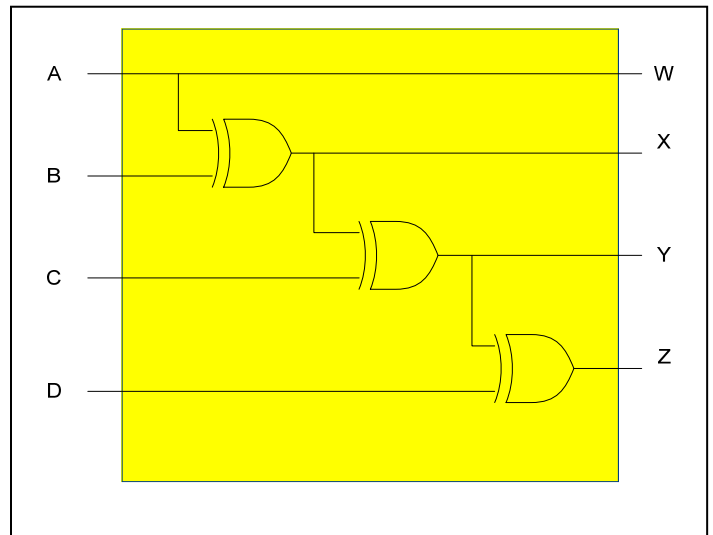

Question 6 (20 points):

Derive the state table and the state diagram of the sequential circuit shown in Fig. FQ-6.


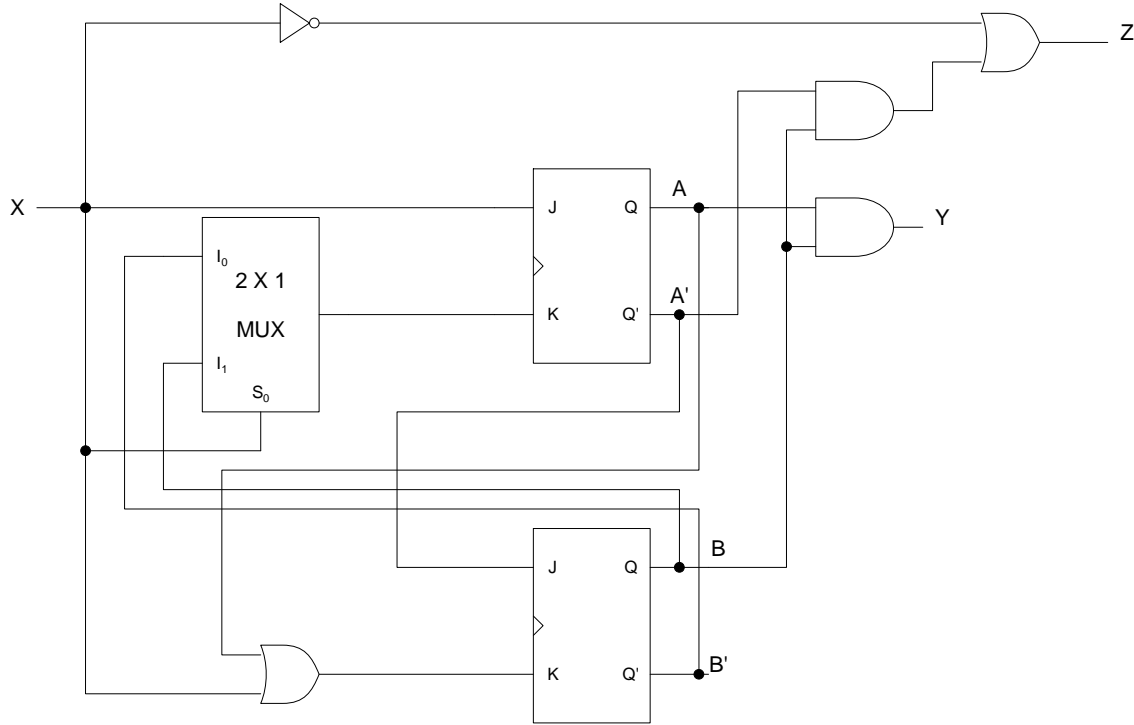


Figure FQ-6

$$\begin{aligned}
 J_A &= x \\
 K_A &= B'x' + Bx \\
 J_B &= A' \\
 K_B &= A + x \\
 Y &= AB \\
 Z &= A'B + x'
 \end{aligned}$$

| Present State | | Input | Next State | | Output | | Flip-flop Input | | | |
|---------------|---|-------|------------|---|--------|---|-----------------|-------|-------|-------|
| A | B | x | A | B | Y | Z | J_A | K_A | J_B | K_B |
| 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 |

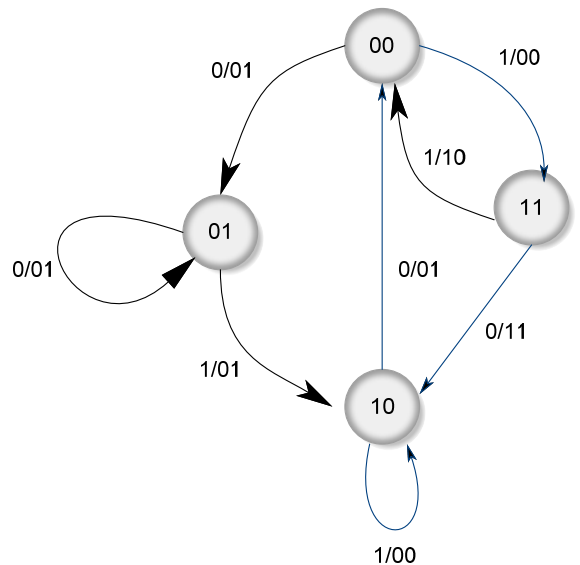

Question 7 (20 points):

Design the sequential circuit specified by the state diagram of Fig. FQ-7 using T flip-flops.


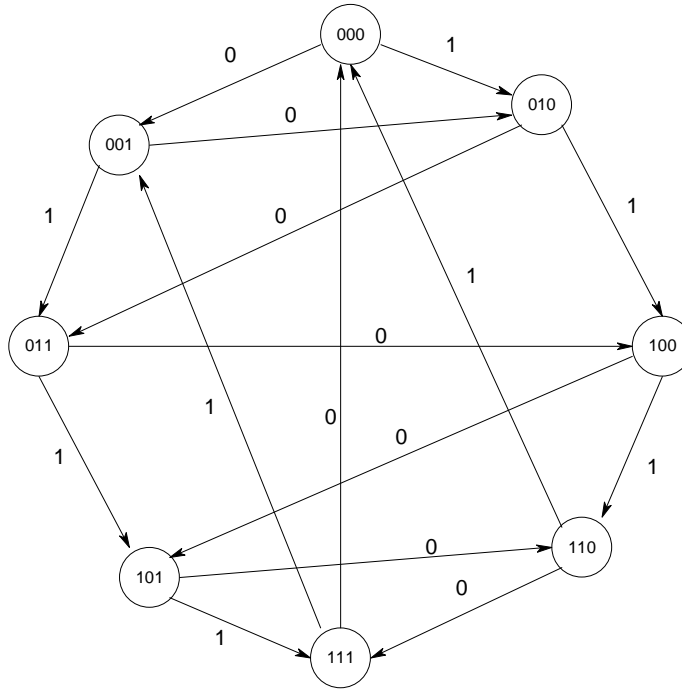


Figure FQ-7

| Present State | | | Input | Next State | | | Flip-flop Inputs | | |
|---------------|---|---|-------|------------|---|---|------------------|----------------|----------------|
| A | B | C | x | A | B | C | T _A | T _B | T _C |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 |

$T_C = x'$

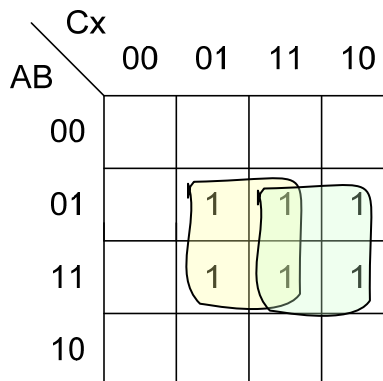

$T_A = Bx + BC = B(x + C)$

| | | | | | |
|----|----|----|----|----|----|
| | | Cx | | | |
| | | 00 | 01 | 11 | 10 |
| AB | 00 | 1 | 1 | 1 | |
| | 01 | 1 | 1 | 1 | |
| | 11 | 1 | 1 | 1 | |
| | 10 | 1 | 1 | 1 | |

$T_A = x + C$

