



Faculty of Engineering
ELECTRICAL AND ELECTRONIC ENGINEERING DEPARTMENT
EENG115/INFE115 Introduction to Logic Design
EENG211/INFE211 Digital Logic Design I

Spring 2009-10

Instructors:
M. K. Uyguroğlu
H. Demirel

Midterm EXAMINATION

Apr. 15, 2010

Duration : 100 minutes

Number of Problems: 5

Good Luck

STUDENT'S	
NUMBER	
NAME	SOLUTIONS
SURNAME	
GROUP NO	

Problem	Achieved	Maximum
1		20
2		20
3		20
4		20
5		20
<i>TOTAL</i>		100

Question 1 (20 points)

- a. Convert the following octal number $(270.4)_8$ to decimal. (5 pts.)

$$270.4 = 2 \times 8^2 + 7 \times 8^1 + 0 \times 8^0 + 4 \times 8^{-1} = 128 + 56 + 0.5 = 184.5_{10}$$

- b. Convert the decimal number $(45.0625)_{10}$ to binary, octal and hexadecimal. (15 pts.)

$\begin{array}{c ccccc} 45 & & & & & \\ \hline 22 & 1 & & & & \\ 11 & 0 & & & & \\ 5 & 1 & & & & \\ 2 & 1 & & & & \\ 1 & 0 & & & & \\ 0 & 1 & & & & \end{array}$		$\begin{array}{cccccc} 0.0625 & \times & 2 & = & 0.125 & 0 \\ 0.125 & \times & 2 & = & 0.25 & 0 \\ 0.25 & \times & 2 & = & 0.5 & 0 \\ 0.5 & \times & 2 & & 1 & 1 \end{array}$ $0.0625 = 0.0001$
$45 = 101101$		$\begin{array}{l} 45.0625 = 101101.0001 \\ 101101.000100 = 55.04_8 \\ 00101101.0001 = 2D.1_{16} \end{array}$

Question 2 (20 points):

- a) Find the $(r-1)$'s and r 's complements of the following numbers in the indicated bases. (10 pts.)

i. $(4190)_{10}$

9's complement of 4190 = **5809**

10's complement of 4190 = **5810**

ii. $(11011000)_2$

1' complement of 11011000 = 00100111

2' complement of 11011000 = 00101000

- b) Perform the following subtractions in the indicated bases by using the r 's complement of the subtrahend. Express the results in decimal. (10 pts.)

i. $(2300 - 2305)_{10}$

$2300 + 7695 = 9995 \Rightarrow - (0005)$

ii. $(11010 - 1101)_2 = 11010 - 01101 \quad 26 - 13 = 13$

$11010 + 10011 = \text{401101}$

Question 3 (20 points):

- a) Construct truth table for the following function (5 pts.)

$$F(a,b,c) = (ab + a'c)' + bc$$

a	b	c	a'	ab	$a'c$	$ab + a'c$	$(ab + a'c)'$	bc	$(ab + a'c)' + bc$
0	0	0	1	0	0	0	1	0	1
0	0	1	1	0	1	1	0	0	0
0	1	0	1	0	0	0	1	0	1
0	1	1	1	0	1	1	0	1	1
1	0	0	0	0	0	0	1	0	1
1	0	1	0	0	0	0	1	0	1
1	1	0	0	1	0	1	0	0	0
1	1	1	0	1	0	1	0	1	1

- b) Use the truth table of (a) to write the function F in sum of minterms form (2.5 pts.)

$$F(a,b,c) = \sum(0, 2, 3, 4, 5, 7)$$

- c) Expand the function $F(x,y,z) = y + x'z$ to product of Maxterms form. (2.5 pts.)


$$F(x, y, z) = y + x'z = (x' + y)(y + z) = (x' + y + zz')(xx' + y + z)$$

$$F(x, y, z) = (x' + y + z)(x' + y + z')(x + y + z)(x' + y + z)$$

$$F(x, y, z) = \prod(0, 4, 5)$$

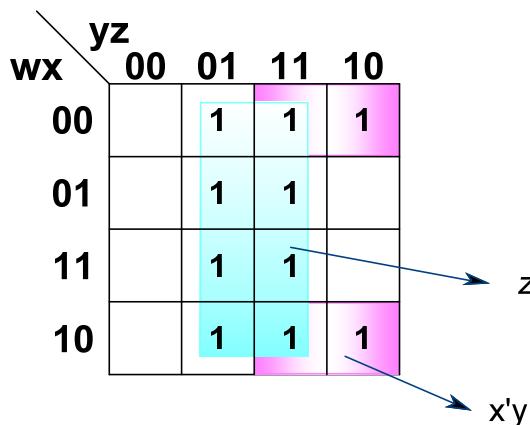- d) Simplify the following function using Karnaugh map. (10 pts.)

$$F(w, x, y, z) = w'z + xz + x'y + wx'z$$




$$F(w, x, y, z) = z + x'y$$

Question 4 (20 points):

Simplify the following function and implement it using

- (i) NOR gates only
- (ii) NAND gates only
- (iii) OR-NAND
- (iv) AND-NOR

$$F(w, x, y, z) = wx' + y'z' + w'yz'$$

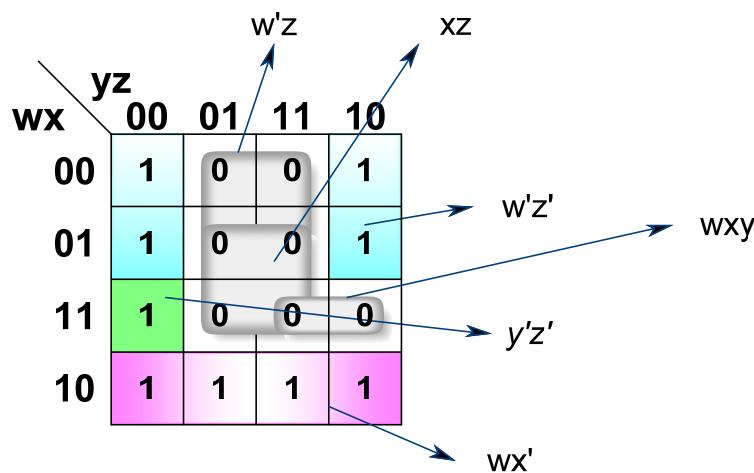

$$F(w, x, y, z) = wx' + y'z' + w'z' \text{ Sum of products (NAND implementation)}$$


$$F'(w, x, y, z) = (w+x)(y+z)(w+z)$$


$$F(w, x, y, z) = (F'(w, x, y, z))' = ((w+x)(y+z)(w+z))' \text{ OR-AND-invert (OR -NAND implementation)}$$

$$F'(w, x, y, z) = w'z + xz + wxy \text{ Product of sums}$$

$$F(w, x, y, z) = (F'(w, x, y, z))' = (w+z')(x'+z')(w'+x'+y') \text{ NOR implementation}$$
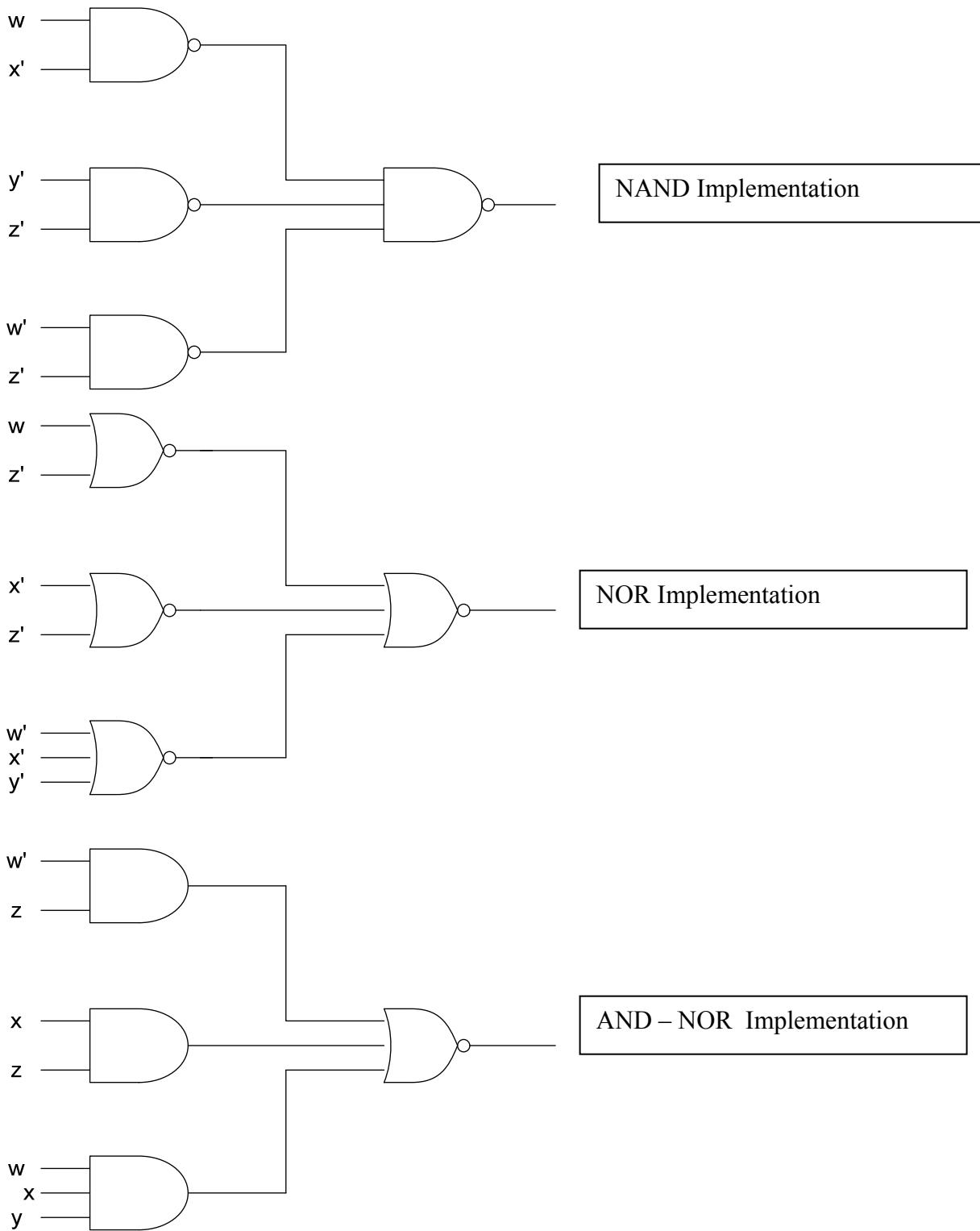
$$F(w, x, y, z) = (F'(w, x, y, z))' = (w'z + xz + wxy)' \text{ AND-OR-invert (AND-NOR)}$$



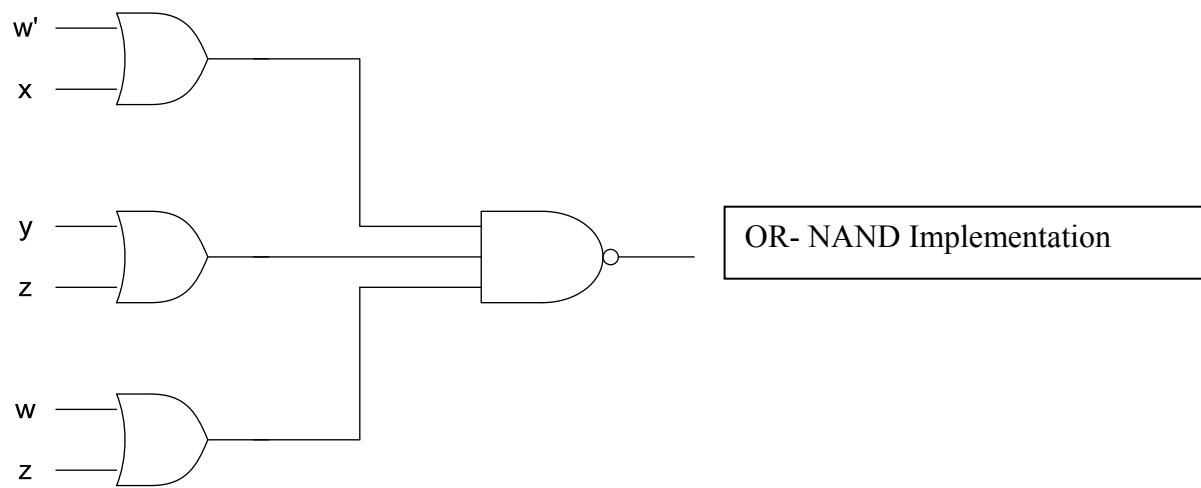

Question 5 (20 points):

Implement the following Boolean function F , together with the don't-care conditions d . Use minimum number of NAND gates for your implementation.

$$F(A,B,C,D) = \prod (8,9,11,12,13,15)$$

$$d(A,B,C,D) = \sum(0,2,7,14)$$

		CD		A'	
		00	01	11	10
AB	00	x	1	1	x
	01	1	1	x	1
11	0	0	0	x	
10	0	0	0		1

$$F(A,B,C,D) = A' + CD'$$

